

Radio- Electronics®

BUILD THE PICTURE PHONE
ADAPTER AND SEND VIDEO
OVER YOUR TELEPHONE

\$1.25 SEPT. 1982

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Build this **HEART RATE MONITOR**

The ins and outs of **BUYING MAILORDER PARTS**

How to **BIAS TRANSISTORS CORRECTLY** when designing analog circuits

Build a **STEREO IMAGE EXPANDER** for concert hall effects

Troubleshoot and repair **MINI-CASSETTE RECORDERS** step-by-step



Kevin J. Carneiro

If we only tell you the features you'll never guess the price.

Leader has 6 great oscilloscopes from 15 to 35 MHz,
with more features and the lowest list prices ever.

We've designed brand new low and medium bandwidth oscilloscopes and built in many features you may never have seen in similar units. Then we priced them well below the units they replace. Surprising? Not any more. It's exactly the kind of innovative technology and superb quality you've come to expect from Leader.

**Ever see trigger holdoff
on a 20 MHz scope?
Or 500 μ V sensitivity?**

Now Leader gives you these
and so much more. Check it out:

LBO-524/LBO-524L: 35 MHz


- CALIBRATED DUAL TIME BASE
- 500 μ V SENSITIVITY
- 7 kV PDA 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- DELAYED SWEEP TRIGGERED FUNCTION
- VARIABLE SWEEP HOLDOFF
- ALTERNATE CHANNEL TRIGGERING
- AUTO FOCUS
- CHANNEL 1 OUTPUT

LBO-523: 35 MHz

- 7 kV PDA 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- 500 μ V SENSITIVITY
- VARIABLE SWEEP HOLDOFF
- ALTERNATE CHANNEL TRIGGERING
- AUTO FOCUS
- CHANNEL 1 OUTPUT

CIRCLE 4 FOR PRODUCT DEMONSTRATION

CIRCLE 5 FOR PRODUCT INFORMATION

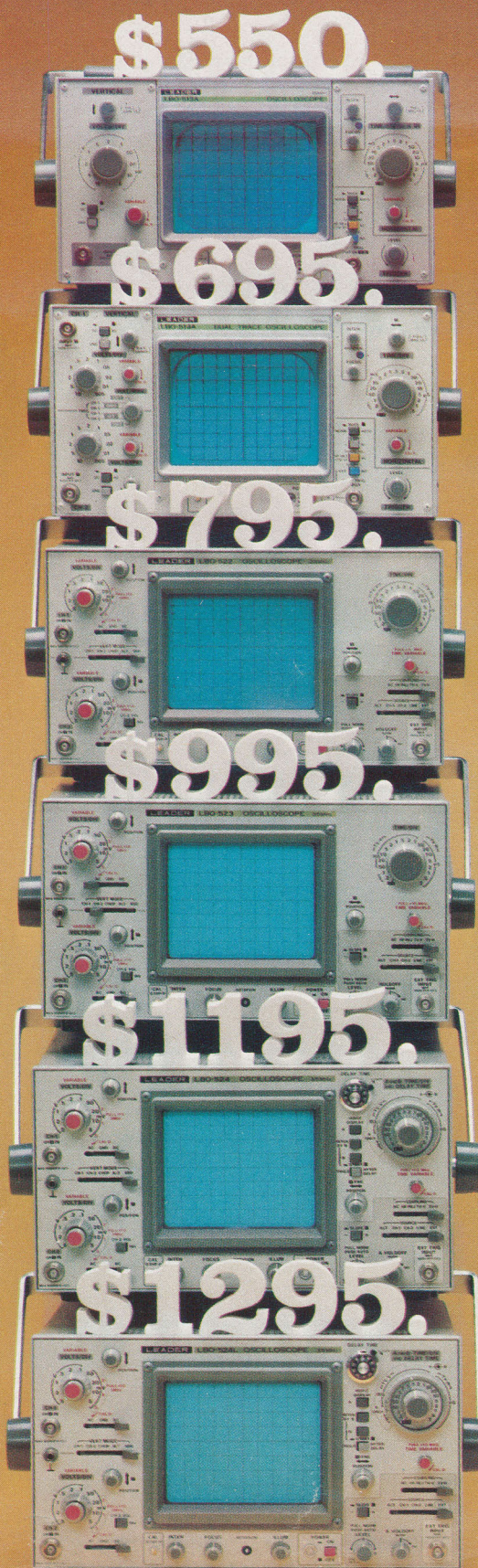

LBO-522: 20 MHz

- 500 μ V SENSITIVITY
- 6" RECTANGULAR CRT
- INTERNAL GRATICULE
- ALTERNATE CHANNEL TRIGGERING
- VARIABLE SWEEP HOLDOFF
- AUTO FOCUS
- CHANNEL 1 OUTPUT

LBO-514A/LBO-513A: 15 MHz

- 1 mV SENSITIVITY
- 0.5 μ S SWEEP SPEED
- X-Y MODE CAPABILITY
- LBO-514A AVAILABLE WITH 6 kV ACCELERATING POTENTIAL

Our two-year warranty (even on the CRT) is backed by factory service depots on both coasts. Evaluation units are available to qualified customers.

**Call toll-free
(800) 645-5104**

Contact us today for an evaluation unit, catalog showing over 60 Leader test instruments, the name of your nearest "Select" distributor and more information.

For professionals
who
know
the
difference.

LEADER
Instruments Corporation

380 Oser Avenue
Hauppauge, N.Y. 11788 (516) 231-6900
Regional Offices:
Chicago, Los Angeles, Dallas

Introducing incredible tuning accuracy at an incredibly affordable price: The Command Series RF-3100 31-band AM/FM/SW receiver.* No other shortwave receiver brings in PLL quartz synthesized tuning and all-band digital readout for as low a price.† The tuner tracks and "locks" onto your signal, and the 5-digit display shows exactly what frequency you're on.

There are other ways the RF-3100 commands the airways: It can travel the full length of the shortwave band (that's 1.6 to 30 MHz). It eliminates interference when stations overlap by narrowing the broadcast band. It improves reception in strong signal areas with RF Gain Control. And the RF-3100 catches Morse

communications accurately with BFO Pitch Control.

Want to bring in your favorite programs without lifting a finger? Then consider the Panasonic RF-6300 8-band AM/FM/SW receiver (1.6 to 30 MHz) has microcomputerized preset pushbutton tuning, for programming 12 different broadcasts, or the same broadcast 12 days in a row. Automatically. It even has a quartz alarm clock that turns the radio on and off to play your favorite broadcasts.

The Command Series RF-3100 and RF-6300. Two more ways to roam the globe at the speed of sound. Only from Panasonic.

*Shortwave reception will vary with antenna, weather conditions, operator's geographic location and other factors. An outside antenna may be required for maximum shortwave reception.

†Based on a comparison of suggested retail prices.



This Panasonic Command Series™ shortwave receiver brings the state of the art closer to the state of your pocketbook.



With PLL Quartz Synthesized Tuning and Digital Frequency Readout.

Panasonic
just slightly ahead of our time.

Why use their flexible discs:

BASF, Control Data, Dysan, IBM, Kybe, Maxell,
Nashua, Scotch, Syncom, Verbatim or Wabash
when you could be using

MEMOREX

high quality error free discs?

Product Description	Part #	CE quant. 100 price per disc (\$)
8" SSSD IBM Compatible (128 B/S, 26 Sectors)	3062	2.09
8" SSSD Shugart Compatible, 32 Hard Sector	3015	2.09
8" SSSD CPT 8000 Compatible, Soft Sector	3045	2.99
8" SSDD IBM Compatible (128 B/S, 26 Sectors)	3090	2.74
8" DSDD Soft Sector (Unformatted)	3102	3.34
8" DSDD Soft Sector (128 B/S, 26 Sectors)	3115	3.34
8" DSDD Soft Sector (256 B/S, 26 Sectors)	3103	3.34
8" DSDD Soft Sector (512 B/S, 15 Sectors)	3114	3.34
8" DSDD Soft Sector (1024 B/S, 8 Sectors)	3104	3.34
5 1/4" SSDD Soft Sector w/Hub Ring	3481	2.34
5 1/4" SSDD 10 Hard Sector w/Hub Ring	3483	2.34
5 1/4" SSDD 16 Hard Sector w/Hub Ring	3485	2.34
5 1/4" DSDD Soft Sector w/Hub Ring	3491	3.09
5 1/4" DSDD 10 Hard Sector w/Hub Ring	3493	3.09
5 1/4" DSDD 16 Hard Sector w/Hub Ring	3495	3.09
5 1/4" SSDD Soft Sector w/Hub Ring (96 TPI)	3504	2.99
5 1/4" DSDD Soft Sector w/Hub Ring (96 TPI)	3501	3.99

SSSD = Single Sided Single Density; SSDD = Single Sided Double Density
DSDD = Double Sided Double Density; TPI = Tracks per inch

Memorex Flexible Discs... The Ultimate in Memory Excellence

Free Memorex Mini-Disc Offer - Save 10%

Every carton of 10 Memorex 5 1/4 inch mini-discs sold by Communications Electronics, now has a coupon good for a free Memorex mini-disc. For every case of 100 Memorex mini-discs you buy from CE, you'll get 10 free mini-discs directly from Memorex. There is no limit to the number of discs you can purchase on this special offer. This offer is good only in the U.S.A. and ends on December 31, 1982.

Quality

Memorex means quality products that you can depend on. Quality control at Memorex means starting with the best materials available and continual surveillance throughout the entire manufacturing process. The benefit of Memorex's years of experience in magnetic media production, resulting, for instance, in proprietary coating formulations. The most sophisticated testing procedures you'll find anywhere in the business.

100 Percent Error Free

Each and every Memorex Flexible Disc is certified to be 100 percent error free. Each track of each flexible disc is tested, individually, to Memorex's stringent standards of excellence. They test signal amplitude, resolution, low-pass modulation, overwrite, missing pulse error and extra pulse error. Rigid quality audits are built into every step of the manufacturing process and stringent testing result in a standard of excellence that assures you, our customer, of a quality product designed for increased reliability and consistent top performance.

Customer-Oriented Packaging

The desk-top box containing ten discs is convenient for filing and storage. Both box labels and jacket labels provide full information on compatibility, density, sectoring, and record length. Envelopes with multi-language care and handling instructions and color-coded removable labels are included. A write-protect feature is available to provide data security.

Full One Year Warranty — Your Assurance of Quality Memorex Flexible Discs will be replaced free of charge by Memorex if they are found to be defective in materials or workmanship within one year of the date of purchase. Other than replacement, Memorex will not be responsible for any damages or losses (including consequential damages) caused by the use of Memorex Flexible Discs.

Quantity Discounts Available

Memorex Flexible Discs are packed 10 discs to a carton and 10 cartons to a case. Please order only in increments of 100 units for quantity 100 pricing. We are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 10% surcharge. **Quantity discounts** are also available. Order 500 or more discs at the same time and deduct 1%; 1,000 or more saves you 2%; 2,000 or more saves you 3%; 5,000 or more saves you 4%; 10,000 or more saves you 5%; 25,000 or more saves you 6%; 50,000 or more saves you 7% and 100,000 or more discs earns you an 8% discount off our super low quantity 100 price. Almost all Memorex Flexible Discs are immediately available from CE. Our warehouse facilities are equipped to help us get you the quality product you need, when you need it. If you need further assistance to find the flexible disc that's right for you, call the Memorex compatibility hotline. Dial toll-free 800-538-8080 and ask for the flexible disc hotline extension 0997. In California dial 800-672-3525 extension 0997. Outside the U.S.A. dial 408-987-0997.

Buy with Confidence

To get the fastest delivery from CE of your Memorex Flexible Discs, send or phone your order directly to our Computer Products Division. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax. Written purchase orders are accepted from approved government agencies and most well rated firms at a 30% surcharge for net 30 billing. All sales are subject to availability, acceptance and verification. All sales are final. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless CE is instructed differently. Minimum prepaid order \$50.00. Minimum purchase order \$200.00. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require bank clearance.

Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$8.00 per case or partial-case of 100 8-inch discs or \$6.00 per case or partial case of 100 5 1/4-inch mini-discs for U.P.S. ground shipping and handling in the continental U.S.A. If you have a MasterCard or Visa card, you may call anytime and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. If you are outside the U.S. or in Michigan, dial 313-994-4444. Order your high quality, error free Memorex discs today.

Copyright © 1982 Communications Electronics™


Ad #051782

Free disc offer Save 10%



Order Toll-Free!
(800) 521-4414

In Michigan (313) 994-4444

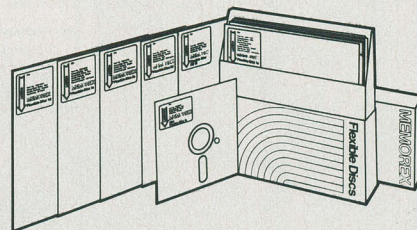

For Data Reliability—Memorex Flexible Discs

COMMUNICATIONS ELECTRONICS™

Computer Products Division

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

SPECIAL FEATURE

- 53 BUYING MAIL-ORDER COMPONENTS**
Mail-order is sometimes the only way to obtain the components you need. Here are some tips you should know and pitfalls you should avoid. **Karl T. Thurber, Jr., W8FX**

BUILD THIS

- 45 HEART-RATE MONITOR**
Know the state of your health and fitness. This project displays your heart rate in beats-per-minute by simply attaching an opto-electronic sensor to your finger. **Robert Grossblatt**
- 49 PICTURE PHONE**
Part 2—Adapter sends video pictures over the telephone line to a remote location. **Josef Bernard**
- 63 STEREO IMAGE EXPANDER**
Part 2—Hi-fi adapter adds an extra dimension to your recorded music. **Joel Cohen**

TECHNOLOGY

- 4 VIDEO ELECTRONICS**
Tomorrow's news and technology in this quickly changing industry. **David Lachenbruch**
- 40 SATELLITE TV NEWS**
The latest happenings in communications technology. **Gary H. Arlen**
- 71 ALL ABOUT PULSE GENERATORS**
How to use a pulse generator to test an analog circuit. **Charles Gilmore**
- 84 STATE-OF-SOLID-STATE**
DC voltage-controlled switches. **Robert F. Scott**

CIRCUITS AND COMPONENTS

- 42 NEW IDEA**
Electronic thermometer.
- 59 HOW TO DESIGN ANALOG CIRCUITS**
Proper transistor operation requires proper biasing. Learn about biasing circuits and how to design them. **Mannie Horowitz**
- 74 HOBBY CORNER**
Learning about microprocessors. **Earl "Doc" Savage, K4SDS**

VIDEO

- 92 SERVICE CLINIC**
Color-burst reference oscillators. **Jack Darr**
- 92 SERVICE QUESTIONS**
Radio-Electronics' Service Editor solves technicians' problems.

AUDIO

- 66 REPAIRING PORTABLE CASSETTE RECORDERS**
How to troubleshoot and repair these popular recorders. **Homer L. Davidson**

RADIO

- 78 COMMUNICATIONS CORNER**
Touch-Tone devices and FM Adjustments. **Herb Friedman**

COMPUTERS

- 80 COMPUTER CORNER**
Electronic worksheets. **Les Spindle**

EQUIPMENT REPORTS


- 26 Sencore Model SC61 Waveform Analyzer.**
- 32 McKay/Dymek General Coverage Receiving System**

DEPARTMENTS


- | | |
|---|---------------------------|
| 12 Advertising and Sales Offices | 22 Letters |
| 138 Advertising Index | 114 Market Center |
| 111 Books | 106 New Literature |
| 14 Editorial | 95 New Products |
| 139 Free Information Card | 6 What's News |

ON THE COVER

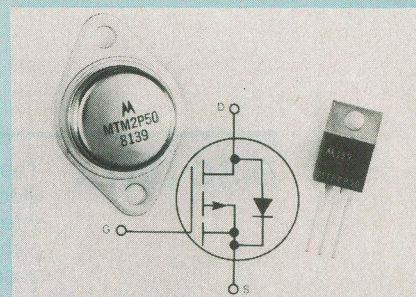Using an opto-electronic sensor that attaches to your finger, this battery-powered monitor displays your heart rate in beats-per-minute on a digital display. Knowing how your heart rate varies under different circumstances can give you an idea of your physical condition. Get started building yours today. The story starts on page 45.



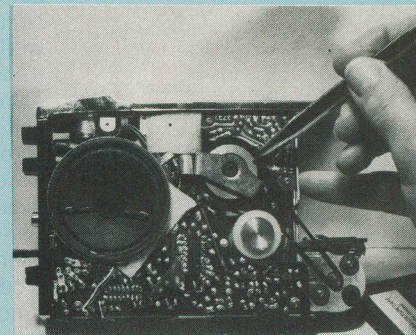HOW TO PROPERLY BIAS a transistor circuit is the subject of this month's analog design series. Must reading if your designs are to function the first time you plug them in. The story starts on page 59.



HOW TO TROUBLESHOOT AND REPAIR portable cassette recorders. The best results are obtained with a logical troubleshooting approach. The story starts on page 66.

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00; Canada, \$16.00; Other countries, \$20.50 (cash orders only, payable in U.S.A. currency.) Single copies \$1.25. © 1982 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.


Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

A service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

VIDEO ELECTRONICS

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

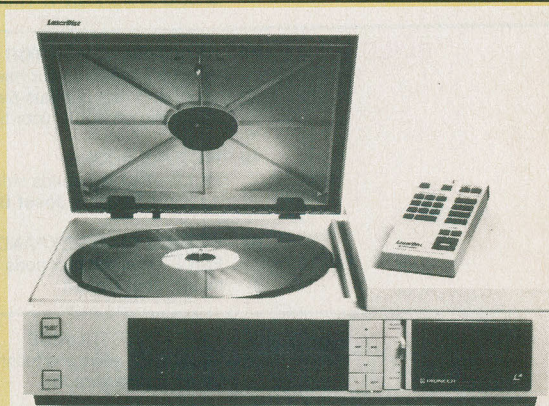

DISC DATA

The often-postponed market launch of the Japanese VHD videodisc system is now scheduled for summer 1983. Pioneer (see photo) has expanded its line of LaserVision players to three—the original model at about \$750, a new remote-control unit at \$800, and a version without remote and random frame access at \$600. RCA added a fourth CED player to its line described here last month—a model with wireless remote control and all-electronic on-set controls at \$449.95.

DIGITAL TV

"Computer TV" could become a byword—or an advertising point—next year when the first sets with completely digital signal-processing circuits are scheduled to be introduced. The circuits are contained on five VLSI IC's developed by ITT Semiconductor and being offered worldwide to TV set makers. ITT claims the IC's replace an average of 20 IC's, 500 to 600 transistors and other components, and make possible production of a better TV set for the same or less money. Among the claimed advantages: The set can be self-testing and self-adjusting, automatically compensating for picture-tube aging. The same set can be "programmed" to accommodate NTSC or PAL color. Stereo audio, when available, comes "free" (except for the speakers), merely by programming. The design will accommodate digital sound input, or digital input from a computer. It makes possible the later addition of low-cost "peripherals," such as digital ghost elimination, high-definition by means of line interpolation, and elimination of flicker by interpolation of additional fields or frames. The first production prototype digital TV will be shown by ITT's Standard Elektrik Lorenz of Germany. Among at least eight set makers working with the ITT circuits is Zenith, which could be the first to introduce a digital set here.

BETA HI-FI

How can you get true high-fidelity stereo from a half-inch home video recorder? The VHS manufacturers are adding a second audio track and Dolby noise reduction, but that provides a 50-10,000 Hz frequency response, at most. Headed by Sony, the Beta group has been showing a proposed new "Beta Hi-Fi" system that can provide better audio specs than an open-reel tape recorder, but is still compatible with existing Beta recorders and tapes.

Beta's magic trick is to leave the current longitudinal audio track alone and put a new stereo sound track on an FM carrier in the helical video track. The result is "nearly digital" sound, an 80-dB range, far above the 30- to 40-dB range of current recorders, with a frequency response of 20-20,000 Hz at 0.3% distortion, and inaudible wow and flutter. Recorders for the hi-fi system would also be able to play the longitudinal track on old tapes, and prerecorded tapes would have a longitudinal mono track plus the helical hi-fi stereo pair, to preserve compatibility. An extra bonus is the ability to have three separate soundtracks on mono tapes—three different languages, for example. Sony claims that such a helical-audio feat can't be accomplished on VHS recorders because their head drums are too small, resulting in picture degradation. But the VHS camp has yet to be heard from on the subject. If they go ahead with the project, Beta manufacturers say they can have recorders in the hi-fi format on the market around mid-1983.

R-I

"No one else gives you as many functions in a handheld DMM."

Now you can move up to Fluke."

We've got great news for people who've been holding out for a high quality, high performance DMM at a moderate price: Fluke's new nine-function model D 804 is now available at select electronics supply stores.

With a suggested U.S. price of only \$249 and features you won't find in any other handheld DMM, the D 804 is an exceptional value. Here's why.

Logic level and continuity testing: A real time-saver for troubleshooting passive circuits in pcb's, cables, relay panels and the like. The D 804 has a switch-selectable audible tone and visual symbols to indicate continuity or logic levels.

Direct temperature readings in °C: Used with any K-type

thermocouple, the D 804 delivers fully-compensated readings in °C from -20°C to +1265°C, for checking heating and refrigeration systems.

Peak hold feature captures transients: A short-term memory in the D 804 captures and holds the peak reading of a motor starting current.

And more: 0.1% basic dc accuracy, conductance, 26 measurement ranges, battery, safety-designed test leads and a one year parts and labor warranty. A full line of accessories is also available to extend the measurement capabilities of your DMM.

Ask your dealer about the powerful, versatile D 804 and the rest of Fluke's new Series D line of low-cost digital multimeters.



From the world leader in DMM's. Now we've designed one for you.



Suggested U.S. list price
technical data circle No. 15
1330-0/D804
RE 9/82

If your dealer doesn't carry Series D
Multimeters yet, call this number. We'll be
happy to tell you who does. 1-800-426-0361

FLUKE[®]

WHAT'S NEWS

Sharp reducing copier talks back to user

A new dry, any-paper desktop copier that talks to its user, makes reduced-size copies, can be automated, and helps diagnose its own troubles, has been introduced by Sharp Electronics Corp., headquartered in the United States at Paramus, NJ.

The new model *SF-781* speaks from a built-in voice synthesizer that emits electronic tones in a series that the ear hears as clear, easily understood sentences. When the user makes a reduced-size copy, the machine reminds

him: "Check the paper size," and if he leaves his material in the machine and starts to walk away, it calls out: "Remove the original." If there is a paper misfeed, the *SF-781* warns the user and tells where to look for the cause.

The machine also warns if paper or toner needs replenishing, and if the machine is out of order. The copier's total vocabulary is nine sentences, all selected to boost efficiency and save time.

An advanced self-diagnostic system, aided by a microcomputer, pinpoints many problems by voice or LED alphanumeric display—quick but thorough diagnos-

tic tests can be run from the front panel by pressing buttons.

The copier will take originals up to 11 × 17 inches. From that size, copies can be reduced to 8½ × 14 or 8½ × 11 inches. Line artwork can often be reduced so cleanly that it can be used for reproduction. Two 8½ × 11-inch pieces can be placed side-by-side for reproduction. The *SF-781* picks up a broad range of colors, including the difficult blue tones.

Transistors move into high-voltage range

Motorola, in what it refers to as "a major expansion of MOS power transistor technology," has introduced eight new devices in the "sparsely populated 550-volt and up" field. The new devices are intended for power supplies operating from 230 and 460-volt lines. They are supplied in four voltages, with breakdown rating from 550 to 900 volts, and up to 3 amperes of continuous drain current.

The new devices are intended for such equipment as transmitters, radar, and medical electronics using high-power, high-voltage, tube-operated circuitry. Prices are in the \$7 to \$10 range. Data sheets are available from Motorola at P.O. Box 20912, Phoenix, AZ 85036.

Children, aged 3 to 13, are new computer market

The Learning Co. of Portola Valley, CA, is henceforth devoting its efforts to developing and selling interactive computer software for children whose ages range from 3 to 13 years. The programs are for use in the home, and include play with learning, encouraging participation by both children and their parents.

The first two programs offered are *Moptown* and *Magic Spells*. They are available from Apple Computer distributors under Apple's Special Delivery Software programs. *Moptown* is a set of 11 logic games; *Magic Spells* is a word game that combines large text, color graphics, and music.

The games are designed for parents who wish to encourage their

children to learn in an entertaining and unthreatening way. The program guides the child through a series of adventures that promote original thinking. There is no violence and no wrong answers to discourage the child.

Founded in 1980 as Advanced Learning Technology by Dr. Ann Piestrup, the company pioneered the development of children's programs with interactive software featuring color graphics and animation, working under grants from the National Science Foundation and the Apple Education Foundation. Its change of name marks its move from a grant-funded organization to a commercial firm.

New plant will meet videodisc demands

RCA has commenced construction in Indianapolis of a new \$19 million facility for manufacturing the compound essential in making "CED" videodiscs. That will be used to support the expanding disc manufacture at the company's Rockville Road plant in Indianapolis, as well as to supply other manufacturers worldwide.

The compounding facility blends the plastic, carbon, and other materials that are used in pressing the conductive RCA discs. The blended material is in the form of pellets, which are formed into a mass and then placed between the two stampers of an automatic compression molding press to make the final disc. The new plant will be able to process 50,000 pounds of raw material daily.

In addition to the new 55,000-square-foot compounding facility, RCA has completed a new power plant that will be able to produce the energy that will be needed for 60 disc presses.

Satellite-to-home broadcasts in sight

The Satellite Television Corp (STC) a subsidiary of COMSAT, has received four bids to construct direct-broadcast satellites (DBS) for STC's satellite-to-home pay-TV service. The companies bidding were Ford Aerospace and Communications Corp, General Elec-

continued on page 12



SECRETARY IS USING THE *SF-781* with *SF-461* automatic document feeder (right) and *SF-410* sorter (in front of the secretary). Those can be added to the copier to permit the equipment to grow as the user's needs may require.

Now! A 60 MHz Tektronix scope built for your bench.

Wide-range vertical sensitivity:
Scale factors from 100 V/div (10X probe) to 2 mV/div (1X probe). Accurate to $\pm 3\%$. Ac or dc coupling.


Two high-sensitivity channels: dc to 60 MHz bandwidth from 10 V/div to 20 mV/div; extended sensitivity of 2 mV/div at > 50 MHz.

Sweep speeds:
from 0.5 s to 50 ns. To 5 ns/div with X10 magnification.

Delayed sweep measurements:
Accurate to $\pm 3\%$ with single time-base 2213; to $\pm 1.5\%$ with dual time-base 2215.

Complete trigger system. Includes TV field, normal, vertical mode, and automatic; internal, external and line sources; variable holdoff.

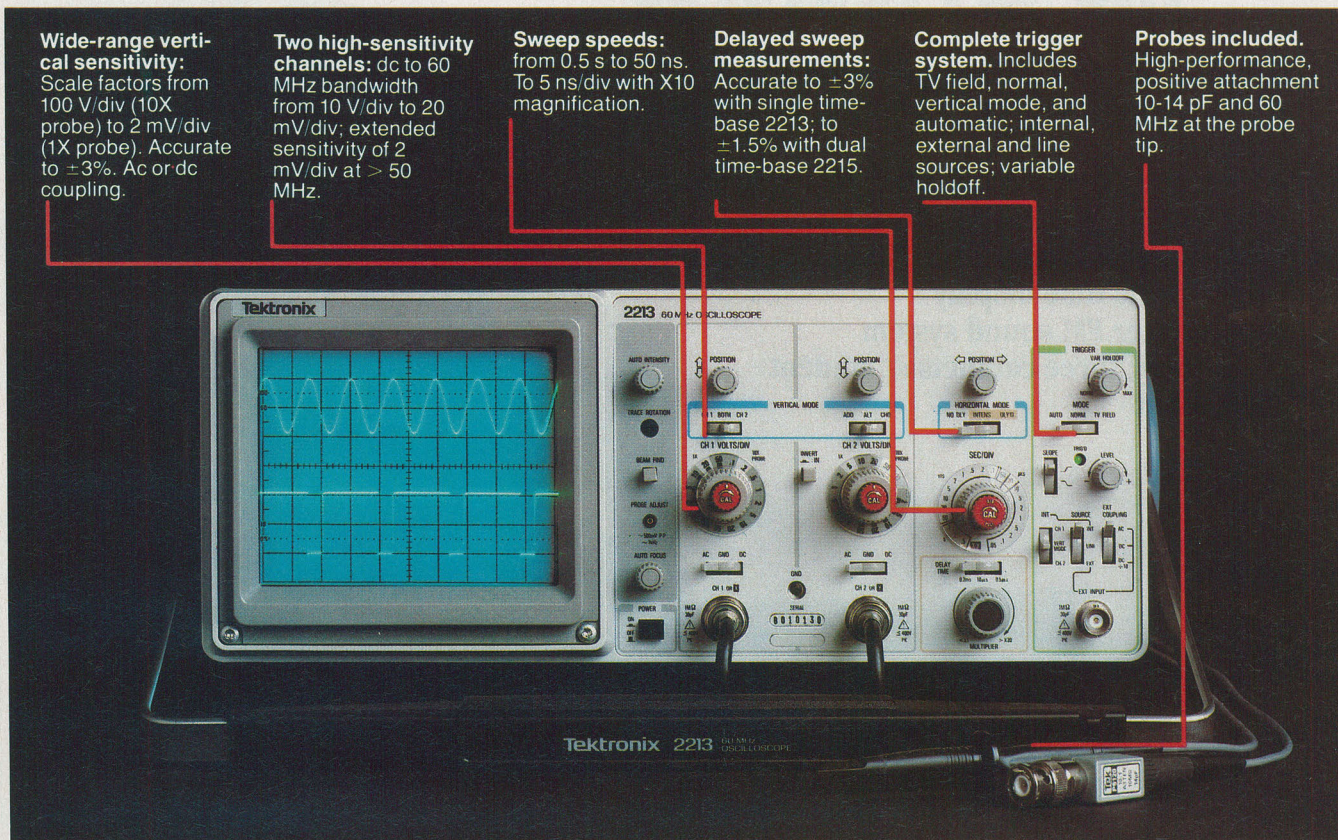Probes included. High-performance, positive attachment 10-14 pF and 60 MHz at the probe tip.



In 30 years of Tektronix oscilloscope leadership, no other scopes have recorded the immediate popular appeal of the Tek 2200 Series. The Tek 2213 and 2215 are unapproached for the performance and reliability they offer at a surprisingly affordable price.

There's no compromise with Tektronix quality: The low cost is the result of a new design concept that cut mechanical parts by 65%. Cut cabling by 90%. Virtually eliminated board electrical connectors. And obviated the usual cooling fan.

Yet performance is written all over the front panels. There's the bandwidth for digital and analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. And delayed sweep for fast, accurate timing measurements.

The cost: \$1100 for the 2213*. \$1400 for the dual time base 2215.

You can order, or obtain more information, through the Tektronix National Marketing Center, where technical personnel can answer your questions and expedite delivery. Your direct order includes

probes, operating manuals, 15-day return policy and full Tektronix warranty.

For a demonstration stop by your local Tektronix Sales Office.

**ORDER TOLL FREE
1-800-426-2200**


Ask for Department J0133
In the state of Washington,
Call (206) 253-5353 collect.

*Price F.O.B. Beaverton, OR

Tektronix
COMMITTED TO EXCELLENCE

Now! Learn on the latest... **NRI training includes** **25" Heath/Zenith** **color TV with state-of-** **the-art features**

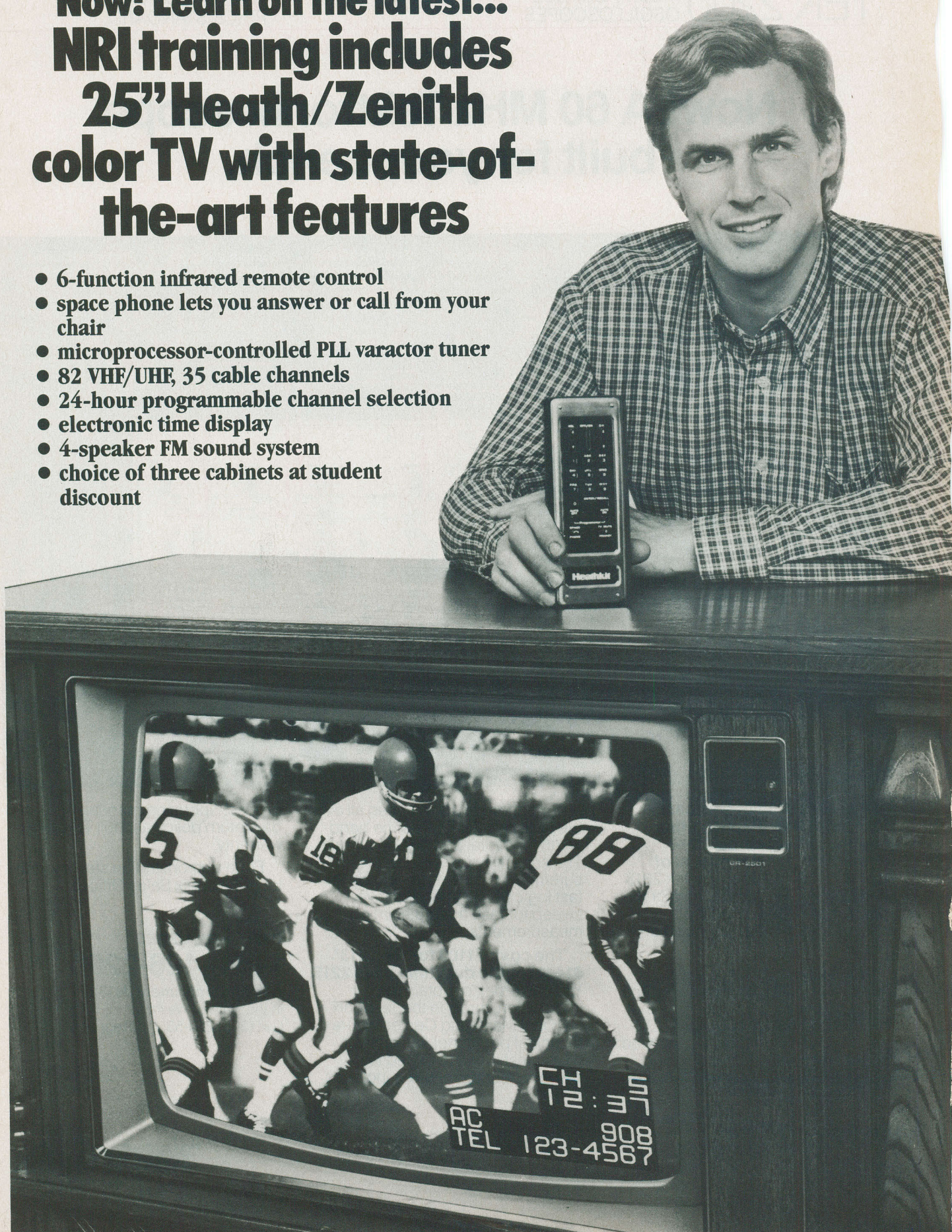- 6-function infrared remote control
- space phone lets you answer or call from your chair
- microprocessor-controlled PLL varactor tuner
- 82 VHF/UHF, 35 cable channels
- 24-hour programmable channel selection
- electronic time display
- 4-speaker FM sound system
- choice of three cabinets at student discount



We've taken the finest, most advanced, most complete TV/Audio/Video course available and made it even better. Now NRI brings your training up to and even beyond today's technology with the exciting, advanced performance Heath/Zenith Model 2501 TV. Now you can learn how to service even the latest circuitry on the most expensive TV sets as you assemble and perform experiments on your Heathkit/Zenith. Only NRI combines such complete training with such up-to-date equipment.



Choice of specialty training on TV, stereo, or VCR

Choice of Three Specialties


And only NRI gives you the opportunity to specialize in any of three areas. You get the same complete training covering TV, audio systems, and video recorders, but you select your own specialty for practical, hands-on training.

You can choose to build the Heath/Zenith color TV; specialize in audio systems and build your own AM/FM stereo system; or take your bench training with remote-controlled videocassette recorder featuring NRI training on videotape. No matter

which specialty you elect, your practical training also includes experiments and demonstrations with the exclusive NRI Discovery Lab® and your own professional digital multimeter. All equipment is yours to use and keep.

Learn in Your Spare Time

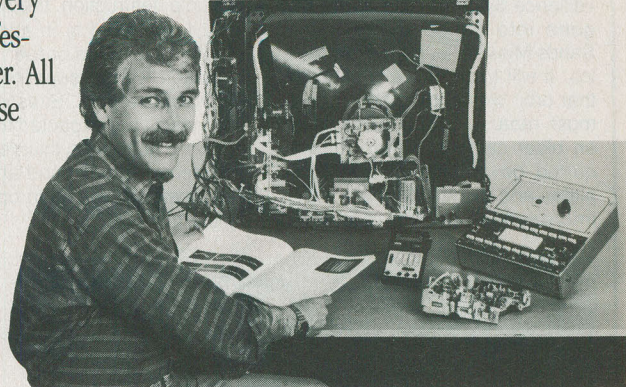No need to quit your job or tie up your evenings with night school...no classroom competition or rigid schedules. NRI trains you in your own home at your convenience. You're a class of one with complete course materials, practical training on the latest equipment, and the backing of a full staff of professional electronics educators. NRI brings it all to you.



Practical training on a real state-of-the-art TV using professional equipment

The Professional's Choice

A million and a half students have already chosen the NRI way. And over half the practicing TV service technicians in the U.S. have advanced their careers with convenient home training. Among them, it's NRI 3 to 1 over any other school (summary of national survey on request).

Free Catalog... No Salesman Will Call

Get all the facts on complete, convenient NRI training. See all the equipment, look over complete lesson plans, check out our convenient time payment plans. And see the many other opportunities in fields like Microcomputers, Electronic Design, Communications Electronics, and more. Send postage-paid card and see what advanced training is all about. If card has been removed, please write to us.



NRI Schools

McGraw-Hill Continuing Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

We'll give you tomorrow.

WHAT'S NEWS

continued from page 16

tric Co., Hughes Aircraft Co., and RCA Astro Electronics.

STC's Request for Proposals (issued January 13) were for construction of two satellites (one operating and one spare) which STC would use for satellite-to-home pay-TV service over an area approximating the U.S. Eastern Time Zone. The satellites are scheduled to operate on the 12- and 17-GHz bands.

The construction program is expected to take more than three years, and the service would begin in late 1985 or early 1986. STC will offer three channels of premium pay television, without advertising. Individual subscribers would receive STC's pay-TV service on small, inexpensive home receiving-antennas.

Optical system tracks distant satellites

The first of five Ground-based Electro-Optical Deep Space Surveillance Systems (GEODSS) has gone into action at the White Sands Missile Range in New Mexico. It will track optically satellites that orbit well above the range of most radars. GEODSS replaces an older camera system that required developing photographic plates and examining them with a microscope, usually about an

hour's work. Sighting and identification with GEODSS is almost instantaneous.

GEODSS's telescopes can pinpoint the location of all satellites above 3,000 miles, especially those that orbit at 22,000 miles above the equator. The telescopes combine camera optics and computers and can see objects 10,000 times dimmer than the human eye can detect. They are able to spot an object the size of a soccer ball more than 22,000 miles away. In operation, they fix on the stars and pick up any objects moving in front of them.

The telescope search is automatic, and the images it captures are recorded on a television camera. One hundred pictures a minute are converted into digital pulses and fed into a computer that filters out the (relatively) stationary surrounding stars and displays the satellites as streaks of light on video monitors.

To protect its own satellites from possible destruction, the Air Force must know what is in space and whether it is friend or foe. That information will be supplied by the GEODSS network. Sites in Korea and Hawaii are expected to be operational sometime this year, and an Eastern Atlantic and an Indian Ocean station will be in operation by the mid-1980's.



AIR FORCE TECHNICIANS TRACK SATELLITES at the ground-based Electro-Optical Deep Space Surveillance System facility in New Mexico. It is the first of five world-wide stations that will keep track of all man-made satellites in orbit within a range of 22,000 miles.

Anti-scanner ordinance tossed out in Philly

Municipal Court Judge J. Earl Simons ruled that Section 10-817 of the Code of Philadelphia Ordinances is unconstitutional. The ordinance, enacted in 1967, made access to police and fire radio channels illegal. It was not enforced until late in 1981, when the city interpreted the law to apply to radio scanners and arrested several owners and employees of retail stores for selling scanners.

The judge stated, among other things: "Individuals use scanner radios for personal entertainment or security purposes. Group use is endorsed—and in fact encouraged—by local law enforcement agencies, which conduct programs to teach the use of such scanner radios as a crime combatant. ... There is no evidence to support the contention that access to police or fire channels increases crime, or the risk thereof ... on the contrary, it demonstrates a markedly decreased risk of criminality when such scanners are employed by the citizenry. The conclusion is compelled that the ordinance is unconstitutional."

The judge then ruled that the citations be dismissed and the defendants discharged.

New state voice network promises greater economy

The State of Washington has contracted with the Action Communications System Div of Honeywell for a *Roadrunner* Network Management System, to replace a Common Channel Switching Arrangement (CCSA) leased from Pacific Northwest Bell.

The state has spent nearly \$12 million annually for long-distance telephone services provided by the CCSA leased network system. It is expected that the new systems can save about \$5 million in annual long-distance costs. Average calling rates will be reduced from 12 cents to 6.5 cents per minute by using the least-cost routing and management possibilities offered.

A network of intermachine trunks and PBX tie lines will interconnect four switching centers at Olympia, Seattle, Spokane, and Vancouver with government PBX

facilities across the state. The 2,656 port statewide network will utilize 4,800-baud data links between the four switching centers for "look ahead" routing and database maintenance and diagnostics.

G-E applies for a new consumer phone service

The General Electric Co. has applied for a total of 9 MHz in the 900-MHz band, for a new consumer-oriented mobile communications service. The allocation would be divided into two 4.5-MHz bands separated by 45 MHz. That would provide 150 channels of 30 kHz each.

The new Personal Radio Home Communications Service (PRCS) would be designed to augment the limited communications services already available to mobile consumers. It would provide the user with an affordable quality service for private communications within a user's normal driving area.

The system will consist of a base station tied into the user's telephone, and mobile units installed by users in their vehicles. The typical range with the system would be in the order of 5 miles, which can be increased to approximately 15 miles by using strategically located repeater stations. There would be a nominal charge access of any of those. Repeaters would not be interconnected.

An additional communications feature is automatic interconnection to the public telephone network through the base station.

New photovoltaic cell works with low light


A high-performance photovoltaic module that produces 40 watts of peak power with 35 solar cells has been developed by Arco Solar (a subsidiary of Atlantic Richfield) at Chatsworth, CA.

Using single-crystal silicon cells, the module can charge batteries at 5 to 10 percent of noonday sun. The manufacturer claims that under such low light conditions, the new cells can deliver up to 25 percent more energy than typical modules of polycrystalline design.

The new module, M51, measures 1 x 4 feet and is 10.75 percent efficient.

R-E

The Workbench

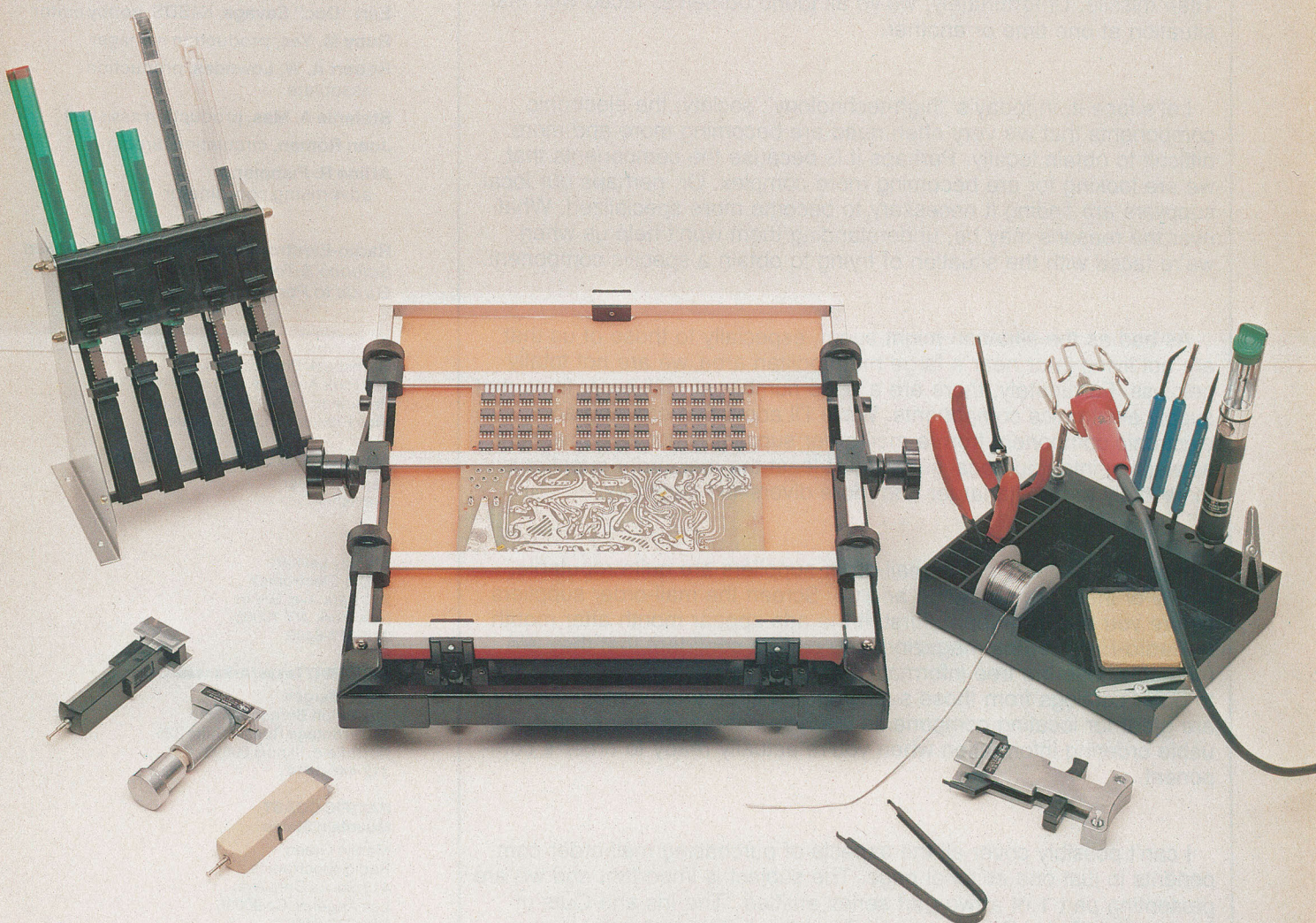

Designed by C.P.A. Graphics and Design Ltd., Bournemouth, England. (202) 294813

SOLDER AID

OK Machine & Tool Corporation
3455 Conner St., Bronx, N.Y. 10475 U.S.A.
Tel. (212) 994-6600 Telex 125091

CIRCLE 17 ON FREE INFORMATION CARD

ok

EDITORIAL

"My Kingdom For A"


How many times have you decided to build a project only to find that the parts list contains components that are almost impossible to obtain locally? Or, how many times have you used your best troubleshooting skills to locate a bad component on a PC board only to find that the component might as well be a proprietary unit from a Titan missile. Unfortunately, we've all found ourselves faced with that situation at one time or another.

Let's face it, in today's "high-technology" society, the electronic components that we very often need are becoming more and more difficult to obtain locally. Perhaps it is because the components that we are looking for are becoming more complex. Or, perhaps our local suppliers are finding it necessary to become more specialized. Whatever the reasons may be, understanding them won't help us when we're faced with the situation of trying to obtain a specific component.

As bad as the situation might seem, especially to those of us that are not living in or near a large metropolitan area, we are not totally helpless. Fortunately, there are a large number of mail-order firms that supply electronics components. While I'll admit that ordering an electronic component from a mail-order supplier is not as convenient as walking into your local supplier, at least the mail-order supplier is more likely to have a larger and more diversified inventory.

While the majority of the mail-order suppliers are quite reputable, not all of them are on the up and up. Screen the mail-order suppliers before you buy from them. First, if the ads appear month after month in **Radio-Electronics** magazine, you can be confident that they are reputable. Use the free information card at the back of the magazine to order catalogs from those suppliers and keep them handy. Catalogs are great for locating components that you need and they contain valuable ordering information when you're actually ready to order a component.

I can't possibly cover all the aspects of purchasing mail-order components in just one editorial page. The subject is important and we are presenting part 1 of a two-part series entitled "The Ins and Outs of Buying Mail-Order Components." Read the series and request as many catalogs as you can from the mail-order suppliers. They will be your best protection against being stuck for hard-to-find components in the future.

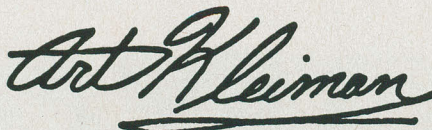

ART KLEIMAN
Editor

Radio- Electronics

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, editor

Josef Bernard, K2HUF, technical editor

Carl Laron, WB2SLR, assistant editor

Jack Darr, CET, service editor

Robert F. Scott, semiconductor editor

Herb Friedman, communications editor

Gary H. Arlen, contributing editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Ruby M. Yee, production manager

Robert A. W. Lowndes, production
associate

Stefanie A. Mas, production assistant

Joan Roman, circulation director

Arline R. Fishman,
advertising coordinator

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
President: M. Harvey Gernsback
Vice President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler
Publisher

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
212-777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co., Inc.
540 Frontage Road—Suite 325
Northfield, Illinois 60093
312-446-1444

PACIFIC COAST Mountain States

Marvin Green
Radio-Electronics
413 So. La Brea Ave.
Los Angeles, Ca 90036
213-938-0166-7

SOUTHEAST

Paul McGinnis
Paul McGinnis Company
60 East 42nd Street
New York, N.Y. 10017
212-490-1021



NEW! Here's a professional, portable DC-20 MHz Oscilloscope with build-it-yourself Heathkit savings



Compact enough to fit under an airplane seat, the Heathkit IO-3220 represents outstanding value in its class. Weighing only 16 pounds, the IO-3220 is designed for field service troubleshooters who need a light, portable battery-operated scope for use where AC power is not available.

Dual-trace versatility: The IO-3220 allows you to compare two different signals simultaneously – to make input/output comparisons, check phase relationships and accomplish other complex measurements. Algebraic functions add versatility.

Special invert display function: Enables you to compare two waveforms that are nearly 180 degrees out of phase – by inverting one of the waveforms.

FREE CATALOG

Complete details on Heathkit oscilloscopes – and nearly 400 other electronic kits for your home, work or pleasure – are in the new Heathkit catalog. Send the coupon at right for yours today, or pick one up at any of the 65 convenient Heathkit Electronic Centers** located throughout the U.S. and Canada. If coupon is missing, write Heath Co., Dept. 020-934, Benton Harbor, MI 49022.



Heathkit®

*Mail Order, F.O.B. Benton Harbor, MI. Also available assembled, mail order priced at \$995.00, F.O.B. Prices, specifications and product availability subject to change without notice. **See the white pages of your telephone book for the Heathkit Electronic Center nearest you. Heathkit Electronic Centers in the U.S. are operated by Veritechnology Electronics Corporation, a wholly-owned subsidiary of Zenith Radio Corporation. GX-387

X-Y inputs for Lissajous measurements: Feed two separate input signals to the IO-3220.

Wide DC-20 MHz bandwidth: The IO-3220 can measure a very wide range of input signals.

Outstanding sensitivity: Vertical signals as low as 2 millivolts can be accurately measured by the very sensitive IO-3220. Accuracy is as

high as 3 percent (from 20-30 deg. C), on both vertical and horizontal measurements.

Save more than 30% when you build it yourself: The IO-3220 Portable 20 MHz Oscilloscope Kit is value-priced at just \$689.95*.

Easy to build: Thorough Heathkit assembly manuals take you step-by-step, from unpacking to final plug-in. Anyone can do it. And experienced service techs are just a phone call away, to help you during building or servicing.

**MAIL TO: Heath Company, Dept. 020-934
Benton Harbor, MI 49022**

☐ YES, Please send me your free Heathkit Catalog.
I'm not currently receiving your catalog.


Name _____

Address _____

City _____ State _____

GX-387 Zip _____

ZX81

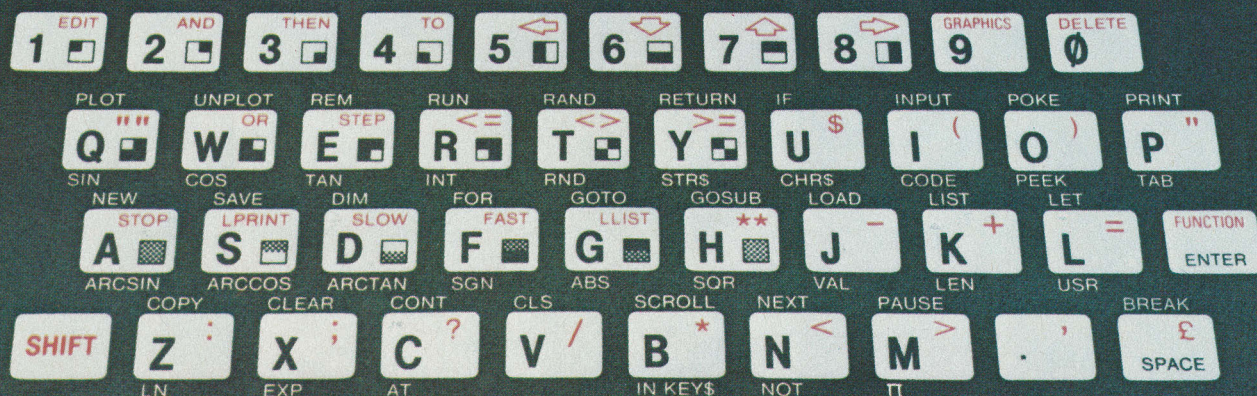

Introducing the Sinclair ZX81.

If you're ever going to buy a personal computer, now is the time to do it.

The Sinclair ZX81 is the most powerful, yet easy-to-use computer ever offered for anywhere near the price: only \$99.95* completely assembled.

Don't let the price fool you. The ZX81 has just about everything you could ask for in a personal computer.

A breakthrough in personal computers.

The ZX81 is a major advance over the original Sinclair ZX80—the first personal computer to break the price barrier at \$200.

In fact, the ZX81's 8K extended BASIC offers features found only on computers costing two or three times as much.

Just look at what you get:

- Continuous display, including moving graphics

THE \$99.95 PERSONAL COMPUTER.

- Multi-dimensional string and numerical arrays
- Mathematical and scientific functions accurate to 8 decimal places
- Unique one-touch entry of key words like PRINT, RUN and LIST
- Automatic syntax error detection and easy editing
- Randomize function

useful for both games and serious applications

- 1K of memory expandable to 16K
- A comprehensive programming guide and operating manual

The ZX81 is also very convenient to use. It hooks up to any television set to produce a clear 32-column by 24-line display. It comes with a comprehensive programming guide and operating manual designed for both beginners and experienced computer users. And you can use a regular cassette recorder to store and recall programs by name.

Order at no risk.**

We'll give you 10 days to try out the ZX81. If you're not completely satisfied, just return it to Sinclair Research and we'll give you a full refund.

And if you have a problem with your ZX81, send it to Sinclair Research within 90 days and we'll repair or replace it at no charge.

Introducing the ZX81 kit.

If you really want to save money, and you enjoy building electronic kits, you can order the ZX81 in kit form for the incredible price of just \$79.95.* It's the same, full-featured computer, only you put it together yourself. We'll send complete, easy-to-follow instructions on how you can assemble your ZX81 in just a few hours. All you have to supply is the soldering iron.

A leader in microelectronics.

The ZX81 represents the latest technology in microelectronics. More than 10,000 are sold every week. In fact, the ZX81 is the fastest selling personal computer in the world.

We urge you to place your order for the ZX81 today.

To order.

To order, simply call toll free. Or use the coupon below. Remember, you can try it for 10 days at no risk.** The sooner you order, the sooner you can start enjoying your own computer.


Call toll free 800-543-3000.

Ask for operator #509.
In Ohio call: 800-582-1364;
in Canada call: 513-729-4300.
Ask for operator #509. Phones open 24 hours a day, 7 days a week. Have your MasterCard or VISA ready.

These numbers are for orders only. If you just want information, please write: Sinclair Research Ltd., 2 Sinclair Plaza, Nashua, NH 03061.

*Plus shipping and handling. Price includes connectors for TV and cassette, AC adaptor, and FREE manual.

**Does not apply to ZX81 kits.

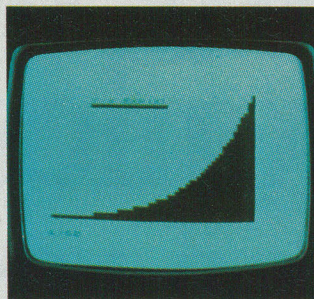

NEW SOFTWARE: Sinclair has published pre-recorded programs on cassettes for your ZX81. We're constantly coming out with new programs, so we'll send you our latest software catalog with your computer.



16K MEMORY MODULE: Like any powerful, full fledged computer, the ZX81 is expandable. Sinclair's 16K memory module plugs right onto the back of your ZX81. Cost is \$49.95, plus shipping and handling.

sinclair

To order call toll free: 800-543-3000

Ad Code 09RE	Price*	Qty.	Amount
ZX81	\$99.95		
ZX81 Kit	79.95		
16K Memory Module	49.95		
Shipping and Handling	4.95		\$4.95
TOTAL			

MAIL TO: Sinclair Research Ltd.,
One Sinclair Plaza, Nashua, NH 03061.

Name _____

Address _____

City _____ State _____ Zip _____

*U.S. dollars



If you have put off learning more electronics for any of these reasons, act now!

- ☐ I don't have the time.
- ☐ High school was hard for me and electronics sounds like it may be hard to learn.
- ☐ I can't afford any more education.
- ☐ I have a family now.
- ☐ I'm here. You're there. I've never learned that way before. I'm not sure it will work for me.

Be honest with yourself. Are the reasons really excuses? You already know enough about electronics to be interested in reading this magazine. So why not learn more? If you need encouragement, read on and see how excuses can be turned into results.

You don't have the time. Be realistic. All you have in life is a period of time. Use it. Try to know more tomorrow than you do today. That's the proven way to success. CIE studies require just about 12 hours of your time a week, two hours a day. You probably do have the time.

Electronics sounds like it may be hard to learn. You already know something about electronics or you wouldn't be reading this. Now, build on that. CIE Auto-Programmed® Lessons help you learn. Topics are presented in simple, logical sequence. All text is clear and concise for quick, easy understanding. You learn step by step, at your own pace. No classes to attend. Nobody pressures you. You can learn.


You can't afford any more education. Actually, you can't afford NOT to gain the skills that can put you ahead of the others. You know what inflation is doing to you now. Education—learning a skill—is an inflation-fighter that can be yours. If you are not able to pay full tuition now, CIE will lend you funds on a monthly payment plan.

You have a family now. All the more reason why you have the responsibility to advance yourself. For the sake of your family. Do you want them to have what you had or have more than you had? The choice is yours. Electronics is a rewarding career choice. CIE can help you to get started on that career.

You're there. We're here. How does CIE help you learn? First, we want you to succeed. You may study at home, but you are not alone. When you have a question about a lesson, a postage stamp gets you your answer fast. You may find this even better than having a classroom teacher. CIE understands people need to learn at their own pace. When CIE receives your completed lesson before noon any day of the week, it will be graded and mailed back the same day with appropriate instructional help. Your satisfaction with your progress comes by return mail. That's how CIE helps you learn.


NOW, IF YOU AGREE CIE TRAINING CAN WORK FOR YOU, HOW ELSE CAN CIE HELP YOU?

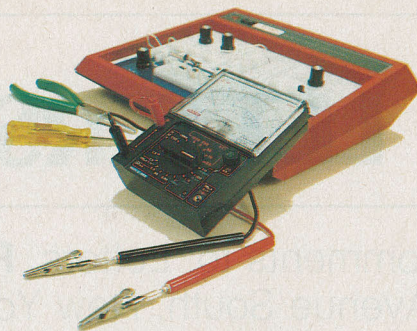Cleveland Institute of Electronics is the largest independent home study school in the world that specializes exclusively in electronics. Although "big" does not always mean "best," it is evidence that CIE is a strong, successful institution with the people and resources to help you succeed.



Step-by-step learning includes "hands-on" training.

The kind of professional you want to be needs more than theory. That's why some of our courses include the Personal Training Laboratory, which helps you put lesson theory into actual practice. Other courses train you to use tools of the trade such as a 5MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a Digital Learning Laboratory to let you apply the digital theory that's essential today for anyone who wants to keep pace with electronics in the eighties.

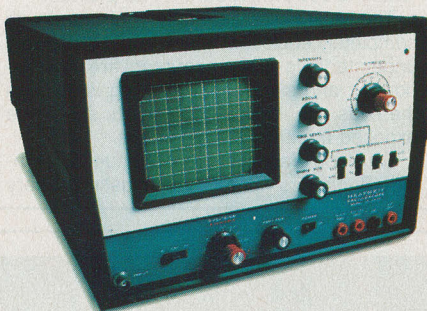

Your FCC License can impress employers.

For some electronics jobs, you must have your FCC License. For others, employers usually consider it a mark in your favor. Either way, your License is government-certified proof of your knowledge and skills. More than half of CIE's courses prepare you to pass this exam. Surveys show that some 80% of CIE graduates who take the exam are successful.

Find out more! Today. Now.

There's a card with this ad. Fill it in and return. If some other ambitious person has already removed it, use the coupon.

You'll get a copy of CIE's free school catalog, along with a complete package of personal home study information.

For your convenience, we'll try to arrange for a CIE representative to contact you to answer any questions you may have.

If you are serious about a rewarding career, about learning electronics or building on your present skills, your best bet is to go with the electronics specialists—CIE. Mail the card or coupon today or write CIE (please mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.

This could be the best decision you've made all year.

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

"If you're going to learn electronics, you might as well learn it right!"

*John Cunningham
Senior Technical Director*



CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

☐ **YES...** I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program...plus my FREE package of home study information.

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill bulletin on Educational Benefits: ☐ Veteran ☐ Active Duty

MAIL TODAY!

RE-44

LETTERS

Address your comments to: Letters, **Radio-Electronics**,
200 Park Avenue South, New York, NY 10003

DATABASE MANAGEMENT SYSTEMS

I have just finished reading the June 1982 issue of **Radio-Electronics**. Your article on database management systems was an interesting summary of available products and vendors, but I should like to correct a few oversights.

First, Compco has had to move to a larger facility. I don't believe that the post office is forwarding our mail any longer (it's been a year), so I would appreciate having this letter published with our correct address. It is:

Compco, 7110 W. Fond Du Lac Avenue, Milwaukee, WI 53218. We can be reached by telephone through calling (414) 438-0610 or (414) 438-8611.

Secondly, Compco carries a wide variety of database management packages, for many different computers. Apple, Altos, and DEC are the principle lines. CP/M, MP/M, Apple

DOS 3.3, Apple CP/M, and RT-11 are the principal operating systems that our products run under. We also carry a variety of word processing, scientific, and entertainment software and hardware.

THOMAS M. PETERS,
Compco, Sales Manager

OPENING THE DOOR

What a wonderful "opening of the door" to the world of electronics the simple building blocks described in "Hobby Corner," in **Radio-Electronics**, June 1982 provide!

The beginner is generally confronted with completely enclosed "black boxes" that defy understanding. First encounters are most important; and since most learning is through the eyes, the inner working parts should be exposed by removing all covers.

Touching is another great avenue for learning. (Beginners will soon be adjusting battery

clips and switch tensions on their own.)


As learning progresses, open-type potentiometers and transformers with visible windings may be added. Also, the *name* of each component may be lettered simply on each block, along with its schematic symbol.

You cannot imagine how fast your youngster can learn, or how importantly those beginning blocks can shape his or her life!

GENE BRIZENDINE, W4ATE,
Huntsville, AL

DIGITAL THERMOMETER

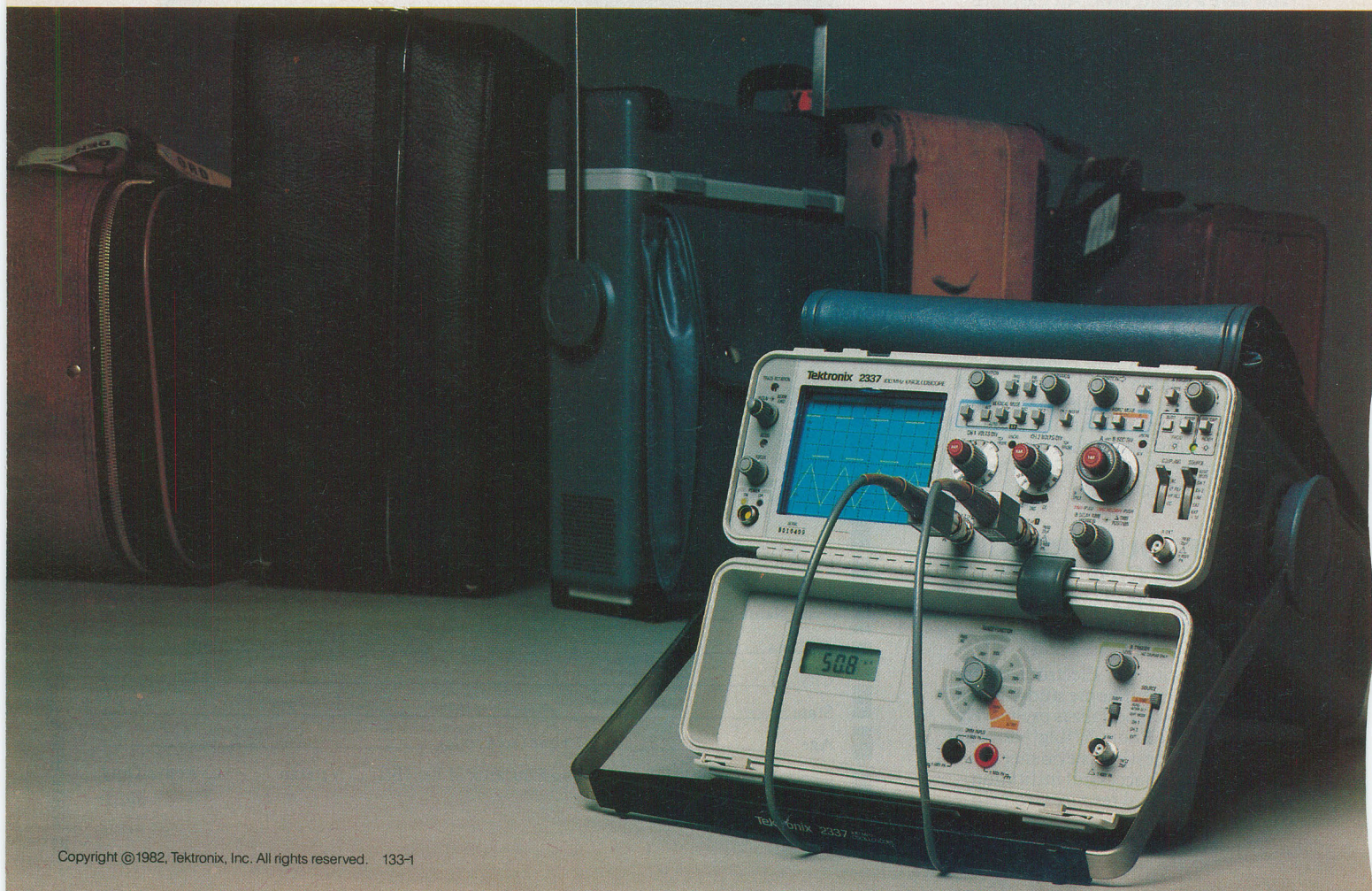This is an addition to the digital thermometer article by Michael Ribby that appeared in the February 1982 issue of **Radio-Electronics**. I have used this circuit on my MA1026 clock module to vary the brightness of the LED display automatically with changes in the room light. The circuit uses only three components, all of which are readi-



ly available, and I have had it in service for over a year.

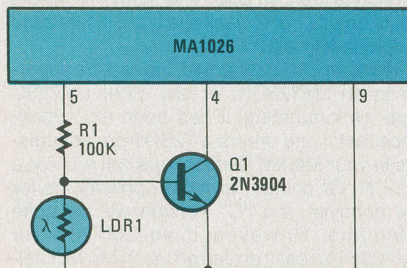


FIG. 1

Figure 1 tells the story. As the room light goes down, the resistance of LDR1 (Radio-Shack No. 276-116) increases. At a given point, determined by the value of R1, Q1 begins to conduct. That lowers the voltage on pin 4, and dims the display. Use any low-leakage transistor for Q1, with a gain (h_{fe}) of 100 or more. Select the value of R1 to get the desired dimming action, and remember that raising the value of R1 will slow the dimming action.

HERBERT DEAN,
Orono, ME

NIKOLA TESLA'S CONTRIBUTIONS

In your comment on Vince Marasco's letter about Nikola Tesla ("Letters," **Radio-Electronics**, June 1982) you pointed out that

Mr. Marasco had failed to list any of the principles relating to everyday things that nearly all of us now take for granted that Tesla discovered.

The list is impressive: First, there is the AC motor. It is doubtful that there are any motor-driven devices in the home that do *not* use an AC motor, rather than the older DC units. Air conditioners, refrigerators, fans—all are built on Tesla's principle that he developed for Westinghouse.

Add to that his discovery in 1890 of applying high-frequency electricity to the body for deep heat treatment. Diathermy, in other words.

Then there is the Tesla coil—an air core transformer with resonating primary and secondary coils. Such units are used to test the effects of high-frequency electricity on switches and regulating circuits in the utility industry.

Marconi's patents on radio were upset by the U.S. Supreme Court, which ruled that they were an infringement on another's idea—Tesla. Robots, radar, and radio-controlled ships for military use, as well as the basic idea for a plane with vertical take-off and landing capabilities give you some idea—though really far from adequate—of the scope of that man's creative genius.

To anyone interested in Nikola Tesla, I recommend Margaret Cheney's book, an excellent biography titled, *Tesla, Man Out of Time*. In spite of one or two technical faults, it is worth reading; you will understand why there are so many who rate Edison second to Tesla, without denying the worth of Edison's contributions.

GEORGE deLUCENAY LEON,
New York, NY

SPEAKING OUT

I can keep silent no longer!

I'm an electronics buff, and have been receiving **Radio-Electronics** for about a year. I am also currently subscribing to a number of other somewhat similar magazines, but have decided that the only ones to which I shall renew my subscription are **Radio-Electronics** and *The Audio Amateur*.

I consider **Radio-Electronics** to be by far the best electronics magazine on the market at the present time, and look forward to receiving it each month. I cannot recommend it too highly!

To date, I have built eight of the construction projects that you have published. They were easy to complete, and all function as intended. I would like to compliment you on the clarity and completeness of your projects—such that one does not need a high degree of electronics theory or expertise to build them, nor run into difficulty because of exotic or highly expensive components. I also applaud the fact that, to date, you have resisted the temptation to make **Radio-Electronics** into a computer magazine; there are a plethora of those available. Please continue your emphasis on construction electronics with a broad-base appeal.

PAUL T. KELLY,
Fort Wayne, IN

POCKET CALIBRATOR

Gary McClellan's statement that the LM723N voltage regulator has more stable temperature characteristics than the LM723C ("Pocket Calibrator for Volts and Ohms," **Radio-Electronics**, June 1982) is

TEK 2300 SERIES
PORTABLE OSCILLOSCOPES

THE FIELD
SERVICE SCOPES

Built for field service. Tough enough for the road.

The 2300 Series is unassailable proof that sensitive instruments needn't be delicate. No other scopes are so immune to abuse and to day-to-day wear and tear. They feature 50Gs shock resistance, our highest electromagnetic compatibility, and high-performance

measurement—all in an ultra-durable 17-lb. package.

Bottom line: the lowest life cycle costs of any high performance portable. Thanks to fewer components. Easier access to internal parts. Plus less downtime and fewer back-up instruments re-

quired, as proven by the toughest reliability testing we know of—our own.

All that, and Tek performance too! Select dc to 100 MHz with 5 ns horizontal sweep. 2mV/div vertical sensitivity. Built-in delta time and DMM.


This time, get the scopes

that can handle the hard knocks of your business ... wherever the business takes you. Order today—or ask for the full Tek 2300 story! Call toll free:

1-800-547-1845

Ask for Department B0129 (Oregon, Alaska and Hawaii: 503-627-5402 Call collect.)

Tektronix®
COMMITTED TO EXCELLENCE

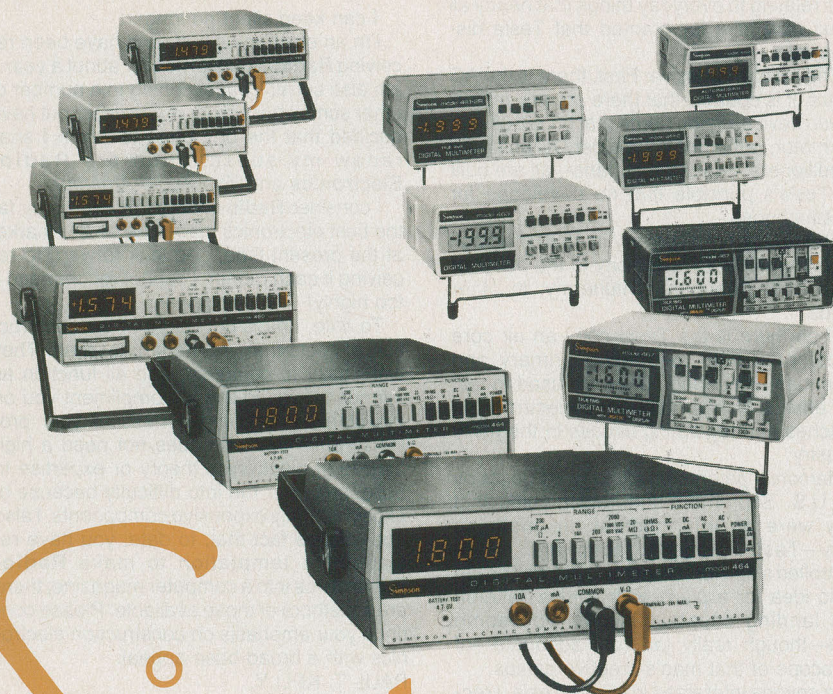

Simpson®

Lets you select from 12 Safety Listed DMMs



Only Simpson offers a full line of DMMs that are listed under UL-1244 Standard for Safety — Electrical and Electronic Measuring and Testing Equipment.

SIMPSON DIGITAL MULTIMETER SELECTION CHART

	Hand portable DMMs All 2x5.6x4.6", weight 1½ lbs.					Bench portable DMMs All 2.7x8.4x9", weight 3 lbs.		
Model	467/467B#	463	461-2	461-2R	462	464-2A/2D*	465-2A/2D*	460-4A/4D*
Features	Deluxe unit with true RMS, pulse detection, differential peak hold, visual/audible continuity indication. #Black case	Basic low cost cordless unit	Low cost basic unit	True RMS responding	Auto and manual ranging	Low cost bench DMM with 10 amp range	Auto and manual ranging, 10 amp range	Deluxe unit. Low power ohms, aux. analog meter, 10 amp range
Ranges	26	26	26	26	23	28	27	32
Display (3½ digit)	LCD Digalog® display	LCD	LED	LED	LED	LED	LED	LED
Basic Accuracy	0.1%	0.1%	0.1%	0.1%	0.25%	0.1%	0.1%	0.1%
Power Source	9 V battery supplied, 200-hour battery life		Rechargeable batteries and AC adapter/charger supplied			AC operation standard. *AC/battery version optional (batteries not included)		
Price	\$257	\$200	\$194	\$234	\$244	\$290/*\$338	\$403/*\$453	\$378/*\$431

Choose the one that's best for you! Available at leading electrical/electronics distributors worldwide.



SIMPSON ELECTRIC COMPANY
A Katy Industries Subsidiary

853 Dundee Avenue, Elgin, IL 60120
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO
IN CANADA: Bach-Simpson Ltd., London, Ontario
IN ENGLAND: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

CIRCLE 21 ON FREE INFORMATION CARD

open to misinterpretation. The premium device is the LM723. The relaxed-specifications version is the LM723C. The suffix "N" refers not to quality but to package type, in this case a dual-in-line plastic one.

Thus, an LM723N would, indeed, be superior to an LM723CN, or any other LM723C type. Unfortunately, it has been my experience that if one orders a 723N from advertisers in your Market Section, one will receive a 723CN. Of course, in most applications for the hobbyist, the "C" version will be quite adequate. However, if an LM723N (or LM723H) is really preferred, as in Mr. McClellan's nice little project your readers may have to order it from one of the major electronics parts distributors.

LAWRENCE WALLCAVE,
Santa Rosa, CA

THE IBM COMPUTER

I have just finished reading your April 1982 issue, and noticed an article about IBM's first personal computer. In 1975, IBM was testing a rather heavy portable computer that was configured much like the Osborne 1. It had a non-removable keyboard, a small (perhaps 5 × 6-inch) monitor screen, and used data cassettes for loading. It was, I believe, the brainchild of Dick Doyle.

Time and time again, we see IBM showing all the youthful vigor of a tortoise, and, in personal-computer hardware, they've shown it again. I think that's a shame, because I like them.

JESSE THARIN,
Tucson, AZ

R-E

ATTENTION SINCLAIR ZX81 OWNERS!!!

Here's an inexpensive little book (Programming With The ZX81) that tells you how to use the features of that ZX81 you recently bought. It shows you programs that fit into the 1K machine and are still fun to use. Learn how the random number generator works and use it to simulate coin tossing and dice throwing. Look at the patterns the ZX81 graphics can produce. Animated graphics are also covered and complete programs for games such as Lunar Lander and Cannon Ball are included. Seven information packed chapters in this quality book. Order your copy today. Price is \$5.75 post-paid in the US.

ELECTRONIC TECHNOLOGY TODAY INC.

9/82

P.O. Box 83, Massapequa Park, NY 11762

☐ Send me my copy of "Programming With The ZX81"

☐ Send me your complete catalog

Price of Book including Postage \$5.75

NY State Residents include Sales Tax

TOTAL ENCLOSED

Name

Address

City

State

Zip

THIS DEVICE MAKES ORDINARY TELEPHONES OBSOLETE.



Actual size.
(1" x 5½" x 2¾")

The Freedom Phone® Cordless Telephone Model FF-3500 has more features than any ordinary telephone. But one ordinary feature is missing.

There's no cord to tie you down. The compact handset measures 1" x 5½" x 2¾" and weighs just 7 ounces. So it's really easy to take or make calls anywhere within its operational range. That's upstairs, downstairs, in the front yard, backyard, at the neighbors, up the street, or down the block.

Instead of going to the phone to talk, you take the phone with you.

Buying a Freedom Phone Cordless Telephone is an intelligent move if you prefer the convenient over the conventional. But there's more to it than meets the eye or ear.

Designed and built exclusively for the Electra Company, makers of Bearcat® Scanners, the Freedom Phone 3500 provides crisp and clear cordless calls. An audible tone and pulsing light confirm dialing. The touch of a button automatically redials the last number entered.

The Freedom Phone Cordless Telephone is as easy to install as it is to use. Its attractive and compact base station plugs into your existing phone line and electrical outlet.

If the idea of using a Freedom Phone Cordless Telephone has a nice ring to it, get up, walk to your obsolete telephone, and call 800-428-4315 (800-382-1076 in Indiana). You'll learn more about the Model FF-3500 and get the name of the nearest Freedom Phone Dealer.

THE FREEDOM PHONE® CORDLESS TELEPHONE.

Electra Electra Company


Division of Masco Corp. of Indiana • 300 East County Line Road • Cumberland, Indiana 46229 • International Business Office • Suite 102, 1828 Swift • North Kansas City, Missouri 64116

© 1981 Masco Corp. of Indiana

CIRCLE 19 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

Sencore Model SC61 Waveform Analyzer

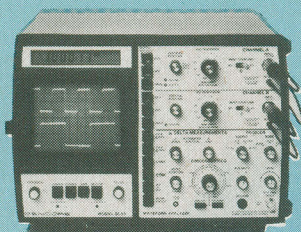

CIRCLE 106 ON FREE INFORMATION CARD

Sencore	model SC61									
OVERALL PRICE										
EASE OF USE										
INSTRUCTION MANUAL										
PRICE/VALUE										
	1	2	3	4	5	6	7	8	9	10
	Poor		Fair		Good		Excellent			

FOR QUITE A FEW YEARS NOW, SENCORE (3200 Sencore Drive, Sioux Falls, SD 57107) has been manufacturing "analyzers"—composite instruments that

are useful for a wide variety of electronics testing and measuring. One of their newest products is the *model SC61* waveform analyzer. Whether you're working with

analog or digital circuitry, you'll find a great many applications for this device no matter what kind of electronics work you do. It is really a quite versatile instrument, as you'll soon see.

The *model SC61* has two main sections. One is a dual-trace scope that can be used with waveforms of up to 100 MHz and voltages from 2 millivolts to 2 kilovolts. The unit's wide bandwidth (60 MHz), which is useable right up to the upper frequency limit, can come in very handy when working with high-speed digital circuitry. All of the standard features are there, including triggered sweep, a special delayed sweep mode called the delta mode (more on that later), and sync separators. The other section of this instrument is a built-in digital voltmeter with a 6-digit LCD display. The DVM display, incidently, is located right across

continued on page 30

137 new RCA flameproof metal resistors.


Now . . . 780 Types For More Applications

With values from 0.1 ohm to 22 megohms, RCA Flameproof Metal Resistors cover the great majority of resistor replacement needs in TV, video, and industrial servicing.

- Can replace composition, carbon film, wire-wound and other metal types.
- Tolerance ratings of $\pm 2\%$ on most values. Ratings of $\frac{1}{4}$, $\frac{1}{2}$, 1 and 2 watts.

Get your RCA Flameproof Metal Resistors in convenient, colorful packages from your RCA Distributor today. Or, for further information, write: RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, N.J. 08096. Attn: Sales Promotion Services.

RCA Flameproof
Metal Resistors

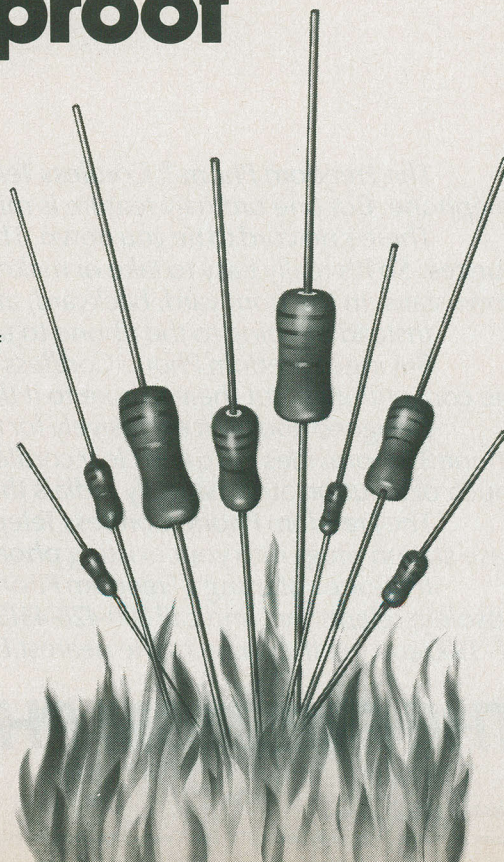

Your guide to the world of microprocessors.

The Micro-Professor™ -A low cost tool for learning, teaching and prototyping.

Here in one attractive package and at a price of only \$149.00 is a Z80* based microcomputer to lead you step by step to a thorough knowledge of the world of microprocessors.

The Micro-Professor is a complete hardware and software system whose extensive teaching

manual gives you detailed schematics and examples of program code. A superb learning tool for students, hobbyists and microprocessor enthusiasts, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

But the Micro-Professor is much more than a teaching device. With it you can do breadboarding and prototyping, designing your own custom hardware and software applications with Z80, 8080 and 8085 compatible code.

The standard 2K bytes of RAM is expandable to 4K, and the standard 2K bytes of ROM can be increased to 8K.


All this plus a built-in speaker, a cassette interface, and

sockets to accept optional CTC/PIO. Bus is extendable.

As well as being an exciting learning tool, the Micro-Professor is a great low-cost board for OEM's. Call for details.


SSB-MPF Speech Synthesizer Board \$129

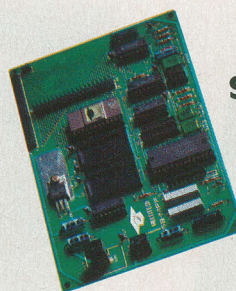A vocabulary of up to 400 words based on the TMS 5200 chip.



EPB-MPF EPROM Programming Board \$169

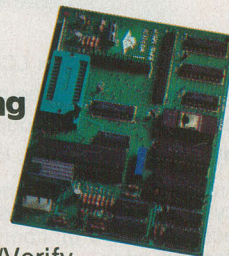For all +5V 1KB/2KB/4KB EPROMs. Read/Copy/List/Verify Capability.



BASIC-MPF Tiny Basic \$19

2KB BASIC interpreter with hardware control capability. Machine-code subroutine accessible.

I'm ready to enter the world of microprocessing

Call toll free to order.

	Price	Qty.	Amount
MPF-I Micro-Professor	\$149.00		
SSB-MPF Speech Synthesizer Board	\$129.00		
EPB-MPF EPROM Programming Board	\$169.00		
BASIC-MPF	\$ 19.00		
Shipping and Handling	\$ 4.95		4.95
California residents add sales tax.			
TOTAL			

In U.S. and Canada mail to:


Multitech Electronics Inc.
195 West El Camino Real
Sunnyvale, CA 94086
California Tel. (408) 773-8400
Elsewhere (800) 538-1542

Outside of North America mail to:


Multitech Industrial Corporation
977 Min Shen E Road, 105
Taipei, Taiwan, ROC
Tel. 02-769-1225
TWX 19162 MULTIC,
23756 MULTIC



Multitech Electronics Inc.

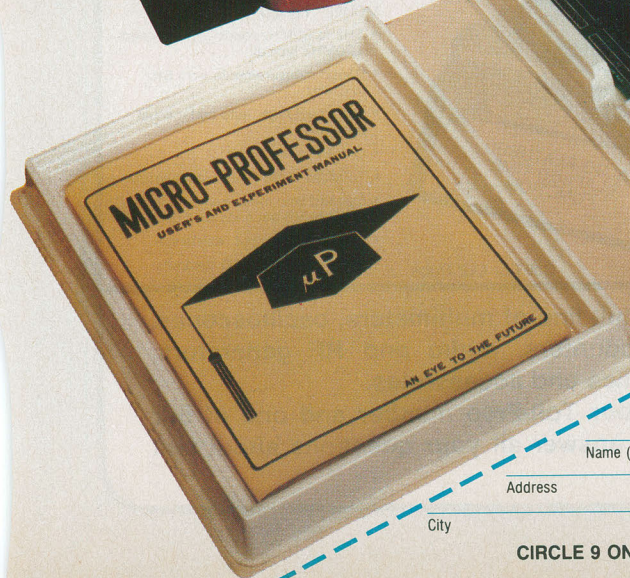

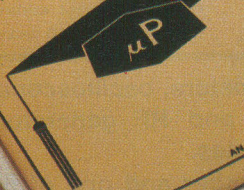MICRO-PROFESSOR
USER'S AND EXPERIMENT MANUAL



AN EYE TO THE FUTURE

☐ Check or money
order enclosed
☐ Visa ☐ Mastercharge

Card No. Expires

Signature

Name (Please Print)

Address

City

State

Zip

CIRCLE 9 ON FREE INFORMATION CARD

* Z80 is a trademark of Zilog Inc.



PHILIPS



TRIPLETT

LEADER



Non-Linear Systems

KEITHLEY

FLUKE[®] DIGITAL MULTIMETERS

- Two New 4½-Digit Handheld DMM's from Fluke
- Wideband True RMS AC Measurements (100 kHz-8060A, 30 kHz-8062A)
- 0.04% Basic DC Accuracy (8062A = 0.05%)
- Full Range Capability (200 μ A, 200 mV, 200 Ω ranges)
- Autoranging M Ω to 300 M Ω
- Relative (Offset or Zero) Mode
- Audible and Visual Continuity Indicators
- Frequency Measurement to 200 kHz, 0.01 Hz Resolution to 200 Hz, 1 Second Response Time (8060A only)
- dBm Referenced to 600 Ω (8060A only)
- Relative dB measurement (8060A only)
- Conductance (8060A only)
- Separate Constant Current Source Diode Test
- Self Diagnostics

\$349.

8060A

\$279.

8062A



Display: 4½ digit duplex LCD (19,999 count)

A/D Converter: Dual slope converter, autozero, autopolarity.

Conversion: TRMS, AC coupled


Display Annunciators: BT, low battery indication.

REL, relative reference mode activated. [8060A: (k)Hz, frequency function activated. dB, dB function activated.] —> continuity activated.)), continuity tone activated.—, continuity detected indicator.

Temperature: 0° to +50°C operating, -35° to +60°C storage.

Temperature Coefficient: (0° to +18°C or +28° to +50°C)° .1 times the applicable accuracy specification per degree C plus the initial +18° to +28° specification.

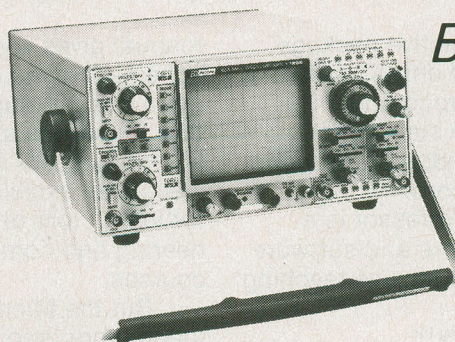THESE 1983 B&K OSCILLOSCOPES ARE IN STOCK AND AVAILABLE FOR IMMEDIATE DELIVERY



BK PRECISION

1590 1500 Dual Trace Dual Time Base 100MHz
1570 Dual Trace Dual Time Base 70MHz

1525 1530 1535 Delayed Trigger Scopes
1466 1476 1477 1479 High Performance Scopes

CALL FOR OUR SPECIAL DEAL ON B&K SCOPES

New Low Distortion Function Generator

BK PRECISION



Call For Our Price

MODEL 3010

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL square-wave outputs
- 0.1 Hz to 1 MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1 Hz to 100kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests

80MHz Counter with Period Function



BK PRECISION

Call For Our Price

MODEL 1820

- 5Hz to 80MHz reading guaranteed—100MHz typical
- Period measurements from 5Hz to 1MHz.
- Period average, auto and manual positions
- One PPM resolution
- Totalizes to 999999 plus overflow
- Elapsed time measurements from .01 to 9999.99 seconds plus overflow
- One-megohm input resistance
- Bright .43" high LED readouts

DATA PRECISION Model 938 0.1%, 3½-Digit, LCD DIGITAL CAPACITANCE METER




\$219

- **WIDE RANGING** — from 199.9 pF full scale (0.1 pF resolution) up to 1999 μ F full scale, in eight ranges...virtually every capacitance you'll ever need to measure.
- **FAST AND EASY TO USE** — Direct reading, pushbutton ranges. Just plug in and read.
- **EXCEPTIONALLY ACCURATE** — provides $\pm 0.1\%$ basic accuracy.
- **TOUGH AND COMPACT** — Built to take rough usage without loss of calibration accuracy. Fits and goes anywhere; takes very little bench space; always handy for quick capacitance checkout, matching, calibration, and tracking.
- **PORTABLE** — Palm-sized, light-weight, operates up to approximately 200 hours on a single 9V alkaline battery.
- **EASY READING** — big, clear, high-contrast 3½-digit LCD display, a full 0.5" high, readable anywhere.
- **VALUE PACKED** — Outstanding measurement capability and dependability. Outperforms DC time-constant meters, and even bridges costing 2 to 5 times as much.
- **RELIABLE** — warranted for 2 full years.

We carry a full line of multimeters, oscilloscopes, frequency counters, audio and RF generators, power supplies and accessories.

Just call our Toll-Free number and one of our experts will answer all your questions about test equipment.

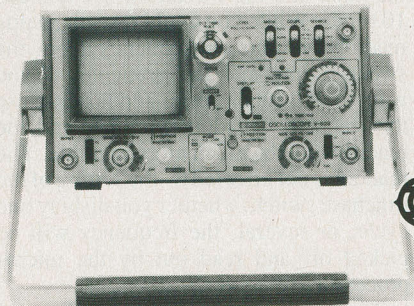
BK PRECISION**HITACHI****FLUKE****VIZ** formerly **ROA****HICKOK****DATA PRECISION****DORIC**

**NEW —
NOW
AVAILABLE**

HITACHI

V209 20 MHz, Dual Trace, Portable,
Complete with built-in Battery Pack.

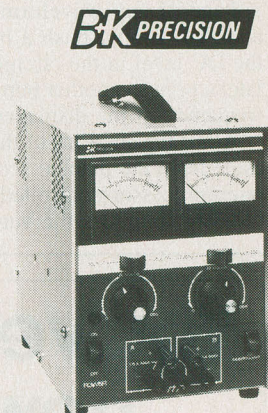V509 50 MHz, Dual Trace, Dual
Time Base, Portable (Battery pack
optional).



**FULL LINE OF THE NEW
B&K POWER SUPPLIES.
CALL FOR OUR PRICES.**

HITACHI

SAVE UP TO \$800

V-151B 15 MHz Single Trace
V-152B 15 MHz Dual Trace
V-202 20 MHz Dual Trace
V-301 30 MHz Single Trace
V-302B 30 MHz Dual Trace
V-352 35 MHz Dual Trace
V-550B 50 MHz Dual Trace,
Dual Time Base
V-1050 100 MHz Dual Trace,
Dual Time Base



**Call For
Special
REBATE OFFER**

**PORTABLE
OSCILLOSCOPES
BATTERY OPERATED**



Non-Linear Systems


Call For Our Prices

MS-15




Single Trace 15MHz

MS-215

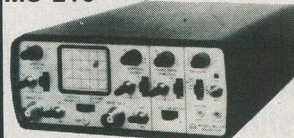

Dual Trace 15 MHz

MS-230

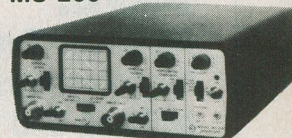


Dual Trace 30MHz

KEITHLEY

**Model 169
BENCH/PORTABLE DMM**

- 3½ Digit liquid crystal display
- 0.25% basic accuracy
- 26 Ranges

\$189.00

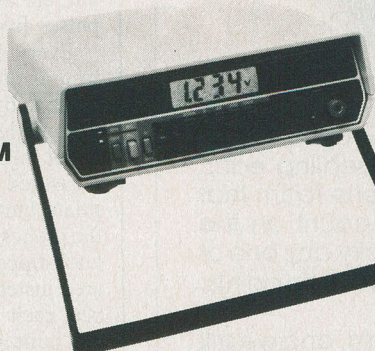

New Sweep/Function Generator

BK PRECISION

MODEL 3020

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs



Call For Our Price

- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel or externally programmable



**TOLL FREE HOT LINE
800-223-0474**

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

THE TEST EQUIPMENT SPECIALISTS

**ADVANCE
ELECTRONICS**

EQUIPMENT REPORTS

continued from page 26

the top of the scope screen for easy reading. Pushbuttons are used for ease of operation. You can read the peak-to-peak voltage of any waveform on the screen and then simply push a button and read the DC level in the circuit (more on that later), or push another button and read the frequency of the displayed signal.

All of the circuitry of the model SC61, aside from the manual scope controls, is microprocessor-controlled. That microprocessor monitors the vertical and hori-

zontal circuits at all times; to make any kind of measurement, just push a button and the microprocessor does the rest. It controls the digital readout, and also "lights" one of the 12 display annunciators that tell you what you're reading, and where (which channel). The decimal point is automatically set for all ranges and functions.

Getting back to the scope, the TIME-BASE-FREQ switch controls the horizontal sweep. That switch has 19 calibrated ranges. Those are set up in the usual 1-2-5 sequence and range from 0.1 microsecond to 100 milliseconds; a frequency scale is also provided. That switch is also used to place the unit in the video-preset


mode that is used to analyze video signals. In the video-preset mode, pushing one of two buttons will display either two vertical fields or two horizontal lines. The sync here is very steady due to the use of special sync-separators. The horizontal position control positions the trace; pull the knob and the waveform is expanded 10 times. While you could take an analog reading of time or frequency from the sweep-setting and the graticule, if you want to, it is much easier and faster to use the frequency readout for that, and the readings will be much more accurate. The readout is not affected by the setting of the timebase switch; whether you display one cycle, or several, the frequency will be picked off and read out by the microprocessor.

The sweep trigger circuits can be used on either channel, the AC line, or external trigger. A LEVEL control selects triggering on either positive- or negative-going edges of the displayed signal. When analyzing video signals, the peak-to-peak voltage of either horizontal or vertical waveforms can be measured by adjusting the LEVEL control. One thing that can cause problems in horizontal waveforms is the presence of some of the vertical sync; that also can be eliminated by adjusting the LEVEL control. The presence of the vertical sync can confuse the microprocessor, which will throw the peak-to-peak voltage readings off.

The unit has special sync-separator circuitry that helps in eliminating that confusion. That circuitry triggers on the vertical or horizontal pulses present in almost all TV signals. However, the manual mentions that if you're trying to read the output of a stage like the color-bandpass amplifier, where sync pulses are removed by the filtering action of the circuits, you may have instability. To eliminate that problem, simply hook the probe of the other channel to some point that does have sync, such as the video-detector output, etc. Now, trigger the sweep with the pulses from that channel.

Every one of the tests mentioned, as well as others we'll look at later on, can be done by just hooking up a probe and a ground lead. When that is done, just about anything about the circuit can be measured simply by pushing the appropriate buttons. Incidentally, while two of the probes supplied look like the standard hook-tipped probes, they are not. They are, instead, 10:1 low-capacitance probes; each has a special "separator" circuit built into it. That circuit lets you read waveforms and DC voltages at the same time! A separate, isolated, DC connector on the probe is plugged into a jack labeled DCV. The DC component is picked off by that separator circuit before the scope input and fed to the microprocessor, which does the rest. Because of that, both the reading displayed on the meter and the trace displayed on the scope are correct.

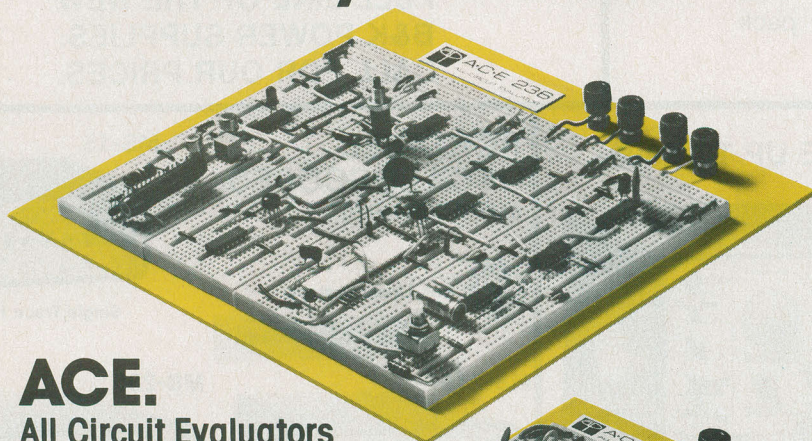You've seen the rest... now try the best.



ACE.

All Circuit Evaluators for solderless circuit building and testing.

A P made the first solderless breadboard way back in 1968, and we still make them best. Because our experience taught us to avoid the pitfalls that can mean circuit errors. We do it by paying attention to details. Like using noncorrosive nickel-silver in our frankly superior terminals. And like sealing each contact cell with an adhesive-coated polyethylene foam that prevents short circuiting. That's why you can count on the reliability of our solderless boards when you specify any one of the 7 different ACE models that offer from 728 to 3648 tie points, and 2 to 36 buses.

A P made the first modern solderless breadboard, and we still make the best.

Call Toll Free 800-321-9668 for the name of the distributor nearest you. In Ohio, call collect (216) 354-2101.



A P PRODUCTS INCORPORATED
9450 Pineneedle Drive
P.O. Box 603
Mentor, Ohio 44060
(216) 354-2101
TWX: 810-425-2250

In Europe, contact A P PRODUCTS GmbH Bäumlesweg 21 • D-7031 Weil 1 • W. Germany

INSTANT PC BOARDS


WITH

E-Z CIRCUIT™ Pressure-Sensitive
by **Bishop Graphics, Inc.**


COPPER DESIGN PRODUCTS!

NO Artwork! NO Photography! NO Screening! NO Etching!


And It's As Easy As 1...2...3...

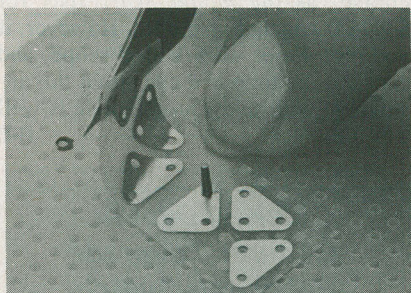

1. APPLY COPPER MTG. CONFIGURATIONS

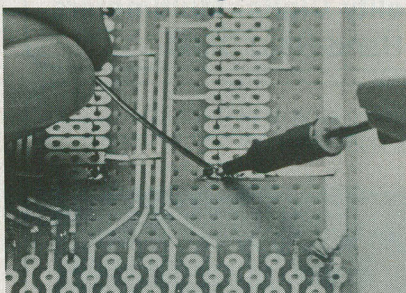

2. SOLDER COMPONENT CONNECTIONS

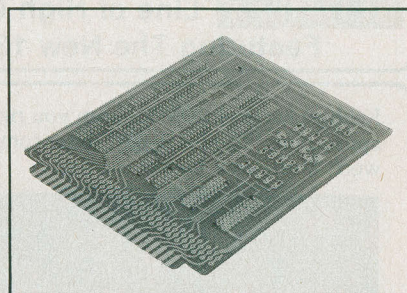

3. IT'S READY TO USE!



Now, thanks to this revolutionary new E-Z CIRCUIT concept, you can build professional quality printed circuit boards right in your own home or shop

- ... **without messy chemicals**
- ... **without artwork**
- ... **without photography**
- ... **without screening or etching**

Read What RADIO-ELECTRONICS Hobby Editor, "Doc" Savage Says About the E-Z CIRCUIT System!

"Those patterns are not for making artwork — they are *copper*. When you have pressed them down on a board, you are ready to mount the circuit components, solder them in place and turn on the power! *That* is what I call instant PC boards."

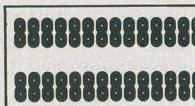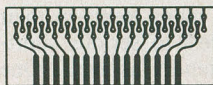"Having used this E-Z CIRCUIT system, I can report that it is quick, easy and reliable. It is the best way I have found to make one or two-of-a-kind PC boards."




The Secret? E-Z CIRCUIT's Unique Pressure-Sensitive COPPER Tapes & Patterns!

Each E-Z CIRCUIT copper mounting configuration is made of super-thin, epoxy

glass with a special two-phase, adhesive on one side, and a one-ounce copper pattern laminated on the other. When applied to your PC board, these copper patterns work like the circuitry on a conventional *etched* printed circuit board. You solder the components directly to them.

Make A Mistake? With E-Z CIRCUIT, You Won't Waste A Board!

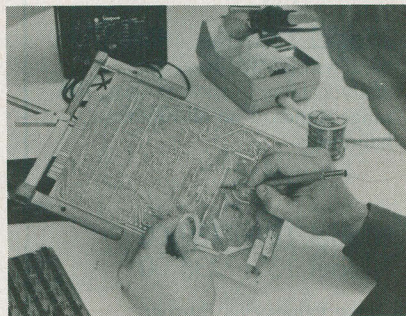Thanks to E-Z CIRCUIT's special, two-phase adhesive, you have — within the first few minutes — the opportunity to reposition the copper patterns and tapes to make corrections, modifications and improvements ... *without* harming the appearance and performance of your board.



Use Them For Repairing And Modifying Existing Circuitry, Too!

Besides creating an actual, professional functioning circuit board, you can use E-Z CIRCUIT Pressure-Sensitive Copper PC design products to repair or modify existing circuitry.

Unique E-Z CIRCUIT Technical Manual ... A "Gold Mine" of Usable, "How To" Information!

We even show you how easy it is. The new E-Z CIRCUIT PC Copper Products Technical Manual & Catalog EZ-3001 leads you through every step with fully illustrated instructions written in clear, simple language to make it easy for you to produce a professional quality, PC board. It's packed with invaluable technical "How To" information that tells you:

- **How to build a PC board**
- **How to repair damaged circuitry**
- **How to solder professionally**



Send For Your
FREE Copy Today To:

E-Z CIRCUIT™
by **Bishop Graphics, Inc.**

P.O. Box 5007RE Westlake Village, CA 91359

**Please send me a free copy of
E-Z CIRCUIT PC Copper Products
Technical Manual & Catalog EZ-3001**

Name _____
Street _____
City _____ State _____ Zip _____
(DEALER INQUIRIES WELCOME)

CIRCLE 10 ON FREE INFORMATION CARD

The scope settings, as we said before, do not affect the meter readings in any way. In addition to the 10:1 low-capacitance probes, the unit is also supplied with a direct-reading DC probe and a 48-inch-long ground lead.

Among the features that sets this unit apart is its special delayed sweep mode that is called the delta-measurement mode. That mode lets you measure the peak-to-peak voltage, frequency, or period of only the section of the waveform that you are interested in. It can be set for any portion of the waveform using the Δ BEGIN and the Δ END controls. Those controls position the beginning and end of a bright "bar" on the display. The part of

the waveform within the span of that bar is the only part that is measured when the scope is in the delta mode. Trigger controls work in the usual manner in that mode.

Among other things, the delta mode is useful for reading the frequency of only one cycle. If you have more than one frequency present, such as with a modulated waveform, you can read any one by isolating that part of the waveform within the delta bar.

To try out the delta mode, we used it to troubleshoot a DC supply in a solid-state television set. That supply's output waveform showed some unusual symptoms, but ones that were obviously caused by


feedback. On what should have been a clean DC signal, we found tiny high-frequency "bursts;" the frequency of those bursts turned out to be about 40 kHz, the ringing frequency of the flyback pulse. As the DC supply came from the flyback, that seemed to indicate that the DC supply was not adequately filtered. From that point it was relatively easy to track the problem down to an open filter capacitor in the DC line; that open capacitor was allowing the ringing to get into the signal circuits.

This instrument is a real pleasure to use. All the controls are grouped by function and channel for maximum efficiency. The built-in digital display eliminates the need for graticule counting, allowing you to analyze a waveform quicker, and more accurately, than ever before. All this sophistication comes at a price, of course, as the *model SC61* lists for \$3275.00, including probes. However, if you do a lot of work with a scope, and consider the time and eye strain this instrument will save you, the price is well worth it.

R-E

ADVANCE IS PROUD TO INTRODUCE the KEITHLEY Line of High Quality Digital Multimeters Featuring The New 130 Hand-Held DMM

Keithley handheld DMMs keep you right on top of your field service applications. They're rugged, offer complete capabilities, are easy to use and won't break your budget.

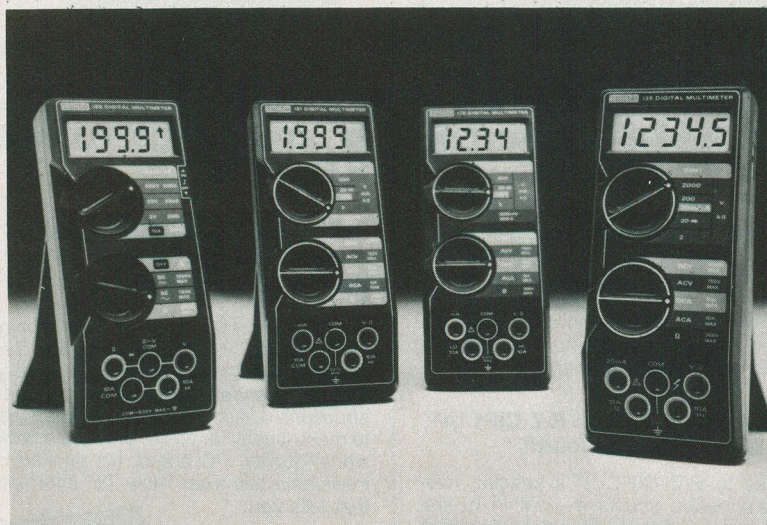

Model 128: Beeper DMM designed to meet the tough specifications of a major computer manufacturer. See/hear display includes over/under arrow and on/off beeper.

Model 131: 0.25% accuracy added to the easiest to use handheld DMM. Color-coded front panels for maximum clarity, minimum confusion.

Model 128: \$139.00
Model 130: \$124.00

Model 130: Keithley user research led to unique DMM designs. Easy to read LCDs, largest DMM displays on the market.

Model 135: First 4½-digit handheld DMM, ideal for analytical/bio-medical service. 10A range standard on all Keithley handhelds.

Model 131: \$139.00
Model 135: \$235.00

A full line of accessories expands these values even further.




THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

ADVANCE
ELECTRONICS

VISA

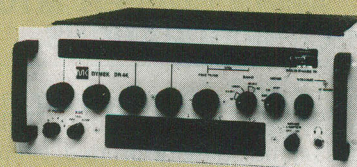McKay/Dymek General Coverage Receiving System



CIRCLE 107 ON FREE INFORMATION CARD

McKay/Dymek					DR-44-6				
OVERALL PRICE									
EASE OF USE									
INSTRUCTION MANUAL									
PRICE/VALUE									
	1	2	3	4	5	6	7	8	9
	Poor		Fair		Good			Excellent	

ALTHOUGH A LARGE PERCENTAGE OF McKay/Dymek (Post Office Box 5000, Department B, Claremont, CA 91711) products are for shipboard use on vessels of foreign registry, many items in their catalog are of interest to serious short-wave/longwave listeners as well. One such system consists of the DR44-6 receiver (shown), the DP4044 preselector, and the DS111 audio processing speaker. We'll look at each one of those individually, with the main emphasis on the DR44-6 receiver.

The DR44-6 receiver

Designed to fit in a standard 19-inch rack-panel mount, the *model DR44-6* is a

When you need a semiconductor that fits and works, turn to the Master.

You can search high and low for some replacement parts. Or you can turn to the Master—the Sylvania ECG® Semiconductor Master Replacement Guide.

It's called the Master because it's far and away the industry's most comprehensive source for getting the parts you need, when you need them. Including most hard-to-find foreign parts. And ECG universal replacement part specifications generally exceed the original JEDEC or application specs.

Not surprisingly, the Master comes from the people who first mastered the universal replacement principle—a system that allows a minimum number of premium quality replacement devices to replace almost every original equipment semiconductor on the market.

With the Master working for you, there is no need to turn elsewhere for replacement semiconductors.

For your nearest ECG distributor, call 1-800-225-8326.



If it's ECG, it fits. And it works.

Philips ECG

A North American Philips Company

general-coverage frequency-synthesized receiver that displays the received frequency on six large (0.5 inch) LED characters with an accuracy of 100 Hz.

The rear panel features a variety of connectors for increased flexibility in custom installations. Those include a high-impedance audio output with an associated level control, a mute jack, a 50-ohm BNC antenna connector, a low-impedance speaker output and a separate 600-ohm line output (both available from spring-loaded terminals), and an IF output (455 kHz) for a panoramic display or teletype converter.

Receiving modes include AM, SSB, CW, and RTTY. A separate rotary switch

allows selection of either 4- or 8-kHz bandwidth filtering of the upper/lower sidebands. Two additional unoccupied positions can accommodate the installation of optional filters by the user.

A noise-limiter circuit provides attenuation of pulse-type interference on any mode except AM. The AGC decay rates (fast or slow) may be selected or defeated entirely.

Frequency is selected through the combined use of 5 rotary controls, each adding or subtracting a frequency interval on the display (10 MHz, 1 MHz, 100 kHz, 5 kHz). The 5th control is variable, providing infinite resolution of the last 5 kHz.

Frequency displacement on upper and

lower sidebands is compensated in the readout so that the user will see the actual window frequency (suppressed carrier) without the mental gymnastics frequently necessary with other receivers.

Our lab tests

The DR44-6 was used with a 135-foot dipole antenna and in conjunction with its companion DP4044 preselector.

We found little advantage in using the preselector for the vast majority of applications; the preselector would best be used when there is a nearby source of strong RF interference.

Thermal and mechanical stability of the receiver were excellent. Little or no frequency drift was observed during reasonable periods of listening time after initial warmup. Frequency coverage for the DR44-6 is specified as 50 kHz through 29.7 MHz. Actual reception over that frequency range was confirmed.

RF sensitivity was excellent, certainly equivalent to or greater than that of most competitors.

"Birdies" are spurious signals caused by the frequency synthesizer. They are always present on receivers that use a frequency synthesizer to generate the local oscillator signal. While also present on the DR44-6, none was found too loud to detract from the readability of incoming radio signals. Two extremely loud birdies appeared to have been generated by the BFO, and were heard on 10 and 20 MHz; but those two frequencies are occupied by full-carrier WWV, and they disappeared in the AM mode.

Image rejection is specified as 70 dB, and in our lab tests images were certainly no problem. Additional specifications include cross-modulation and intermodulation suppression of 65 dB (referred to 1 microvolt) and RF blocking of 100 dB (also referred to 1 microvolt). A 25-dB 5-kHz audio-notch filter removes any heterodyne interference from adjacent channel broadcasts.

A 2-MHz high-pass filter provides useful suppression of interfering signals from the AM broadcast bands and below when the receiver is being used only for shortwave reception. RF signal attenuation may be used to reduce overload from strong signals.

Two watts of audio output into a 4-ohm load impedance is available at the rear panel as well as a 1-volt RMS line output (5,000-ohms impedance). AC power required is 120 or 240 volts, 50/60 Hz (30 watts).

The internal circuitry is very clean and well laid out, featuring 56 IC's, 31 FET's, 20 transistors, and 66 diodes.

The accompanying instruction manual is well written and comprehensive, presenting descriptions of each portion of the receiver's circuitry, including both component layout and schematic drawings.

continued on page 104

PRINT THE WORLD



See What You've Been Missing!

Stay in touch with world events, monitor weather, ship traffic, and radio amateurs. Connect to your receiver and display shortwave radio teleprinter and Morse code transmissions with the new receive-only HAL CWR-6700 Telereader.

- Receive ASCII or Baudot RTTY
- Six standard RTTY speeds
- 3 RTTY shifts for low or high tones
- Adjustable space for fine tuning
- Receive Morse code — 4 to 50 wpm
- 16 lines by 36 or 72 character display
- Two page video display
- Parallel ASCII printer output
- Requires +12 VDC and external TV monitor
- One year limited warranty
- Small size (8" x 3" x 12.75")

Write or call for more details. See the CWR-6700 at your favorite HAL dealer.



HAL COMMUNICATIONS CORP.


BOX 365

URBANA, ILLINOIS 61801


217-367-7373

Modular Components... The Soldering Choice is Yours

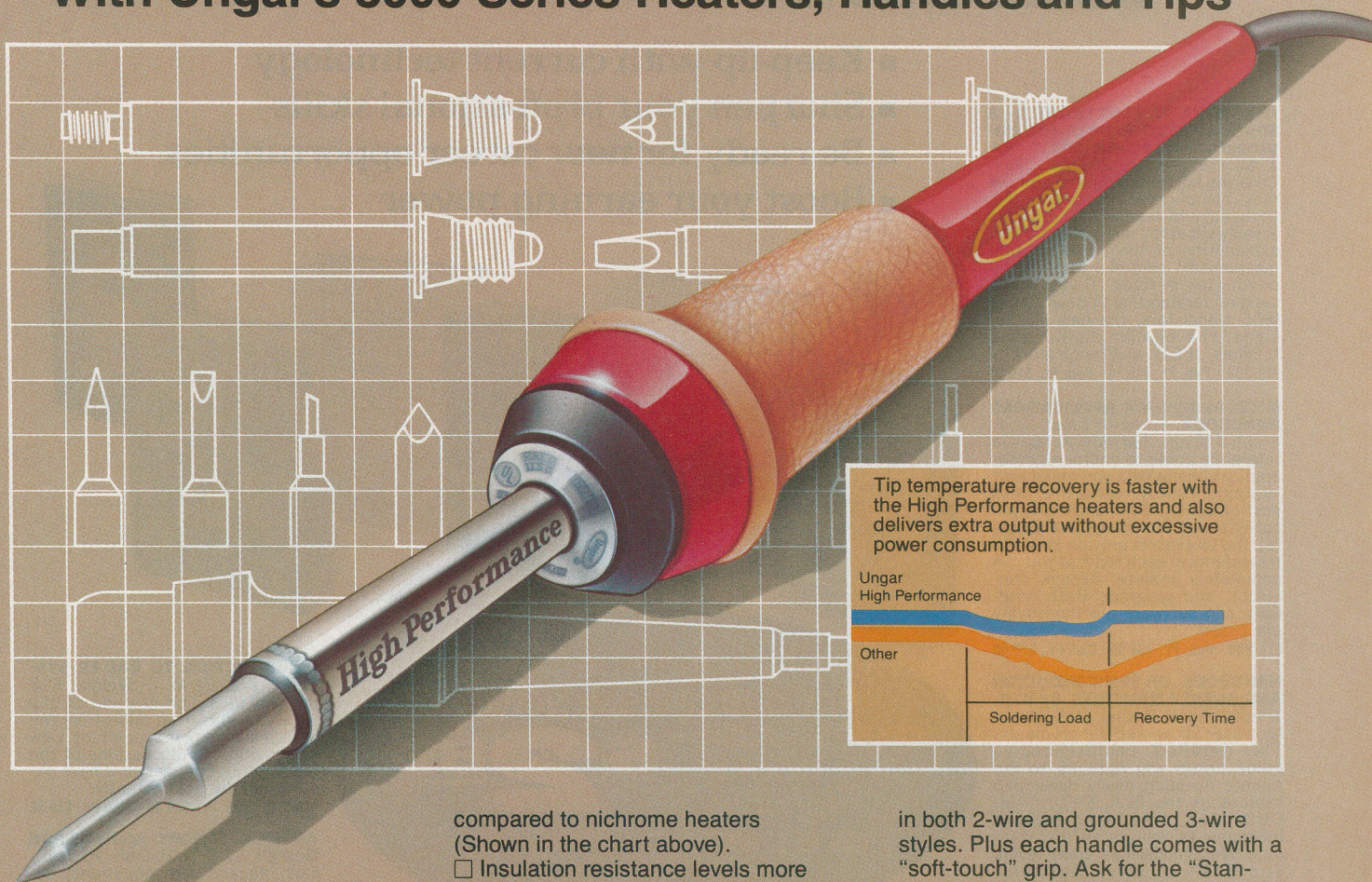With Ungar's 3000 Series Heaters, Handles and Tips



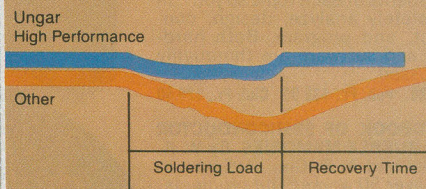Tip temperature recovery is faster with the High Performance heaters and also delivers extra output without excessive power consumption.



When it comes to making a choice, Ungar gives you lots to choose from. We have one of the broadest lines of soldering components available to precisely meet your needs.

Take our lineup of heaters, handles and tips, for example. We've got you covered with a variety of heat ranges and tips so you can custom-design the soldering iron to fulfill your requirements.

15 NEW THERMO-DURIC™ HIGH PERFORMANCE HEATERS

Our 3000 Series heaters are the state-of-the-art in soldering today. Their improved performance is thanks to modern "thick film" technology, which has allowed the design of our exclusive, revolutionary THERMO-DURIC™ heater element.

The benefits include:

- ☐ Faster heat-up—typically 1.5 minutes vs. 2.5 minutes.
- ☐ Quicker temperature recovery

compared to nichrome heaters (Shown in the chart above).

- ☐ Insulation resistance levels more than ten times greater than wire-wound elements. This means significant reduction in leakage currents that can damage sensitive micro-electronics.
 - ☐ Lower power consumption—our 50 watt heater outperforms a conventional 80 watt iron.
 - ☐ Less energy consumed at no-load idle temperatures—typically 15% less!
 - ☐ Better results with thread-in and thread-on tips.
- And that's not all!

You can choose from a wide selection of body styles. Ranging from integral tip models to the thread-in and thread-on styles. Plus each style is available in wattage ratings to cover soldering temperatures from approximately 700°F to 1,000°F.

HANDLES—WE OFFER YOU THREE CHOICES

To complement our 3000 Series heaters, we have three handles. They are perfectly balanced for added comfort and reduced fatigue. They're available

in both 2-wire and grounded 3-wire styles. Plus each handle comes with a "soft-touch" grip. Ask for the "Standard Line" of Ungar handles to match up with the ultimate in heaters, the 3000 series!

SELECT FROM 15 TIPS

No matter your requirements, we've got the tip for you! Available in both thread-in and thread-on styles to mate with our 3000 Series heaters.

AND IT'S ALL MODULAR!

That's the beauty of the Ungar system. Every piece is modular, so if one unit wears, instead of buying a totally new soldering iron—simply replace that one component. Fast, Easy, and Economical. You have unparalleled flexibility to combine handle, heater and tips to create any one of 234 custom irons.

To find out more about this amazing lineup from Ungar, call the Ungar Hotline, toll-free 1-800-421-1538, in California, call collect, 1-213-774-5950.



Division of Eldon Industries,
Compton, California 90220
In Canada, Markham,
Ontario, Canada L3R 1H5

Professional Books That Help You Get Ahead—And Stay Ahead!

Join the **Electronics and Control Engineers' Book Club** and...

- Keep up with current technology
- Sharpen your professional skills
- Be ready for new career opportunities
- Boost your earning power

INTUITIVE IC ELECTRONICS: A Sophisticated Primer for Engineers and Technicians.

By T. M. Frederiksen. 208 pp., illus. Covering both the simplest and the most complicated IC designs, this lively, easy-to-read volume provides a sophisticated, nonmathematical explanation of the basic internal mechanisms common to all semiconductor devices. Gives you a solid understanding of devices like MOS transistors, the new I²L designs, the bipolar digital logic families, JFETs, and much more.

219/230 Pub. Pr., \$18.50 Club Pr., \$14.50

MICROPROCESSOR APPLICATIONS HANDBOOK.

Editor-in Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective. Emphasizing applications that are immediately useful, the 16 experts provide in-depth treatments of each topic so you can completely analyze, design, construct, and program. Both hardware and software are thoroughly discussed.

617/988 Pub. Pr., \$35.00 Club Pr., \$26.50

HANDBOOK OF SEMICONDUCTOR AND BUBBLE MEMORIES.

By W. A. Triebel and A. D. Chu. 416 pp., illus., over 50 worked-out problems. This detailed, comprehensive guide brings you right up to the minute on such newly developed devices as the PLA, FIFO, CAM, CCD, and magnetic bubble memory—as well as all the standard storage devices from ROMs and RAMs to shift registers. Analyzes, categorizes, and explains in full working detail more than 75 different semiconductor ICs and MBM devices.

582376-4 Pub. Pr., \$24.95 Club Pr., \$18.50

PCM AND DIGITAL TRANSMISSION SYSTEMS.


By R. Owen. 320 pp., 186 illus. This useful volume arranges the latest thinking in pulse code modulation (PCM) and digital transmission technology into a logical, step-by-step format. The result is a book which allows newcomers to this field to familiarize themselves with its problems and equipment in two weeks, instead of the three months it would ordinarily take.

479/542 Pub. Pr., \$30.00 Club Pr., \$23.50

MAGNETIC CORE SELECTION FOR TRANSFORMERS AND INDUCTORS: A User's Guide to Practice and Specifications.

By W. T. McLyman. 768 pp., 400 illus. This giant volume is brimming with time-saving tips, plus tables to help you select the right magnetic core for virtually any application. The book instantly gives you everything from strip width to window length to iron weight to the area product. Sixteen different variables are provided, all in standard units of measurement for ease of comparison, and data are provided for more than 6,000 different cores.

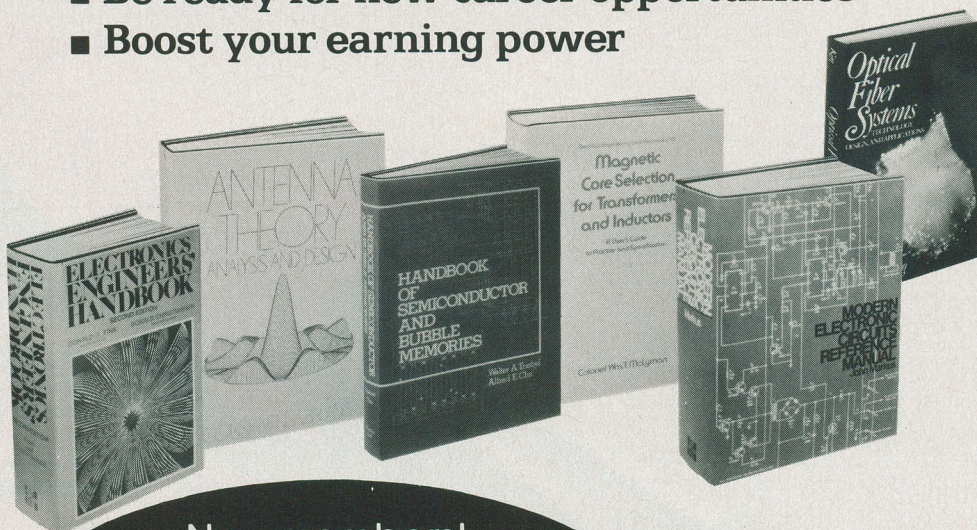582494-9 Pub. Pr., \$65.00 Club Pr., \$45.00



New members!
Any one of these great
professional books
for only **\$2⁸⁹**
as a premium with your
1st selection!

Spectacular values up to **\$75.00**

INTRODUCTION TO RADAR SYSTEMS, 2/e. By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently.

579/091 Pub. Pr., \$38.50 Club Pr., \$30.50

ANTENNA THEORY: Analysis and Design. By C. A. Balanis. 816 pp., illus. Packed with equations, design procedures, and plenty of nuts-and-bolts know-how, this is the first place to turn for answers to all your antenna design questions. But it's much more than a valuable on-the-job reference. It's a complete A-to-Z course in antenna design for those who are new to the field.

582493-0 Pub. Pr., \$39.50 Club Pr., \$29.95

RADAR TRANSMITTERS. By G. W. Ewell. 252 pp., 211 illus. This all-around reference provides complete, up-to-date details on device capabilities and design procedures—with plenty of specific design examples. Helps you know your radar transmitter capabilities inside out—brings you abreast of latest design techniques to improve your designs—cuts your design time in half!

198/438 Pub. Pr., \$24.50 Club Pr., \$18.50

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL. By J. Markus. 1,264 pp., 3,666 circuit diagrams. This 103-chapter guide means you can speed up the production of new electronic devices with ease and thereby lower your production costs. Complete with values of components and suggestions for revisions, plus the original source of each circuit in case you want additional performance or construction details.

404/461 Pub. Pr., \$61.50 Club Pr., \$48.50

OPTICAL FIBER SYSTEMS: Technology, Design, and Applications. By C. K. Kao. 197 pp., illus. From a basic explanation of optical fiber systems to the economic ramifications of their use, this volume provides full coverage of a rapidly changing field. The working engineer will find this a valuable source of both data and design concepts—and newcomers will appreciate its step-by-step explanation of component technology, and design processes.

332/770 Pub. Pr., \$23.50 Club Pr., \$17.95

ELECTRONICS ENGINEERS' HANDBOOK. Edited by D. O. Fink; D. Christiansen, Associate Editor. 2nd Ed., 2,272 pp., 2,189 illus., 43 photos. The leading electronics reference work is now totally revised and updated to cover the latest developments in the field. Its 28 giant sections cover everything from basic principles, materials, devices, and components to electronic circuits and their functions and electronic systems and applications.

209/812 Pub. Pr., \$75.00 Club Pr., \$57.50

ELECTRONICS CIRCUITS NOTEBOOK: Proven Designs for Systems Applications. By S. Weber, Editor in Chief. 344 pp., illus. Containing 268 ready-to-use or adapt circuits—each a proven solution—this book brings you the best of the best articles published in *Electronics'* popular Designer's Casebook section. Covers display circuits, encoders and decoders, filters, function generators, logic and memory circuits, microprocessors, and more.

192/448 Pub. Pr., \$32.50 Club Pr., \$25.50

RADIO HANDBOOK. By W. Orr. 22nd Ed., 1,136 pp., more than 1,300 illus. Here's the latest edition of what is universally regarded as the most useful reference in the industry. All the newest technology is explained and illustrated, and there's a wealth of data about receivers, transmitters, antennas, and auxiliary equipment of every description. It's a "course" in communications, a fact-packed reference, and a how-to guide—all in a single book!

582442-6 Pub. Pr., \$39.95 Club Pr., \$33.95

McGraw-Hill's NATIONAL ELECTRICAL CODE® HANDBOOK, 17/e. By J. F. McPartland. 1,162 pp., 1,096 illus. Bigger and better than ever! This mammoth reference explains and clarifies the many complex provisions of the current (1981) Code® to help you meet rules exactly and pass inspections the very first time.
456/933 Pub. Pr., \$26.50 Club Pr., \$20.50

DIGITAL HARDWARE DESIGN By J. B. Peatman. 428 pp., over 400 illus. Taking you beyond the microcomputer, this guide re-examines traditional techniques and focuses maintainability as a key goal, on the design of circuitry too fast for the microcomputer alone, and on designing for usefulness. It covers everything from algorithmic state machines to separately clocked circuits—with scores of examples.
491/321 Pub. Pr., \$33.00 Club Pr., \$26.00

INTRODUCTION TO THE THEORY AND DESIGN OF ACTIVE FILTERS. By L. P. Huelsman and P. E. Allen. 430 pp., illus. Once you add active filter design to your repertoire of specialties, you'll possess a skill that's in great demand today. Here's one of the best texts we know on the theory, design, application, and evaluation of modern active filters and the various techniques used today.
308/543 Pub. Pr., \$32.50 Club Pr., \$25.50

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.
254/303 Pub. Pr., \$24.75 Club Pr., \$19.50

ELECTRONIC COMMUNICATION, 4/e. By R. L. Shrader. 801 pp., 870 illus. This thoroughly updated edition offers all the theory and fundamentals you need to prepare yourself for the FCC commercial and amateur grade license examinations—and pass them the first time!
571/503 Pub. Pr., \$24.10 Club Pr., \$18.95

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts and how-to on the generation, transmission, distribution, control, conversion, and application of electric power.
209/74X Pub. Pr., \$65.95 Club Pr., \$48.95

DIGITAL CIRCUITS AND MICROPROCESSORS. By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and microprocessor-based designs. Anticipates every conceivable question you could have to make sure you understand every detail.
629/455 Pub. Pr., \$29.95 Club Pr., \$23.50

Be sure to consider these important titles as well!

USER'S GUIDEBOOK OF DIGITAL CMOS INTEGRATED CIRCUITS. By E. R. Hnatek.
290/679 Pub. Pr., \$26.90 Club Pr., \$20.50

DESIGNING WITH FIELD-EFFECT TRANSISTORS. By Siliconix, Inc.
574/499 Pub. Pr., \$26.90 Club Pr., \$20.50

BIT-SLICE MICROPROCESSOR DESIGN. By J. Mick & J. Brick.
417/814 Pub. Pr., \$26.50 Club Pr., \$20.50

MICROPROCESSORS/MICROCOMPUTERS/SYSTEM DESIGN. By Texas Instruments Learning Center & Engineering Staff.
637/58X Pub. Pr., \$26.95 Club Pr., \$20.95

ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma.
654/298 Pub. Pr., \$29.50 Club Pr., \$22.95

HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. E. Stout & M. Kaufman.
617/97X Pub. Pr., \$38.00 Club Pr., \$29.00

OPTICAL FIBRE COMMUNICATION. By Technical Staff of CSEL.
148/821 Pub. Pr., \$39.50 Club Pr., \$29.50

ELECTRONIC FILTER DESIGN HANDBOOK. By A. B. Williams.
704/309 Pub. Pr., \$37.50 Club Pr., \$28.50

MICROCOMPUTER-BASED DESIGN. By J. Peatman.
491/380 Pub. Pr., \$35.00 Club Pr., \$27.00

MICROELECTRONICS. By J. Millman.
423/27X Pub. Pr., \$34.00 Club Pr., \$26.50



MAIL THIS COUPON TODAY

McGraw-Hill Book Clubs
Electronics and Control Engineers' Book Club
P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for the \$2.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of
\$2.89 selection here

Write Code No. of
first selection here

Signature _____

Name _____

Address/Apt. # _____

City _____

State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. Orders from outside the U.S. cannot be accepted.

E33564

Why YOU should join now!

■ **BEST AND NEWEST BOOKS IN YOUR FIELD** — Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS** — Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices — usually 20% to 25%.

BONUS BOOKS — You will immediately begin to participate in our Bonus Book Plan that allows you savings of between 70%—80% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE** — 12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an Alternate Selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books. Orders from outside the U.S. cannot be accepted.

Other McGraw-Hill Book Clubs:
Accountants' and Controllers' Book Club • Architects' Book Club • Chemical Engineers' Book Club • Civil Engineers' Book Club • Computer Professionals' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs, 26th fl., 1221 Avenue of the Americas, New York, NY 10020

SATELLITE/TELETEXT NEWS

GARY ARLEN
CONTRIBUTING EDITOR

WIRELESS CABLE PLAN

Urbanet, a multi-channel microwave hybrid service that can be used for teletext, data transmission, pay-TV, and other entertainment services, is being proposed by Microband Corp. of America, the nation's largest operator of Multipoint Distribution Service (MDS) stations. Microband's proposal for "wireless cable" would create up to 14 video channels in the top 50 U.S. cities. The channels would operate in the 2500 MHz band, and would be first cousins of the MDS pay-TV services now offered in many markets in the 2160 MHz range. The *Urbanet* arrangement would accommodate national and local transmissions in a variety of modes: one-way, two-way, interactive, and asymmetrical. For example, the broadband MDS channel could be used to transmit video programming; an asymmetrical variation could be used to download video-games or for electronic mail.

For services requiring two-way or interactive capability, the telephone will be used in conjunction with value-added data communications networks. By augmenting current software and data-storage capabilities, services can be developed to handle teletext and home banking. The Microband plan comes in response to a long-simmering FCC study about reallocating the 2500 MHz band that is now underused as an educational TV band.

HIGH- DEFINITION TV

High-definition television (HDTV), with 1125-line video resolution, stereo sound, wide-screen pictures, and other enhanced features, seems to be moving ever closer to reality—and satellite distribution will be a major factor in its development. CBS and Japanese-TV network NHK recently demonstrated their latest refinements of HDTV, along with a hint that the service could begin in less than five years on a limited basis. Because of its sizeable spectrum demands—about 30 MHz-per-channel (five times the bandwidth of conventional TV)—HDTV will probably be used for special purposes. Direct-broadcasting satellites (DBS), cable-TV, and home-videocassette/disc distribution are possible, because bandwidth limitations are not a problem as they are on current broadcast-TV systems. However, engineers are now working on bandwidth-compression systems to bring down the spectrum requirements for HDTV.

Satellite service is a high priority because a DBS transmission of a high-definition TV signal would offer theater-quality video projection. The 1125-line resolution will provide picture quality at least five times better than today's TV signal—richer colors, higher resolution, and better contrast. The 3 × 5 screen ratio (compared to today's 3 × 4 ratio) provides wide-screen capabilities. HDTV also offers Hollywood studios a new opportunity to produce movies directly as electronic cinema, rather than shoot on film and then transfer to videotape.

TEXT VIA SATELLITE

Text and data services will be transmitted nationwide via subcarriers on National Public Radio's transponders aboard Westar starting late this year. The project is part of public radio's effort to find new financial sources to support its non-commercial audio programming. According to this plan, the national satellite feed will be transmitted in hundreds of communities by local public radio stations, again using subcarriers on their standard broadcast signals. In many cases, the local stations will also insert additional data aimed solely at receivers in their communities.

Data will be transmitted using an SCA (Subsidiary Channel Authorization) that is piggy-backed to an audio circuit. Each signal will carry an identifying code, and customers will be equipped with an addressable receiver to pick up the data. Customers would only be permitted to receive material designated for their specific decoder. Initially, most receiver locations would plug their decoders into hard-copy printers, but the data could also be displayed on a video screen.

A new organization, Information Network Corp. (INC) has been set up by NPR and a Washington-area company called National Information Utilities Corp. that will develop databases and services for the network, including videogames, shopping information, computer information, and business information. INC expects to deliver services almost entirely to business customers. The plan, however, is one of a growing number of projects seeking to piggy-back auxiliary services into the scarce satellite circuits.

R-E

Moving up to Philips just moved down in price.

Make your move today. To top quality professional test equipment—Philips.

All over the world Philips produces the test that more people trust. That's because the same superior engineering and ergonomic principles that go into our over \$6000 digital storage scope can be found in our 15MHz scope and our super smart counters.

We put more into every scope and counter. More wanted features. More precision. More rock-solid

quality. So you get more. And now for a whole lot less!

Check our specs. Check our new low prices. Then check yourself into the world of professional testing—with Philips.

Philips PM3207 Dual Trace Scope

- 15MHz/Dual Trace • Auto triggering • Bright, clear CRT • 5mV sensitivity • Same sensitivity X and Y • B-Invert • Triggering from A or B • TV triggering

Super Smart Counters with seven digit high/low frequency readouts in one second!

- Microprocessor control • 120MHz or 1GHz frequency range • Auto triggering on all waveforms • High-contrast liquid crystal display • High stability TCXO oscillator: 10^{-7} /mth • Line and battery options • 15mV RMS sensitivity • Self-test and self-diagnosis routine • Easy operation through built-in intelligence

PM6667
120MHz
High Resolution
Counter
\$430

PM3207
15MHz Dual Trace
Oscilloscope
\$725

PM6668
1GHz
High Resolution
Counter
\$595

From Philips, of course.



**Test & Measuring
Instruments**

**ORDER TOLL-FREE
800-631-7172**
Call now or mail coupon
for further information

Send me spec sheets on the following:

- ☐ PM3207 15MHz/Dual Trace Oscilloscope
☐ PM6667 120MHz High Resolution Counter
☐ PM6668 1GHz High Resolution Counter

NAME: _____

STREET: _____

CITY: _____ STATE: _____ ZIP: _____

RE-09-2

PHILIPS

For more information call 800-631-7172, except Hawaii, Alaska and New Jersey. In New Jersey call collect (201) 529-3800, or contact Philips Test & Measuring Instruments, Inc., 85 McKee Drive, Mahwah, NJ 07430. In Canada: 2375 Steeles Ave. W., Unit 126, Downsview, Ont., Can. M3J 3A8. (416) 665-8470.

CIRCLE 13 ON FREE INFORMATION CARD

NEW IDEAS

Electronic Thermometer

HERE IS AN INEXPENSIVE ELECTRONIC thermometer than can be built in just one evening. It is capable of measuring temperatures over a range of from -30°F to $+120^{\circ}\text{F}$.

The circuit is shown in Fig. 1; its operation is fairly straightforward. A diode-connected 2N3904 transistor forms a voltage divider with R1. The transistor is used as the temperature sensor and, for best results, should be connected to the rest of the circuit using twisted wire as shown. As temperature increases, the voltage drop across the transistor changes by approximately -1.166 millivolts-per- $^{\circ}\text{F}$. As a result, the current at pin 3 of IC1, a 741 op-amp with a gain of 5, decreases as the temperature measured by the sensor increases.

A second 741 op-amp, IC2, is configured as an inverting amplifier. Since pin 3 of that IC is grounded, pin 2 is at a virtual ground and the sum of all currents into that pin must be zero. Resistors R5 and R6 are used to calibrate the circuit. Once R6 is adjusted (more on that later), the current flow through those resistors will be constant. At a temperature of about -30°F , the current through R4 (that resistor is formed by connecting a 910- and a 1600-ohm resistor in parallel) should equal the current through R5 and R6.

At higher temperatures, the current through R4 will be less than the current through R5 and R6. Since the sum of the currents at pin 2 of IC2 should be zero, current will be drawn from the output (pin 6) of that IC to offset the difference. That current must pass through M1, and the

amount of current drawn is, of course, measured by the meter. As the relationship between the amount of current drawn and the measured temperature is linear, it is relatively easy to calibrate the meter to indicate measured temperature.

If the temperature goes below -30°F a reverse current will be generated. As that reverse current is undesirable, its flow is prevented by inserting D1 into the circuit as shown.

Calibration is also straightforward. When properly done, a temperature of -30°F will result in a meter reading of 0 milliamps, while a temperature of 120°F will result in a meter reading of 1 milliamp. Divide the scale between those points into equal segments and mark the divisions with the appropriate corresponding temperatures. Note that dividing the scale into more parts will result in greater accuracy; if you divide it into 150 equal segments, for instance, each division will equal one degree. The calibration is completed by placing the sensor in an environment with a known temperature, such as an ice-point bath. The ice point of water is approximately 32°F . That is the temperature at which water and ice can co-exist in the same container. To prepare the bath, place water and ice in a large glass beaker or similar container, wait a few minutes for the temperature of the bath to stabilize, and verify that the temperature is indeed 32°F using another thermometer that is known to be accurate. Then, simply place the sensor in the bath and adjust R6 until you get the correct meter reading.

—David McNeill

R-E


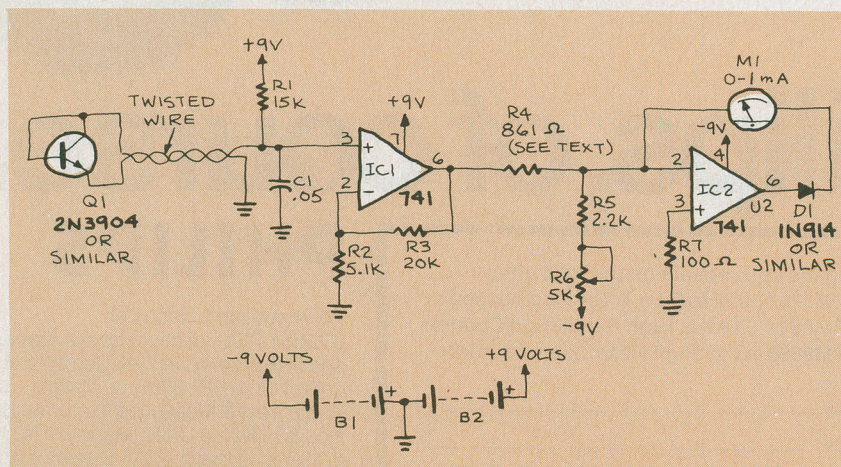


FIG. 1

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, Panavise will donate their *model 333*—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working. (See photo below.)

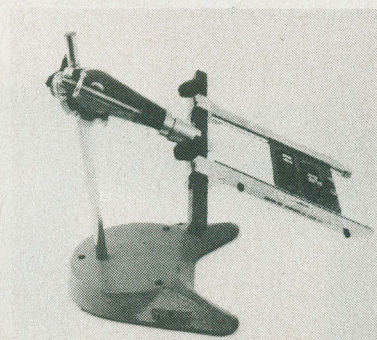

I agree to the above terms, and grant **Radio-Electronics** Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City


State

Zip

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**, 200 Park Ave. South, New York, NY 10003

NEW!

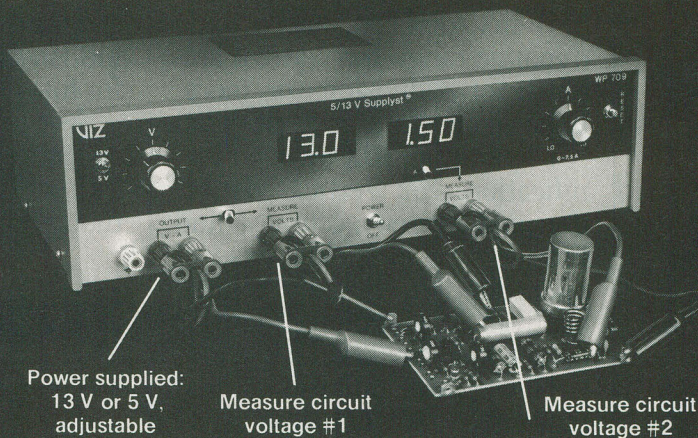WP-709.
Double-slot
Supplyst™
power supply.



Power supplied:
13 V or 5 V,
adjustable

Measure circuit
voltage #1

Measure circuit
voltage #2

Outputs: 5V or 13V DC,
adjustable $\pm 1\frac{1}{2}$ V
Zero to 7.5 amp, each voltage.
Two LED displays,
monitor V or A—
or two DC voltmeters
Adjustable current limiting

Only
\$324.95

DC power to test logic or mobile equipment. Another VIZ Value

HERE'S REAL PRECISION

Select the precise voltage you want: 5V or 13V, adjustable $\pm 1\frac{1}{2}$ V at each range. Output is laboratory quality. Ripple less than 10mV, peak to peak. Regulation better than 0.1%.

HERE'S REAL POWER

Up to 7.5 amp. at each voltage—

plenty for computer circuits, PA systems, mobile transmitters, autos, boats, planes.

HERE'S REAL CONVENIENCE

Front panel controls for instant voltage adjustment and precise fine adjustment to within 0.1V. Two 3-digit LED displays permit continuous

monitoring of both voltage and current during use. Current limiting control with instant pushbutton reset.

The WP-709 is like two precision power supplies for a price less than you might pay for one— PLUS two digital DC voltmeters.


VIZ Supplyst™

power supplies with digital displays of voltage and current



WP-705 \$315.95

Single output
0-50VDC. 0-2A.

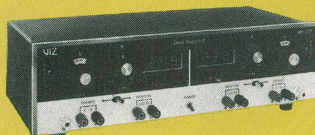


WP-707 \$409.95

Dual output
Two 0-25VDC. 0-2A.

WP-706 \$329.95

Single output
0-25VDC. 0-4A.

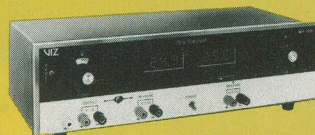

WP-708 \$479.95

Triple output Two 0-20VDC, 0-2A.
One 5VDC, 0-4A.




VIZ DC power supplies


Fully regulated, continuously adjustable voltage outputs with short circuit protection. Analog meters and overload indicators.



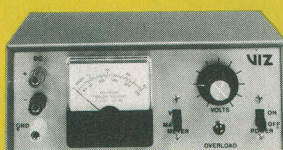Dual WP-702A Two 0-20VDC. 0-200mA **\$167.00**



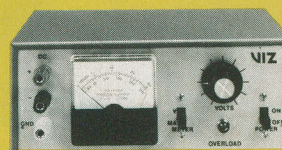Single WP-703A
0-20VDC. 0-500mA **\$119.00**



Single WP-704A
0-40VDC. 0-250mA **\$125.95**

VIZ RELIABILITY

VIZ is a 50 year-old company. Our instruments are fully warranted, parts and labor, for a year. All items tested to NBS standards. We offer service and parts availability for a minimum of ten years. Over 15 repair depots in U.S.A.

Want full technical details and a demonstration? Call toll-free. 1-800-523-3696, for the VIZ distributor nearest you



Look to VIZ for value, quality, availability.
Over 70 instruments in the line— PLUS full accessories.

VIZ Mfg. Co., 335 E. Price St., Philadelphia, PA 19144

CIRCLE 8 ON FREE INFORMATION CARD

Hitachi V-202 and V-352 Dual Trace Oscilloscopes

When you get exceptional capability per dollar, that's superior cost-performance. And that's the 35 MHz Hitachi V-352 and the 20 MHz Hitachi V-202 dual trace oscilloscopes.

Proof? Just skim these features, then note the price. For starters, both scopes have a 2-year limited warranty. And then there are features like square CRT's with internal graticules, vertical sensitivity

of 1 mV/division, and a wide dynamic range for vertical amplifier of 8 divisions or more. Each scope features front panel X-Y operation, 10X sweep magnification, 3% vertical deflection and sweep accuracy, and low vertical drift. For ease of operation, functionally related controls are grouped into 3 color-coded front panel blocks.

How do we build in all that capability at such low cost? Chalk it up to two decades of oscilloscope design experience and some of the most modern production methods around.

Hitachi V-352 and V-202 are

stocked by your authorized industrial distributor and ready for fast delivery.

Ask for a demonstration and see more performance than you expected for less than you thought possible.

**Hitachi...
the measure of quality.**




HITACHI

Hitachi Denshi America, Ltd.

175 Crossways Park West
Woodbury, NY 11797
(516) 921-7200

CIRCLE 14 ON FREE INFORMATION CARD

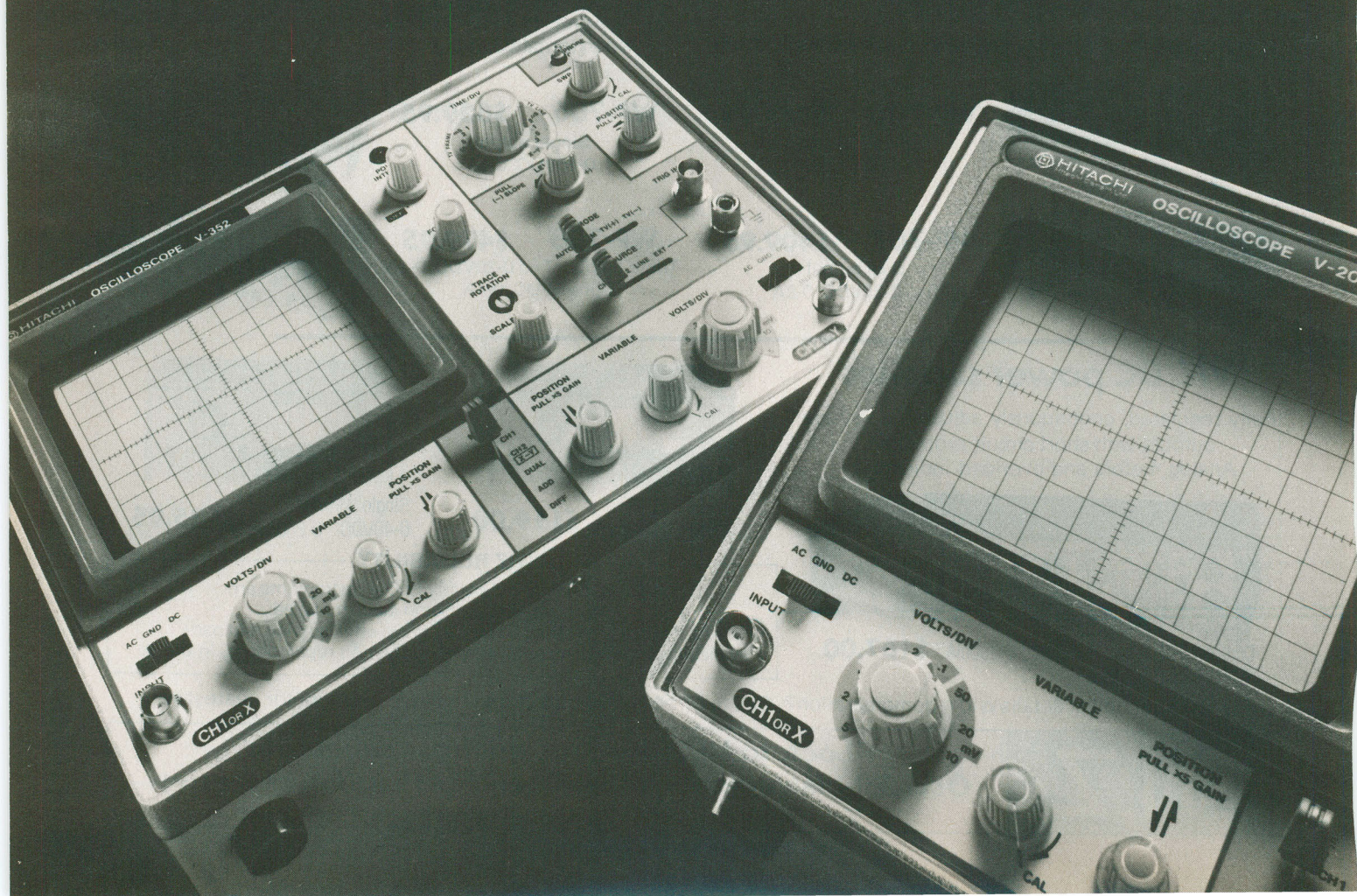You'll recognize the name... appreciate the quality.



BUILD THIS

ROBERT GROSSBLATT

MEDICAL TECHNOLOGY HAS GROWN tremendously over the past 20 years. So much so that the consumer now has instruments available to him that at one time could only be found in hospitals. One such instrument, a machine to monitor a heart rate, used to occupy an entire room and required a sizeable endowment to buy; now you can build one that runs on batteries for under a hundred dollars.

The Heart-a-Matic described here gives a digital readout of your heart rate and can be built from readily available parts; it features both an audible and a visual heart-rate indication.

Design considerations

There are two basic problems that have

Heart Rate Monitor

Knowing your heart rate and how it varies under different circumstances can give you an idea of your physical condition. Build the Heart-a-Matic and keep track of the state of your health and fitness.

to be overcome in designing a reliable heart-rate monitor. The first is that each heartbeat is actually made up of several beats; the second is that the heart is not crystal-controlled—even a healthy heart beats somewhat irregularly.

The heart is a four-chambered pump and consequently each heartbeat is composed of several parts (everyone is familiar with the "lub-dub" heard through a stethoscope). Figure 1 shows the various components of a heartbeat. The Heart-a-Matic is designed to integrate the "P" and "T" portions of the waveform with the "R" portion.

Even during rest, the rate at which the heart beats varies; irregularity between beats is a natural characteristic of the heart. Several beats have to be sampled and averaged to provide a result that has any useful meaning. The Heart-a-Matic heart-rate monitor uses an eight-beat sample to obtain an average reading. That number of beats was chosen as a good middle ground to minimize irregularity, on the one hand, and to provide reasonable response-time, on the other. Commercially available machines use multi-beat samples and update at the end of each sampling period.

The Heart-a-Matic, however, gives a running average. In other words, whenever it adds a new beat to its sample,



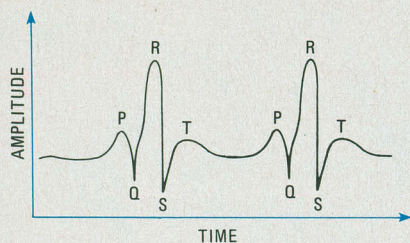


FIG. 1—THE PARTS OF A HEARTBEAT. The Heart-a-Matic integrates the P and T portions with the R portion.

it drops the first beat of the sample. Consequently, it's able to update with each beat and still give a meaningful readout.

How it works

As shown in Fig. 2, the Heart-a-Matic is composed of eight sections. A complete schematic of the device is shown in Fig. 3. The sensor, IC24, is an FPA104 infrared emitter-sensor combination in one housing. The two elements are side by side and there is no direct way for the radiation from the emitter to be seen by the detector, because they are separated by part of the case. The sensor is designed to be placed against a person's finger. The IR (InfraRed) radiation emitted by the LED in IC24 penetrates the outer skin-layer and is reflected back to the detector. As the heart beats, a new volume of blood is pumped into the finger and changes the amount of infrared light reflected back to the photo-transistor. That change in blood density (and, consequently, in reflected IR) is used by the Heart-a-Matic to determine the heart rate.

The input amplifier, composed of Q1 and IC1, has two main jobs. It amplifies the weak signal from the detector, and integrates the several components of the heartbeat into one pulse. The waveform emerging from the output of IC1, however, is far from being a clean single pulse. Even though the peaks and valleys of the heartbeat have been smoothed out, the

pulse still has to be conditioned before it can meet the somewhat snobbish square-wave requirements of the digital circuitry that will process it later. That is a problem with *any* system that combines digital and analog techniques. While digital systems require strictly "yes" or "no" answers, the analog world usually provides just "maybes."

The conditioning circuit, consisting of Q2 and IC2, squares the wave presented to it by IC1 and raises its voltage level so it can be reliably detected by IC2, a 555 configured as a monostable multivibrator, or pulse generator. Capacitor C8 and resistor R9 give the output pulse of the 555 a width of about 100 milliseconds. That serves two purposes. First, it insures that the high level of the pulse will be seen as a logic one by the digital circuitry that follows and, second, it helps eliminate the "maybes" of the analog world. Once the 555 is triggered, it ignores all other signals for 100 milliseconds.

Should some signal ambiguity still manage to emerge from the analog portion of the heart-rate monitor, the first part of the digital portion should take care of it. Integrated circuit IC3-a is a Schmitt trigger set up as a half monostable with an output-pulse width of about 20 milliseconds. That signal is one of the two that control the interlock portion of the circuit made up of the three other NAND gates of IC3 and IC5. A set-reset latch formed by IC3-b and IC3-c controls the calculation of the heart rate started by each heartbeat detected.

When a positive pulse appears at the output of IC3-a it causes the output of the latch to go—and remain—high. That output is inverted by IC3-d and presented, through inverter IC22-f, to the clock input of IC21, a 4017 decade counter. Each pulse will make one of that IC's outputs go high in sequence.

We are sure of starting with number one because C18 performs a power-on-

reset function. That means that IC21 will start with its first output at a logic-high and will then clock along with incoming heartbeats for eight beats, at which point it will reset back to one. That happens because the ninth output (which, coincidentally, is also pin 9) is also connected to the RESET pin. The outputs of the IC21 are connected in successive pairs to IC20's 2-input NOR gates. As a result, we have repeating sequential logic ones that are used in the section of the heart-rate meter that measures the period and calculates the heart-rate frequency.

Integrated circuit IC23 and its associated components provide an extremely accurate source of 60-Hz square waves that are counted by IC16-IC19, 4040 binary ripple counters. Each of the 4040's is connected to the "D" inputs of a 4508 (IC12-IC15) configured as 3-state eight-bit hold-and-follow latch.

When a heartbeat is detected, one of the outputs of IC20 goes high and causes two things to happen. The first is that its associated 4508 is enabled, and the data present at that moment at its "D" inputs is stored in the latch and presented at its "Q" outputs. The second thing that happens is that an inverter (a section of IC22) set up as a half-monostable outputs a positive pulse, lasting about 70 microseconds, that resets the 4040 to zero. The counter immediately starts counting again; but the latch is now disabled and it ignores the changing data at its inputs. The period of each heartbeat is counted at a 60-Hz rate and appears on the data bus.

Next comes a bit of arithmetic. Since the device knows the period of the heartbeat, it now has to calculate its frequency. Those are reciprocals of each other and the form of the calculation that has to be performed is also simple. Sixty Hz (cycles-per-second) times 60 (seconds-per-minute) equals 3600 cycles-per-minute. The number of beats per minute is therefore the number of cycles per minute divided by the number of cycles per beat. Since we are using a period of eight heartbeats, the magic number becomes 28,800 (8×3600). The division is carried out in two ways. The first way is sneaky and the second is interesting.

The sneaky way is to ignore the two least-significant outputs of the 4040's. By doing that we immediately divide the count by four. That also gives us the advantage of smoothing out any "bobble" in the circuitry by dropping the two least-significant figures, which is where it would show up. All we have to do now is divide by 7200 ($28,800 \div 4$), and the way that is done is one of the most interesting features of the Heart-a-Matic. The secret lies in an often overlooked, frequently misunderstood, and extremely useful type of IC—the rate multiplier.

There are two types of rate multipliers—binary and decimal. The difference between them is much the same as

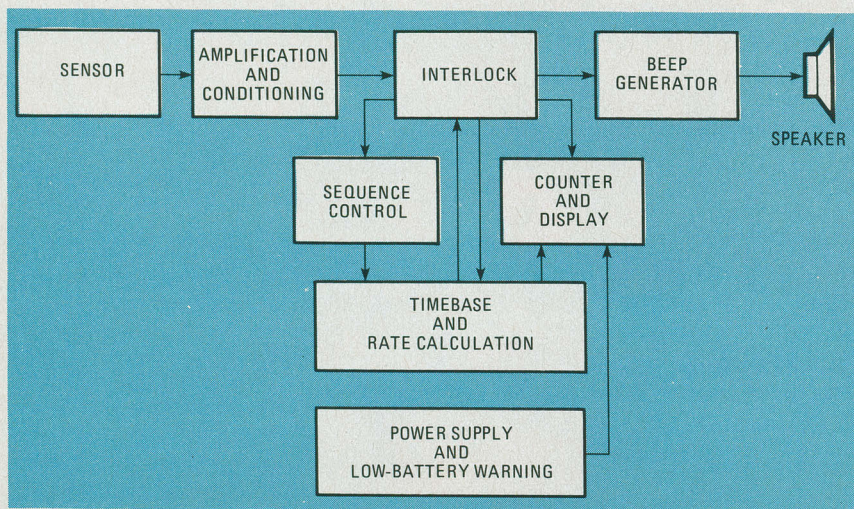


FIG. 2—THE HEART-A-MATIC is made up of eight main sections as shown in this block diagram of the device.

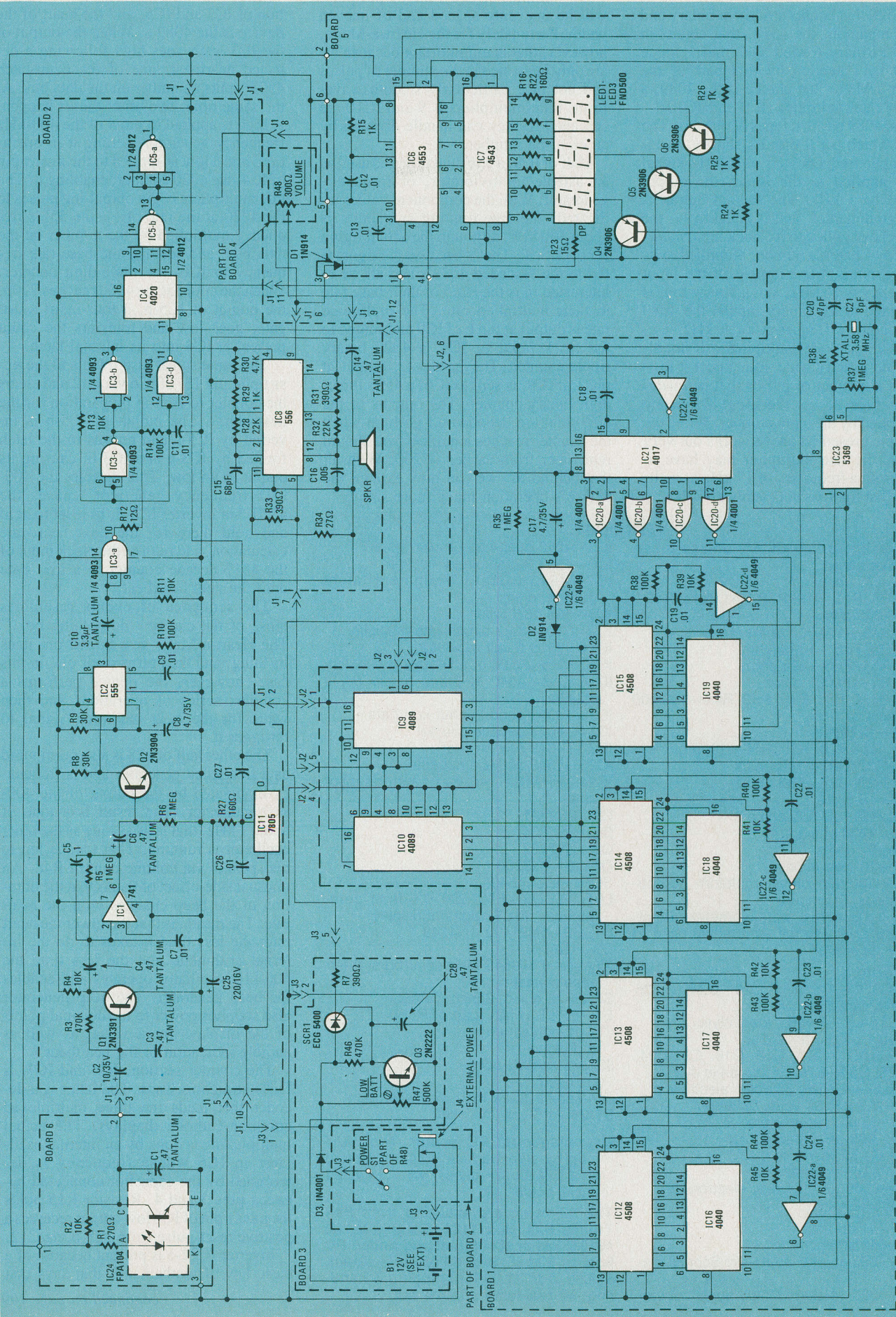


FIG. 3 SCHEMATIC DIAGRAM of the Heart-a-Matic. The device is built on six separate PC boards.

the difference between a counter such as the 4520 that counts strictly in binary and its companion, the 4518, that counts in BCD (Binary-Coded Decimal). Since BCD isn't needed by this part of the Heart-a-Matic, the choice is the 4089, a binary rate-multiplier (IC9 and IC10).

The 4089 has two types of outputs. The first, which we'll discuss shortly, is $\frac{1}{16}$ the input frequency; if a 16-kHz signal were applied to the input, the output would be 1 kHz. The second output is "programmable" and is equal to $\frac{1}{16}$ the frequency applied to its clock input *multiplied* by whatever number is applied to its binary inputs. For example, if the input frequency is 16 kHz, and a binary four is presented to the binary inputs, the 4089 will output a frequency of 4 kHz. Unfortunately, a rate multiplier will not always do exactly what you expect it to—output a number of pulses that is *always* an *average* of $\frac{1}{16}$ the input frequency multiplied by the input number. While the example presented above works out very nicely, the rate multiplier may have to work with a frequency of 17 kHz as well. Since that figure is not evenly divisible by

2 (or multiples of two), the output pulse will be unevenly spaced and of uneven width. Fortunately for the Heart-a-Matic, however, that is unimportant because we are only interested in the number of pulses and not in a particularly smooth waveform. Rate-multipliers IC9 and IC10 are cascaded so they can handle division by an eight-bit number.

Half of IC8, a 556 dual timer, is used as an astable multivibrator, or frequency generator. With the component values indicated, the free-running frequency is about 400 kHz, although the actual figure is not critical. That's because the signal is fed to the cascaded 4089's and all we're interested in is the *ratio* of their base rate to their multiplied rate. The multiplied rate is output at pin 6 of IC9 and routed to the clock input of IC4, a 4020 binary ripple-counter. The base rate, output at pin 1 of IC9, is sent to IC6, a 4553 three-digit binary counter. The outputs of the 4020 that are decoded all go high when the counter reaches a number you should remember from earlier—7200. With all that behind us, we can now explain the device's operation much more simply.

The controlling key is the interlock section of IC3 and IC5, and the heart of the device is the 4089's. When the output of the IC3 latch goes high following a detected heartbeat, one of the octal-latch 4508's puts a number on the data bus. At the same time, two other things happen. A high is applied to pin 4 of the 400-kHz frequency generator, setting it in operation, and a low is applied to the RESET pin of IC4, the 4020 counter, enabling it. The rate multipliers begin outputting pulses to the 4020 at the rate of $\frac{1}{16}$ the 556's frequency multiplied by the number on the data bus, and sending the base-rate frequency to IC6, the three-digit counter. When the count at the 4020 reaches 7200, the output of IC5-b, a four-input NAND gate, goes low and transfers the count present at IC6 into its internal latch.

The same signal also travels to the RESET pin, pin 13, of IC6 via C12 and clears the counter to zero in preparation for the next count. The output of IC5-b is inverted by IC5-a and returns to the latch formed by IC3-a and IC3-b, causing its output to go low. That disables the 400-kHz frequency generator, causes the 4020, via inverter IC3-d, to reset to zero and hold there for the next heart-rate calculation, and returns the clock input of the 4017 decade counter to a low state until the next heartbeat.

The sequence of events resembles those of the classic "do-nothing box." The Heart-a-Matic gets turned on, does its thing, and then turns itself off. In this case, however, the device performs a complex series of operations and then waits for the next incoming signal to retrigger it.

The other half of IC8 is also configured as a frequency generator and is frequency-modulated by the output of the 400-kHz generator. The result is a tone of about 1 kHz, that lasts as long as the other oscillator is running. That tone is fed to the speaker via volume-control R48. An unusual side-effect of that is that the duration of the beep changes with the heart rate. The reason is that the lower the heart rate, the less time it takes to do the internal arithmetic and the less time the 400-kHz oscillator operates and enables the beep generator. The beep generator also supplies power to the decimal points of the displays for a visual as well as audible indication of the heartbeat.

The counter section, IC6 and IC7, is fairly straightforward. The latter is a decoder that feeds the three multiplexed common-cathode displays. The actual multiplexing is done by an internal oscillator in IC6 whose frequency is determined by the capacitor connected between pins 3 and 4. Resistor R15 holds the RESET pin of IC6 low until it receives a positive reset-pulse from IC5-b via C12.

Inverter IC22-e is present because of a basic law of mathematics that says that

PARTS LIST

All resistors $\frac{1}{4}$ -watt, 5% unless otherwise noted

R1—270 ohms
R2, R4, R11, R13, R39, R41, R43, R45—10,000 ohms
R3, R46—470,000 ohms
R5, R6, R35—1 megohm
R7, R31, R33—390 ohms
R8, R9—30,000 ohms
R10, R14, R38, R40, R42, R44—100,000 ohms
R12—12 ohms
R15, R24-R26, R29, R36—1000 ohms
R16-R22, R27—160 ohms
R16-R22, R27—160 ohms
R23—15 ohms
R28, R32—22,000 ohms
R30—4700 ohms
R34—27 ohms
R37—10 megohms
R47—500,000 ohms, multiturn potentiometer, PC-mount
R48—300 ohms, potentiometer, panel-mount with switch (commonly used in TV receivers)

Capacitors

C1, C3, C4, C6, C14, C28—0.47 μ F, 35 volts, tantalum
C2—10 μ F, 35 volts, electrolytic
C5—0.1 μ F, ceramic disc
C7, C9, C11-C13, C18, C19, C22-C24, C26, C27—0.01 μ F, ceramic disc
C8, C17—4.7 μ F, 35 volts, electrolytic
C10—3.3 μ F, 35 volts, tantalum
C15—68 pF, ceramic disc
C16—.005 μ F, ceramic disc
C20—47 pF, ceramic disc
C21—8 pF, ceramic disc
C25—2200 μ F, 16 volts, electrolytic

Semiconductors

IC1—741 op-amp
IC2—555 timer
IC3—4093 quad 2-input NAND Schmitt trigger
IC4—4020 14-stage binary ripple counter

IC5—4012 dual 4-input NAND gate
IC6—4553 3-digit binary counter
IC7—4543 BCD-to-7-segment latch/decoder/driver
IC8—556 dual timer
IC9, IC10—4089 binary rate multiplier
IC11—7805 5-volt regulator
IC12-IC15—4508 dual 3-state 4-bit latch
IC16-IC19—4040 12-stage binary ripple counter
IC20—4001 quad 2-input NOR gate
IC21—4017 decade counter
IC22—4049 hex inverter
IC23—5369 60-Hz timebase
IC24—FPA104 infra-red emitter/sensor array
Q1—2N3391
Q2—2N3904
Q3—2N2222
Q4-Q6—2N3906
SCR1—ECG 5400
LED1-LED3—FND500 0.5-inch common-cathode 7-segment display
D1, D2—1N914 or 1N4148
D3—1N4001
XTAL1—3.579545 MHz color-burst reference crystal
SPKR—8 ohms, 2-inch diameter
S1—SPST switch (part of R48)
J1—12-contact edge connector
J2, J36—contact edge connector
J4—subminiature N.C., chassis-mount
B1-B8—1.5-volt "AA" cell

Miscellaneous: PC boards, two "AA" side-by-side battery holders, Velcro strip, plastic for cases, wire, shielded cable, solder, etc.

The following are available from Hal-Tronix, P.O. Box 1101, Southgate, MI 48195: Set of six etched and drilled PC boards, \$29.95; Board 1 (double-sided), \$19.95. Add \$2.00 for shipping & handling; MI residents add 4% tax.

the difference between a counter such as the 4520 that counts strictly in binary and its companion, the 4518, that counts in BCD (*Binary-Coded Decimal*). Since BCD isn't needed by this part of the Heart-a-Matic, the choice is the 4089, a binary rate-multiplier (IC9 and IC10).

The 4089 has two types of outputs. The first, which we'll discuss shortly, is $\frac{1}{16}$ the input frequency; if a 16-kHz signal were applied to the input, the output would be 1 kHz. The second output is "programmable" and is equal to $\frac{1}{16}$ the frequency applied to its clock input *multiplied by whatever number is applied to its binary inputs*. For example, if the input frequency is 16 kHz, and a binary four is presented to the binary inputs, the 4089 will output a frequency of 4 kHz. Unfortunately, a rate multiplier will not always do exactly what you expect it to—output a number of pulses that is *always* an *average* of $\frac{1}{16}$ the input frequency multiplied by the input number. While the example presented above works out very nicely, the rate multiplier may have to work with a frequency of 17 kHz as well. Since that figure is not evenly divisible by

2 (or multiples of two), the output pulse will be unevenly spaced and of uneven width. Fortunately for the Heart-a-Matic, however, that is unimportant because we are only interested in the number of pulses and not in a particularly smooth waveform. Rate-multipliers IC9 and IC10 are cascaded so they can handle division by an eight-bit number.

Half of IC8, a 556 dual timer, is used as an astable multivibrator, or frequency generator. With the component values indicated, the free-running frequency is about 400 kHz, although the actual figure is not critical. That's because the signal is fed to the cascaded 4089's and all we're interested in is the *ratio* of their base rate to their multiplied rate. The multiplied rate is output at pin 6 of IC9 and routed to the clock input of IC4, a 4020 binary ripple-counter. The base rate, output at pin 1 of IC9, is sent to IC6, a 4553 three-digit binary counter. The outputs of the 4020 that are decoded all go high when the counter reaches a number you should remember from earlier—7200. With all that behind us, we can now explain the device's operation much more simply.

The controlling key is the interlock section of IC3 and IC5, and the heart of the device is the 4089's. When the output of the IC3 latch goes high following a detected heartbeat, one of the octal-latch 4508's puts a number on the data bus. At the same time, two other things happen. A high is applied to pin 4 of the 400-kHz frequency generator, setting it in operation, and a low is applied to the RESET pin of IC4, the 4020 counter, enabling it. The rate multipliers begin outputting pulses to the 4020 at the rate of $\frac{1}{16}$ the 556's frequency multiplied by the number on the data bus, and sending the base-rate frequency to IC6, the three-digit counter. When the count at the 4020 reaches 7200, the output of IC5-b, a four-input NAND gate, goes low and transfers the count present at IC6 into its internal latch.

The same signal also travels to the RESET pin, pin 13, of IC6 via C12 and clears the counter to zero in preparation for the next count. The output of IC5-b is inverted by IC5-a and returns to the latch formed by IC3-a and IC3-b, causing its output to go low. That disables the 400-kHz frequency generator, causes the 4020, via inverter IC3-d, to reset to zero and hold there for the next heart-rate calculation, and returns the clock input of the 4017 decade counter to a low state until the next heartbeat.

The sequence of events resembles those of the classic "do-nothing box." The Heart-a-Matic gets turned on, does its thing, and then turns itself off. In this case, however, the device performs a complex series of operations and then waits for the next incoming signal to retrigger it.

The other half of IC8 is also configured as a frequency generator and is frequency-modulated by the output of the 400-kHz generator. The result is a tone of about 1 kHz, that lasts as long as the other oscillator is running. That tone is fed to the speaker via volume-control R48. An unusual side-effect of that is that the duration of the beep changes with the heart rate. The reason is that the lower the heart rate, the less time it takes to do the internal arithmetic and the less time the 400-kHz oscillator operates and enables the beep generator. The beep generator also supplies power to the decimal points of the displays for a visual as well as audible indication of the heartbeat.

The counter section, IC6 and IC7, is fairly straightforward. The latter is a decoder that feeds the three multiplexed common-cathode displays. The actual multiplexing is done by an internal oscillator in IC6 whose frequency is determined by the capacitor connected between pins 3 and 4. Resistor R15 holds the RESET pin of IC6 low until it receives a positive reset-pulse from IC5-b via C12.

Inverter IC22-e is present because of a basic law of mathematics that says that

continued on page 109

PARTS LIST

All resistors $\frac{1}{4}$ -watt, 5% unless otherwise noted

R1—270 ohms
R2, R4, R11, R13, R39, R41, R43, R45—10,000 ohms
R3, R46—470,000 ohms
R5, R6, R35—1 megohm
R7, R31, R33—390 ohms
R8, R9—30,000 ohms
R10, R14, R38, R40, R42, R44—100,000 ohms
R12—12 ohms
R15, R24-R26, R29, R36—1000 ohms
R16-R22, R27—160 ohms
R16-R22, R27—160 ohms
R23—15 ohms
R28, R32—22,000 ohms
R30—4700 ohms
R34—27 ohms
R37—10 megohms
R47—500,000 ohms, multiturn potentiometer, PC-mount
R48—300 ohms, potentiometer, panel-mount with switch (commonly used in TV receivers)

Capacitors

C1, C3, C4, C6, C14, C28—0.47 μ F, 35 volts, tantalum
C2—10 μ F, 35 volts, electrolytic
C5—0.1 μ F, ceramic disc
C7, C9, C11-C13, C18, C19, C22-C24, C26, C27—0.01 μ F, ceramic disc
C8, C17—4.7 μ F, 35 volts, electrolytic
C10—3.3 μ F, 35 volts, tantalum
C15—68 pF, ceramic disc
C16—.005 μ F, ceramic disc
C20—47 pF, ceramic disc
C21—8 pF, ceramic disc
C25—2200 μ F, 16 volts, electrolytic

Semiconductors

IC1—741 op-amp
IC2—555 timer
IC3—4093 quad 2-input NAND Schmitt trigger
IC4—4020 14-stage binary ripple counter

IC5—4012 dual 4-input NAND gate
IC6—4553 3-digit binary counter
IC7—4543 BCD-to-7-segment latch/decoder/driver
IC8—556 dual timer
IC9, IC10—4089 binary rate multiplier
IC11—7805 5-volt regulator
IC12-IC15—4508 dual 3-state 4-bit latch
IC16-IC19—4040 12-stage binary ripple counter
IC20—4001 quad 2-input NOR gate
IC21—4017 decade counter
IC22—4049 hex inverter
IC23—5369 60-Hz timebase
IC24—FPA104 infra-red emitter/sensor array
Q1—2N3391
Q2—2N3904
Q3—2N2222
Q4-Q6—2N3906
SCR1—ECG 5400
LED1-LED3—FND500 0.5-inch common-cathode 7-segment display
D1, D2—1N914 or 1N4148
D3—1N4001
XTAL1—3.579545 MHz color-burst reference crystal
SPKR—8 ohms, 2-inch diameter
S1—SPST switch (part of R48)
J1—12-contact edge connector
J2, J36—contact edge connector
J4—subminiature N.C., chassis-mount
B1-B8—1.5-volt "AA" cell

Miscellaneous: PC boards, two "AA" side-by-side battery holders, Velcro strip, plastic for cases, wire, shielded cable, solder, etc.

The following are available from Hal-Tronix, P.O. Box 1101, Southgate, MI 48195: Set of six etched and drilled PC boards, \$29.95; Board 1 (double-sided), \$19.95. Add \$2.00 for shipping & handling; MI residents add 4% tax.

BUILD THIS

Part 2 THE FIRST PART OF THIS article discussed the theory of operation of a good portion of the main board of the Picture Phone. We'll now complete that discussion; it will be helpful if you have Part 1 handy.

Fast-scan counters

The fast-scan counters are IC6, IC8, IC23 and IC39. Each IC is a four-stage binary counter that is cleared to all zeroes when pin 1 is taken to a logic-low state. When pin 9 is low, the counter stages are preset to the value hard-wired at pins 3-6. Pin 2 receives the clock pulses, and responds to their positive-going edges. Both clear and load operations are synchronous—that is, they take place only on the positive-going edge of the clock pulse. When the LOAD or CLEAR pin is taken low, the counter stops and retains its value. If a clock pulse occurs while the appropriate pin is low, the counter will load or clear.

The fast-scan dot counters are IC6 and IC8 (dots are the pixels along a line of video). The dot counter is analogous to the horizontal sweep in the camera and display. The dot counters have two modes, one for the camera and one for all other operations.

Let's consider non-camera operation first. The crystal oscillator supplies clock pulses to pin 2 of the dot counters. Note that pin 15 of IC6 is connected to pin 10 of IC8. That is the "carry" from the first IC to the second, and provides synchronous operation of both IC's.

Figure 5 shows the timing of the dot counters. The counter CLEAR pulse is provided by IC10 at a count of 215. That means that the counter advances to 215, is reset to zero, and begins to count again. The internal horizontal-sync pulse (IFH) is produced by counter inputs applied to IC42. The clock frequency, divided by 216 (the count from zero to 215), generates the correct horizontal-sync frequency.

Signal "J," which is low between the counts of zero and 127, serves several purposes. It is delayed by one clock pulse

to form IFHB, the internal fast-scan blanking signal, which blanks the display in all modes. That signal is also applied to IC28 to control when data can be written to memory. Memory-write takes place, and the display is unblanked, when the counter is between zero and 127.

Now let's look at the operation of the dot counter in the "snatch" and camera-display modes. The clocking signal is derived from the synchronous oscillator;

starts with the same polarity.

The fast-scan line counters are IC23 and IC39. Let's first look at how they work during the non-camera mode. Dot-counter signal "J" is used as the clock pulse, making the line counter advance one step for each line. Nine count-stages are needed; the extra stage is supplied by IC32 and is the least significant bit.

Figure 6 shows that the counter advances to a count of 262, is cleared, and starts again at zero.

The clear pulse is supplied by IC47, which is hard-wired with the eight most-significant bits of the line counter. The CLEAR pin is held inactive when the camera is in use by connecting it to the logic-1 present at pin 10 of IC48.

The internal fast-scan vertical sync (IFV) comes from IC31.

When the camera display is viewed, the CLEAR function is disabled and the line counter is preset whenever a vertical-sync pulse occurs. When the counter is preset and the sync pulse from the camera is completed, the counter starts counting. When the count reaches 511, the next count, zero, allows display and writing to memory to begin. The time that is spent in counting from the preset


value to zero is used to allow the camera's blanking-function to be completed.

The line counter advances two counts for each slow-scan line to allow each line to be displayed twice for an easier-to-view picture. There are 128 slow-scan lines, which means that 256 lines-per-field (or 512 lines-per-frame) will be displayed. Since NTSC standards call for 525 lines per frame, a small portion of the picture at the top and bottom is blanked.

Slow-scan clocks

There are two slow-scan clocks. One is derived from the master crystal oscillator and is used for all functions except slow-scan reception. The second clock is free-running, and is synchronized to the slow-scan horizontal-sync pulses. The clocks are selected by IC13, a 4PDT multiplexer.

Picture Phone

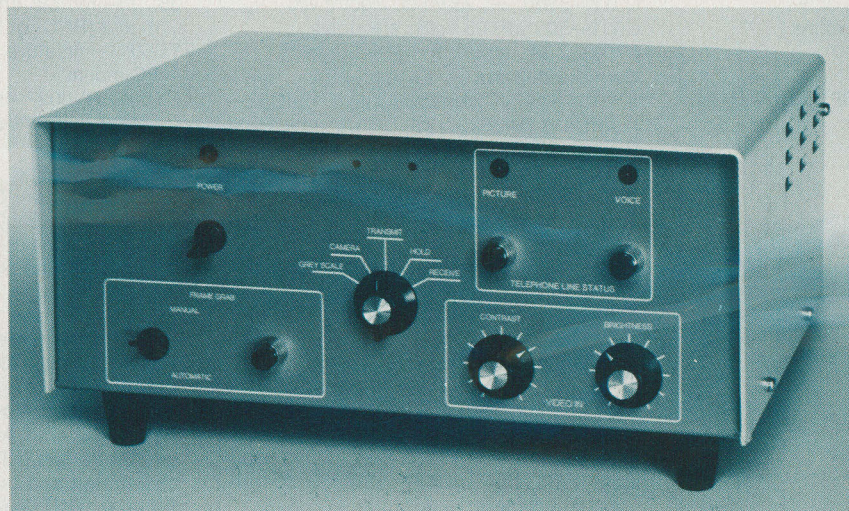

Before you build your Picture Phone, you should know how the device works. We'll conclude our discussion of that topic in this part.

JOSEF BERNARD,
TECHNICAL EDITOR

and IC10, which supplies the CLEAR pulse, is disabled. The counter advances until a horizontal-sync pulse from the camera (EFH) takes the LOAD pin low. The counter is preset to a value of 217, as determined by the fixed inputs to pins 3-6 of IC6 and IC8. The counter resumes counting at a preset value of 217 when EFH is no longer present. When it reaches its maximum count of 255, it resets to zero and starts counting again. The time spent counting from 217 to 255 represents blanking of the left-hand edge of the picture; the time between 128 and EFH is used for right-hand blanking.

The LOAD pin is controlled by an RS flip-flop made from IC15-c and IC15-d. That flip-flop insures that the LOAD pin remains low until a clock pulse to load the counter has arrived.

The EFH signal is applied to the CLEAR pin of IC32 to insure that the clock always

PARTS LIST

All resistors 1/4-watt, 5% unless otherwise noted

R1-R3, R43, R78, R139, R202—22,000 ohms
 R4, R201—10 megohms
 R5, R6, R8, R9, R50, R80—15,000 ohms
 R7—620 ohms
 R10, R12, R15, R54, R93-R95, R102, R110, R209, R211, R714-R716—4700 ohms
 R11, R13, R14, R16-R18, R86, R99—10,000 ohms, 1%
 R19, R20, R27, R147—39,000 ohms
 R21—20,000 ohms
 R22, R23—18,000 ohms
 R24—8200 ohms
 R25, R26, R145, R146—82,000 ohms
 R28, R42, R51, R136, R140, R142, R204, R205, R710, R711—10,000 ohms
 R29—470,000 ohms
 R30, R47-R49, R53—2200 ohms
 R31, R79, R148—100,000 ohms
 R32, R108—2700 ohms
 R33—150,000 ohms
 R34, R40, R52, R96, R109, R137, R144, R704, R717—1000 ohms
 R35-R39—not used
 R41—680,000 ohms
 R44—47,000 ohms
 R46—33,000 ohms
 R55, R76, R112, R707—100 ohms
 R56—100 ohms, trimmer potentiometer
 R57—3300 ohms
 R58, R77, R111—330 ohms
 R59, R703, R712, R713—470 ohms
 R60—100 ohms, 1%
 R61-R75—26.1 ohms, 1%
 R81-R84—not used
 R85, R98—20,000 ohms, 1%
 R87, R100—4990 ohms, 1%
 R88, R101—2490 ohms, 1%
 R89-R91—not used
 R92, R200—680 ohms
 R97—47 ohms
 R103—820 ohms
 R104—2000 ohms, trimmer potentiometer
 R105—1200 ohms
 R106, R107, R138, R141, R143, R203—1000 ohms, trimmer potentiometer
 R113-R116, R125-R135—33 ohms
 R117-R123—not used
 R144—68,000 ohms
 R149-R199—not used
 R206, R207—220 ohms
 R210—560 ohms
 R212, R213—33.2 ohms, 1%
 R314, R315, R317, R318—0.33 ohms, 2 watts
 R316—220 ohms, 2 watts
 R601—130 ohms, 2 watts
 R701—1000 ohms, panel-mount potentiometer
 R702—10,000 ohms, panel-mount potentiometer
 R706—1 megohm
 R708, R709—1800 ohms, 1 watt

All capacitors Mylar or mica unless otherwise specified

C1-C6—.022 μ F
 C7, C24, C25, C38, C200, C240-C243—.01 μ F ceramic disc
 C8, C10, C12, C17—.0047 μ F
 C9—.0068 μ F
 C11, C207—.018 μ F
 C13, C15, C18, C19, C23, C263-C266—22 μ F, tantalum

C14—10 μ F, tantalum
 C16, C22, C206, C703—.001 μ F, monolithic or ceramic disc
 C20, C201—27 pF, monolithic or ceramic disc
 C21, C28-C31—470 pF
 C26—not used
 C27—33 pF, monolithic or ceramic disc
 C32, C220-C227—0.1 μ F, ceramic disc
 C33, C41, C208, C317-C320—2.2 μ F, tantalum
 C34, C230-C237, C250-C262, C702—0.1 μ F, ceramic disc
 C35, C202-C205—100 pF
 C37, C39—not used
 C40—.047 μ F
 C309—500 μ F, 12 volts, electrolytic
 C310—9200 μ F, 15 volts, electrolytic
 C311—450 μ F, 25 volts, electrolytic
 C312—5800 μ F, 25 volts, electrolytic
 C601—500 μ F, 25 volts, electrolytic
 C701—2 μ F, tantalum

Semiconductors

IC1-IC4, IC17-IC20, IC33-IC36, IC49-IC52— μ PD411 (MM5280) 4K \times 1 dynamic RAM
 IC5, IC13, IC21, IC37, IC46, IC48, IC55—74LS157 quad 2-1 multiplexer
 IC6, IC8, IC9, IC23, IC24, IC39-IC41—74LS163 presetable binary counter W/ clear
 IC7, IC26, IC57, IC58, IC61—75LS04 hex inverter
 IC10, IC31, IC47—74LS30 8-input NAND gate
 IC11, IC32—74LS107 dual JK negative-edge-trigger flip-flop
 IC12—4046 CMOS phase-locked loop
 IC14, IC15, IC45—74LS00 quad 2-input NAND gate
 IC16, IC29, IC65—74LS74 dual D flip-flop
 IC22, IC38, IC71, IC72—74LS153 dual 4-input multiplexer
 IC25, IC42, IC88—74LS20 dual 4-input NAND gate
 IC27, IC67, IC68—74LS10 triple 3-unit NAND gate
 IC28, IC43, IC66—74LS25 dual 4-input NOR gate
 IC30—74LS221 dual one-shot
 IC44, IC62—74LS32 quad 2-input positive OR gate
 IC54, IC56—74LS175 quad D flip-flop
 IC59—74LS08 quad 2-input AND gate
 IC60, IC63, IC64—74LS13 dual Schmitt trigger
 IC66—3245 quad TTL-to-NMOS memory driver
 IC69, IC70—74LS02 quad 2-input NOR gate
 IC73-IC80—LM711 dual difference-comparator
 IC81-IC84—not used
 IC85, IC86—74LS86 quad EXCLUSIVE-OR gate
 IC87—4066 CMOS quad bilateral switch
 IC89—566 function generator
 IC90-IC94, IC105—1458 dual 741 op-amp
 IC95-IC104—not used
 Q1, Q2, Q4, Q5, Q8-Q13—2N4124 or equivalent
 Q3, Q6—not used
 Q7—2N4126 or equivalent
 LED1-LED3—jumbo red LED
 D1-D11, D13-D18, D27-D33—1N914 or 1N4148
 D12—not used
 D19-D26, D601, D602—1N4007
 DT601—gas discharge tube (Joslyn Electronics type 2022-44 or equivalent)

CB1—0.6-amp circuit breaker
 T1—dual-secondary type: 1st secondary: 25VCT, 1 amp; 2nd secondary: 12.6VCT, 1.5 amps (see text and below)
 T601—phone-line matching transformer (Microtran type 6112 or equivalent)
 S1—4P5T rotary switch
 S2-S4—N.O. momentary pushbutton switch
 S5—SPDT toggle switch
 S6—SPST toggle switch
 J1-J2—not used
 J3—36/72-pin PC-board edge connector (36 contacts for *each side* of board, two contacts per pin)
 J4—socket for modular telephone connector, panel-mount
 J5—DB25-S 25-pin female "date-type" socket, panel-mount
 J6, J7—RCA-type phone jack, panel-mount
 J8, J9—female coaxial connector, panel-mount (BNC- or SO230-type)
 TB601—miniature 8-terminal barrier strip, PC-mount
 RY601, RY602—4P2T 12-volts, PC-mount (Potter & Brumfield T10-E2-Z4-12VDC or equivalent)

Miscellaneous: PC boards, perforated construction board, IC sockets, RG59 cable, shielded audio cable, 4-conductor telephone cable w/modular plug, 3-conductor line cord w/plug, enclosure, hardware, etc.

The following are available from Robot Research Inc., 7591 Convoy Court, San Diego, CA 92111, (714) 279-9430: **Assembled & tested Model 535 Picture Phone**, FCC registered for direct connection to telephone line (KIT-1) (14 lbs.), \$1195.00; **assembled and tested No. 400929C main PC board (KIT-2)** (4 lbs.), \$495.00; **assembled and tested Picture Phone chassis, including telephone adaptor board, but less main board, (KIT-3)** (12 lbs.), \$695.00; **kit of No. 400929C main PC board with all main-board parts (KIT-4)** (5 lbs.), \$295.00; **kit including chassis and chassis parts, and telephone adaptor board and parts, but less main board, (KIT-5)** (12 lbs.), \$445.00; **telephone adaptor board kit including board and parts (KIT-6)** (3 lbs.), \$79.50; **etched, drilled, and plated-through main board (KIT-7)** (3 lbs.), \$59.00; **etched, drilled, and plated-through telephone adaptor board (KIT-8)** (2 lbs.), \$19.95; **T1 (KIT-9)** (4 lbs.), \$29.50; **T601 (KIT-10)** (2 lbs.), \$24.50; **DT1 (KIT-11)** (1 lb.), \$8.50; **kit of 32 1% resistors for main board (KIT-12)** (1 lb.), \$12.00; **individual 1% resistor (KIT-13)** (1 lb.), \$0.35; **Model 535 Picture Phone enclosure kit with mounting rails for main board and back plate for controls (KIT-14)** (6 lbs.), \$99.50; **kit of front panel parts only, (KIT-15)** (2 lbs.), \$59.50; **assembled & tested RF modulator, less power supply and enclosure (KIT-16)** (1 lb.), \$29.00; **RF-modulator kit, less power supply and enclosure (KIT-17)** (1 lb.), \$19.50. For information on other parts, write to Robot Research.

CA residents please add 6% sales tax. All prices F.O.B. San Diego—check with UPS for shipping charges; please add \$0.50 per \$100.00 of value above first \$100.00 for insurance. MC and Visa accepted.

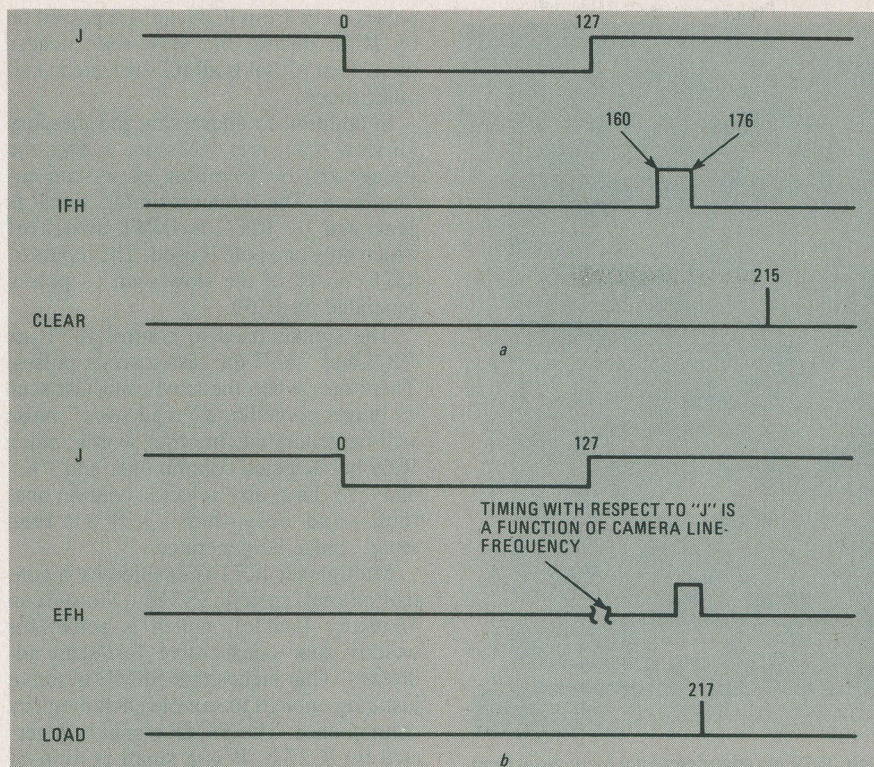


FIG. 5—FAST-SCAN dot counter has two modes—*a* is used for memory display, *b* for frame grabbing and camera display.

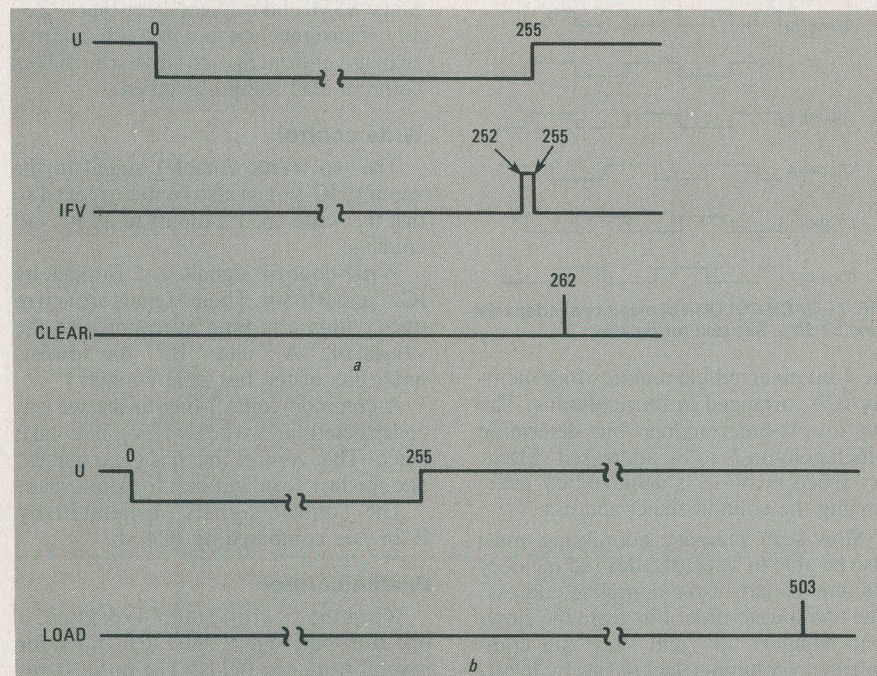


FIG. 6—FAST-SCAN line counter timing for memory display (*a*), and camera display (*b*).

The crystal-derived clock pulses begin with the 60-Hz "U" output of the fast-scan counter. It is divided by four by IC11. The resulting 15-Hz pulse train is applied to one input of PLL (Phase-Locked Loop) IC12. The other input to that IC is the clock oscillator's output divided by 139, making the output of the PLL 15×139 , or 2085 Hz. That becomes the slow-scan clock. It allows for 128 pixels and 11 sync counts per slow-scan line.

The synchronized clock pulses are

generated by IC60. Its free-running frequency is controlled by R143. As the frequency is increased, the counter takes less time to address 128 memory "cells" and a shorter line is displayed. The clock is synchronized with the incoming signal by having the incoming slow-scan sync pulses cause the oscillator to stop and restart in phase with them.

The slow-scan clock is aligned with the fast-scan system by retiming the leading and training edges of the clock pulses with a section of IC16. A control signal,

CAUTION:

FCC regulations prohibit the connection of this device to telephone lines without the use of an approved coupling device. The *only* exception to this is the assembled and tested unit available from the suppliers indicated in the Parts List. A coupler that meets FCC requirements will be described in the next part of this article. *Do not attempt to connect the Picture Phone you build without it—it's illegal to do so.*

"Z," controls all the slow-scan functions. It is in operation only for the duration of the slow-scan memory-write cycle. Its use for retiming the slow-scan insures that the clock will not change during a slow-scan read or write memory access.

Slow-scan counters

The slow-scan counter is made up of IC9, IC24, IC40 and IC41. They function the same way as their counterparts in the fast-scan circuit.

The slow-scan dot counter uses IC9 and IC24. It has two modes of operation—one to write slow scan to memory, and one to read it. Let's look at the read-mode first. The clock signal is derived from the crystal oscillator. The CLEAR signal is derived from IC25; the LOAD function is inactive. The counter is cleared at a count of 139 to provide 128 memory "cells" per line and 11 sync counts.


When slow scan information is to be written to memory, the free-running clock is used. The CLEAR signal is derived from a flip-flop formed from IC14-a and IC14-b. The flip-flop is set by an incoming sync pulse, and reset by a clock pulse. That is done to make sure that a clock pulse to clear the counter occurs while the CLEAR pin is low. The slow-scan sync pulse is allowed to reset the counter only after 128 counts (the end of a line) to insure noise immunity. In other words, false pulses can't interrupt a line as it is being written.

The line counter uses IC40 and IC41. A clock pulse occurs when each slow-scan line has been completed. The counter is reset to zero in the "read" mode at a count of 127 by the "U" signal. In the "write" mode it is cleared by the external vertical-sync signal applied to an RS flip-flop made from IC14-c and IC14-d. The flip-flop is reset by IC43 and IC45-a.

When a picture is grabbed from the camera, the line counter is set to all ones, and on the next clock pulse to all zeroes. That one-line time generates a slow-scan vertical-sync pulse.

Address selector

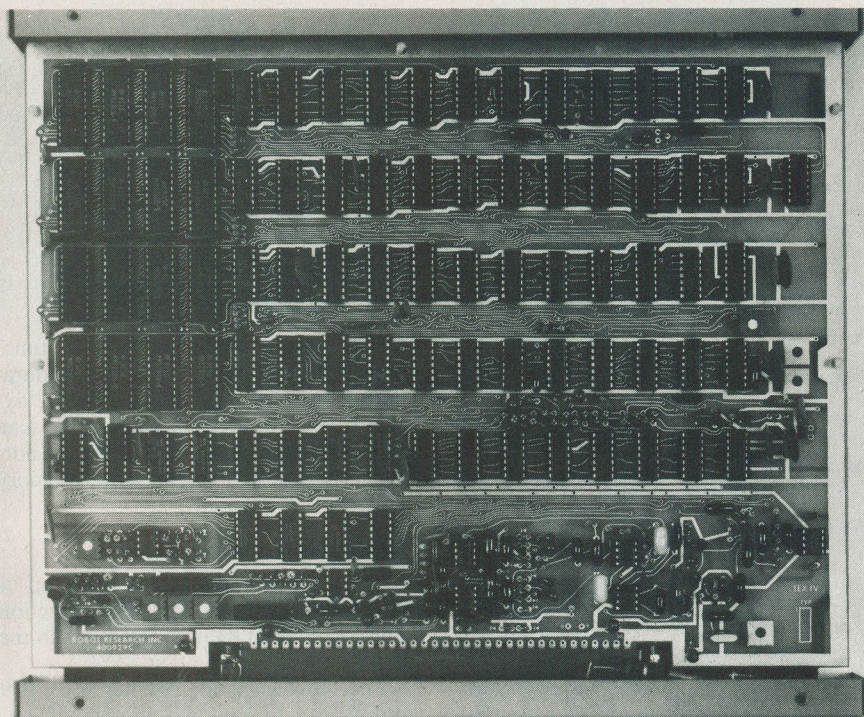The memory address-lines are driven by the fast-scan counter to generate a video signal for fast-scan display, and also by the slow-scan counter to generate a slow-scan signal. The memory address-



COMPLETED MAIN BOARD of the Picture Phone plugs into 36/72-pin edge connector mounted at front of enclosure.

lines are connected to the appropriate counter by an address multiplexer made up of IC5, IC21 and IC37—4PDT switches, each of which switches four address lines. Resistors on the leads to the memory IC's damp reflections so that the address voltages will not ring.

The address lines are in the "slow scan" mode during time "Z," which takes place for 16 dots following the right-hand edge of the fast-scan picture. In other words, slow-scan memory access takes place just after fast-scan access for the current line is completed. When "Z" becomes active, the address multiplexer switches to slow scan, and the slow-scan counter is inhibited from changing state. The "Z" signal is generated by IC25-b.

Fast-scan memory multiplex

To obtain the speed required for fast-scan operation, memory operation is multiplexed. The multiplexing is done with the memory CE (Chip Enable) pulse. Figure 7 shows the CE pattern. Note that successive memory columns are overlapped by 50%.

The CE signal is formed by a delay flip-flop, IC65, that uses "B" as data and "A" (delayed) as a clock signal. Signal "A" is delayed by an RC circuit that feeds Schmitt trigger IC60. The delay is provided to insure that memory address-lines are stable before CE goes high.

The CE signal is a zero-to-+12-volt pulse translated from 5-volts by IC66.

Slow-scan memory multiplex

Memory multiplexing is performed by the two lowest-order bits on the memory address-lines. In other words, each bit of

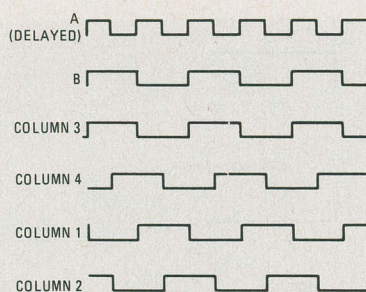


FIG. 7—EACH COLUMN of memory overlaps the next by 50%. See text for details.

the 4-bit pixel nybble requires four memory IC's, arranged in four columns. The two lowest-order address bits determine which column is to be addressed. Memory-speed increase is achieved by overlapping the column-select address.

Slow-scan memory addressing must also be able to select the desired memory column as part of the complete address. The two lowest-order bits from the slow-scan counter, "a" and "b," are combined into column-select pulses by IC69.

Each of the 16 memory IC's has a CS (Chip Select) pin that is used for slow-scan memory column selections. The CS

pulses come from IC69 and are passed on by IC70 during the slow-scan access time. That IC holds all IC's selected at all other times.

In addition to addressing the memory for slow scan, it is necessary to time the storage of the incoming slow-scan information. The required timing signal is generated by IC71, a DP4T switch of which only one pole is used. The inputs of IC71 consist of the slow-scan CS pulses generated by IC69.

The signals used to control IC71 are "X" and "Y," the fast-scan CS pulses. Therefore, when the slow- and fast-scan CS pulses coincide, a "read store" pulse will be generated. In other words, when IC69 has selected column one, and "X" and "Y" have also selected column one, then—and only then—will a "read store" pulse be generated.

Multiplexer IC71 is enabled by a control signal called SSME (Slow-Scan Memory Enable), which is active for exactly four consecutive fast-scan addresses. That means that SSME is active just long enough to sample each memory column once. The SSME signal is generated by IC27-b. It is a small portion of "Z," which is the time for slow-scan address to be applied to the memory. Since SSME takes place later than "Z," any transients created by the address switchover from fast- to slow-scan die out before a read sample is taken.

Write control

The WE (Write Enable) signal to the memory IC's must also be multiplexed so that the write and CE inputs to an IC will coincide.

Write-control signals are formed by IC67 and IC68-b. Those signals are active one column at a time in response to the values of "A" and "B," the lowest-order bits of the fast-scan counter.

A common control-line to the WE encoder determines when writing is to take place. That control line has two sources, one for fast scan and one for slow scan.

The control signals, generated by IC28, are combined by IC44-b.

Snatch control

When the SNATCH button is pressed, a one-shot puts out a pulse that lasts for several fast-scan fields. The pulse is retimed by a section of delay flip-flop IC29 so that the useful SNATCH command starts and ends at the bottom of a TV picture. That prevents any errors that might result from the SNATCH pulse ending in the middle of a picture. Another section of IC29 retimes display selection so that the changeover between display memory and the camera takes place when the picture is blanked.

In the next part of this article we'll discuss the telephone interface and power-supply circuits. We will also begin to look at the construction and alignment of the device.

R-E



REAR PANEL of Picture Phone. Circuit-breaker reset is located above line cord at left.

HOW TO

The INS and OUTS of BUYING MAILORDER COMPONENTS

Often, the hardest task in building a project is obtaining the various parts that you need. Keeping a well-stocked junk box can save you a considerable amount of time, effort, and money!

KARL T. THURBER, JR., W8FX

ONE OF THE MOST REWARDING WAYS TO GAIN EXPERIENCE IN ELECTRONICS IS to build electronics projects. Besides the satisfaction of accomplishment, you learn a great deal in the process involved.

Today, it isn't an easy matter to obtain the right parts, at the right time, and at the right price. The search for and selection of electronic components for projects can be a very disheartening job, particularly when it's seemingly impossible to obtain certain parts, or the price you must pay for them is excessive. You *can* get the parts you need, when you need them, and at a reasonable price, if you are willing to take an organized approach to parts procurement and do a good deal of preparatory spade work before picking up soldering iron and pliers.

In this article, we will examine the need to get organized for the task; look at parts-selection criteria and the question of substitutions; review various sources of parts; and discuss details of component identification and testing.

As you'll see, once you have a clear view of the process, shopping for parts is no longer the formidable challenge it might otherwise be.

Catalogs and reference material

Before buying parts, it pays to be organized—to have done some pre-planning before you start looking for specific parts for a given project. Some of the things you can do in advance include laying in a good store of catalogs, reference sheets, and reference books; buying-in-advance “staple” and bargain-priced parts; and setting up a well-stocked junk box.

It surely pays to accumulate a broad range of catalogs. No builder's library is complete without them. With a little effort, you will find that virtually any desired part, or a usable substitute, will be listed in *some-one's* catalog or cross-reference. You may also find that a single firm may

have all, or almost all, of the parts required for a given project, eliminating the need for repeated shopping forays or inefficient orders to a number of mail-order firms. Having a number of catalogs at hand also allows ready price comparisons between firms.

Having a good reference file, or recent issues of major electronics publications such as **Radio-Electronics**; amateur magazines such as *CQ*, *Ham Radio*, and *QST*; and a variety of computer-oriented magazines, *Byte*, *Microcomputing*, and *Popular Computing* will provide a good background. The magazines also list the addresses of the major suppliers, along with their ordering policies. Of course, single-page magazine ads can't include a supplier's full stock, and are no substitute for the catalogs themselves.

Another reason for obtaining the larger catalogs is that those serve as excellent reference files for various components, and often provide good sources of cross-reference data, particularly for solid-state components. Note that many of the distributors offer two or more catalogs, such as a consumer-type catalog oriented to hi-fi or CB, and an industrial catalog that would normally be more suitable.

In addition, you should acquire the factory service manual, schematic diagram, and component parts list for any item of electronics gear you buy. A surprising quantity of semi-professional and professional-electronics equipment is sold today with no more than a *user's manual*, which is of little help in servicing and parts replacement. Obtaining the proper manuals and parts lists while equipment is currently being manufactured is much easier than trying to obtain such materials later on, when needed information may no longer be readily available.

To facilitate original construction, it's worthwhile to have on hand a selection of standard reference books and manuals, as well. The publications required, of course, will depend upon the particular type of project work undertaken. Some of the more important, all-round useful reference texts include the Editors and Engineers' *Radio Handbook*, the *Master Tube Substitution Handbook*, *Transistor Substitution Handbook*, *TTL Data Book*, *Transistor Specifications Manual*, and *Reference Data for Radio Engineers*; the ARRL *Electronics Data Book* and *Radio Amateur's Handbook*, and several others. A handy cross-reference manual is the *Archer Semiconductor Reference Handbook*, a useful guide to Radio Shack's semiconductors that's also a substitution and cross-reference guide for more than 100,000 solid state devices. Another Radio Shack reference is Forrest Mims' *Engineers Notebook*, which contains tried-and-tested applications for most popular linear and digital IC's. Other helpful parts information sources are

Motorola's *Semiconductor Cross-Reference Guide* and *Discrete Hybrid Components Handbook*, Sylvania's *ECG Semiconductor Replacement Guide*; and RCA's *SK Replacement Guide*.

Buying in advance of needs

Is stocking parts in advance of specific project needs a good idea? It's true that with a few judicious purchases, you can stockpile many of the components needed for future projects. On the other hand, an apparent bargain isn't one, unless there's a real prospect of the part or parts ultimately being used.



BUYING LARGE ASSORTMENTS of components and hardware can result in savings, but only if the parts are likely to be used.

Mail-order dealers offer all kinds of special deals—hardware assortments, resistors, knobs, transistors, IC's, potentiometers, transformers, diodes, capacitors, and various surplus components and assemblies. Many of those offerings are indeed bargains, if carefully surveyed and even more carefully purchased. It's generally worthwhile to take advantage of quantity offerings and specialized assortments, tempering one's enthusiasm for a "good deal" with a realistic expectation of when, and if, the contemplated bulk purchase will likely be put to use. A small investment in component assortments usually represents money well spent; however, there is usually little that can be done about a poor choice—you take what you get and hope to be able to use most of it.

For initial stock-up, some useful components include poly-bag assortments of disc ceramic, mica, and small electrolytic capacitors; low-wattage resistors; diodes, and hardware. On the other hand, assortments of precision resistors, large electrolytic capacitors, IC's, and transistors are probably *too* specialized and may not represent good value. The key to selecting true bargains lies in choosing components that you are most likely to use in your projects.

There are some cautions to keep in

mind. Buying in advance of your needs is intended to build an inventory of common parts, not to produce specific parts for an intended project. It's unusual to find just what you need for a particular project from a grab-bag assortment. Whenever you need a *specific* part, order *that* part.

Carefully note the makeup of parts assortments. Are the parts offered all of one (possibly oddball) value, or are they of different values? What are the tolerances and power ratings? Are the leads full-length or too-short PC-board length? Are the components new, used, or surplus; tested or untested; firsts or seconds; marked or unmarked; old or fresh; usable or dubious?

All of those considerations play an important part in determining whether buying in advance of needs is a worthwhile approach or a waste of money.

Acquiring a junk box

Most builders have a junk box that can be a handy and money-saving device for both construction projects and repair jobs. Not only does the well stocked junk box satisfy convenience and economic needs, but it can also provide a valuable educational experience in component identification and substitution practices for the beginner.

Assembling a useful junk box is a prime objective of most electronics hobbyists. The accumulation gives you the parts you need for projects, when you need them, at reasonable prices—sometimes even at *no* cost. While you may have to spend some money to acquire a foundation, it's possible to accumulate a large assortment of components inexpensively, if you aggressively search for bargains.



ELECTRONICS FLEA MARKETS often are a good place to acquire parts at a reasonable cost.

The sources for junk box parts are myriad, and they include local purchases, surplus/salvage, mail order, flea markets, auctions, and other sources. Probably the best, lowest-cost way to build an initial parts inventory is to salvage usable components from junked electronics gear. Components such as switches, potentiometers, coils, diodes, transformers, resistors, and capacitors are often salvaged from such equipment. In earlier days many of those components could be obtained from old radios, defective TV

Photos courtesy of Radio Shack and GC Electronics.

sets, discarded amateur equipment, and government surplus gear—components large and small being saved with the expectation that they could be used again in some future project.

Those were the good old days, and by and large, junked gear—particularly that of the tube-type variety—provides a shrinking source of junk box parts. With the advent of solid-state equipment, printed circuits and specialized transistors, and IC's, it's harder to "recycle" those components into useful junk box parts than it was 15 or 20 years ago. The trend in junk box acquisition is toward judicious buying of discrete components in advance. We've already discussed parts-selection tips and cautions, and they apply equally to purchases for the junk box.


Regardless of what methods are used to procure for the junk box, the components—particularly the smaller, easily damaged ones—should be carefully segregated by type and value, and placed in labeled jars, plastic drawers, or even small boxes—whichever suits your particular style. The key is that the storage procedures used should allow fast and positive recovery of the parts when needed. Components that can be tested should not be used without first checking their electrical condition, regardless of how good they may look physically. We'll delve into component identification and testing later; suffice it to say at this point that a multimeter and grid-dip oscillator are two very important testing devices for builders.

A final point on junk boxes: After you've developed a respectable junk box, don't hesitate to *use* it for your projects or repairs. You will save money using "pre-owned" parts, and the risk of improper substitution of a part in a circuit is *usually* not too great (except to that particular part). Even if a substituted junk box part fails, a good deal of learning has taken place!

Developing the parts lists

Most published projects include an itemized parts list that identifies the various components' size, value, and nomenclature, as well as required voltage, current, and power-handling capability. Some parts lists even state brand names and recommend sources for hard-to-find and critical components.

Even when a clear and definitive parts list is provided, you should carefully review the construction project, looking closely at the schematic diagram, photos, and explanations of special circuitry and parts requirements. In many cases, the author will point out critical components that should not be changed. Based on your judgment, other parts may be substituted, possibly from existing junk box stocks. We'll talk more later on the question of parts substitution and how far one can deviate from specified values without

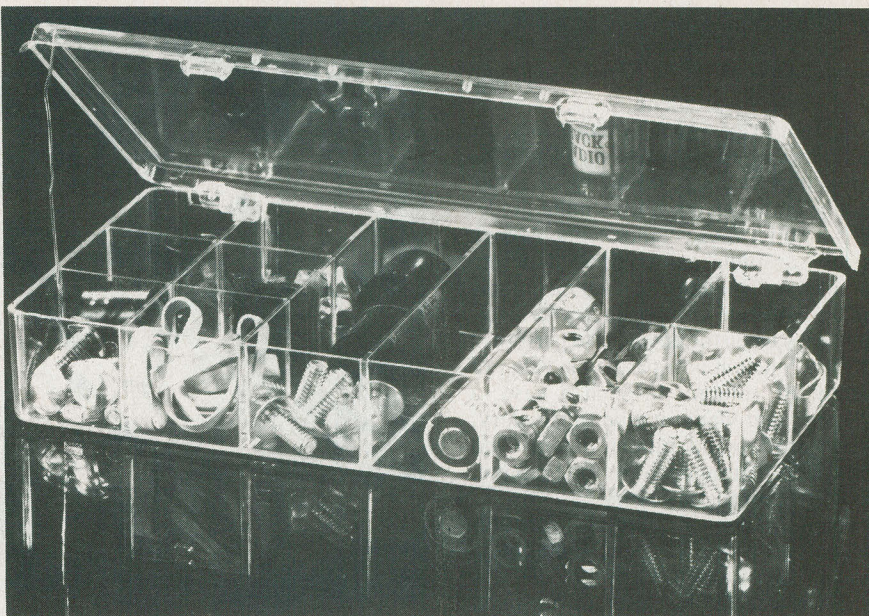

CLEAR PLASTIC STORAGE BOXES can be extremely useful for quick, positive part identification.

affecting performance.

The author's parts list should trigger you to work up additional subsidiary parts lists. Those may logically take the form of lists showing which parts are best procured from your junk box; which are best procured by mail-order; which are best acquired from surplus or salvage sources, and which can be purchased locally. After checking your junk box, look over the local purchase and surplus lists next, with unavailable items added to the mail-order list. In large, complicated projects, it may also be useful to have each list further divided by type of component for convenience in searching for the required parts.

From practical and economic standpoints, it's often wise—even necessary—to make appropriate component substitutions. We'll turn to those next.

Parts selection and substitution

As the prices of individual components increase, it's important to "make do" with the parts you have on hand. It's possible to substitute components within limits, and yet have a device function as intended. Besides the financial advantages of using existing stocks, it's a real time saver to be able to use on-hand components rather than having to shop for new ones. Also, it's worthwhile to get a feel for the range and types of substitutions that can be made so as to develop flexibility when shopping for components—since local suppliers and mail-order houses will not always have exact specified components in stock.

Many inexperienced electronics enthusiasts have an unnecessary fixation on obtaining the exact parts and values indicated in a construction piece, fearing that the finished equipment will not function correctly if any liberties are taken

with the stated parts list. Usually such fears are exaggerated. Unless a "mirror image" of the item is required, *identical* parts are not needed. In most cases, parts substitutions can be made, within reasonable bounds. Component specifications are not "graven in stone," as the saying goes. There is usually a tolerance range within which the hobbyist may work. Sometimes those are stated, though mostly they are not. The trick to intelligent parts substitution, of course, lies in knowing just what the boundaries of wise substitution are.

Obviously, if the construction article's author or circuit designer has highlighted critical components, you shouldn't change them. Special-purpose or close-tolerance IC's, transistors, tubes, capacitors, resistors, and other parts are best not substituted. But in many cases the component specified is what the designer had on hand, and represents an arbitrary specification. So, bearing in mind that most hobbyists are also experimenters, when you have trouble finding components with the exact specifications, try some substitutions of your own, using a combination of good judgment and close attention to available reference guides, catalogs, and substitution manuals. You may not have the experience to ascertain whether or not you'll be successful in making the substitution, but you'll never know unless you try!

Most components, such as resistors, capacitors, inductors, transformers, and transistors, have *ratings* that are important. Those include power and maximum voltage and current ratings. The ratings of substituted components should be equal to or greater than those specified for the project. Generally speaking, over-rated components *can* be used in electronics projects. For example, a 1-watt resistor

can be substituted for a 1/2-watt resistor of the same value without concern, unless the larger physical size of the 1-watt unit causes a space problem.

Active devices, such as transistors, are more difficult to substitute on a "rating" basis, due to the multiplicity of rating parameters involved. Still, similar guidelines hold for those components, as long as the substitute has equivalent design parameters. One must be cautious in trying to substitute components with over-rated ones when the device is to perform a specific function at a particular value of current or voltage. In such a case, a "larger" unit would not be satisfactory. Zener diodes and other current- and voltage-regulating devices, for example, would fit into that category.

Making a proper "ratings" substitution is a great deal easier than making a "value" substitution. Each type of component is affected by different rules and guidelines, so it's worthwhile to look at each individually:

1. Resistors. Fixed resistors are often easily substituted. Unless specified otherwise, fixed resistors commonly have a tolerance of ± 10 or 20% . Knowing that, you can usually safely substitute any resistor. If no tolerance is specified, working in the $\pm 10\%$ or 20% range is usually safe. One general exception is high-voltage power-supply bleeder resistors—those can be as much as 25% lower or 50% higher than specified.

In some applications, metal-film precision resistors, manufactured to tolerances of $\pm 1\%$ or better, are required. That type of resistor is frequently specified for high-stability/ultra-low-noise circuits in computers, voltage dividers, test equipment, and active filters. The stated tolerance must be maintained when substituting those types of resistors.


Frequently, you can find resistors in your junk box that can be adapted for a substitution, using series and parallel combinations whose net resistance is close to the desired value. Resistors connected in series have the total resistance of the sum of the resistors—two 2000-ohm resistors in series have a total resistance of 4000 ohms. To find the effective resistance (R_t) for resistors in series use the formula:

$$R_t = R_1 + R_2 + R_3 + \dots$$

Two or more resistors can be connected in parallel to obtain the desired circuit resistance. When you do that, total resistance is always less than the lowest value used in the combination. Use the following simple formula to calculate the value of two resistors connected in parallel:

$$R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

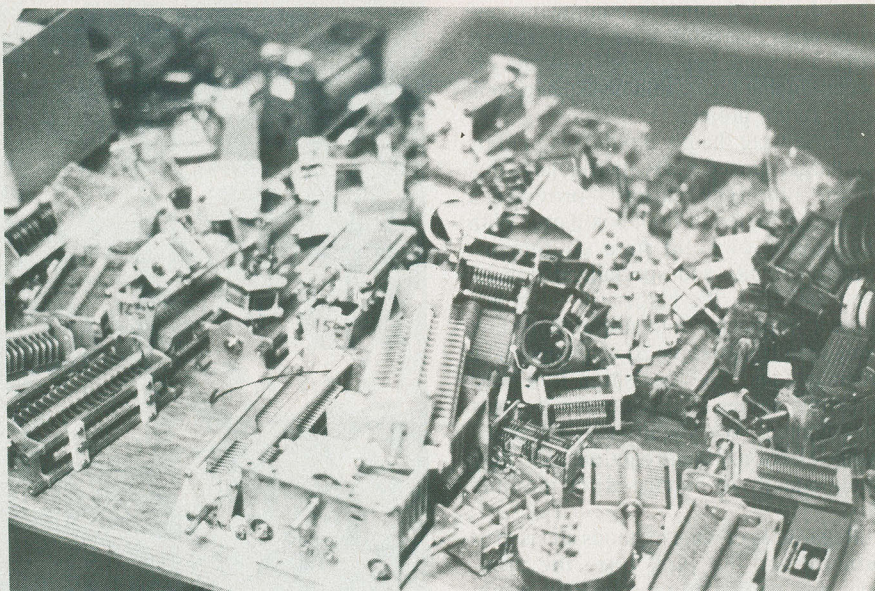There are two major kinds of fixed resistors: composition or carbon, and wire-wound. Normally, do not use wire-wound resistors in circuits carrying RF



APPROPRIATE SUBSTITUTES can be found for most electronic components, including variable capacitors. Flea markets are a good source for those components.

since they have a certain amount of inductance that can upset the associated RF circuit. However, carbon-type resistors of the appropriate power rating can be used to substitute for wire-wound types.

2. Potentiometers. Substitutes can usually be made having somewhat higher or lower values than those specified. Surplus pots can be bargains, but physical characteristics such as shaft length and type of shaft are important. Consider: Is the unit for screwdriver adjustment, or is the shaft designed to accept a knob? What about the pot's electrical characteristics, such as the "taper"—is it usable? Pots with "linear" or "audio" tapers are the types most frequently called for in construction projects. And is an on-off switch required on the control?

One caution: Wire-wound pots are frequently found in surplus. Those pots are most suitable for low-frequency, high-power applications, not for delicate solid-state circuitry. They are not for circuits that require high precision (resolution). Thus, for most work, standard carbon-composition pots represent the best selection.

When shopping for new pots, quality is paramount; cheap materials are synonymous with inferior performance, often evidenced by a pot that is hard to turn because of high-friction bearings. Cheap imports should be avoided; stick to top-quality pots in all construction projects.

3. Capacitors. Fixed capacitors come in a surprising variety. There are mica, Mylar, silver-mica, ceramic, oil-filled, paper, and electrolytic types. Each has specific applications. Mica types (especially silver-micas) and zero-temperature-coefficient ceramics are usually specified where low losses and high stability are essential; normally, you

should not substitute other types for them. Probably the best all-round capacitor for general purpose use is the Mylar polystyrene type—also one of the cheapest, and typically available for values between 5 pF and 0.5 μ F.

Standard tolerance ratings for most project-grade capacitors is ± 10 to 20% , though for some inexpensive general-purpose ceramic capacitors (including disc types) it's as wide as -30% to $+100\%$. Exact capacitance is relatively unimportant in typical bypassing/filtering and coupling applications, and you can easily deviate as much as 50% from the spec value without trouble, sometimes much more (except at VHF and UHF). Mylar polystyrene capacitors also run in the 10 – 20% tolerance range, with 5% Mylars readily available, and 2.5% and 1% units available at somewhat higher prices.

As with resistors, capacitors can be substituted in series or parallel to yield different equivalent values, though the combining effects are the opposite to those of resistors: capacitors in series act like resistors in parallel, while capacitors in parallel act like resistors in series.

When two capacitors are placed in series, the total capacitance is less than that of either one, as determined by the simplified formula:

$$C_t = \frac{C_1 \times C_2}{C_1 + C_2}$$

Capacitors are additive when placed in parallel:

$$C_t = C_1 + C_2 + C_3 + \dots$$

Another handy formula is one to use when you need a lower value of capacitance and want to find the value needed to place in series with an available unit to

obtain the desired value. That value is given by the formula:

$$C_1 = \frac{C_2}{(C_2/C_1)-1}$$

The voltage-handling capability of the resulting capacitor chain should be considered, as should power-handling capability of series/parallel resistors. A standard electronics text should be consulted for more on that.


Most capacitors above 1 μ F are aluminum electrolytics and are polarized. Tolerances tend to be fairly loose because filtering and coupling applications usually don't call for precise values. Those types are often available with capacitances of 100,000 μ F or more, though usually at very low voltage ratings at those high capacitances. A related though more expensive capacitor is the tantalum type. The tantalum capacitor is generally superior to the standard electrolytic, and boasts tighter tolerance, smaller size (for equivalent capacitance), and lower leakage.

Except in specialized applications, such as in timing circuits where tantalums are generally preferred over aluminum electrolytics, exact capacitance isn't terribly important. When substituting, it's generally wise to err on the side of too-high capacitance rather than too-low. Surplus oil-filled types can normally be substituted for electrolytics having equivalent characteristics.

Substitutions are also possible with variable capacitors. The main considerations here relate to minimum and maximum capacitance. As a general rule, you can substitute a capacitor having a greater capacitance than the value specified. It may also be possible to substitute a variable capacitor that has somewhat less range than that specified, if you can determine the actual tuning range required in the circuit. That involves figuring the amount of circuit inductance and amount of capacitance required for a given tuning range, and is best done with the aid of a device such as the ARRL *LCF Calculator*, or using a computer. Note that junk box variables can be modified to become lower-value capacitors simply by removing rotor plates, and multi-section receiving variables can be paralleled to get higher capacitance.

In high-voltage circuits, be sure you observe maximum operating voltages that depend on plate spacing. Plate spacing should be equal to or greater than that specified by the designer, or you can refer to a catalog to convert spacings to voltage-handling capacities. Knowing the voltages in the circuit, you can easily check to see if your particular substitute is adequate for your purpose.

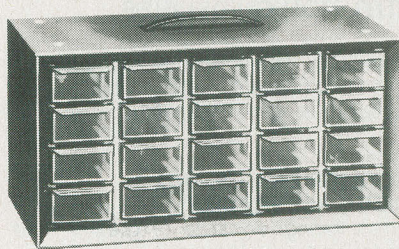4. Diodes. Besides resistors and capacitors, you'll often be faced with making substitutions for diodes of various kinds, both rectifier and small-signal types. The



A 20-DRAWER CABINET such as this is ideal for maintaining a well-organized junk box.

former are generally specified according to their maximum current and reverse breakdown ratings. It's possible, in many instances, to come up with a suitable replacement without having to resort to checking a data book. The 1N4148 is a good all-around small-signal type diode to have in the junk box as it is able to meet a wide range of substitution needs.

5. Transistors. Besides diodes, other types of discrete semiconductors that present substitution questions include bipolar transistors, FET's, SCR's, and UJT's. As with diodes, practically everyone sells some transistors, but few distributors stock each and every part number, particularly highly specialized and Japanese types.


Many transistor suppliers and manufacturers overly emphasize the difficulty of transistor substitution. From a practical standpoint, the many different types of transistors and related economic con-

siderations make it imperative that some substitutions be attempted. You'll need a transistor data book to determine proper specifications; once those numbers are available, you can apply them to select appropriate substitutes. Even using abbreviated substitution guides such as found in the Radio Shack catalogue can make the purchase of bargain-priced blister-pack replacement transistors practical and useful.

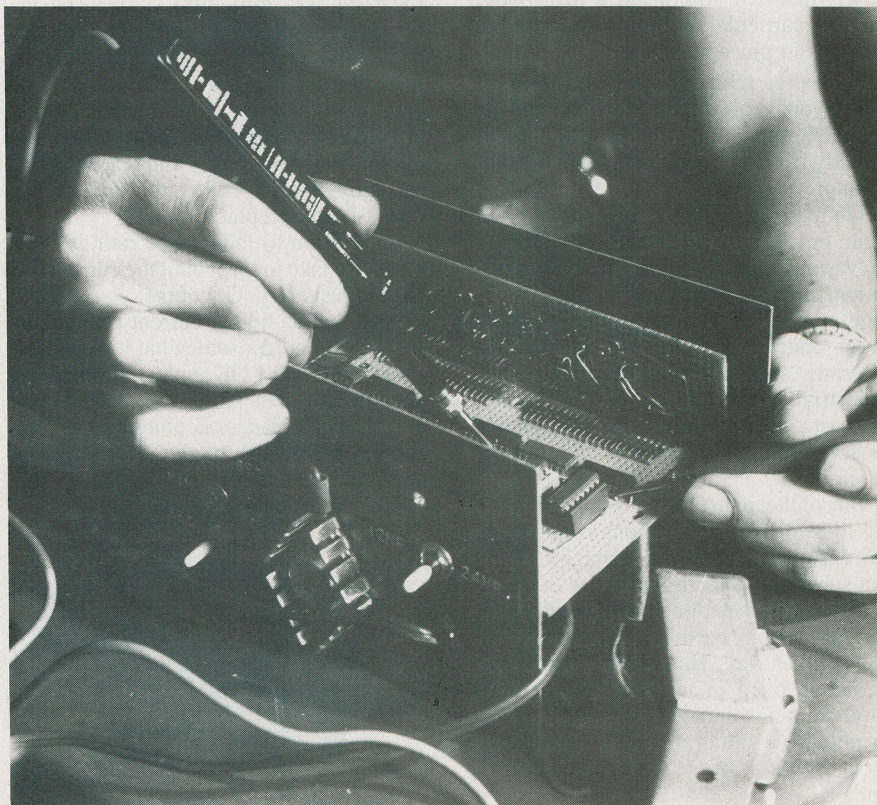6. Integrated Circuits. The silicon chemistry of integrated circuitry constitutes a key element of most sophisticated electronics construction projects. Because of their importance and widespread use, those devices are sold by most electronics suppliers. The devices range over a wide spectrum, and include linear, CMOS, TTL, DTL, ECL, LSI, and other types. The variety encountered precludes stocking up on any but the most common types.

There is little latitude in substituting IC types. A circuit specifying a particular IC usually requires *that* particular IC. In fact, it's usually not worthwhile to salvage IC's from scrap equipment unless the IC's can be clearly identified and there is some prospect of actual use for that particular device.

However, it's important to point out that IC designations often include alphabetical prefixes that simply indicate the device's manufacturer. There is no need to use an IC made by a particular manufacturer if the same basic device is available from other firms. You'll find that IC suffix letters aren't terribly critic-



A MULTI-FUNCTION TEST PROBE, such as the one shown here, is handy for finding good components in surplus or salvaged equipment.

TABLE 1—COMPONENT SUBSTITUTION GUIDELINES

The following constitute *general* guidelines for substitution of the most-used components: resistors, capacitors, inductors, rectifier diodes, and transistors. Refer to the text for discussion of other factors that should be considered in making parts substitutions, and for guidelines for other components.

RESISTORS

Resistance value: within $\pm 20\%$ of that specified.

Resistance tolerance: equal to or better than specified, but usually not critical.

Power rating: equal to or greater than specified.

CAPACITORS

Capacitance value: within $\pm 20\%$ of that specified, except in critical timing and tuning circuits.

Capacitance tolerance: equal to or better than specified, but usually not critical.

Voltage rating: equal to or greater than specified, or twice the maximum supply voltage.

Type: generally not important except in critical timing and tuning circuits.

COILS/INDUCTORS

Inductance value: within $\pm 20\%$ of that specified.

Current rating: equal to or greater than specified.

RECTIFIER DIODES AND BRIDGE ASSEMBLIES

Current rating: equal to or greater than specified.

Reverse breakdown voltage: equal to or greater than specified.

TRANSISTORS

Type: as specified (PNP or NPN, etc.).

Collector current rating (I_c): equal to or greater than specified.

Reverse breakdown voltage: equal to or greater than specified.

Gain (β or h_{fe}): equal to or greater than specified.

Power rating: equal to or greater than specified.

Cutoff frequency: equal to or greater than specified.

Case style: usually not important.

NOTE: A transistor data book must be consulted for determining most of the specifications necessary for making substitutions.

al, either. They usually indicate a change in the internal IC configuration that does not alter the basic function, though the suffix letter may indicate the package style. But, if you find a letter (or two) inserted between some of the numbers, it may indicate a significant modification that precludes easy substitution. In such cases, it's wise to consult a data book, paying particular attention to possible changes in pin numbering.

7. Power transformers and chokes.

When your project requires a very specific transformer, it may be best to order it directly from the manufacturer or his distributor.

On the other hand, if specs aren't too tight, or it's possible to connect windings in various configurations to obtain required voltages, it may pay to take advantage of specials and closeouts by mail-order distributors—though transformer offerings are usually limited in variety. Industrial surplus dealers generally have the best selection; transformers with the most unusual characteristics can turn up in surplus.


One of the main considerations in making transformer substitutions is adequate current/power handling capacity. You can substitute if the transformer in question has the same voltage rating with more current-carrying capacity, but it's risky to go the other way. However, if the transformer is rated in terms of continuous duty, and its intended use will be intermittent, a rating reduction of up to about 25% may prove to be quite acceptable.

Minor primary and secondary voltage substitutions can be made without

adverse effect. If you have a transformer that delivers a higher voltage than you want, you can drop the voltage with a series resistor or a voltage-divider system.

As for power-supply chokes, substitutions are usually easy. The specified value of a filter choke can usually be regarded as a minimum value. The inductance of chokes in series is additive; conversely, chokes in parallel function like resistors in parallel. The amount of capacitance required in a power supply is affected by the power-supply choke inductance—the choke and electrolytic capacitor work together to bring ripple down to an acceptable level.

In addition to inductance ratings, you must also take into account the current the choke must carry. Of course, you can use a choke with a higher current rating than specified. Using a somewhat lesser-rated choke is probably OK, unless the choke is rated at less than 75 % of expected current. The inductance becomes less if more current is drawn through the choke than the unit is rated for, thus reducing the choke's filtering effectiveness.

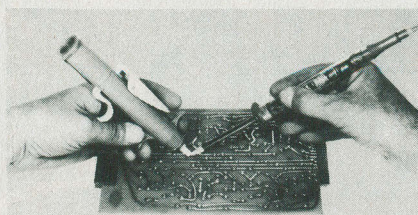

A DESOLDERING TOOL makes removing parts from a surplus or salvaged piece of equipment simple.

8. Switches. Substituting switches can be tricky because of the numerous possible switching configurations and applications. You can always use a switch that has more contacts or sections than are required for a given circuit, as long as it has an adequate voltage rating. Often that information can be obtained from manufacturers' and distributors' catalogs. Similar considerations apply to relays, but selection criteria are complicated by relay coil voltage and current, and other operating characteristics.

9. Tubes. Most contemporary circuitry has abandoned the once-common vacuum tube, though a few tube designs survive, and there is still demand for tubes for replacement purposes. Tubes are becoming extremely expensive and difficult to find, and few are still manufactured in the United States. One good, low-cost source of once-common receiving tubes is *Cornell Electronics Company*, 4217 University Avenue, San Diego, CA 92105; the firm stocks a wide variety of bargain-priced receiving tubes. *Radio Shack* also provides a special-order service that includes about 2000 different types. If you don't have the tube you need, of course, you'll have to buy it. But a quick check of a tube-substitution manual, or the ARRL's *Radio Amateur's Handbook* (it lists different tube types and possible substitutions if available) may prove worthwhile.

10. Other components. There are many other components that the project builder will find useful to keep in his junk box or bench stock for the purpose of convenient substitution in construction projects.

We can't treat all of them here. But some that come to mind include plugs, jacks, audio and IF transformers, transistor and IC sockets, battery clips, terminals, hardware, alligator and crocodile clips, meters, connectors, chassis, PC boards, and cabinets.

In many instances your best guide to making intelligent substitutions is simple, ordinary common sense, as well as an understanding of when not to use substitute parts but to go out and acquire a specified part.



Getting into the practice of breadboarding project circuitry will not only help refine a circuit before commitment to a final design, but will make substitutions easier because it gives you a chance to double-check your choices. Solderless breadboards eliminate a great deal of the trouble involved in circuit development and make desk-top experimentation—and substitution—much easier.

Table 1 lists popular component substitution considerations in tabular form.

When we continue this article, we'll take a closer look at where you can obtain your parts for projects. Among the topics we'll cover will be how to successfully use surplus and salvaged parts, including how to test and identify them

R-E

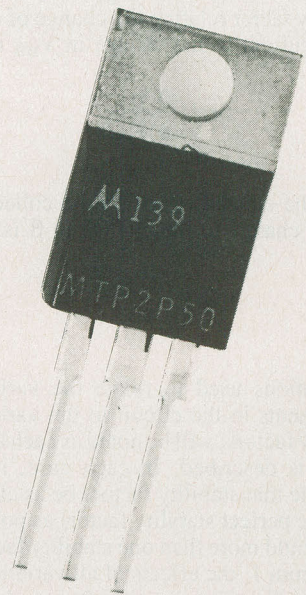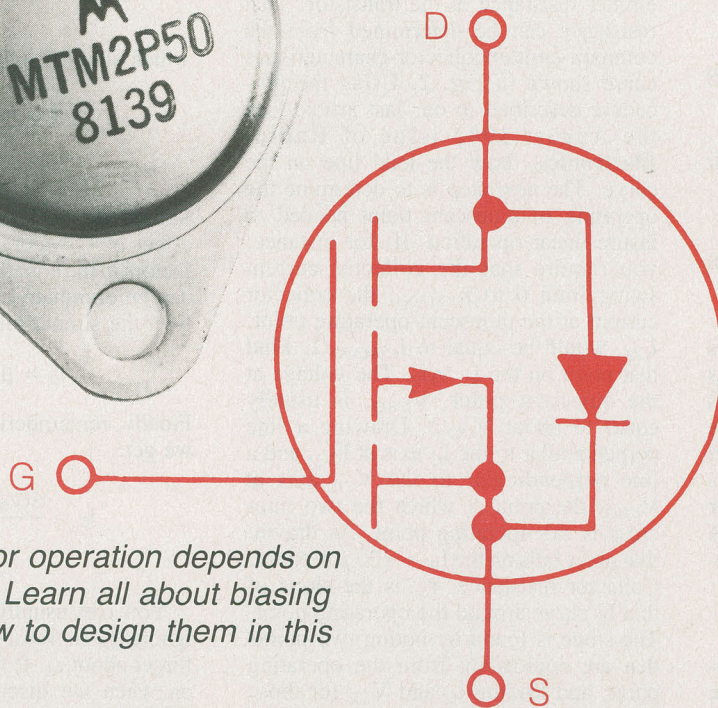How How to Design Analog Circuits - Biasing Transistors



Proper transistor operation depends on proper biasing. Learn all about biasing circuits and how to design them in this month's article.

MANNY HOROWITZ

Part 5 LAST MONTH, WE BEGAN our discussion of bipolar and FET transistors by looking at the structure of those devices and at some basic transistor circuits. One of the things we mentioned was that if a bipolar device were used in a Class A common-emitter circuit, for linear operation the collector voltage (with no input signal present), should be set at one half the supply voltage. The no-input-signal condition is commonly referred to as the quiescent operating point. (Similarly, in the case of an FET in a common-source circuit, the drain voltage should be one half the supply voltage). That, however, is merely an approximation; the actual operating point varies with the specific requirements of the circuit. In any event, once the proper operating point has been selected, the device must be *biased* for that point. Just how that is done is the topic of this month's article.

Bipolar transistors

There are essentially two types of bias circuits that are used with bipolar devices. Although there may appear to be many more, the others are simply variations of

those two circuits. And even the two circuits are variations of each other.

But why do we need many bias circuits? They arose mainly because of the high leakage current, I_{CBO} , that flowed from the collector to the base in early germanium transistors. If that leakage current also flowed through the base-emitter junctions (as it normally did), it was multiplied by beta (β) to make it into a large undesirable leakage current, I_{CEO} , that flowed in the collector and emitter circuits. And to compound the problem, I_{CBO} and I_{CEO} doubled every time the temperature of the transistor increased by 10°C . Although those factors are still important in modern silicon transistors, the effect on the collector current is reduced considerably because the leakage current in silicon transistors is frequently low enough to be ignored.

In addition to leakage current, variations in the operating parameters from device to device, as well as with temperature, can cause problems. The value of β , for instance, will vary from device-to-device of the same type, as well as with

temperature and collector current, I_C . In addition, the value of I_C at the operating point will vary with several parameters. Among those are V_{BE} , the voltage drop across the base-emitter junction, which itself varies with temperature; V_{BB} , the base supply-voltage; r_c , the collector-to-base resistance in a common-base circuit, and r_d the collector-to-base resistance in either a common-emitter or common-collector circuit.

But, once the operating point has been established for a circuit, ideally it should not be effected by differences in parameters from device-to-device, or by any external factors such as temperature. That is the reason for all of the bias-circuit variations—they are designed to help stabilize the operating point. In theory, if the proper bias circuit is used, the operating point will not change regardless of any change in any of the factors mentioned. However, theory and what really happens are not always the same. But even so, using the proper bias circuit will minimize any variations of the operating point sufficiently so that the circuit will

still operate as intended.

To design a bias circuit properly, it is important to know how a variation in one variable will effect the other variables in the circuit. Because of that, three *stability factors* that relate the change of one factor to the change in another have been derived. They are:

$$S = \frac{\Delta I_C}{\Delta I_{CBO}} \quad (1)$$

which relates the change of collector current to the change in leakage current. The stability factor relating the change of collector current to the change in V_{BB} is:

$$S_E = \frac{\Delta I_C}{\Delta V_{BB}} \quad (2)$$

while the equation relating the collector current change to the change in β is:

$$S_\beta = \frac{\Delta I_C}{\Delta \beta} \quad (3)$$

Equations used to relate the various components in the circuit to the various stability factors, will be noted as each bias circuit is described. In each case, it is desirable that stability factors be as close to 1 (the perfect stability factor) as possible. Should more than one stability factor differ from 1, the effects of all variations must be taken into account when evaluating the design.

Bipolar transistor bias circuits

The simplest bias circuit to be described here is shown in Fig. 1. The base current, I_B , originates at V_{BB} and is delivered to the base through R_B . However, V_{BB} often does not exist as an independent supply; instead V_{CC} is used to supply both base and collector current. In that case, R_B is connected to V_{CC} , and that supply serves as both V_{CC} and V_{BB} .

In Fig. 1, all base current from V_{BB} flows through the base-emitter junction. If we consider the voltage across that junction, V_{BE} , as negligible when compared to V_{BB} , the base current due to the supply is V_{BB}/R_B . Collector current due to that base current is approximately equal to βI_B .

Next, let us add the effect of I_{CBO} , the leakage current that flows from the collector to the base. After flowing through the base-emitter junction, it is multiplied by beta. That βI_{CBO} flows in the collector and emitter circuits and substantially effects the collector and emitter currents. Collector current due to I_{CBO} is thus $\beta I_{CBO} = I_{CEO}$. (Note that in our discussions beta has been assumed to be much greater than 1. Thus only β is shown in formulas rather than $\beta + 1$.)

Finally, we have some collector current flowing due to r_d , the collector-to-

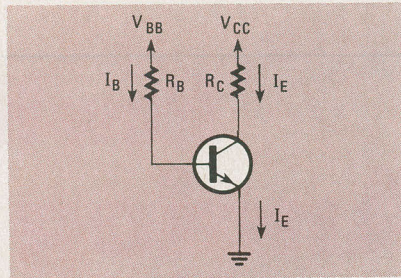


FIG. 1—A SIMPLE CIRCUIT for biasing bipolar transistors. Often there is no separate V_{BB} supply; instead V_{CC} is used to supply both the collector and base.

emitter resistance of the transistor. That resistance can be determined from the common-emitter collector-characteristics curve shown in Fig. 2. Using the procedure described in our last article (see the August 1982 issue of **Radio-Electronics**, draw the load line on the curve. The next step is to determine the operating or quiescent point needed to insure linear operation. If, for instance, you require that the collector current swing from 0 to $I_{C(MAX)}$, the collector current at the quiescent operating point, I_{CQ} , would be equal to $I_{C(MAX)}/2$. Find that point on the I_C axis. The voltage at the quiescent point, V_{CEQ} , is usually equal to about $V_{CC}/2$. Drawing a line perpendicular to the I_C axis at I_{CQ} , and a line perpendicular to the V_{CE} axis at V_{CEQ} , the point at which the two lines cross is the operating point. As drawn, that point falls on the $I_B = 100 \mu A$ curve. Collector resistance, r_d , is the slope of that I_B curve around the operating point. The slope is found by noting two points that are equidistant from the operating point, and finding I_C and V_{CE} for those points. Assuming that the collector voltage and current at one point are V_{CE1} and I_{CE1} , and V_{CE2} and I_{CE2} at the other, then:

$$r_d = \frac{V_{CE2} - V_{CE1}}{I_{CE2} - I_{CE1}} \quad (4)$$

As indicated, r_d is the collector-emitter resistance of the transistor when it is used

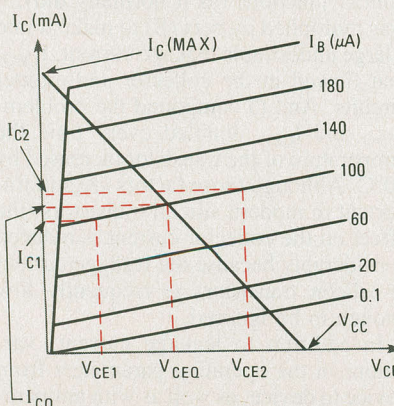


FIG. 2—ONCE THE QUIESCENT POINT has been found, the value of r_d is equal to the slope of the I_B curve around that point.

in a common-emitter or common-collector circuit. In a common-base circuit, that collector-emitter resistance is much higher and equal to βr_d ; that quantity is called r_c .

A portion of the total collector current is due to the presence of r_d in the circuit. It is equal to the collector-emitter voltage, V_{CE} , divided by r_d . Obviously, V_{CE} is equal to the supply voltage less the voltage drop across the collector resistor, R_C , or $V_{CC} - I_C R_C$. Consequently, the total quiescent collector current flowing in the circuit of Fig. 1 is:

$$I_C = \beta I_B + I_{CEO} + \frac{V_{CC} - I_C R_C}{r_d}$$

which simplifies to:

$$I_C = \frac{\beta I_B + I_{CEO} + V_{CC}/r_d}{R_C/r_d + 1} \quad (5)$$

Should R_C be less than 10% of r_d , the effect of r_d becomes negligible, and all factors in the equation involving that term can be eliminated. We will then end up with the simple relationship:

$$I_C = \beta I_B + I_{CEO}$$

Finally, remembering that $I_B = V_{BB}/R_B$, we get:

$$I_C = \frac{\beta(V_{BB} + R_B I_{CBO})}{R_B} \quad (6)$$

You can usually use equation 6 and ignore r_d in most designs. But do not forget about r_d . It will be important later on when we discuss AC gain and the output impedance of transistor circuits.

The various stability factors for the circuit shown in Fig. 1 are:

$$S = \beta \quad (7)$$

$$S_E = \beta/R_B \quad (8)$$

$$S_\beta = \frac{I_{CBO} R_B + V_{BB}}{R_B} \quad (9)$$

Equation 9 indicates by how much the collector current will change for a specific change in β . Thus if a transistor with a β of 80 is substituted for one with a β of 40, the quiescent collector-current will double. To see how we came to that conclusion, let's digress a bit. First, as we saw in equation 3, $S_\beta = \Delta I_C/\Delta \beta$. Expanding further, equation 3 can be rewritten as $\Delta I_C = \Delta \beta(I_B)$. Secondly, since I_{CBO} is generally small enough to be ignored, and since V_{BB}/R_B is equal to I_B , in this case, the stability factor, S_β , defined by equation 9 is approximately equal to I_B . Thus $\Delta I_C = \Delta \beta(I_B)$. Originally, I_C was equal to the initial β of 40 multiplied by I_B , or $40I_B$. If $\Delta \beta = 40$, and $\Delta I_C = \Delta \beta I_B$, then

$\Delta I_C = 40I_B$. Finally, the total collector current when β is increased from 40 to 80 is $I_C + \Delta I_C$, or $40I_B + 40I_B = 80I_B$.

Improving stability

Stability can be improved by adding an emitter resistor, R_E , to the circuit in Fig. 1. If that is done, equations 7, 8, and 9 are modified to become:

$$S = \frac{\beta(R_E + R_B)}{\beta R_E + R_B} \quad (10)$$

$$S_E = \frac{\beta}{\beta R_E + R_B} \quad (11)$$

$$S_\beta = \frac{(R_E + R_B) V_{BB} + I_{CBO} R_B (R_E + R_B)}{(\beta R_E + R_B)^2} \quad (12)$$

In this arrangement, base current is less than it was when there was no emitter resistor. It is reduced because the emitter resistor, R_E , is reflected into the base circuit as a resistor equal to βR_E . Because of that, the base current becomes $(V_{BB}/(R_B + \beta R_E)) + I_{CBO}$. In addition, I_C becomes equal to βI_B .

The bias circuit shown in Fig. 3 is used when stability is a very important consideration. The circuit in Fig. 1, and the variation we created by adding an emitter resistor, are simplified versions of that circuit. In it, V_{BB} has been eliminated; instead, V_{CC} is used as both the collector and base supply.

Thevenin's theorem must be used in order to determine the base current in the circuit in Fig. 3. That theorem states, in part, that any network of voltage sources and resistances can be simplified to a single voltage source in series with a single resistance. Use the following steps to apply that theorem to the circuit. Those steps are shown in Fig. 4.

First, as shown in Fig. 4-a, separate the bias resistor circuit from the rest of the circuit.

The second step, as shown in Fig. 4-b, is to determine the voltage at the junction of R_B and R_X . That voltage is called the *Thevenin voltage*, V_{TH} , and, since R_B and R_X make up a simple voltage divider, is

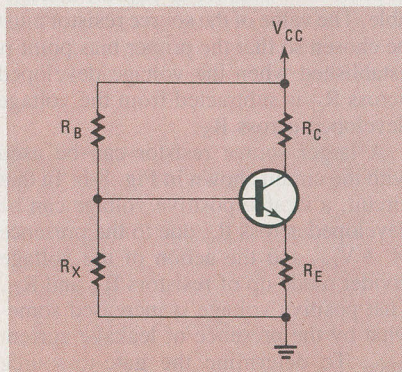


FIG. 3—IF BETTER STABILITY IS REQUIRED, the bias circuit shown here can be used.

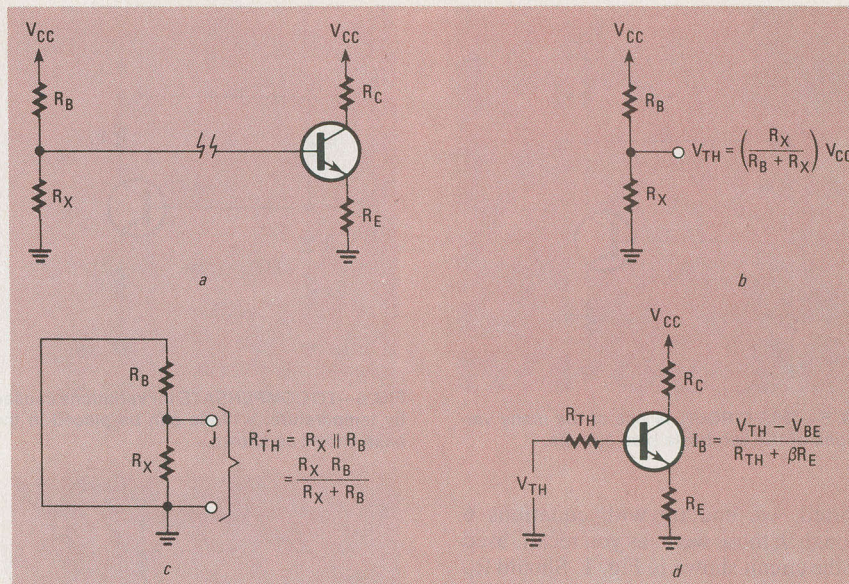


FIG. 4—TO EVALUATE THE BASE CURRENT of the circuit shown in Fig. 3, Thevenin's theorem must be used. The steps followed in applying that theorem are shown here.

equal to $V_{CC}(R_X/(R_B + R_X))$.

The third step, as shown in Fig. 4-c, is to short the supply to ground and determine the *Thevenin resistance*, R_{TH} . That is the resistance seen when looking back toward R_X ; in other words, the resistance between the junction "J" and ground. In this case, it is the parallel combination of R_X and R_B , which, of course, is equal to $R_X R_B / (R_X + R_B)$.

The fourth, and final step, shown in Fig. 4-d, is to reconstruct the original circuit, substituting V_{TH} for V_{CC} , and R_{TH} for R_B and R_X . The Thevenin voltage, V_{TH} and the Thevenin resistance, R_{TH} , are connected in series with the base of the transistor as shown. The base current can now be calculated from the formula:

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + \beta R_E}$$

The value of V_{BE} is usually .017-volt for a silicon transistor, and 0.2- to 0.3-volt for a germanium device. Once you've calculated I_B , the collector current is simply βI_B .

In this type of circuit, the effect of leakage current, I_{CBO} , is reduced because some of it is diverted from the base-emitter junction to R_X . A good rule of thumb to use when designing this type of circuit is to make R_X equal to less than ten times the size of R_E .

As we mentioned earlier, there are two basic types of bias circuits. So far, all of the circuits we've examined were variations of one type. Let's now turn our attention to the second type. It is shown in Fig. 5. Here, R_B is connected to the collector of the transistor being biased instead of to V_{CC} . In that circuit, negative feedback from the collector to the base acts to reduce the value of the stability

factors, a desirable result. In determining the operating point, the simplest approach is to again use Thevenin's theorem. Just adapt the method described for the circuit in Fig. 3 to this circuit, using the value of V_{CE} that you are designing for instead of V_{CC} . A reasonably accurate formula for determining collector current is shown as equation 13. Note that R_C and I_{CBO} are included in the equation. Stability factors for this circuit are shown in equations 14, 15, and 16.

$$I_C = \frac{\beta[R_X V_{CC} + I_{CBO}(A + R_X R_B)]}{\beta A + R_X R_B} \quad (13)$$

$$S = \frac{\beta(A + R_X R_B)}{\beta A + R_X R_B} \quad (14)$$

$$S_E = \frac{\beta R_X}{\beta A + R_X R_B} \quad (15)$$

$$S_\beta = \frac{(R_X V_{CC} + R_X R_B I_{CBO})(A + R_X R_B)}{(\beta A + R_X R_B)^2} \quad (16)$$

Where $A = R_E R_C + R_E R_B + R_E R_X + R_X R_C$.

Those current and stability equations can be applied easily, with just slight modifications, to the circuit in Fig. 3. In equations 13 through 16, R_C is an important factor in determining the bias. It plays no part, however, in determining the stability and quiescent current for the circuit in Fig. 3. When applying those equations to that circuit, let R_C equal 0. That eliminates all terms containing R_C . If, in addition to setting R_C equal to 0, R_X was made infinite by removing it from the circuit and R_E was made equal to 0, or

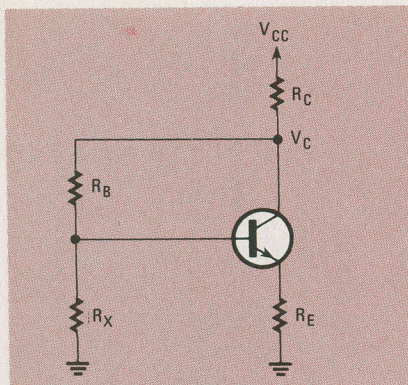


FIG. 5—THIS CIRCUIT is one of the many variations of the two basic bias circuits.

shorted, we end up with equations 6 through 9; those were, as you recall, used for the circuit shown in Fig. 1. Should R_E be left in the circuit, the equations will be identical to equations 10, 11, and 12. Thus, equations 6 through 12 are simply variations of equations 14, 15, and 16.

There are many variations of the simple circuits we have presented thus far. One of those is to remove R_X from the circuit of Fig. 5. That does reduce stability somewhat, however. Equations 13 through 16 still apply, but are modified by removing all terms containing the expression R_X .

Temperature compensation

Base-emitter voltage variation with temperature is an important consideration, especially in power circuits, because in those the temperature of the transistors tends to increase by a considerable amount. The circuit most-commonly used to compensate for that is shown in Fig. 6.

Diode D is placed into the circuit as shown so that it is always on. The diode used should have the same voltage/temperature characteristic as the forward biased base-emitter junction of the transistor. It should also be placed close to the transistor so that both of their temperatures will vary in a similar manner. With this configuration, the voltages across the diode and the base-emitter junction are always identical. Because of that, the voltage across R_E and R_X are also always identical, regardless of any changes in V_{BE} caused by temperature. Thus stability is improved.

The final variation we'll discuss here, is the one shown in Fig. 7. In most bias circuits, R_E is connected between the emitter and ground. Here, however, a battery or other voltage source, V_{EE} , is inserted between the emitter and ground. As a result, the base current, I_B is approximately equal to $V_{EE}/(R_X + \beta R_E)$; the collector current, as usual, is equal to βI_B . The stability factors for that circuit are essentially the same as those calculated using equations 10 through 12. When applying the equations here,

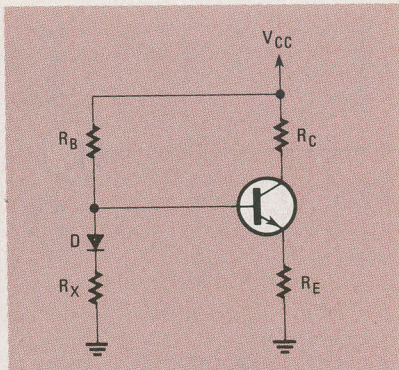


FIG. 6—TO COMPENSATE for variations caused by temperature, a diode can be placed in the base circuit as shown.

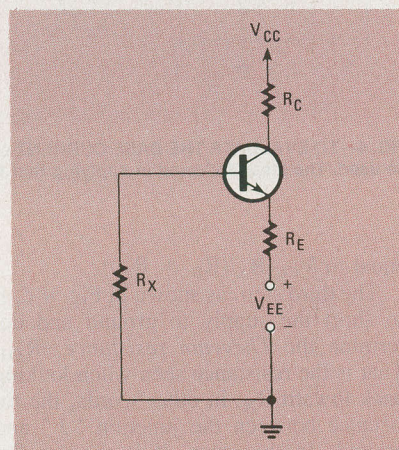


FIG. 7—IN THIS VARIATION, a battery or other voltage source is inserted between the emitter and ground.

however, substitute V_{EE} for V_{CC} , and R_X for R_B .

In summary, as a general procedure when designing bias circuits, first determine the ideal quiescent collector voltage and current. Divide the collector current by β to find approximately what the base current should be. Next design a base circuit to establish those conditions. Remember that those conditions should be relatively insensitive to temperature changes, as well as parameter variations from device to device. To make certain that they are, you must check the stability factors. Any of the circuits we've discussed, as well as many other variations, can be used when biasing bipolar transistors. You must determine how much operating point instability your design can tolerate. Start with the simplest circuit and calculate the stability factors. If collector current variations due to these factors are too great, increase the complexity one step at a time. Never go beyond the simplest circuit you can use to satisfy your requirements.

Biasing JFET's

Gates of n-channel JFET's are usually made negative with respect to the source. But, as no gate current flows if the gate is made just slightly positive with respect to

the source of a JFET, up to +0.5 volt may be placed at the gate. Two arrangements used for establishing the proper bias voltage are shown in Fig. 8.

In Fig. 8-a, drain current, I_D , flows through R_D and R_S . Thus, the source current, I_S , and I_D are equal to each other. A voltage equal to $I_D R_S$ is developed across R_S . That voltage is called V_{RS} and has the polarity shown.

A leakage current, I_{GSS} , flows from the gate to the source. The value of I_{GSS} at 25°C is often found on the specification sheets of the device. That leakage current, however, increases with temperature—usually doubling with each increase of 10°C. The leakage current flows through R_G , developing a voltage, V_{RG} equal to $I_{GSS} R_G$. The polarity of that voltage is also shown in Fig. 8-a.

Voltage between the gate and source is equal to $V_{RS} - V_{RG}$. The value of V_{RS} is usually adjusted to be larger than the value of V_{RG} so that the gate will be biased negative with respect to the source. That's how the bias for the circuit shown in Fig. 8-a is established.

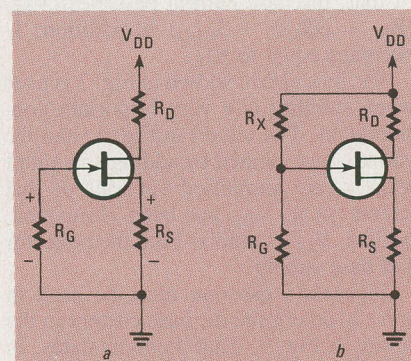


FIG. 8—EITHER OF THESE CIRCUITS can be used when biasing either JFET's or MOSFET's.

The source resistor is an important factor in enhancing the stability of the circuit as it is used to counteract any increase of I_{GSS} caused by a change in temperature. Circuit stability can be improved by increasing the size of R_S . But there is a limit to this. Should R_S be increased too much, the voltage developed across it can be high enough to bias the transistor near or at pinch-off. That is, of course, undesirable. The value of the source resistor must be chosen so that the proper bias point is established when the voltage developed across R_G is subtracted from the voltage developed across R_S .

A larger source resistor can be used with the circuit shown in Fig. 8-b. In that circuit, a sizable positive voltage can be developed across R_G due to the presence of $+V_{DD}$ and the action of the voltage divider made up of resistors R_X and R_G . That positive voltage is increased somewhat by the presence of leakage current I_{GSS} . To determine the gate-to-source bias voltage, subtract the voltage de-

continued on page 102

BUILD THIS

STEREO IMAGE



EXPANDER

Add an extra dimension to your recorded music with this Stereo Image Expander. Build it and hear what you've been missing.

JOEL COHEN

Part 2 IN THE FIRST PART OF this article, we looked at the theory behind the Stereo Image Expander. This time we'll apply what we've learned and build our own.

Assembly

A foil pattern for the expander PC-board is shown in Fig. 11, and a parts placement diagram in Fig. 12. Figure 13 will also help you in completing the board. Some of the instructions here pertain specifically to the parts supplied with the kit available from the supplier indicated in the Parts List, but may also be applicable to you if you're building from scratch.

Pin 1 of each IC is indicated by an indented dot and all but IC5 are mounted with pin 1 facing towards the rear of the board. The bucket-brigade device, IC6, is subject to damage from static charge—it's a good idea to be sure that you are grounded before handling it. The use of IC sockets is recommended.

The BBD, incidentally, can be either an SAD512 or SAD1024—the pinouts are identical. The SAD1024 contains two SAD512's, and one of them will simply not be used.

Be sure to observe the polarities of the electrolytic capacitors and diodes. Note that regulators IC1 and IC2 are mounted

with their center leads bent back toward the curved part of the package, while the transistors they resemble have their center leads bent slightly forward, toward the flat sides of the packages. Don't forget the two jumpers shown in the parts placement diagram.

The transformer must be installed with pins 1 and 2 toward the rear of the board. Bend the two mounting tabs away from the transformer and solder them to the foil side of the board. If you are using the phono jacks provided by the supplier shown in the Part List, cut off the plastic tabs at their rear corners before attaching them and be sure they are firmly seated parallel to the board before soldering. The switch bodies must be spaced .093-inch above the top of the board if the cabinet supplied with the kit is used. If the switches do not have shoulders on their mounting pins, use three plastic spacers over the pins at the front of S3 and the rear of S1 and S2. Be sure the switches and IMAGE control are seated parallel to the board so they will fit into the holes in the chassis.

To mount the LED, bend its leads at a 90° angle while holding it towards you with the anode lead on your right. Solder it in so that the bend is 1/2-inch above the top of the board. Install the completed board in its enclosure, and attach the line cord. Be careful of stray strands of wire,

especially near the grounded board-mounting screw at the rear corner.

Alignment

Only one adjustment is required; the BBD bias which is set by R7. There is about a 2-volt window for signals to pass through the BBD and the bias is set for the center of that range so that the maximum peak-to-peak signal can pass through without clipping. There is enough headroom in the design of the expander to allow for individual IC variations if the bias is simply set to +3.5 volts.

If you want to "fine tune" the expander, apply about 1.5-volts RMS at 1 kHz to just the left input and observe the waveform present at jumper J1. If the bias is too high, the top of the sinewave will be clipped; if it's too low, the bottom will be clipped. At the optimum setting the waveform will be just slightly clipped at both top and bottom.

Rooms and loudspeakers

While most of us would find it difficult to tell the difference between one amplifier and another by ear, we all know that different speaker-systems have different qualities and that the sound from a particular system can vary depending on where it is located in a room. Most of the sound energy reaching our ears comes not

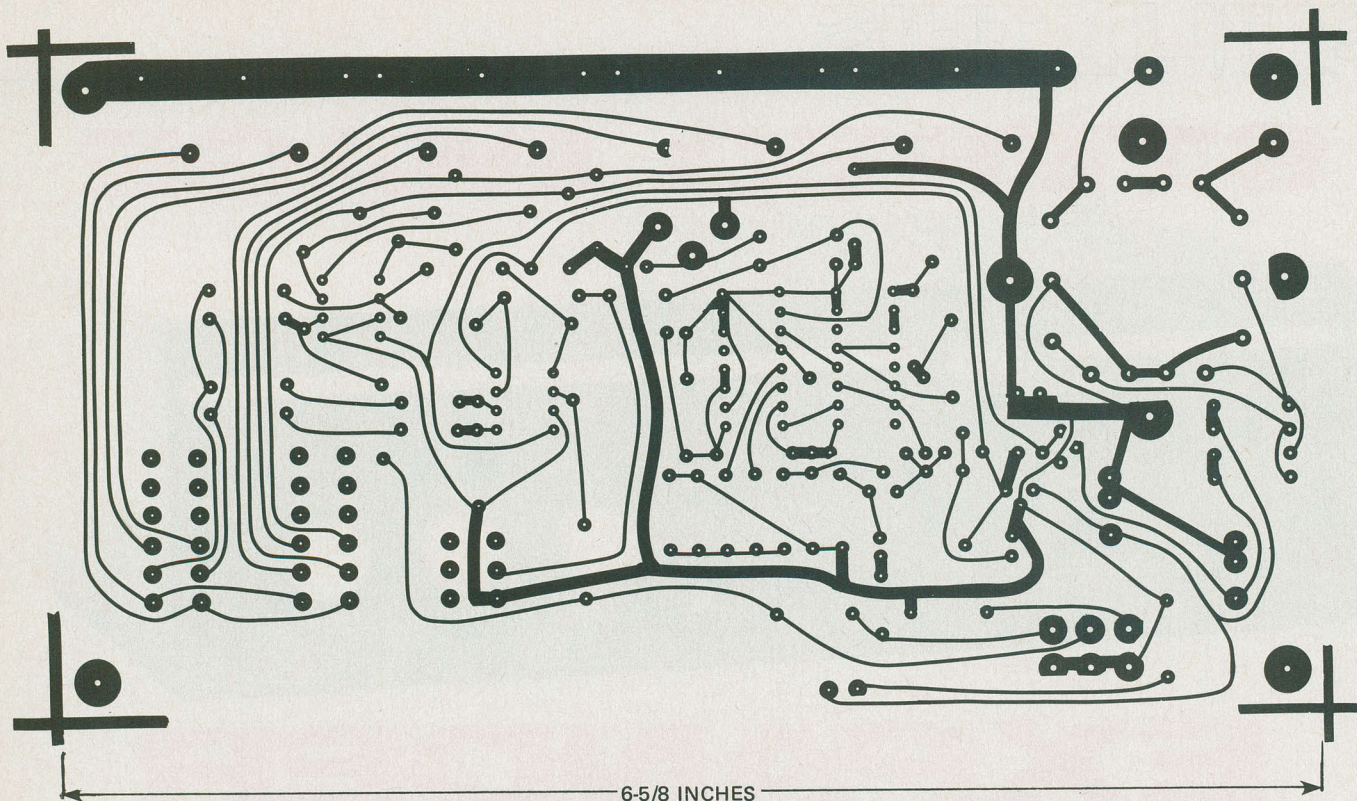


FIG. 11—STEREO IMAGE EXPANDER is constructed on single-sided PC board. The use of IC sockets is recommended.

directly from the speakers, but from secondary reflections of the sound from the walls, floor, and ceiling. The frequency response of that sound energy is shaped by the absorption characteristics of the surface it reflects from. The stereo image, however, is formed entirely by the first-arrival sound traveling directly from the loudspeakers to our ears.

Several conditions are needed for a good stereo image, and they are the same whether that image is expanded or not. First, the listening position must be the same distance from each speaker so that each ear hears its own speaker first. It is also helpful to point the speakers in toward the listening position. Second, the first-arrival sound from the speakers should precede the arrival of the first *reflected* sound by as long a time as practical, with one or two milliseconds being the minimum. That usually requires that the speakers be two feet or more from any wall or large piece of furniture and no more than 10 or 12 feet from the listening position. Third, the two speakers should be separated by an angle of 40°; that is, an imaginary line drawn to each speaker should form a 20° angle with one drawn from the listener to a point directly between them. That means that the distance between the centers of the two speakers should be 7/10 of the distance from each speaker to the listening position. Fourth, the speakers must be connected in phase. The easiest way to test that once they are positioned is to tune in some FM interstation hiss or a monophonic program. If the

All resistors 1/4-watt, 5%, unless otherwise specified

R1, R6, R14, R16, R17—1000 ohms
 R2, R4, R25, R26, R30, R31—100,000 ohms
 R3, R5—47,000 ohms
 R7, R15, R23, R24, R27-R29—20,000 ohms
 R8—100,000 ohms, PC-mount potentiometer
 R9, R13—4.7 ohms
 R10, R20, R22, R34—4700 ohms
 R11—100 ohms
 R12—2000 ohms
 R18, R19—10,000 ohms
 R21—100,000 ohms, potentiometer, audio taper
 R32, R33—390 ohms

Capacitors

C1, C2—470 μ F, 35 volts, electrolytic
 C3, C4, C6-C8, C12—0.1 μ F, ceramic disc
 C5—47 μ F, 16 volts, electrolytic
 C9, C17, C18—0.01 μ F, axial ceramic or ceramic disc
 C10, C13, C16—10 μ F, 16 volts, electrolytic
 C11—100 pF, axial ceramic or ceramic disc
 C14—390 pF, axial ceramic or ceramic disc
 C15—1500 pF, axial ceramic or ceramic disc

Semiconductors

IC1—LM340L15, 15-volt positive regulator

PARTS LIST

IC2—LM320L15, 15-volt negative regulator
 IC3, IC4—MC4558 dual op-amp
 IC5—CD4049 CMOS hex inverter
 IC6—SAD512 or SAD1024 N-channel bucket-brigade device (Reticon. Also Radio Shack 276-1761.) (See text.)
 Q1, Q2—2N2222, 2N3904 or similar
 D1-D4—1N4002 or 1N4003
 LED1—jumbo red LED
 T1—35 volts, center-tapped, PC-mount (Dale PL-12-09 or similar)
 S1-S3—pushbutton switch assembly: 3 DPDT or 1 DPDT, 2 4PDT (Schadow F-series or Centralab PB20-series)
 J1-J8—RCA-type phono jack, right-angle PC-mount

Miscellaneous: PC board, IC sockets, enclosure, line cord, strain relief, hardware, etc.

The following are available from Sound Concepts, Inc., P.O. Box 135, Brookline, MA 02146: assembled and tested IR2200 stereo image expander, \$169.00; kit of all parts (KIR-1), \$95.00; PC board (KIR-2), \$16.00; T1 (KIR-3), \$7.50; all pots, knobs, switches and jacks (KIR-4), \$12.50; all semiconductors and sockets for them (KIR-5), \$19.00. Please add \$2.00 for shipping and handling; MA residents add 5% sales tax. If at all possible give street address for UPS delivery. Please add 10% (\$5.00 minimum) for parcel post outside continental U.S.A.

speakers are in phase the sound will appear to come from a point directly between them. If they are out of phase, it will seem to come from the sides, or from each speaker individually. If the apparent

source is diffuse, the speakers should be repositioned as described above and again checked for phasing.

Finally, the speakers themselves must produce a sharp coherent wavefront.

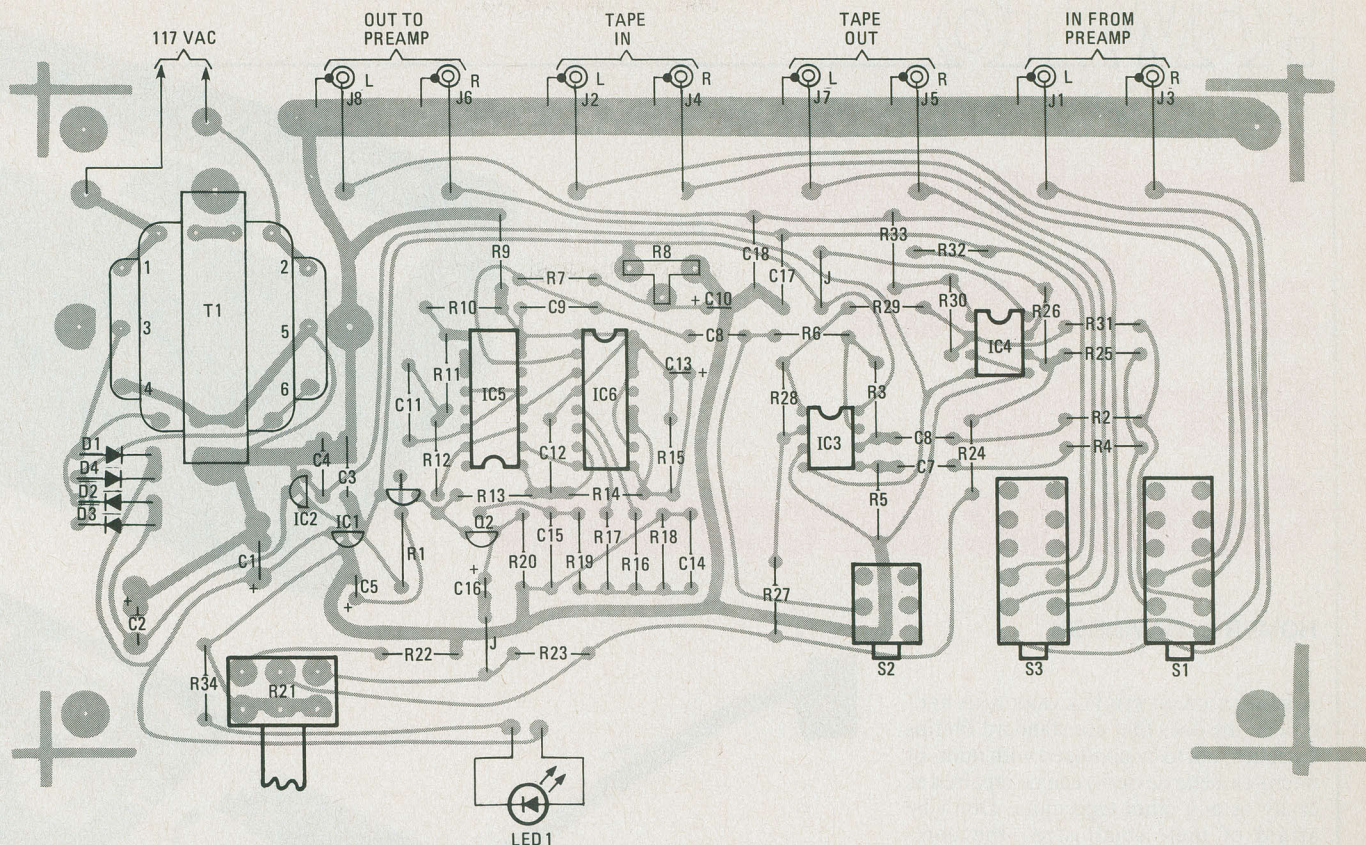


FIG. 12—PROVISION IS MADE for mounting right-angle input and output jacks directly on board.

Two- and three-way speaker systems with a single in-line vertical array of drivers usually work best. Omnidirectional speakers, or those with multiple drivers covering the same frequency range, cannot create as sharply focused an image.

You can actually check all this out before trying an image enhancer. Using a mono signal to get a tightly focused single sound-source located between the speakers is the best and easiest way to judge the imaging capability of your speakers in your listening room. Once you are set up correctly, you will probably be impressed with how much better your stereo system sounds—even without expansion.

Installation and use

The stereo image expander is intended to be connected in the tape-monitor loop of your preamplifier or receiver. Provision is made in the expander for connecting a tape recorder. The recorder can be used in the normal manner when the pre-amp's tape-monitor switch is on and S1 of the expander is in the TAPE position. Image-enhanced tapes that can be played back *without* the expander can be made when S3 is in the REC position. You should never have S1 and S3 pushed in at the same time since that effectively connects the recorder's output back to its input.

The recorder-output jacks from your receiver or preamp should be connected to the INPUT FROM PREAMP jacks, J1 and

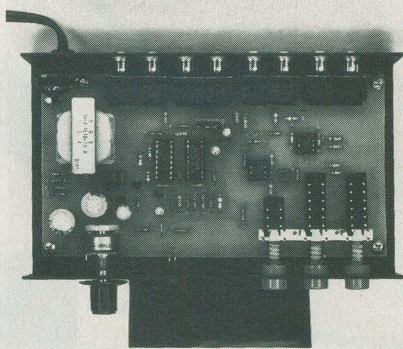


FIG. 13—NOTE HOW LED is mounted *above* the board, not flush with it. All components including transformer and switches, are soldered to board.

J3, on the expander and the OUTPUT TO PREAMP jacks, J6 and J8, to your tape-input or tape-monitor jacks. The expander's TAPE OUTPUT jacks, J5 and J7, are connected to the line-input jacks on the recorder and its line-output jacks connected back to the TAPE INPUT jacks, J2 and J4, on the expander.

If you are using two tape-loops and two recorders, place the expander in loop 2. To play unenhanced tapes through the expander, use the tape-monitor switch corresponding to the loop the recorder is in. With S1 in the **TAPE** position, the signal comes directly from the recorder connected to the expander, and in the **SOURCE**

position the signal is supplied by the receiver or preamp. If the expander is in loop 2 and you want to listen to the recorder in loop 1, either engage both tape monitor switches or—if you have them—the TAPE MONITOR 2 and DUB 1 TO 2 switches on the preamp or receiver.

If you have other signal processors in your system the expander should be the last one in the chain so that there is a minimum loss of phase integrity. If, for example, you already have an equalizer in your tape loop with a recorder plugged into it, plug the expander into the equalizer's tape jacks and the recorder into the expander's tape jacks. The expander can also be connected to the external-processor loop or between the preamp and power amp if you don't wish to use it for recording.

Listening

Before you make a critical evaluation of the stereo image expander's capabilities, make sure your system is set up as described earlier. Start with a record or tape of a good live or concert hall performance, preferably of a large orchestral work so you have a realistic frame of reference. (Most of the recent Telarc records have excellent imaging.) You may want to turn up the image level slightly with some other records, particularly those that were originally recorded using multiple-mike techniques and whose

continued on page 91

continued on page 91

HOW TO

Troubleshoot and Repair Portable Cassette Recorders

HOMER L. DAVIDSON

PORTABLE CASSETTE PLAYERS AND RECORDERS (the ones that use standard Philips cassettes, not to be confused with mini- or micro-cassette devices) can be repaired as easily as any other tape units. Don't be afraid of their small size—the components may be a little closer together and you may have to work in a tighter space, but that's all. Servicing them can be easy when you follow the tips and information here.

If you have a well-equipped workbench you shouldn't need much in the way of additional equipment. If you don't have one, a take-up torque gauge may be needed for mechanical components. A VTVM (Vacuum Tube Volt-Meter) will do nicely for making head-azimuth adjustments, and for troubleshooting the amplifier section, you can use your signal generator, signal tracer, and scope.

Cleaning and lubrication

Most sound and speed problems can be solved by a good clean-up and "lube job." A dirty record/playback head may be responsible for weak and distorted sound, and under- (or over-) lubrication can cause tape-speed to vary erratically.

When a recorder develops speed or sound problems, it's time for a cleanup and lubrication. Start at the erase and record/playback heads and clean them with alcohol and a soft-tipped cleaning stick. Critical points for cleaning are shown in Fig. 1. *Do not* use rubbing alcohol—it contains an additive that may leave a gummy deposit. Use pure isopropyl alcohol (available at your drugstore's prescription counter). If some oxide is packed into the gap area of the record/playback head, gently use the round end of the cleaning stick to remove it. You can get at the heads easily by putting the recorder in the RECORD mode; that moves them out into the open.


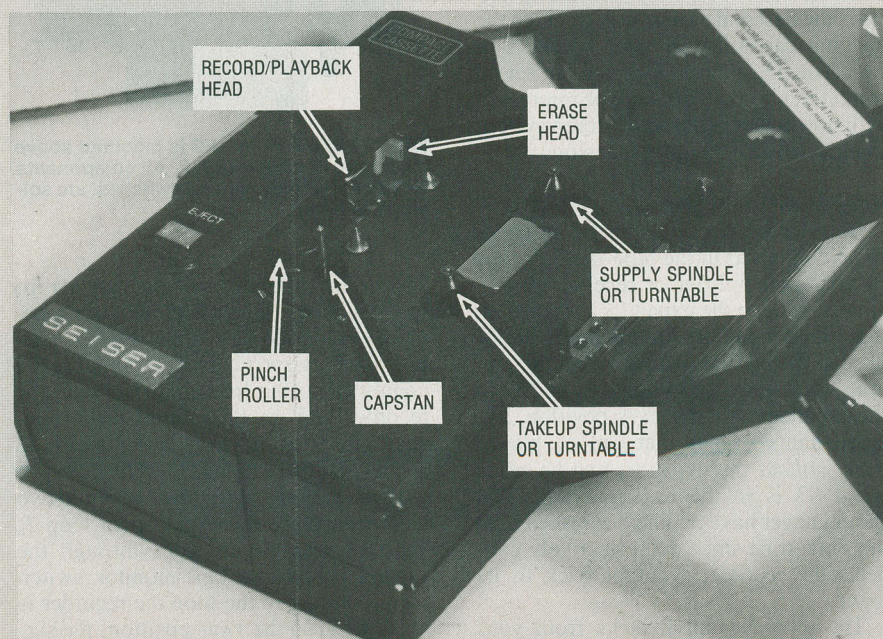


FIG. 1—CRITICAL POINTS FOR CLEANING are indicated above. A good cleaning can be all that's needed to solve many problems.

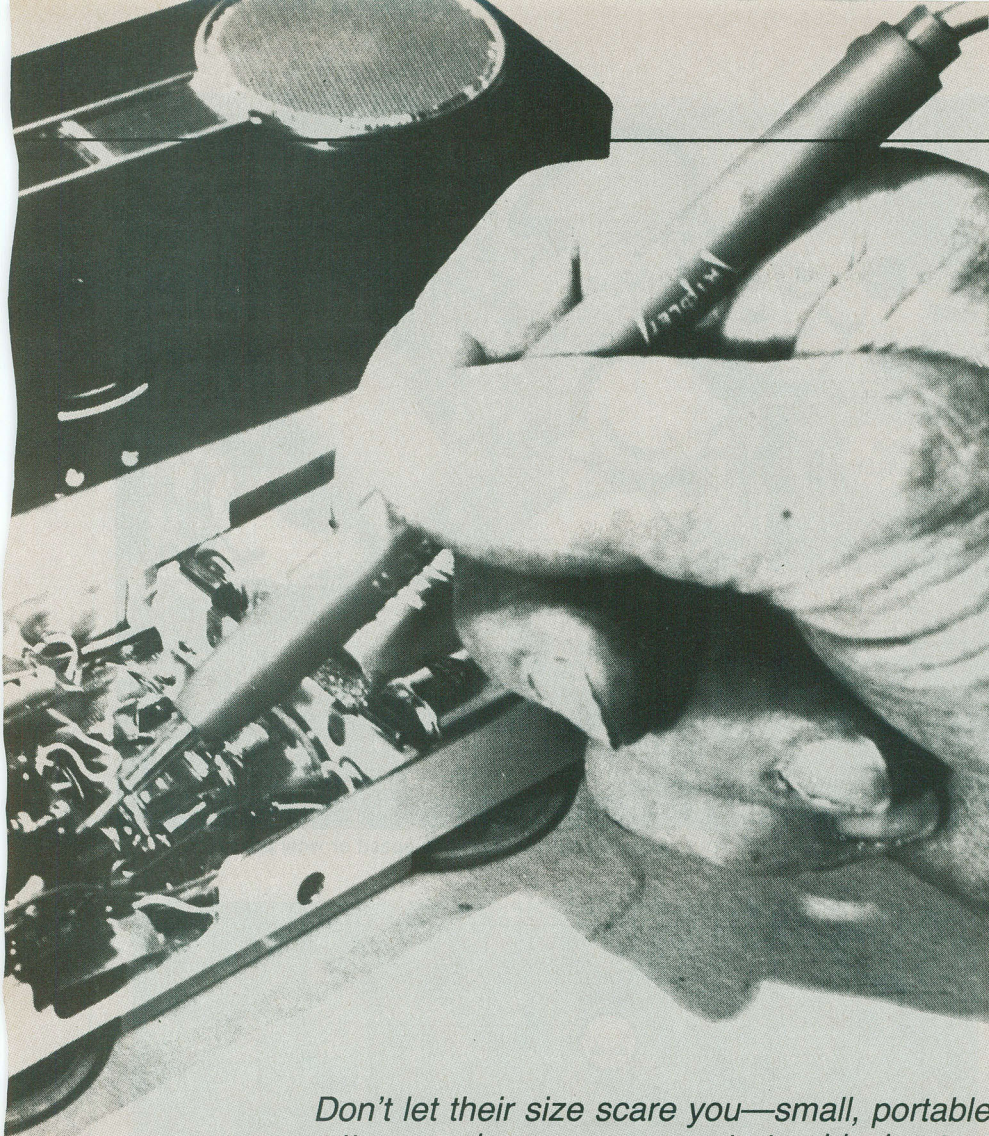

Don't let their size scare you—small, portable cassette recorders are as easy to troubleshoot as their larger brothers. Here are a number of hints and kinks to help you out.

You may find more oxide on the pinch roller and capstan than on the tape heads. Remove it with alcohol. Apply a drop of light oil to the pinch-roller bearing and wipe off any excess. Also, always dry off parts that have been cleaned with alcohol since it can damage many rubber and plastic components if it remains on them too long.

If the capstan flywheel appears sluggish, remove it and clean it with alcohol. Also clean around the flywheel-bearing area using a cleaning stick dipped in alcohol. Place a drop of oil upon the capstan bearing and replace the capstan. Wipe off any excess oil with a paper towel or cloth. Clean the capstan-drive area well to remove any remaining oil.

A dry capstan-bearing may be responsible for erratic or slow tape motion, and noisy and squeaky sounds may be caused by dry motor or pulley bearings. Excess oxide on the pinch roller can also be the cause of slow speed or tape pulling. Oil on any drive surface may produce slow—or no—motion in the parts it contacts.

Erratic bunching of tape from the cassette may be caused by a drop of oil on the drive surface of the take-up turntable.

All rubber or plastic drive-pulley surfaces should be cleaned with a cleaning stick, and a drop of light oil placed on the pulley bearings. Any excess oil should be wiped off. All sliding parts should receive a thin coat of light grease. Finally, most motors have sealed bearings and never needed lubricating.

After cleanup and lubrication, it's always a good idea to demagnetize the record/playback head to insure best frequency-response, and then to check the unit out to see how it performs.

Now we'll discuss some commonly encountered problems, and their causes and remedies.

No play or fast-forward

When the recorder's in the PLAY or RECORD mode, the capstan and pinch roller pull the tape across the record/playback head, with the takeup turntable causing the tape to be wound on the cas-

sette's takeup hub. In FAST FORWARD, the tape moves in the same direction, but the takeup turntable runs at a faster rate of speed; the capstan and pinch roller are disengaged. It's possible for one defective component to affect *all* of those functions.

If the capstan or tape will not move with the PLAY switch engaged, check for a defective ON/OFF switch. Hold the unit close to your ear and see if you can hear the motor running. If the motor is dead, check the power switch and see whether the voltage is being applied to the motor. If the motor is operating, check for a loose or broken drive belt. If the unit works on AC, but not from its batteries, make sure that batteries are not weak or dead.

Erratic fast-forward action can be caused by a dirty, worn, or binding turntable. Check for oil on the idler wheel or drive pulley (see Fig. 2).

Sometimes the fast-forward lever may bend and not permit the drive pulley to

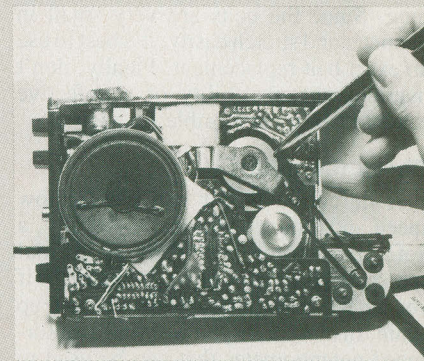


FIG. 2—FAST-FORWARD problems may be caused by oil on the idler pulley or capstan/flywheel.

engage the capstan. Check for a weak spring or an out-of-position lever mechanism. A good cleanup of the take-up turntable and a drop of oil on the drive pulley bearing may cure erratic fast-forward motion.

No rewind

If a recorder/player operates normally in the PLAY and FAST FORWARD modes, but not in REWIND, suspect that the idler or drive pulley is not engaging the supply turntable. In some units the idler pulley gets shifted to the left and rotates the supply spindle in the opposite direction. A dry or worn supply turntable may be the cause of erratic rewind, as well as of slow speeds.

To remedy erratic rewind, remove the supply turntable and clean it with a cloth dampened with alcohol. Don't forget to dry it off afterwards. Place a drop of light oil on the turntable bearing, and then replace the turntable. Clean the rubber or plastic drive area with alcohol and use a

cleaning stick to clean off the idler or drive-pulley surface area. Also check for a worn or binding idler-pulley.

If a loud chattering noise is heard when the cassette is almost rewound, suspect dry hub areas in the cassette itself. A tiny drop of oil in the plastic hub area may help, but be careful; you don't want to ruin the tape.

Slow speed and wow

Slow-speed problems may be caused by a dry-capstan-bearing or by oil on the drive surface. A dry or worn pinch roller can also be responsible for slow speeds or wow. Replace the pinch roller if you find it's out of round after cleanup. (A defective pinch roller can also cause the tape to ride high or to pull from the cassette.)

Check for a loose drive belt, or oil on it, when wow or slow-speed symptoms are noted. You may find that the motor belt slips right at the drive-motor pulley. Some of the important points to check are shown in Fig. 3.

Also, look for a black area or small particle of rubber on the motor pulley; those signs indicate that the belt is slipping. Since the belts are very small in diameter and stretch easily, it's best to use an exact belt replacement. Finally, don't overlook the possibility of a defective cassette being responsible for wow.

Check the motor

A defective motor can cause slow speed and wow conditions. Generally, a defective motor will start at normal speed, and then slow down. Sometimes if you tap the motor housing, it will speed up again. In most units you will find a motor-speed potentiometer that can be used to adjust the speed over a certain range. If the speed adjustment has no effect, check the speed-control circuit and motor. (A typical circuit is shown in Fig. 4.)

In some cases you may find that the motor is running too fast. Adjust the speed control, using a piano or music selection as a reference. You can also use a frequency counter to determine the correct speed.

If the motor is still running too fast, see whether the belt is riding too high on the motor pulley. If none of the above adjustments help, install a new motor, using an exact replacement.

Pulling and bunching tape

Bunching and unraveling of tape in a cassette player may be caused by an erratic or inoperative take-up turntable. The take-up turntable or spindle winds the tape coming from the capstan into the cassette. When the take-up spindle becomes dirty or starts to bind, the excess tape will bunch up and pull out of the cassette. Remove the take-up turntable and clean it with alcohol. Apply a drop of oil to the bearing area. Also, clean the turntable-drive area. Check the idler and

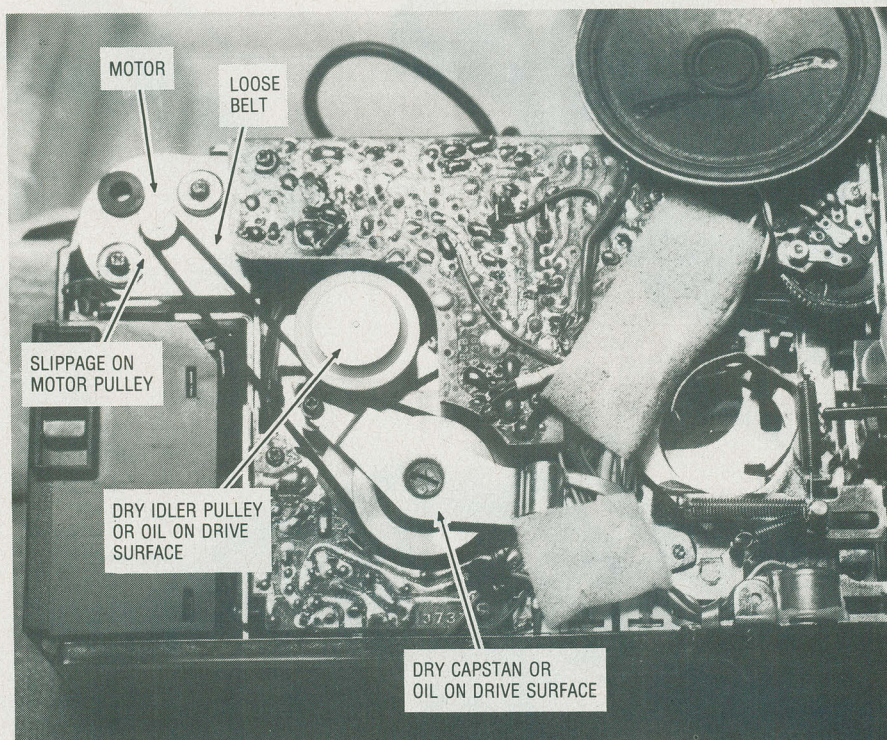


FIG. 3—CHECK THESE AREAS if you are experiencing slow-speed or wow problems.

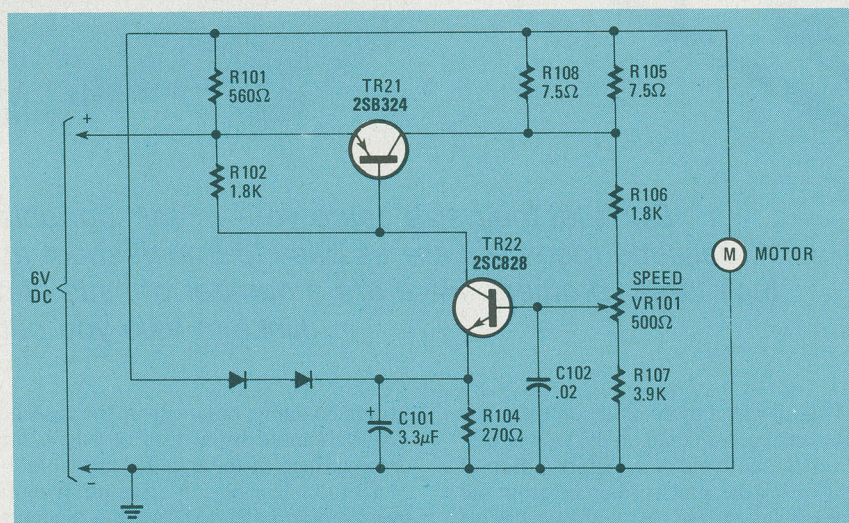


FIG. 4—MOTOR-SPEED CONTROL circuit used by J.C. Penny model 6541. Circuits in other recorders should be similar.

drive pulleys for oil or dirty drive-surfaces.

Sometimes the pressure roller may become worn or out of round, and cause the tape to ride high and pull out of its proper path. In that case, try cleaning the pinch roller and capstan with alcohol. A bent capstan may also cause tape pulling.

If the take-up turntable, pinch roller, and capstan appear to be normal and the player is still pulling tape, check the take-up torque with a torque gauge. Finally, remember that a defective cassette can cause tape to unravel or bunch up.

No sound

If the tape is moving but there's no

sound, suspect the record/playback head or the amplifier section. Quickly rotate the volume control up and down and listen for a scratchy sound from the speaker. If you can hear some noise, it's an indication that the amplifier is working, so suspect the record/playback head. If you hear a loud hum with the volume wide open, check for a broken wire at the record/playback head. Since the head assembly moves forward every time the PLAY or RECORD buttons are pushed, the wires leading to it have a tendency to break with time.

To determine whether the record/playback head is defective, pass a small screwdriver-blade rapidly across the head

area. You should hear a flutter from the speaker. If you don't, dismantle the player by removing both the top and bottom covers. Check the head connections for broken wires. Touch the screwdriver blade to the ungrounded side of the tape head. With volume wide open you should hear a loud hum; a loud noise would indicate that the tape head may be defective. Remove the cable-leads and measure the resistance of the head. Normally, that resistance will be between 50 and 800 ohms.

Defective components in the audio stages can be located with an audio-generator/signal tracer and through voltage measurements. Start at the first AF transistor and inject a 1-kHz signal to the base of each transistor. Step by step, check each stage. When the signal appears, you have located the defective stage. Check each transistor in the problem area for out-of-line voltages. (A schematic is a must when servicing cassette-recorder amplifier circuits.)

In some earlier units you may find five or more small transistors in the amplifier stages, while in present-day ones only one or two transistors may precede a power-IC output circuit. Such a circuit is shown in Fig. 5. To signal-trace the IC circuits, inject an audio signal at the IC's input pin and use the speaker as the indicator. To make sure the IC really is defective, measure the voltages at each pin. With correct voltages, but no signal from the IC, you can safely assume that the IC is defective. If the IC is leaky, even the supply voltage may be affected.

Weak and distorted sound

Weak and distorted sound may be caused by a dirty record/playback head. Clean the head with alcohol and a cleaning stick, as described earlier, before tearing into the amplifier. A weak battery or insufficient operating voltage can also affect the quality of the sound.

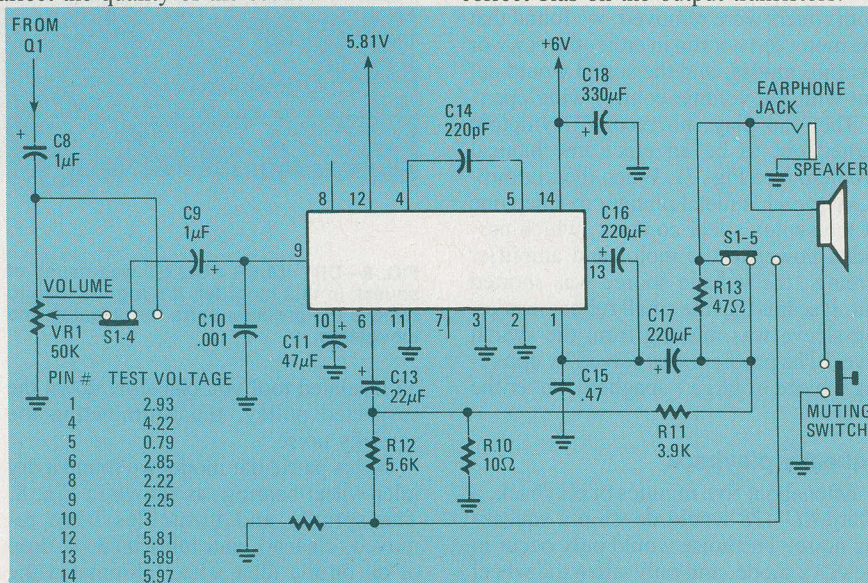


FIG. 5—IC OUTPUT CIRCUIT used in Sanyo model M1000. Voltages shown are typical for this unit but may be different in others.

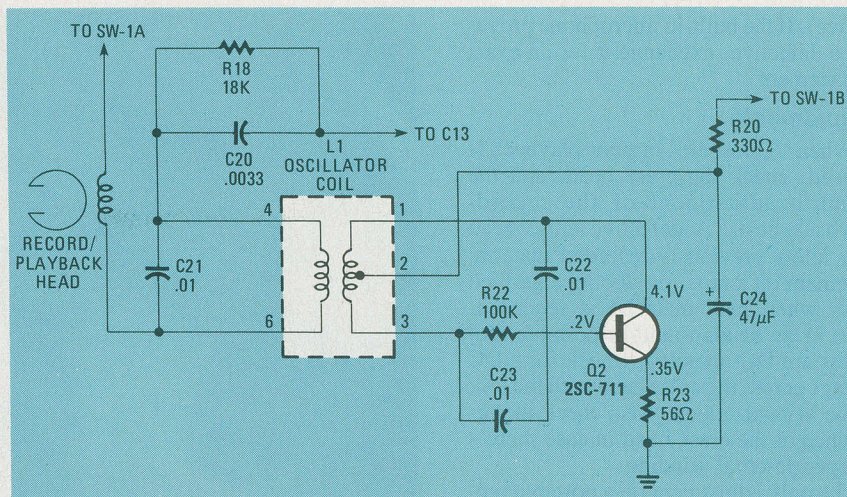


FIG. 6—RECORD OSCILLATOR CIRCUIT used by Sharp model RD-428UA. Use a scope on L1 to determine whether the oscillator is working.

The best method for locating a weak audio-stage is to inject an audio signal, with a scope connected to the output of the recorder/player so that you can observe the audio waveform. Start at the record/play-head connections. The signal should be the same on both sides of the electrolytic coupling-capacitor. (Most weak-sound problems are caused by small coupling-capacitors and transistors in the amplifier section.) If it is not, shunt a new capacitor across the suspected one and see whether the sound returns. Each transistor in the amplifier section should have a large gain from its base to collector terminals.

Excessive distortion may accompany a weak-signal condition. Most distortion in small amplifiers takes place in the output stages. In push-pull transistor output-circuits, an open or leaky transistor can produce weak and distorted sound. Since most circuits of that type are DC-coupled, check the driver or AF transistor for incorrect bias on the output transistors.

Remove both transistors when distortion is located in a push-pull output circuit—it's best to check each transistor for leakage out-of-circuit. Before replacing the output transistors, check the emitter and bias resistors for correct values. Generally, a burnt emitter-resistor will be found along with a shorted or leaky output-transistor.

A leaky IC can also produce weak and distorted audio. Replace the suspected IC when no signal will pass through it or if incorrect voltages are measured at its pins. Use a wick-type solder absorber (like *Solder-Wik*) to remove the excessive solder from the IC pins to make removing the part easy. Then use a low-wattage pencil iron to install the new IC.

No record function

If the unit will play but not record, suspect a dirty PLAY/RECORD switch or defective record circuits. First, make sure the record/playback head is clean. Then spray the PLAY/RECORD switch with contact-cleaner. Work the switch back and forth to clean the contacts and then try to record once again.

Although most portable recorders do not have an oscillator stage to excite the record tape-head, you may run across one that does. A representative circuit is shown in Fig. 6. To determine whether the oscillator is operating, use the scope and check the waveforms at the primary and secondary windings of L1. Transistor testing of Q2 and voltage measurements can indicate whether the transistor is functioning properly.

Check for poor connections to the built-in microphone. Most built-in mikes are electret-capacitor types and require a DC-voltage to work, so test for that voltage at one of the microphone terminals. A defective microphone may be responsible for weak or erratic recordings. Substitute a dynamic microphone across the shielded wires to the built-in mike terminals (but do not connect it to the DC

source). If the built-in microphone proves to be defective, exchange it for an exact replacement.

Adjustments

When "crosstalk" or poor playback is noticed, check the erase head, and the azimuth adjustment of the record/playback head. A defective erase head may allow previously-recorded material to remain on a tape, producing a garbled mess when new material is recorded. Most erase heads found in portable recorders are DC-operated. Check for a DC voltage across the erase head with the unit in the RECORD mode. Also check the resistance of the erase head in case there's an open internal winding.

The only adjustment on a portable recorder's record/playback head is for azimuth (elevation). The azimuth-adjustment screw is usually located on one side of the head, with a coiled spring underneath it. Connect a VTVM with an eight-ohm dummy load to the earphone jack. Insert a 3-kHz or 6.3-kHz test tape and start it playing. Adjust the azimuth screw for the highest reading on the VTVM. After that has been done, you may want to dab the adjustment screw with paint or glue to secure it in place.

The only other mechanical adjustments are for take-up torque and adjustment of the pressure roller. (You may find that either one or both adjustments are fixed in some models.) The pressure-roller adjustment can be made using a spring scale and changing the position of the pressure-roller spring to vary the tension it puts on the mechanism.

Take-up torque should be measured on the take-up turntable with a torque gauge while in PLAYBACK mode. Most take-up torque readings should be between 35-60 gr-cm. For greater tension, bend the tension spring and, if necessary, replace the take-up pulley. It's best to follow the manufacturer's service literature for correct tension adjustment.

Now let's take a look at some typical case histories.

Weak and distorted output

A GE NBR-35311C had weak and distorted sound. Although the symptoms indicated possible output-transistor problems, the tape head, pinch roller, and capstan were cleaned with alcohol as a matter of routine. The weak condition still remained, as expected.

When the back cover was removed we noticed that new batteries had been installed. Only 2.7-volts was measured at the adjustment transistors. Either the transistors were defective or something in the circuit was loading down the voltage source. A bench supply was connected to the player for servicing and everything worked normally. It turns out that one of the new batteries was practically dead, and the battery terminals were corroded. A good cleanup of the battery terminals

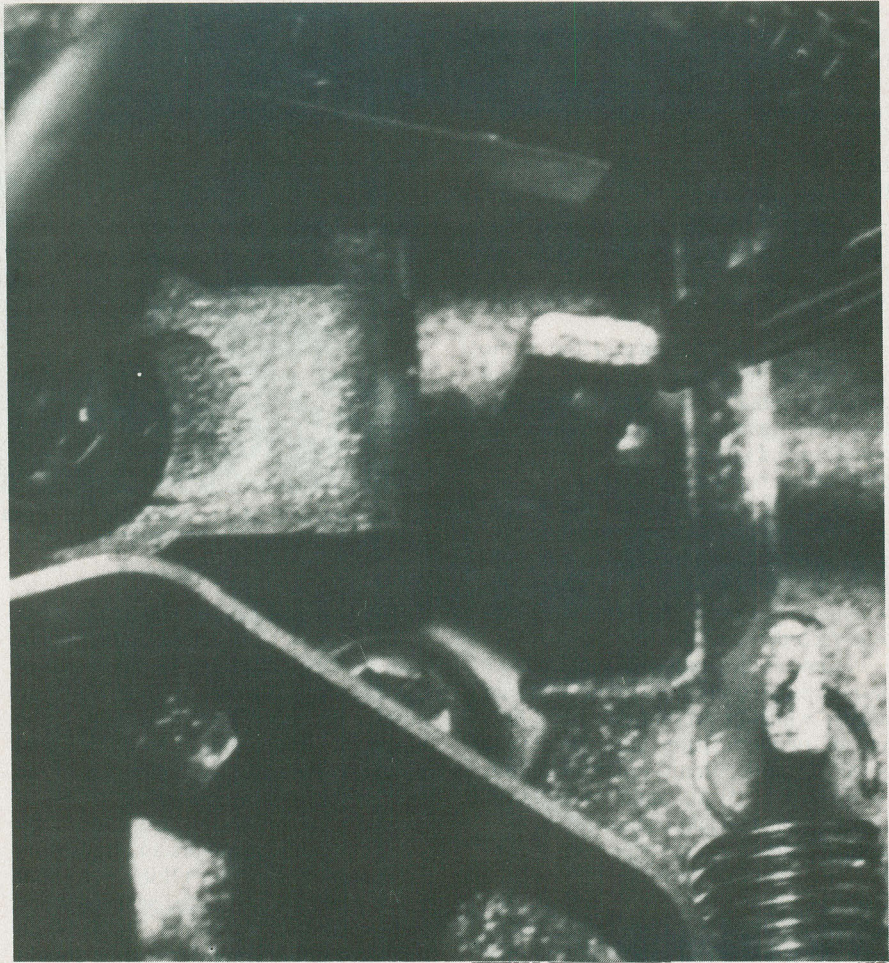


FIG. 7—THE UNINSULATED switch lever shorted out the power-supply voltage in this Sharp model RD-428UA.

and a set of fresh batteries solved the weak-audio/distortion condition.

No play, no record

In a Sharp RD-428UA, we found that the motor was turning, but we couldn't play or record. Both REWIND and FAST FORWARD modes were normal. When both covers were removed, we found that the motor did not run in either the PLAY or RECORD modes, and the sound would cut out with the volume control wide open.

The "no play, no record" symptom turned out to be an electromechanical problem (see Fig. 7). When the RECORD/PLAY switch's metal plunger touched one of the switch's leaf contacts, which provided power to the motor and amplifier circuits, the voltage source was shorted out. It seems that the small rubber insulating sleeve was missing from the switch lever. The problem was solved by epoxying a piece of large "spaghetti" over the lever.

Squeaky playback

After about five minutes of playback, a Sharp RD-428 would develop a squeaking noise. The noise would only occur in the PLAY mode, and only when the wheel or pulley came around to a certain position. Sometimes by probing around with

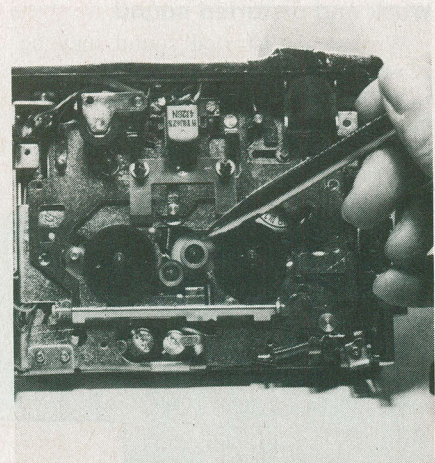



FIG. 8—DRY IDLER PULLEY was cause of squeak in this recorder. It's a good idea to remove the problem parts for cleaning and lubrication.

an insulated tool you can slow down the suspected pulley, thus eliminating the squeaky noise.

In this particular model we found a dry idler-wheel bearing, as shown in Fig. 8. The spindle and turntables were removed, cleaned, and lubricated. A drop of oil on the idler wheel eliminated the squeaking noise.

continued on page 107

ALL ABOUT PULSE GENERATORS

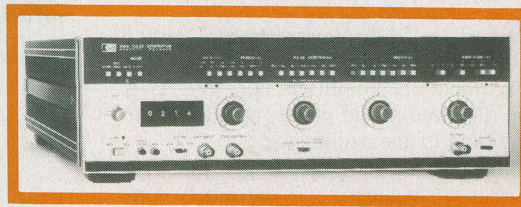

This month we'll look at another pulse-generator application, testing analog circuits, as well as some problems that you might run into when you use that device.

CHARLES GILMORE

Part 4 SO FAR WE HAVE CONFINED our discussion to using the pulse generator in logic-circuit analysis. While that is one of the prime functions of the pulse generator, it is not its only one. Let's begin this month by looking at another area where the pulse generator is useful—testing and analyzing analog circuitry.

Analog circuits

Using a pulse generator as a signal source can simplify many of the measurements that are often made when testing analog circuits. That's because, generally speaking, pulse generators are useful over a very wide frequency range, which can come in handy when working with broadband amplifiers, etc.

For instance, a single, conventional, pulse generator is the only signal source you need to test an amplifier whose frequency response extends from below 1 Hz to considerably more than 10 MHz. Otherwise, testing that amplifier would require using an audio generator for the low end and an RF generator for the upper end, or perhaps a very wide-range function generator.

The reason for that becomes apparent if the nature of a pulse is analyzed. Such analysis would reveal that the pulse's fast rise and fall times are caused by the pulse's high-frequency components, while the interval between the rise and fall times (i.e. the top of the pulse) is caused by the low-frequency components; in some cases, the frequency of those components is so low that it is approaching DC. Those high- and low-frequency components are what gives the pulse generator its wide frequency range.

Frequency-response measurements on an amplifier are usually made at the 3-dB points; that is, the point at which amplifier delivers half its rated power output, or

70 percent of its rated voltage output. That 3-dB point is considered the upper and lower cutoff frequency of an amplifier. The simplest method to measure the low-frequency 3-dB cutoff is by adjusting the pulse generator so that the pulse *droop* is 25 percent. Pulse droop (the difference between the amplitude immediately following the leading edge and the amplitude at which the trailing edge begins) is expressed as a percentage of the amplitude at the leading edge (see Fig. 11).

When the pulse droop is adjusted to 25 percent, the width of the pulse is related to the frequency (in Hz) of the lower 3-dB point through the formula:

$$f_{\text{low}} \approx \frac{0.0456}{t}$$

where t is the width of the pulse. The constant (0.0456) is derived from a Fourier analysis of the pulse.

To measure the frequency of the upper 3-dB cutoff, the following formula is used:

$$f_{\text{upper}} = \frac{0.35}{t_r}$$

where f_{upper} is the upper 3-dB cutoff frequency (MHz), and t_r is the pulse risetime in nanoseconds.

While that formula has been idealized and is for a circuit where the product of the capacitance and inductance is 0, the formula will hold until that product exceeds 0.25. After that point, some overshoot begins to occur at the end of the leading edge, lowering the value of the constant, 0.35, in the formula. With overshoot of 25 percent, for instance, that constant would be lowered to 0.28.

Some additional information about the frequency response of a broadband amplifier can be obtained using a pulse generator. Remember that a pulse con-

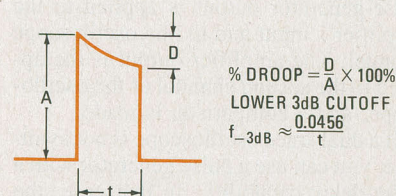


FIG. 11—PULSE DROOP is useful in finding the lower 3-dB point of an amplifier.

sists of a fundamental frequency plus a great number of even and odd harmonic components with specific phase relationships with each other, as well as with the fundamental frequency. If that phase relationship is not maintained, the waveshape of the pulse deteriorates. If an essentially stable pulse waveform is passed through an amplifier, the amplifier's output can be examined for any aberrations in that waveform. The presence of those aberrations indicates that the phase response of the amplifier is not uniform—i.e., that there are peaks and/or valleys in the amplifier's frequency-response curve. That would be caused by either leading or lagging reactive elements in the circuit. At that point, further analysis with a sweep generator or a low-distortion audio oscilloscope is needed.

As noted earlier, rise-time measurements let you determine approximately the upper frequency-response limits of a broadband amplifier. A few precautions must be taken when making such rise-time measurements. One thing that must be considered is the effect of the test setup. Each part of that setup plays a role in determining the rise time of the output that is displayed; in other words, the rise time of the pulse is changed slightly as it passes through the various parts of the test setup. The displayed rise time, therefore, is actually a function of the rise times

through each part of that setup and can be found from:

$$T_R = 1.1 \sqrt{T_G^2 + T_A^2 + T_P^2 + T_O^2}$$

where T_R is the display rise time, T_G is the rise time of the pulse generator, T_A is the rise time of the amplifier under test, T_P is the rise time of the probe, and T_O is the rise time of the oscilloscope.

Because of its exceedingly fast rise time, a pulse generator is extremely convenient for measuring propagation delay and phase delay. Both analog and digital circuits introduce some fixed time delay to signals that pass through them. For example, if a J-K flip-flop is clocked, it will take several nanoseconds for the results of that clocking to appear at the output of the flip-flop. That delay in response is called the propagation delay of the flip-flop.

Analog amplifiers also suffer from propagation delay. The easiest way to measure that delay is to use a dual-trace oscilloscope and a pulse generator. The pulse-generator output is applied to the amplifier's input and to one oscilloscope channel. The amplifier output is the applied to the second channel of the oscilloscope, and a comparison is made.

If a dual-trace oscilloscope is not available, you can use a pulse generator with a pulse-delay capability. In that case, the input to the amplifier is connected to the delayed generator output. The amplifier output and the non-delayed pulse-generator output are both applied to the oscilloscope. The pulse-delay control of the generator is then adjusted until a single pulse is obtained. The amount of delay necessary to display the single pulse is equal to the propagation delay of the amplifier.

In order to successfully combine the amplifier output with the pulse-generator output, some series-limiting resistance must be used. Great care must be taken to insure that the added circuitry does not contribute additional phase shift. Figure 12 shows an example of such a situation.

Pulse generators are also useful in evaluating the high-frequency characteristics of diodes and transistors. The diodes used in either radio-frequency or digital applications are required to recover very rapidly from switches between reverse- and forward-bias.

When a diode is forward-biased, the area at the junction is filled with majority carriers. ("Majority carrier" is a term used in semiconductor electronics to describe the predominant type of carrier in a semiconductor material. In n-type material, the predominant carrier is the electron; in p-type material it is the absence of an electron, which is called a *hole*.) When the diode is reverse-biased, the junction has few majority carriers. Obviously, the change in the number of majority carriers at the junction can not occur instantaneously.

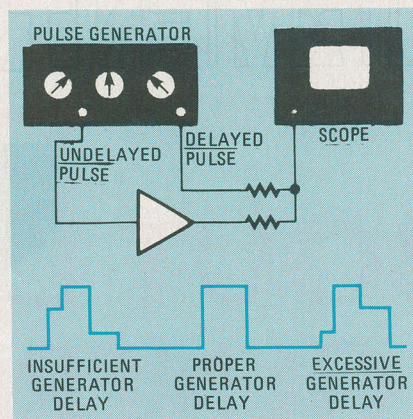


FIG. 12—A PULSE GENERATOR is used here to measure the propagation delay through an amplifier.

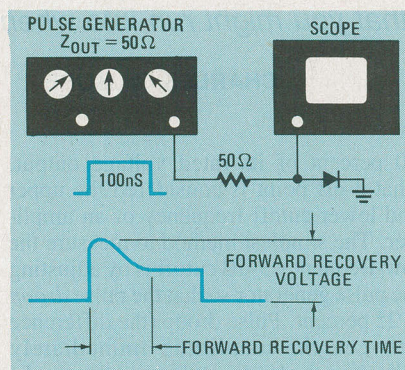


FIG. 13—MEASURING THE FORWARD recovery voltage and forward recovery time of a switching diode. The pulse generator should be set for a 100-nanosecond pulse width with a less than 1 percent duty cycle. The output voltage of the generator should be set to produce a specified steady-state current in the diode.

Let's first look at what happens when a diode is suddenly switched from reverse- to forward-bias. When that happens, the majority carriers move to the area around the junction. But, until that area is filled with those majority carriers, the voltage across the diode is considerably greater than its normal forward-biased voltage. That voltage *transient* is of concern if the diode is to be used in switching applications. Figure 13 shows a test setup that can be used to measure that *transient*, as well as the waveform that would be displayed on the scope. The size and duration of the transient can be found by inspecting the waveform as shown.

The forward-recovery specifications of a diode are normally given for some steady forward-current value, once the transient conditions have subsided. It is that forward current, combined with a 50-ohm resistor, that determines the pulse generator's output voltage; pulse duration should be 100 nanoseconds. A generator having a 10- to 20-nanosecond rise time is suitable for that test, and no offset voltage is required.

Now, let's consider what happens when a diode is suddenly reverse-biased.

When that happens, a large reverse current flows until there are few majority carriers left around the junction. How long that current flows is important if a diode is to be used in a switching application. Figure 14 shows the test setup used to measure that, as well as the waveform that is likely to be seen on the scope.

The requirements placed on the pulse generator and the oscilloscope used to measure reverse-recovery time are somewhat greater than those for forward-recovery time. Reverse-recovery time in diodes is on the order of a few nanoseconds, and the rise time of the pulse generator must be considerably less. In many cases, the rise time of both the pulse generator and the scope must be less than 1 nanosecond. However, generators with more moderate specifications can be used to test slower diodes.

Figure 15 shows the test setup used to measure the turn-on and turn-off times of a switching transistor, as well as the typical waveforms that would be displayed on the scope. That test is one of the most important ones done when you are analyzing the operation of a switching transistor.

As with a diode, transistor specifications are given at some specified base- and collector-current levels. The bias and $B+$ voltages supplied to the circuit establish proper transistor operation and should be selected so that those currents are at the proper level. Note that turn-on time is determined by noting the point where the generator's output rises to 10 percent of its final value and the point where the transistor's output drops to 90 percent of its initial value. Conversely, turn-off time is measured between the points where the generator's output drops 10 percent from its maximum level, and the transistor's output rises to 90 percent of its initial value. Once again, for transistors with reasonable switching speeds, the pulse generator and the oscilloscope must have relatively good rise-time specifications. However, pulse generators with more moderate capabilities can be used to perform those tests on some slower transistors. Other transistor measurements that can be made include storage time, stage rise time, and voltage breakdowns.

Using a pulse generator when testing transistors and diodes has several advantages. Two of the most obvious are that they can be used to supply a bias offset voltage, (eliminating additional power supplies) and that their sharp rise times eliminate the need to measure the rise time of the generator itself. In addition, pulse generators can be operated at extremely low duty cycles. For instance, in the diode and transistor tests we just discussed, duty cycles of one percent or less are called for. Such low duty cycles let you perform tests that could not be safely done under steady-state conditions. Such steady-state testing would overheat many

of the devices, possibly destroying them, or at least changing their electronic characteristics. Even though peak power developed in a circuit when using a pulse generator may far exceed the maximum permissible continuous power, with that device's low duty-cycle the average power is well within its ratings.

Sources of error

A pulse generator is probably one of the easiest instruments to use improperly. The vast number of settings and modes make it easy to set up improperly. Therefore, using a pulse generator without an oscilloscope is not advisable. With a scope, you can easily spot setup errors and correct them.

The most frequent errors in using a pulse generator are human errors. For example, a common mistake is exceeding the allowable duty cycle. As noted earlier, a 70 percent duty cycle is common for most pulse generators. The most usual mistake here, however, does not involve exceeding the duty cycle by a small amount (such as 75 percent as opposed to 70 percent, for example), but by exceeding it by orders of magnitude. That happens when, for instance, a pulse-repetition rate of 1 kHz has been established, but a pulse width of 10 milliseconds is chosen instead of 10 microseconds. In that situation, the duty cycle has been exceeded by a factor of 10.

On pulse generators with a pulse-delay feature, a similar error occurs. In that case, the delay time exceeds the time established by the pulse-repetition rate. A pulse generator set for a repetition rate of 1 pulse-per-millisecond might have the delay generator set at 10 milliseconds. Due to the nature of the monostable multivibrator used to generate the delay time, the first pulse is chosen to generate the 10-millisecond delay interval, and the following nine pulses are ignored. The result is one pulse-per-10 milliseconds, even though the pulse-repetition rate has been set for 1 pulse-per-millisecond.

Variable rise- and fall-times, although a useful feature, can also give rise to errors. For instance, assume a pulse width of 20 nanoseconds is desired. If, however, the rise- and fall-times are set at 15 nanoseconds, the time required to reach the maximum output and drop back to zero would be a total of 30 nanoseconds, 10 nanoseconds greater than the pulse width. Thus, the pulse does not have enough time to reach the proper levels, making any measures of amplitude incorrect.

As noted previously, improper transmission lines or terminations can seriously degrade pulse characteristics. Care must be taken to prevent pulses that are distorted beyond recognition.

In similar fashion, certain situations require the pulse to be split between two different transmission lines and later re-

combined by some form of circuitry. If narrow pulses at a high rate, and relatively long cables are used, great care must be taken to insure that both pulses arrive at the proper termination simultaneously. If that is not done, pulse-stretching may occur.

In many cases, both the amplitude and the offset controls of the pulse generator have extremely coarse calibration; that can cause misadjustment. Errors can easily occur when setting the generator's output amplitude. A 50 percent setting, for instance, does not mean 50 percent of the rated amplitude. The output specification of the generator indicates a maximum output, but that output is usually given in terms of "not less than." In many cases, the actual output can exceed that rated output by as much as 20 to 25 percent. As

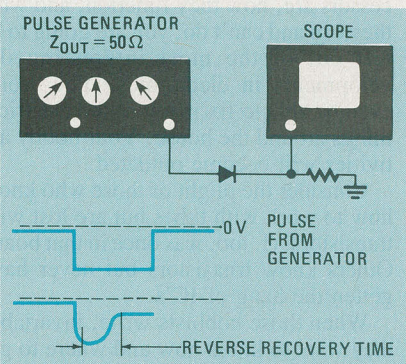


FIG. 14—MEASURING DIODE reverse-recovery time. A 100-nanosecond pulse-width with a duty cycle of less than 1 percent should be used. The generator rise time should be less than the expected reverse-recovery time. The positive pulse offset is set to generate the specified forward current. A 60-ohm resistor converts the output current to voltage for display on the oscilloscope.

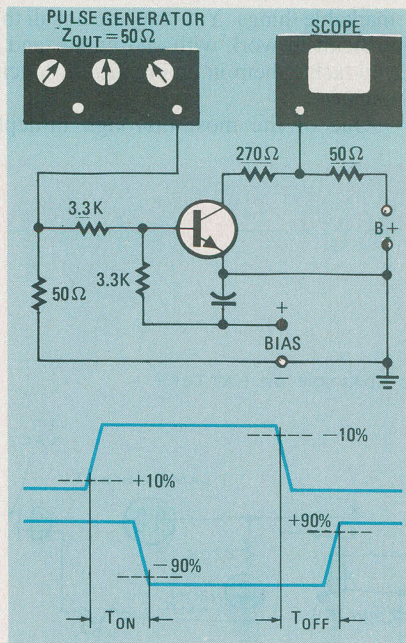


FIG. 15—MEASURING THE SWITCHING time of a transistor. The pulse generator is set for a 100-nanosecond pulse-width with a duty cycle of less than one percent.

a result, the most accurate way to set the output amplitude is to monitor the generator's output on a scope. Another possible error in setting the output amplitude can be introduced by using an output attenuator. Those errors are caused by using the wrong level of attenuation and are quite large—at least one order of magnitude.

Generator-induced errors

A pulse generator is usually not calibrated very precisely. However, if you are fully aware of all its specifications and what they mean, you will have little or no problem in getting maximum use from the instrument. However, failure to recognize some of these specifications can result in generator-induced measurement errors. Jitter can occur in the repetition rate, the amount of pulse delay, and the pulse width. The amount of jitter must be taken into consideration when a rather stable pulse-width, delay, or repetition-rate is required.


When using a pulse generator, especially over extended periods of time, it is necessary to reset the operating parameters, many of which can vary over time, or with changes in temperature and other factors. Certain pulse-generator characteristics are affected by changes in the load (for example, the baseline offset, which is often simply a current generator operating into a known load).

Frequently, certain pulse-generator controls interact somewhat. For example, any changes in the rise time and fall time of the output pulse can cause changes in the pulse width and amplitude.

When you use the dual-pulse or twin-pulse mode, make sure that the delay time is long enough to permit the first pulse to return to zero before the second pulse is generated. It is possible to set two pulses with such a short delay time between them that they never return to the baseline.

Finally, it is important to remember that the best way to get the most out of a pulse generator is to use it with a good oscilloscope.

R-E

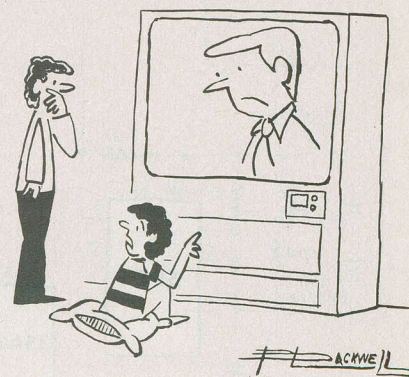

"I'd like to turn it off, father, but he's telling me to stay tuned, and he's bigger than you!"

74 RADIO-ELECTRONICS

EARL "DOC" SAVAGE K4SDS, HOBBY EDITOR

FOR ONLY \$129.95 Learn Computing From The Ground Up

Build a Computer kit that grows with you, and can expand to 64K RAM, Microsoft BASIC, Text Editor/Assembler, Word Processor, Floppy Disks and more.

EXPLORER/85

Here's the low cost way to learn the fundamentals of computing, the all-important basics you'll need more and more as you advance in computer skills. For just \$129.95 you get the advanced design Explorer/85 motherboard, with all the features you need to learn how to write and use programs. And it can grow into a system that is a match for any personal computer on the market. Look at these features: 8085 Control Processing Unit, the microprocessor "heart" of the Explorer/85. (Join the millions who will buy and use the 8080/8085 this year alone) ... Four 8-bit plus one 6-bit input/output ports from which you can input and output your programs, as well as control exterior switches, relays, lights, etc. ... a cassette interface that lets you store and reload programs you've learned to write ... deluxe 2,000 byte operating system/monitor makes it easy to learn computing in several important ways ... It allows simpler, faster writing and entering of programs ... It permits access by you to all parts of the system so you can check on the status of any point in the program ... It allows tracing each program step by step, with provision for displaying all the contents of the CPU (registers, flags, etc.) ... and it does much more!

You get all this in the starting level (Level A) of the Explorer/85 for only \$129.95. Incredible! To use, just plug in your ACDC power supply and terminal or keyboard/display ... if you don't have them, see our special offers below.

□ Level A computer kit (Terminal Version) ... \$129.95 plus \$3 P&I.*
□ Level A kit (Hex Keypad/Display Version) ... \$129.95 plus \$3 P&I.*

LEVEL B — This "building block" converts the motherboard into a two-slot S100 bus (industry standard) computer. Now you can plug in any of the hundreds of S100 cards available.

□ Level B kit ... \$49.95 plus \$2 P&I.*
□ S100 bus connectors (two required) ... \$4.85 each, postpaid.

LEVEL C — Add still more computing power: this "building block" mounts directly on the motherboard and expands the S100 bus to six slots.

□ Level C kit ... \$39.95 plus \$2 P&I.*
□ S100 bus connectors (five required) ... \$4.85 each, postpaid.

LEVEL D — When you reach the point in learning that requires more memory, we offer two choices either add 4k of a memory directly on the motherboard, or add 16k to 64k of memory by means of a single S100 card, our famous "JAWS".

Level D kit: (CHECK ONE) ... □ 4k on-board ... \$49.95 plus \$2 P&I.* □ 16k S100 "JAWS" ... \$149.95 plus \$2 P&I.* □ 32k S100 "JAWS" ... \$199.95 plus \$2 P&I.* □ 48k S100 "JAWS" ... \$249.95 plus \$2 P&I.* □ 64k S100 "JAWS" ... \$299.95 plus \$2 P&I.*

LEVEL E — An important "building block," it activates the 8k ROM/PROM space on the motherboard. Now just plug in our 8k Microsoft BASIC or your own custom programs.

□ Level E kit ... \$5.95 plus 50¢ P&I.*
MICROSOFT BASIC — It's the language that allows you to talk English to your computer! It is available three ways: □ 8k cassette version of Microsoft BASIC (requires Level B and 12k of RAM minimum; we suggest a 16k S100 "JAWS" — see above) ... \$64.95 postpaid.
□ 8k ROM version of Microsoft BASIC (requires Level B & Level E and 4k RAM; not plug into your Level E socket). We suggest either the 4k Level D RAM expansion or a 16k S100 "JAWS" ... \$99.95 plus \$2 P&I.*

□ Disk version of Microsoft BASIC (requires Level B, 32k of RAM, floppy disk controller, 8" floppy disk drive) ... \$325 postpaid.

TEXT EDITOR/ASSEMBLER — The editor/assembler is a software tool (a program) designed to simplify the task of writing programs. As your programs become longer and more complex, the assembler can save you many hours of programming time. This software includes an editor program that enters the programs you write, makes changes, and saves the programs on cassettes. The assembler performs the clerical task of translating symbolic code into the computer-readable object code. The editor/assembler program is available either in cassette or a ROM version.

□ Editor/Assembler (Cassette version; requires Level B and 8k (min.) of RAM — we suggest 16k "JAWS" — see above) ... \$59.95 plus \$2 P&I.*

□ Editor/Assembler (ROM version; supplied on an S100 card; requires Level B and 4k RAM (min.) — we suggest either Level D or 16k "JAWS") ... \$99.95 plus \$2 P&I.*

8" FLOPPY DISK — A remarkable "building block." Add our 8" floppy disk when you need faster operation, more convenient program storage, perhaps a business application, and access to the literally thousands of programs and program languages available today. You simply plug them into your Explorer/85 disk system — it accepts all IBM-formatted CP/M programs.

□ 8" Floppy Disk Drive ... \$499.95 plus \$12 P&I.*
□ Floppy Controller Card ... \$199.95 plus \$2 P&I.*
□ Disk Drive Cabinet & Power Supply ... \$69.95 plus \$3 P&I.*

□ Drive Cables (set up for two drives) ... \$25.00 plus \$1.50 P&I.*
□ CP/M 2.2 Disk Operating System: includes Text Editor/Assembler, dynamic debugger, and other features that give you Explorer/85 access to thousands of existing CP/M-based programs ... \$150.00 postpaid.

NEED A POWER SUPPLY? Consider our AP-1. It can supply all the power you need for a fully expanded Explorer/85 (note: disk drives have their own power supply). Plus the AP-1 fits neatly into the attractive Explorer steel cabinet (see below).

□ AP-1 Power Supply kit (8V @ 5 amps) in deluxe steel cabinet ... \$39.95 plus \$2 P&I.*

NEED A TERMINAL? We offer you choices: the least expensive one is our Hex Keypad/Display kit that displays the information on a calculator-type screen. The other choice is our ASCII Keyboard/Computer Terminal kit that can be used with either



1. Plug in Netronic's Hex Keypad/Display
2. Add Level B to convert to S100
3. Add 4k RAM
4. Plug in Level E here: on-cassette Microsoft BASIC or Editor/Assembler in ROM
5. Add two S100 boards
6. Add your own custom circuits (prototyping strips)
7. Connect terminal

a CRT monitor or a TV set (if you have an RF modulator).
□ Hex Keypad/Display kit ... \$69.95 plus \$2 P&I.*

□ **FASTERM - 64 TERMINAL KIT** — Featuring a 56 key ASCII Keyboard, 128 character set upper and lower case, 75 ohm output, 8 baud rates: 150 to 19,200 (switch select), RS232C or 20 MA output, 32 or 64 character by 16 line formats, complete with Deluxe Steel Cabinet and Power Supply ... \$199.95 plus \$3 P&I.*

□ RF Modulator kit (allows you to use your TV set as a monitor) ... \$8.95 postpaid.
□ 12" Video Monitor (10MHz bandwidth) ... \$139.95 plus \$3 P&I.*

□ Deluxe Steel Cabinet for the Explorer/85 ... \$49.95 plus \$3 P&I.*
□ Fan for cabinet ... \$15.00 plus \$1.50 P&I.*

ORDER A SPECIAL-PRICE EXPLORER/85 PAK — THERE'S ONE FOR EVERY NEED.

□ **Beginner Pak** (Save \$26.00) — You get Level A (Terminal Version) with Monitor Source Listing (\$25 value) AP-1, 5-amp. power supply, Intel 8085 Users Manual ... (Reg. \$199.95) SPECIAL \$169.95 plus \$4 P&I.*

□ **Experimenter Pak** (Save \$53.40) — You get Level A (Hex Keypad/Display Version) with Hex Keypad/Display, Intel 8085 User Manual, Level A Hex Monitor Source Listing, and AP-1, 5-amp. power supply ... (Reg. \$279.95) SPECIAL \$226.55 plus \$6 P&I.*

□ **Special Microsoft BASIC Pak** (Save \$103.00) — You get Levels A (Terminal Version), B (4k RAM), E, 8k Microsoft in ROM, Intel 8085 Users Manual, Level A Monitor Source Listing, and AP-1, 5-amp. power supply ... (Reg. \$439.70) SPECIAL \$336.70 plus \$6 P&I.*

□ **Add a Rom-Version Text Editor/Assembler** (Requires levels B and D or S100 Memory) ... \$99.95 plus \$2 P&I.*

Starter 8" Disk System — Includes Level A, B floppy disk controller, one CDC 8" disk-drive, two-drive cable, two S100 connectors, just add your own power supplies, cabinets and hardware ... □ (Reg. \$1065.00) SPECIAL \$999.95 plus \$13 P&I.* □ 32k Starter System, \$1045.95 plus \$13 P&I.* □ 48k Starter System, \$1095.95 plus \$13 P&I.* □ 64k Starter System, \$1145.95 plus \$13 P&I.* □ Add to any of above Explorer steel cabinet, AP-1, 5-amp. power supply, Level C with two S100 connectors, disk drive cabinet and power supply, two sub-D connectors for connecting your printer and terminal ... (Reg. \$225.95) SPECIAL \$199.95 plus \$13 P&I.*

□ **Complete 64k System** — Wired & Tested ... \$1650.00 plus \$26 P&I.*

□ **Special! Complete Business Software Pak** (Save \$625.00) — Includes CP/M 2.2 Microsoft BASIC, General Ledger, Accounts Receivable, Accounts Payable, Payroll Package ... (Reg. \$1325) SPECIAL \$699.95 postpaid.

*P&I stands for "postage & insurance." For Canadian orders, double this amount.

Continental Credit Card Buyers Outside Connecticut:


TO ORDER

Call Toll Free:

800-243-7428

To Order From Connecticut, or For Technical Assistance, Call (203) 354-9375

 CP/M is a reg. trademark of Digital Research



SEND ME THE ITEMS CHECKED ABOVE

Total Enclosed (Conn. Residents add sales tax) \$
Paid by:

□ Personal Check □ Cashier's Check/Money Order

□ VISA □ MASTER CARD (Bank No. _____)

Acct. No. _____ Exp. Date _____

Signature _____

Print Name _____

Address _____


City _____

State _____ Zip _____

ANNOUNCING TWO NEW TERMINALS

Smart • Fast • Graphics • Matching Modem and \$295 Printer

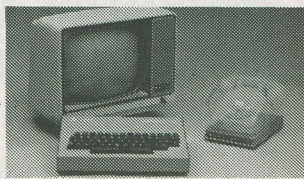Netronics announces a state of the art breakthrough in terminals, now at prices you can afford, you can go on-line with data bank and computer phone-line services. It's all yours: "electronic newspapers," educational services, Dow-Jones stock reports, games, recipes, personal computing with any level language, program exchanges, electronic bulletin boards, ... and more every day!!



Netronics offers two new terminals. Both feature a full 56 key/128 character typewriter-style keyboard, baud rates to 19.2 kilobaud, a rugged steel cabinet and power supply. The simplest one, FASTERM-64, is a 16 line by 64 or 32 character per line unit, with a serial printer port for making hard copy of all incoming data, and optional provisions for block and special character graphics. The "smart" version, SMARTERM-80, features either 24 line by 80 characters per line or 16 by 40 characters per line, it offers on-screen editing with page-at-a-time printing, 12,000 pixel graphics, line graphics, absolute cursor addressing, underlining, reverse video, one-half intensity and much more ... simply plug them into your computer or our phone modem and be on-line instantly. Use your TV set (RF modulator required) or our deluxe green-phosphor monitor pictured above. For hard copy just add our matched printer.

Price breakthrough!!! Own the FASTERM-64, a complete terminal kit, ready to plug in for just \$199.95 or order the SMARTERM-80 kit for just \$299.95, (both available wired and tested.) Be on-line with the million-dollar computers and data services today ... we even supply the necessary subscription forms.


More good news: All the components in our terminals are available separately (see coupon), so you buy only what you need!!!

FASTERM-64 ... DISPLAY FORMAT: 64 or 32 characters/line by 16 lines ... 96 displayable ASCII characters (upper & lower case) ... 8 baud rates: 150, 300, 600, 1200, 2400, 4800, 9600, 19, 200, (switch sel) ... LINE OUTPUT: RS232C or 20 ma current loop ... VIDEO OUTPUT: 1V P/P (EIA RS-170) ... CURSOR MODES: home/clear screen, erase to end of line, erase cursor line, cursor up & down, auto carriage return, line feed at end of line & auto scrolling ... REVERSE VIDEO ... BLINKING CURSOR ... PARITY: off, even or odd ... STOP BITS: 1, 1.5, 2 ... DATA BITS PER CHARACTER: 5, 6, 7 or 8 ... CHARACTER OUTPUT: 5 by 7 dot matrix in 2K ON BOARD RAM ... PRINTER OUTPUT: prints all incoming data ... 1K ON BOARD RAM ... 7 ON BOARD ROM ... CRYSTAL CONTROLLED ... COMPLETE WITH POWER SUPPLY

OPTIONAL GRAPHICS MODE: includes 34 Greek & math characters plus 30 special graphics characters ... ASCII ENCODED KEYBOARD: 56 key/128 characters.
SMARTERM-80 ... DISPLAY FORMAT: 80 characters by 24 lines or 40 characters by 16 lines 128 displayable ASCII characters (upper & lower case) 8 baud rates: 110, 300, 600, 1200, 2400, 4800, 9600, 19, 200 ... LINE OUTPUT: RS232C or 20 ma current loop ... VIDEO OUTPUT: 1V P/P (EIA RS-170) ... EDITING FEATURES: insert/delete line, insert/delete character, forward/back tab ... LINE OR PAGE TRANSMIT ... PAGE PRINT FUNCTION ... CURSOR POSITIONING: up, down, right, left, plus absolute cursor positioning with read back ... VISUAL ATTRIBUTES: underlining, blink, reverse video, half intensity, & blank ... GRAPHICS: 12,000 pixel resolution block plus line graphics ... ON-SCREEN PARITY INDICATOR ... PARITY: off, even or odd ... STOP BITS: 110 baud 2, all others 1 ... CHAR. OUTPUT: 7 by 11 character in a 9 by 12 block ... PRINTER OUTPUT ... 60 OR 50 Hz VERTICAL REFRESH ... BLINKING BLOCK CURSOR ... CRYSTAL CONTROLLED ... 2K ON BOARD RAM ... ASCII ENCODED KEYBOARD: 56 key/128 character ... 4K ON BOARD ROM ... COMPLETE WITH POWER SUPPLY

TELEPHONE MODEM 103 O/A ... FULL DUPLEX, FCC APPROVED ... DATA RATE: 300 baud ... INTERFACE: RS232C and TTY ... CONTROLS: talk/data switch (no need to connect and disconnect phone), originate/answer switch on rear panel ... NO POWER SUPPLY REQUIRED.

ASCII KEYBOARD ASCII-3 ... 56 KEY/128 CHARACTER ASCII ENCODED ... UPPER & LOWER CASE ... FULLY DEBOUNCED ... 2 KEY ROLL-OVER ... POS OR NEG LOGIC WITH POS STROBE ... REQUIRES +5 & -12V DC (SUPPLIED FROM VIDEO BOARDS)
PRINTER COMET I ... SERIAL I/O TO 9600 BAUD ... 80 CHARACTER COLUMN (132 COMPRESSED) ... 10" TRACTOR FEED ... UPPER/LOWER CASE ... INDUSTRY STANDARD RIBBONS ... 4 CHARACTER SIZES ... 9 BY 7 DOT MATRIX ... BI-DIRECTIONAL PRINTING

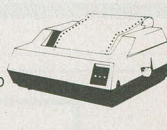

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Tech. Assist. Call (203) 354-9375

NETRONICS R&D LTD. Dept.

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

□ **COMPLETE FASTERM-64 TERMINAL** (includes FASTVID-64 video board ASCII-3 keyboard, steel cabinet and power supply) ... kit \$199.95 plus \$3 P&I ... wired & tested \$249.95 plus \$3 P&I ... graphics option: add \$19.95 to each of above

□ **COMPLETE SMARTERM-80 TERMINAL** (includes SMARTVID-80 video board, ASCII-3 keyboard, steel cabinet and power supply) ... kit \$299.95 plus \$3 P&I ... wired and tested \$369.95 plus \$3 P&I

□ **FASTVID-64 VIDEO BOARD** (requires +5 & -12V DC) ... kit \$99.95 plus \$3 P&I ... graphics option add \$19.95 ... wired & tested \$129.95 plus \$3 P&I ... graphics option add \$19.95

□ **SMARTVID-80 VIDEO BOARD** (requires +5 & +/-12V DC) ... kit \$199.95 plus \$3 P&I ... wired & tested \$249.95 plus \$3 P&I

□ **DELUXE STEEL TERMINAL CABINET** ... \$19.95 plus \$3 P&I

□ **ASCII-3 KEYBOARD** (requires +5 & -12VDC) ... kit \$69.95 plus \$3 P&I ... wired and tested \$89.95 plus \$3 P&I

□ **POWER SUPPLY** (powers ASCII-3 keyboard & video boards) ... kit only \$19.95 plus \$2 P&I

□ **ZENITH VIDEO MONITOR** (high resolution green phosphor) ... wired & tested \$149.95 plus \$6 P&I

□ **TELEPHONE MODEM MODEL 103 O/A** ... wired & tested \$189.95 plus \$3 P&I

□ **DOT MATRIX PRINTER Comet I** ... wired & tested \$299.95 plus \$10 P&I

□ **RF MODULATOR MOD RF-1** ... kit only \$8.95 plus \$1 P&I

□ **3FT-25 LEAD MODEM/TERMINAL OR PRINTER/TERMINAL CONNECTOR CABLE** ... \$14.95 ea plus \$2 P&I

For Canadian orders, double the postage. Conn. res. add sales tax.

Total Enclosed \$

□ Personal Check □ Cashier's Check/Money Order

□ VISA □ MasterCard (Bank No. _____)

Acct. No. _____ Exp. Date _____

Signature _____

Print Name _____

Address _____

City _____ State _____ Zip _____

28K Commodore VIC Personal Computer \$299 (60% more powerful than VIC-20)

FOR THE SPECIAL SALE PRICE of \$299.00, you get the Commodore VIC-20 computer, plus we add 60% more programming power. This powerful full sized extra featured computer includes the 6502 microprocessor (LIKE APPLE), 20,000 bytes ROM with a 16K extended microsoft LEVEL 11 BASIC, 8000 bytes user RAM, plug in expandable to 32K RAM, 66 key typewriter professional keyboard with graphic symbols on keys, 16 colors with command keys, sound and music, real time, upper/lower case, full screen editing cursor, floating point decimal and trig functions, has high resolution graphics, 512 displayable characters, test display is 23 lines, 22 characters, will accept TAPE-DISK-PLUG IN CARTRIDGES. We have great games and many other programs. It has low cost, direct plug in peripherals, does not require an expensive interface board for modems, printers or floppy disks, connects to any TV, includes AC adapter, RF modulator, switch box, self teaching instruction book, 90 day immediate replacement warranty! Comes in a beautiful console case for only \$299. (You can get a 41K COMMODORE VIC for \$379). We stock more VIC-20 programs than anyone! — WRITE FOR FREE CATALOG!

15 DAY FREE TRIAL Return within 15 days complete and undamaged for refund of purchase price.

DON'T MISS THIS FANTASTIC SALE!! Phone 312/382-5244 to order and get delivery in 2 to 7 days, or send a certified check, money order or personal check to **PROTECTO ENTERPRISES, BOX 550, BARRINGTON, ILLINOIS 60010**. We honor Visa and Master Charge, Ship C.O.D Add \$10.00 for shipping, handling and insurance. Illinois residents add 6% tax.

CIRCLE 38 ON FREE INFORMATION CARD

Someone with a weak heart could brush by it accidentally and suffer a fatal shock.

The letter reminded me of a guy who wired his garbage cans to raw AC "to keep the dogs out of them." That nut could have electrocuted someone.

Be smart. Don't let your knowledge of electronics overcome good sense. I don't know about the laws in Australia, but I suspect that there, as well as here, a guy could get himself in serious trouble by pulling a stunt like that.

Something for nothing

Seldom, if ever, does one get something for nothing. There is another scam going around that I'd like to warn you about; you should be on guard if it comes your way.

You know, of course, about the illegal chain letters that promise riches. It seems that someone has come up with a new version.


One of our readers from Welland, Ontario, Canada sent me a "membership form" from a "Book Club." Most of the chain letters that I've seen ask for money, but this one asks for books and magazines instead. Interestingly, almost half of the names/addresses on the list are from Central America (the rest are from the U.S.). The reader thinks that they got his name and address from a letter published in a magazine.

R-E

TOTAL CONVENIENCE

**Model 324
THE ELECTRONIC
WORK CENTER**

**SUGGESTED
RETAIL PRICE
\$49.95**

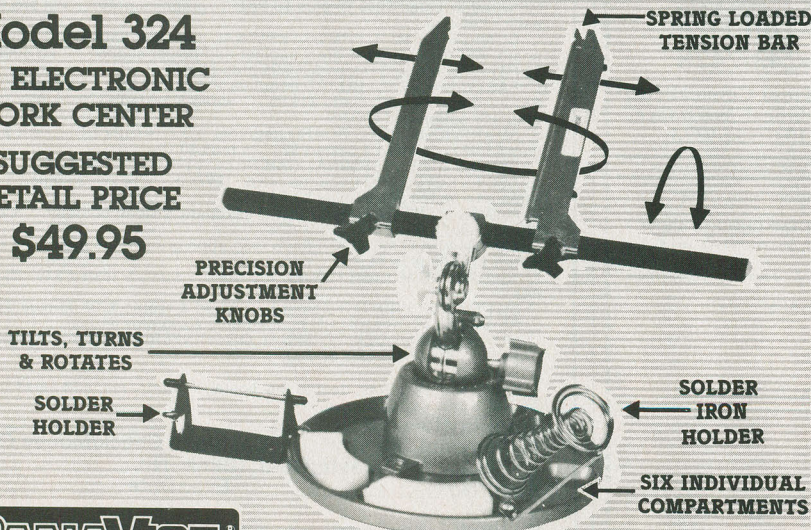

PANAVISE

Contact your local dealer today.


PANAVISE PRODUCTS, INC. 2850 E. 29th St., Long Beach, Ca. (213) 595-7621

CIRCLE 39 ON FREE INFORMATION CARD

**Aaron-Gavin
Kits**




LED meter

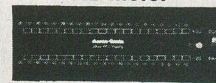

**EQUALIZERS PRICED
FROM \$119. to \$690.
LED METERS PRICES
\$48. to \$219.**

A Unique MIXER for DJ's — Studio's — Broadcaster's

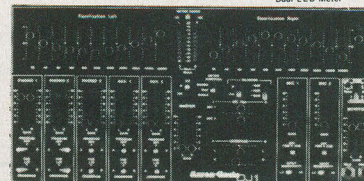Two MIC Inputs
Two AUX channels
3 Turnable Inputs
Talkover Switch
Crossfade
ANY Channel
Beat Match
Subsonic Filters
Eleven Band Stereo
EQUALIZER
Headphones
Monitor Switchable
Dual LED Meter




Call or write for full product information, and pricing to:

AARON-GAVIN
123 South McClay Street, Unit F,
Santa Ana, CA 92701, (714) 957-8710

**ADVANCE IS PROUD
TO INTRODUCE
The  HITACHI Line
of High Quality Oscilloscopes
All Hitachi Instruments
Are Backed by
A Two-Year Warranty**

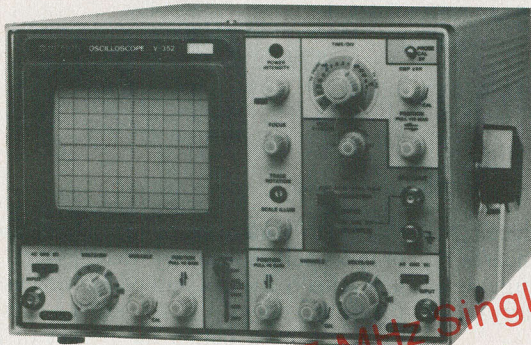**V-202 & V352
20MHz & 35MHz DUAL TRACE
OSCILLOSCOPES**



1. Square CRT with internal graticule (illuminated scale)
2. High-accuracy voltage axis and time axis set at $\pm 3\%$ (certified at 10° to 35°C)
3. High-sensitivity 1mV/div
4. Low drift
5. Dynamic range 8 div.
6. TV sync-separator circuit
7. Built-in signal delay line (V-352)
8. X-Y operation
9. Sweep-time magnifier (10 times)
10. Trace rotation system
11. Fine-adjusting, click-positioning function

**ADVANCE
ELECTRONICS** 


**THE TEST EQUIPMENT
SPECIALISTS**

**TOLL FREE HOT LINE
800-223-0474**



54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

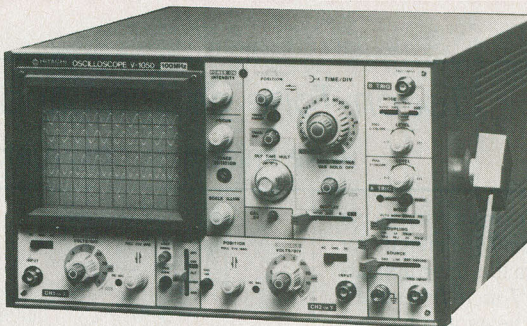**AT LAST A 100MHz OSCILLOSCOPE
WORTH WAITING FOR
WITH NO WAITING**



**CALL FOR
INTRODUCTORY
OFFER**

**HITACHI
100MHz
OSCILLOSCOPE
MODEL V-1050**

- 20kV CRT supply
- Large, bright 8 x 10 cm screen
- Four-trace operation (Ch1, Ch2, A trigger, B trigger)
- High sensitivity 500 $\mu\text{V}/\text{div}$ (5MHz)
- High accuracy $\pm 2\%$ ($+10^\circ\text{C}$ to 35°C)
- Alternate timebase operation
- Full TV triggering

**IN STOCK FOR
IMMEDIATE DELIVERY**

CRT.

Type
Hitachi 150BNB31 rectangular mesh type tube with 20kV acceleration potential and metal backed phosphor.


VERTICAL DEFLECTION (2 Identical Channels)

Bandwidth and Rise Time
DC to at least 100MHz and rise time 3.5ns or less. DC to at least 5MHz and rise time 70ns or less at 10 X magnification. Lower 3db point. AC coupling 10Hz or less. 10x probe: 1Hz or less.

HORIZONTAL DEFLECTION

Time Base A
20ns/div. to 0.5s/div. in 23 calibrated steps, 1-2-5 sequence. Uncalibrated continuous control between steps 1: < 2.5
Time Base B
20ns/div. to 50ms/div. in 20 calibrated steps 1-2-5 sequence. 10x mag extends fastest sweep rate to 2ns/div.
Calibrated Sweep Delay
Continuous calibrated control between 0.5 and 10x time base A setting.

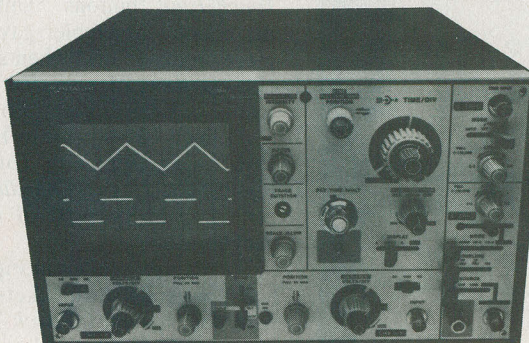**V-550B 50MHz, DUAL TRACE DELAYED SWEEP
PORTABLE OSCILLOSCOPE**



Delayed sweep
permits 1,000 X
Magnification

Variable Hold-off
Circuitry Facilitates
Pulse Measurement

- Large, Bright 8 x 10cm Screen
- High Sensitivity 1mv/div (10MHz)
- 5 ns/div Sweep Rate
- 3rd Channel Display (Trigger View)
- Variable Trigger Hold-off
- Full TV Triggering
- Single Sweep
- Automatic Focus Correction

COMMUNICATIONS CORNER

Touch-Tone devices and FM adjustments

HERB FRIEDMAN, COMMUNICATIONS EDITOR

AS MORE AND MORE COMMUNICATIONS systems requiring *Touch-Tone* signals for access and operation made their appearance, I found that the *Touch-Tone* pad I had purchased several years ago had become a constant companion.

The pad was purchased from a **Radio-Electronics** advertiser and was either standard Bell System "surplus," or salvage from a *Touch-Tone* phone. I installed it in a matching plastic case, for which I paid a couple of dollars (it's now selling for \$10-\$15), added a battery for power and a set of output-signal clip leads, and I carried it in my attache case or the glove compartment of my car.

If I needed to access my 2-meter repeater's autopatch I plugged the pad into a small jack I had installed on my 2-meter mobile rig. (That was before I got Heathkit's combination mobile mike and *Touch-Tone* pad.) To enter information into my computer from a remote point I clipped the leads from the pad across the phone line if I couldn't locate a *Touch-Tone* phone during my travels.

Like just about all other Bell System equipment, the gadget has never failed. The only problem is that its frequencies

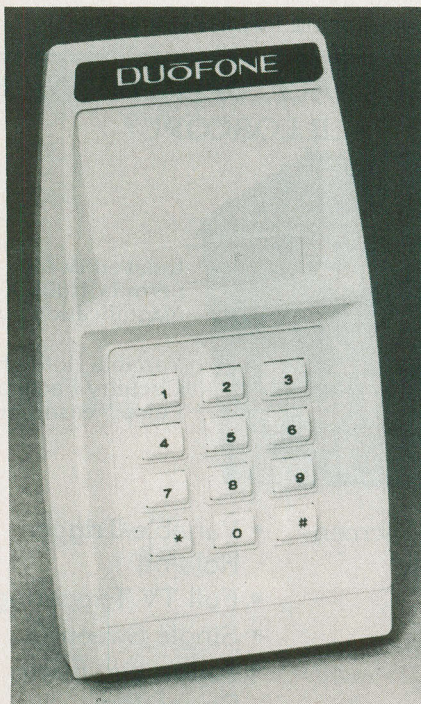


FIG. 1

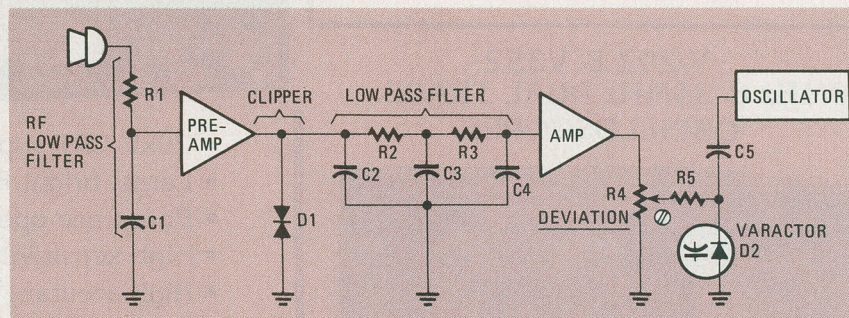


FIG. 2

are determined by pot coils (inductors) that are huge by contemporary standards. Until recently I was always lugging around some sort of case just to carry the pad.

Though the earliest users of portable *Touch-Tone* pads were radio amateurs and other hobbyists, with the tremendous expansion in communications circuits and computers requiring *Touch-Tone* signals for control or data, there has been created a need for a truly portable *Touch-Tone* generator that can be easily coupled to a standard telephone. One of the earliest—and still popular—devices was the *Soft Touch*. That was a gizmo the user substituted for the telephone transmitter (mouthpiece) by unscrewing the handset's transmitter and temporarily replacing it with the device, which consists of a small microphone surrounded by 12 *Touch-Tone* "buttons." Unfortunately, if the phone's assembler gave the mouthpiece an extra twist when assembling it, nothing short of a special strap wrench would be able to get it loose.

A much easier way to handle "portable" signaling with *Touch-Tones* is Radio-Shack's *Mini Tonedialer*, which is certain to be the first of many similar gadgets.

The device, shown in Fig. 1, is a battery-powered, shirt-pocket-sized device with the standard *Touch-Tone* keypad arrangement on one side and a small speaker on the other. To transmit *Touch-Tones*, you simply place the side with the speaker against a telephone's transmitter (or a microphone), and press the key corresponding to the desired number (0-9) or symbol (* or #). The speaker reproduces the corresponding tones for as long as the key is depressed.

Unlike my old authentic telephone pad

that had to be carried around in a briefcase or in a small camera bag, Radio Shack's unit actually fits in a shirt pocket because it measures only $2.4 \times 4.4 \times 0.7$ inches. (You can even button the pocket of a Western-style shirt with it inside.) Its overall weight, including batteries, is about 1.5 ounces—less than that of some pocket pens.

What makes all that possible, of course, is the integrated circuit. The entire dialer consists of a single IC that generates the tones; a miniature crystal for the time-base reference; a transistor "output" stage that drives a 1.6-inch speaker; three resistors, and a capacitor. Except for the speaker, everything—including the batteries—is installed on a printed-circuit board whose foils also serve as the switch contacts. The low parts-count is the reason the whole thing costs only about \$35.

Setting FM levels

Lately, it seems that there's a lot of commercial VHF and UHF FM gear floating around the surplus dealers and flea markets. The stuff is obviously good because I've worked on many that were converted to the amateur frequencies. Often, though, I've found that the hobbyists get lost in the modulator.


Actually, frequency-modulation systems are rather simple: A typical block diagram is shown in Fig. 2. The output from the microphone is usually fed to the preamplifier through an R-C network (R1/C1) that serves as a low-pass filter to keep RF that might be picked up by the microphone cable out of the preamplifier. To equalize the loud and soft voice levels, the preamp's output is clipped by diode(s) D1. The clipper simply sets a ceiling on

continued on page 110

"Mobile antenna mounting and cable routing on today's cars are a nightmare"




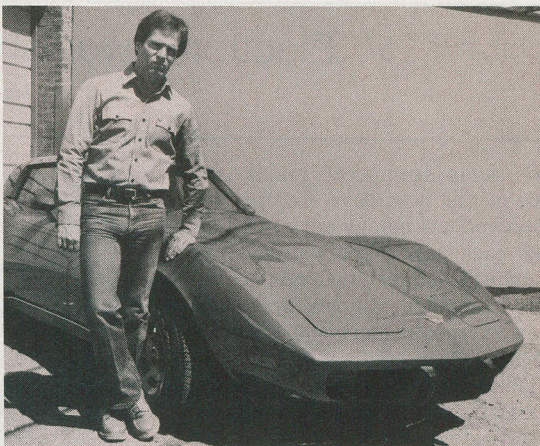
"We just can't find a high performance antenna that doesn't need a ground plane"




Avanti. The on-glass, halfwave, 15-minute solution from the antenna specialists co.

Model AV-240 Moon Phantom™ CB antenna, ideal for vans, motorcycles... even apartment windows!

- **Co-inductive coupling** establishes highly tuned circuit through glass or any non-conductive material up to $\frac{3}{4}$ " thick, with no measurable signal loss.
- **No ground plane:** full electrical halfwave design provides omnidirectional performance equal to practical $\frac{5}{8}$ wave installations.
- **New DUO-BOND mounting system** for firm, resilient, waterproof bonding in minutes—yet removable without damage to car or antenna.
- **No holes to drill, no damage to vehicle**... easy, fast cable routing.

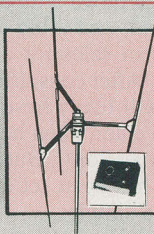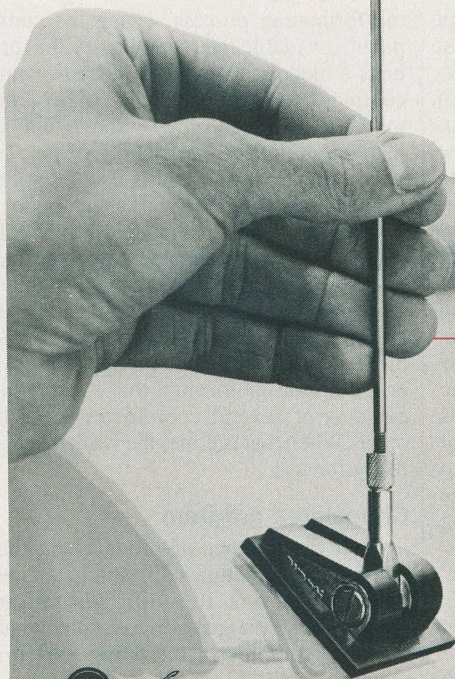

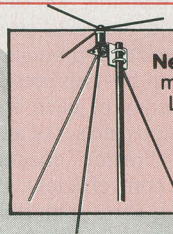MS-119 Super Scanner™
Search with 5.75 dB gain... instantly zero in with 8.75 dB electronic beam—no rotator.



New MON-64 DISCAN™
monitor antenna. Lightweight, economical. Excellent performance, all bands.

the antenna specialists co.

the antenna specialists co.
a member of The Allen Group Inc.
12435 Euclid Ave., Cleveland, OH 44106
Canada: A. C. Simmonds & Sons, Ltd.



® "Stripes of Quality"

we design solutions.



Support your local REACT Team... We do!

CIRCLE 20 ON FREE INFORMATION CARD

SEPTEMBER 1982

79

COMPUTER CORNER

Electronic worksheets for your computer

LES SPINDLE*

THE BUSINESS SOFTWARE FIELD IS A dynamic market nowadays. Competition and improved technology are combining to make each new product just a little more sophisticated than the one that preceded it. Computer programs now serve not only as proofreaders and grammarians, but also as program writers, teachers of languages and operating systems, and sophisticated accountants. But no single software development has had the impact of VisiCorp's (formerly Personal Software) 1980 introduction of *VisiCalc*.

Dozens of current software releases are fashioned after the simple, but revolutionary, concept that *VisiCalc* pioneered—the micro as an electronic worksheet for financial planning.

The “Visiclones” (as they are sometimes referred to) enable the user to format a “worksheet” of figures on the screen, then modify those figures in any number of different ways and see the results of the modifications.

Mathematical relationships between any of the rows and/or columns can be defined. Suppose, for instance, that you want the bottom row to be the sum of all the rows above it. That can be accomplished with one simple command. Other mathematical calculations—log and trig functions, percentages, etc.—can easily be accomplished in the same manner.

If one item on the worksheet is changed, every other item whose value depends on that item is automatically changed at the same time. It is possible to add new rows and columns or to change the order of existing ones. Meanwhile, the items whose values depend on the new setups are also automatically changed.

The program is an ideal tool for projecting budgets, planning expenditures, and charting various business strategies. Printouts of the various combinations can be made, for a step-by-step presentation of the pros and cons of each strategy. Presenting the various phases of an operation to a board of directors' meeting, for instance, can be both efficient and impressive. But even more important than that is the time saved by the user as he works out his options in the planning process.

For example, suppose a retail sales manager wants to make an intelligent guess as to sales trends over a yearly



FIG. 1

period. He devices a format consisting of several variables, such as interest rates, his best-selling products, his slow-moving merchandise, the number of salesmen in the field, and the previous year's sales. To further enhance the credibility of the outcome, he takes into account the fact that in his line, winter is the heaviest selling season. With his format completed, he enters all the necessary data, then begins to examine the results.

His analysis will take much less time than if he had sat down with adding machine, scratchpad, and a big eraser. His report will project sales for each of the next 18 months. After consulting with his associates, he will likely have dozens of data changes to enter when he returns to re-work the projections. But, once the initial program has been set up, making those changes is simple.

How they're used

How does a user format the worksheet to fit his particular application? Most of the programs are well-documented with simple commands and self-prompting menus that lead him step-by-step through

the formatting process. Using his computer's available internal memory, he formats a model consisting of the rows and columns that he will need. The size of the model is restricted only by the available memory. Filing and retrieving of data is done using disks, so that is usually not a factor in the size of the worksheet model.

Once the model is visible on the CRT screen, the user can decide how to define each row and column on the “blank” worksheet. Each coordinate location is assigned either an alphanumeric comment, a label (such as a row description), or a constant or formula that relates the contents of several coordinates to each other. When that is done, the worksheet is ready for use.

Choosing a program

With the number of products on the market, it is sometimes difficult to decide on the best one for your particular application. You are restricted somewhat by your computer's operating system, memory capacity, and microprocessor. Some versions are configured for a particular computer and its specific operat-

*Managing Editor, *Interface Age* magazine

How to get an 8-channel scope for \$349.50


Add our Model 8001 8-channel multiplexer to your present oscilloscope: It's the perfect way to view and compare signals occurring at different points in a circuit or system—in their real time and amplitude relationships. As well as one of the best bargains in test equipment today.

Now you can have multi-channel capability wherever and whenever you need it. In the lab. On the production line. In quality control. And service—on the bench or in the field. All for just \$349.50*!

Just connect its eight 1-megOhm inputs to your circuit via the front-panel BNC connectors. It's flat to 12MHz (-3dB at 20MHz) and will handle digital and analog signals up to $\pm 5\text{V}$ (10V p-p) in any combination. There's plenty of flexibility, too. Thanks to a variety of switch-select-

able display/output combinations, multiplexer rates and operating modes that enable you to view each channel individually or all, simultaneously—with pushbutton calibration. And a vertical master gain control that's continuously variable from 0-75mV/cm/channel.

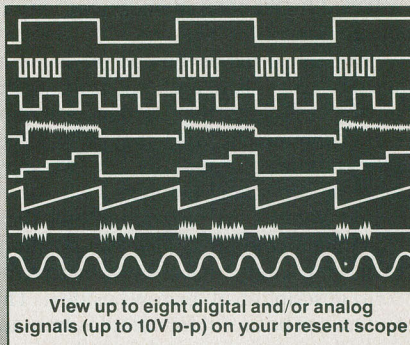The trigger input, with switch-selectable polarity, is assigned to



channel one with continuously variable trigger level ($\pm 5\text{V}$ range). And you can choose a switch-selectable 0.1 or 1.0 usec TTL-level pulse at the trigger output.

It's simple: When you consider how much time our 8001 multiplexer can save you... how much versatility it offers... and how little it costs, there's only one thing you'll want to know. How quickly you can get your hands on one. Which we'll be glad to tell you when you dial the toll-free number below.

GLOBAL SPECIALTIES

70 Fulton Terr., New Haven, CT 06509
(203) 624-3103, TWX 710-465-1227

*Suggested U.S. resale. Prices, specifications subject to change without notice.

Call Toll-Free for Details 1-800-243-6077


During Business Hours, 9AM to 5PM Eastern Time

OTHER OFFICES: San Francisco (415) 648-0611, TWX 910-372-7992,
Europe: Phone Saffron-Walden 0799-21682, TLX 817477, Canada: Len Finkler Ltd., Downsview, Ontario.

CIRCLE 11 ON FREE INFORMATION CARD

WE TAKE YOU BY THE HAND!

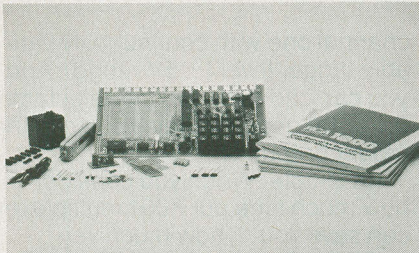You'll learn all about computers: how to build, program, service, even play TV games—without knowing the first thing about it!



The New ELF II "Beginners" Package

Your own expandable micro-computer kit, 5 diagnostic analyzers plus circuit, programming, diagnostic manuals, even games you can play on TV. All only \$139.95.

Even if you don't know bits from bytes, now it's easy and inexpensive to build your own micro-computer, learn how it works, program it, service it—even play games with it on your TV! It's here in the New ELF II "Beginners" Package, only from Netronics. Only \$139.95. Here's the package: 1. your own micro-computer, the famous ELF II (featuring the RCA 1802 CMOS microprocessor) in kit form with step-by-step instructions on how to build it. Diagnostic Analyzers including 2. your own Logic Probe, 3. Pulse Catcher, 4. 8 bit Test Register, 5. Logic Analyzer, 6. Gate Arrays, 7. Non-Technical Manuals on how to use analyzers, how to get into the guts of the computer, what makes it tick, how to service it. 8. Sample Programs that teach you machine language programming plus how to correct or "debug" any programming mistakes. 9. TV games you can play. If your TV set has no video input, an optional converter (RF Modulator), is available. Then, once you've got this "Beginners" Package under your belt, keep on expanding your ELF II with additions like the Typewriter Key Board, added RAM, Full Basic Interpreter, Electric Mouth Talking Board, Color/Music, A/D-D/A Boards for Robot Controls and much, much more. We'll take you by the hand with the New ELF II "Beginners" Package. Only \$139.95. Mail or phone in your order today and begin.

Specifications: ELF II "Beginners" Package
The computer features an RCA CMOS 1802 8 bit microprocessor addressable to 64K bytes with DMA, interrupt, 18 Registers, ALU, 256 byte RAM expandable to 64K bytes. Professional-Hex keyboard, fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion BUS (less connectors), stable crystal clock for timing purposes and a double-sided, plated through PC Board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with the logic and support circuitry you need to learn every one of the RCA 1802's capabilities. The diagnostic analyzers aid in understanding and trouble shooting your ELF II, as well as other computer and microprocessor products.

Continental U.S.A. Credit Card Buyers Outside Connecticut
CALL TOLL FREE 800-243-7428
To Order From Connecticut or For Technical Assistance, Etc.,
Call (203) 354-9375

NETRONICS R&D LTD. [Dept. RE 32]
333 Litchfield Road, New Milford, CT 06776
Please send the items checked below:

☐ ELF II "Beginners" Kit \$139.95
☐ RF Modulator \$ 8.95

Plus \$3.00 for postage, handling and insurance
(\$6.00 Canada)

Connecticut Residents add sales tax

Total Enclosed \$

☐ Personal Check ☐ Cashier's Check/Money Order
☐ Visa ☐ Master Charge (Bank No. _____)

Acct. No. _____
Signature _____ Exp. Date _____

Print Name _____
Address _____

City _____
State _____ Zip _____

ing system, such as TRSDOS for the TRS-80 or CDOS for Cromemco. A number of new products, though, are CP/M-based, and can be used on any computer that can run the CP/M disk-operating system. In most cases, however, you should be able to find several options for your setup.

Once you've found the products, you can examine the specific features offered by each program to determine which is best suited for your applications. Following are some of the features to keep in mind as you make your choice. Keep a checklist handy as you shop.

First, determine the size of the matrix. Find out how many rows and columns are possible and analyze your needs to see whether their capacity is sufficient for your applications. Be aware that it is seldom possible to use all the rows and columns at the same time since both are affected by the total memory-capacity of the computer.

Investigate the arithmetic precision of the program. There are limitations on the number of digits that certain programs can accommodate, and they may affect you if your calculations involve very large or very small numbers.

See whether the program allows for a "comment column." That is a position, of varying length, that allows you to write some description of the row beside it. The feature can be useful for complex transactions that require more description.

Does the program include graphics capabilities? Bar charts and the like are sometimes desirable, especially for meetings and formal presentations.

Is split-screen capability available? Some of the more advanced programs allow it, and it can be a tremendous asset in comparing the results of related plans.

Can the program interface with other programs? If data from word-processing, general ledger, payroll, or other programs at work in your system can be used directly by your worksheet, or vice-versa, the door is opened for a wealth of time-saving features. Suppose you are producing a written sales-report and would like to integrate a worksheet as part of the presentation. Without word-processor-interfacing capabilities, you would have to re-enter the entire sheet in order to integrate it into the report.

For clarity of reading, the ability to line up figures in a row correctly is crucial. For instance, if the decimal points in the numbers 596.83 and 9344.7 were not aligned vertically, it would be hard to distinguish which were the fractional elements simply by glancing at the column.

Does the program allow for partial printouts? Can you print one row or column, or a section of a report without taking the time to run the entire program?


Is it possible to jump to one point in the model instantaneously from another? If you are in column C, row 7, can you

continued on page 108

The FEATURES you want in a

20 MHz DUAL TRACE OSCILLOSCOPE

DC-20 MHz dual trace @ 5mV to 10V/Div on 11 ranges. Operating modes Ch 1, Ch 2, dual, add, sub., chop, X-Y. Sweep Time 0.5 μ sec to 0.5 sec/Div on 19 ranges plus X5 mag. 5 trigger selections; 3 filters; auto free run; TV-V/H. 5 1/2" rect. CRT with internal graticule and 2kV acceleration. TTL intensity modulation. Switching regulator power supply. Comes complete with two 10:1 hook-on probes. Detachable 3 conductor AC cord, spare fuses, and full one year ltd. warranty.

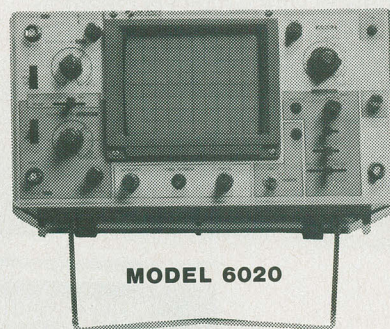


At PRICES you can AFFORD!

	1-9 Ea.	10 up Ea.
MS-6020 Described	\$649.00	\$585.00
MS-6021 with Delay Sweep	699.00	630.00
MS-6120 with Built-in 3 1/2 DMM	765.00	690.00

Available at selected distributors or write/phone:

NORTH AMERICAN 

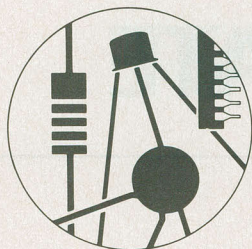
1126 Cornell Avenue
Cherry Hill, NJ 08002
Tel. (609) 488-1060



Looking for new ideas,
projects, and
money-saving tips?

The **ELECTRONICS BOOK CLUB**
has hundreds of titles
most-wanted by hobbyists
and experimenters!

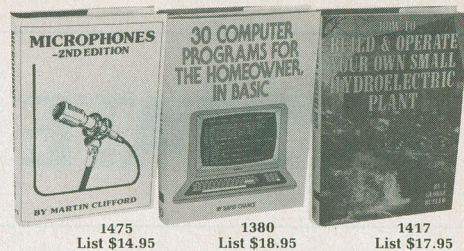
Select 6 info-packed volumes
for only **\$2.95** (total value up to \$115.70)



1475
List \$14.95

1380
List \$18.95


1417
List \$17.95

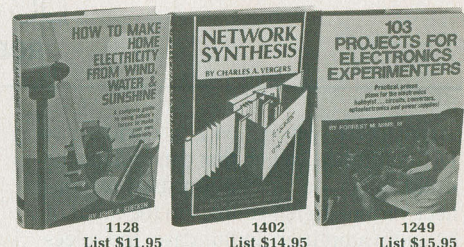


1128
List \$11.95

1402
List \$14.95

1249
List \$15.95

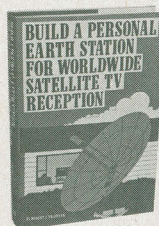


1409
List \$15.95

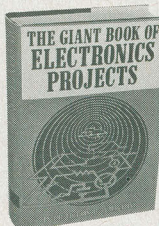


1367
List \$19.95




1306
List \$15.95

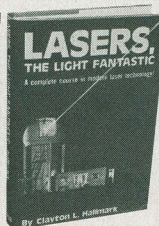


1108
List \$13.95

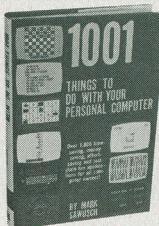


1160
List \$13.95

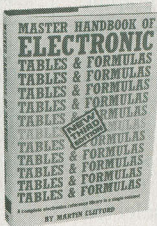


1225
List \$9.95

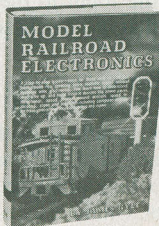

926
List \$8.95

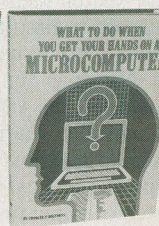


1397
List \$16.95

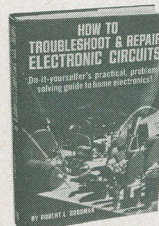


1218
List \$16.95




829
List \$11.95

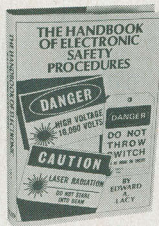

1420
List \$17.95

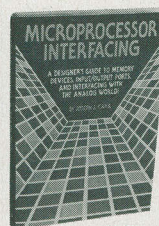

1396
List \$13.95

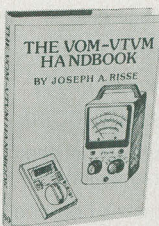


1390
List \$14.95




1316
List \$16.95




1406
List \$17.95

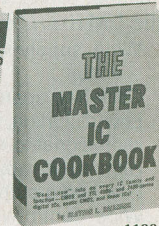

1199
List \$17.95

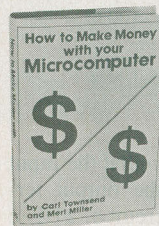


335
List \$14.95

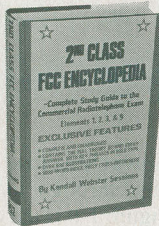


652
List \$12.95



1169
List \$16.95

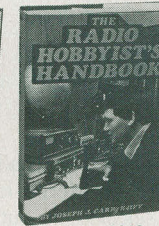


1346
List \$19.95

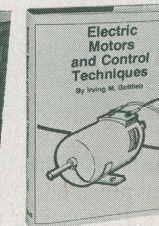

1465
List \$15.95



1337
List \$9.95

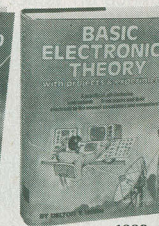

1338
List \$19.95



1296
List \$18.95

Join the Electronics Book Club! Get 6 Best
Selling Books for only **\$2.95** (VALUES TO \$115.70)

Seven reasons why you belong
in the Electronics Book Club

- You save money.** Save up to 75% on books and ideas sure to increase your know-how. You'll save even more because you'll be able to perform many tasks without calling in outside help.
- Your satisfaction guaranteed.** Any book you buy is returnable within 10 days without obligation.
- You receive news of new books and ideas.** About 13 times a year, you will get a Club News Bulletin with current book selections and bonus offers—dozens of up-to-the-minute titles you can pick from, each with exciting new ideas.
- You receive books automatically.** You will receive automatically a new book selected by the Editorial Board as a Main Selection. But, you can choose another book or no book at all by mailing the business reply form contained in each News Bulletin.
- You get special bonuses.** The club has special sales and added-value promotions for members to increase your library of knowledge. And, after fulfilling your membership obligation, you will receive a dividend certificate with each book purchased to qualify for even greater discounts.
- You'll have a library of exceptional quality.** Each Electronics volume is a full-length publisher's edition, filled with useful, up-to-the-minute information.
- You'll gain practical knowledge and confidence.** EBC will add to your practical skills about jobs that you face every day. All books contain easy-to-understand language that will add to your confidence in completing almost any task.



ELECTRONICS BOOK CLUB
Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below. I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

335 652 829 926 1108 1128 1160
1169 1199 1218 1225 1249 1296 1306 1316
1337 1338 1346 1367 1380 1390 1396
1397 1402 1406 1409 1417 1420 1465 1475

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(Valid for new members only. Foreign and Canada add 20%. Orders outside U.S. or Canada must be prepaid with international money orders in U.S. dollars.)
This order subject to acceptance by Electronics Book Club RE-982

CIRCLE 18 ON FREE INFORMATION CARD

SEPTEMBER 1982

83

STATE OF SOLID STATE

DC voltage-controlled switches

ROBERT F. SCOTT, SEMICONDUCTOR EDITOR

THIS MONTH WE'LL TAKE A LOOK AT A DC-controlled switch that can replace the usual rotary or pushbutton used to connect various signal sources to the input of an audio amplifier. In this case, the selector switch feeds the input to the graphic equalizer circuit that we discussed in the June 1982 issue.

National Semiconductor has just announced the LM1037 and LM1038 DC Controlled Audio Switches. Both are designed to allow any one of four stereo-input sources to be connected to the stereo-output lines. Channels are selected by applying a DC voltage level to the channel-select control pins. Features of the LM1037/38 switches are:

- Wide supply-voltage range (5 to 30 volts)
- Click-free operation
- Low distortion, 0.04% typical
- High signal-to-noise ratio
- High audio-input impedance
- Low audio-output impedance
- Wide control-voltage range (2 to 50 volts)
- High input-impedance on select pin

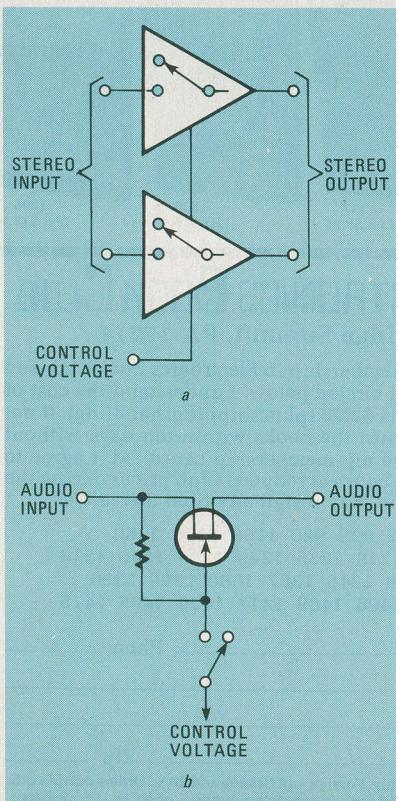


FIG. 1

TABLE 1					
Parameter	Min	Typ	Max	Units	Conditions
Supply voltage	5	12	30	volts	
Supply current (LM1037)		7		mA	$V_{\text{supply}} = 12$
Supply current (LM1037)		10		mA	$V_{\text{supply}} = 30$
Supply current (LM1038)		14		mA	$V_{\text{supply}} = 12$
Supply current (LM1038)		20		mA	$V_{\text{supply}} = 30$
Voltage gain	-0.2	0		dB	
Signal handling			3.2	volts _{rms}	$V_{\text{supply}} = 12$
Distortion (THD)		0.04	0.1	percent	1V _{rms} input @ 1 kHz
S/N Ratio (CCIR)		-100		dB	1V _{rms} input @ 1 kHz
Crosstalk between stereo channels	-80	-100		dB	1V _{rms} @ 1 kHz
Crosstalk between connected and unconnected channels	-80	-100		dB	1V _{rms} @ 1 kHz
Relative output in muted state	-80	-90		dB	1V _{rms} @ 1 kHz

The LM1037 has four control or channel-select pins; one for each stereo-input source. If no channel is selected, the outputs are muted and clamped to the DC output level.

The LM1038 is designed so that channels can be selected by BCD input pulses. Two input pins feed clock-enabled latches so that the BCD pulses can be strobed from a bus. Or, the clock-input pin can be permanently enabled and the channels selected by DC voltage levels. A separate pin allows the output to be muted, via either a pulse or a DC level.

To date, only preliminary specifications (Table 1) on the LM1037/38 have been released, so we don't have complete details on the structure of the semiconductor device used as the switch elements; but I'll bet that the switch is some form of FET. In similar analog switches from other manufacturers, JFET's, MOSFET's and CMOS (N-channel and P-channel FET's in parallel) have been used as gates or switches. Figure 1-a is a functional diagram of a stereo-audio switch. When the control voltage is ap-

plied, the switches close so that the input signals pass through to the output terminals. Figure 1-b is the circuit of a basic analog switch using a JFET as the switch element.

Figure 2 is the functional block diagram of the LM1037. The channel-selection details are outlined in Table 2 (See page 86).

Emitter and detector product guide

The *Infrared/Photodetector Product Guide* lists a line of GaAs IR emitting diodes and photodiodes, phototransistors, and photovoltaic cells. The IR emitters develop a wavelength of either 820 or 950 nm (nanometers) depending on the device. Detectors can be selected with maximum sensitivity specified at wavelengths ranging from 555 to 950 nm. The guide includes dimensioned outline drawings.—**Litronix**, 19000 Homestead Road, Cupertino, CA 59014.

Unique monolithic active filter

National Semiconductor's MF10 is the first monolithic active filter that does not

SWD-1 VIDEO CONVERTER

FOR CABLE TV



The SWD-1 Video Converter is utilized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms. 117VAC.

SWD-1 Video Converter Kit \$69.95

VTR ACCESSORIES

SIMPLE SIMON VIDEO STABILIZER



Simple Simon Video Stabilizer, Model VS-125, eliminates the vertical roll and jitter from "copy guard" video tapes when playing through large screen projectors or on another VTR. Simple to use, just adjust

the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments. Includes 12V power supply.

VS-125 Video Stabilizer, wired \$54.95

SIMPLE SIMON VIDEO SWITCHING BOX



The Affordable Video Control Center

Excellent in isolation and no loss routing system. Simple Simons VSB-300 Video Switching Box enables you to bring a variety of video components together for easy viewing/dubbing. Also you gain the ability to record one channel while viewing another. Unit includes two F-type quick connector ended cables.

VSB-300 Video Switching Box, wired \$19.95

UHF ANTENNAS and ACCESSORIES

MDS-AMATEUR-ETV 32 ELEMENT YAGI ANTENNA



- Not A Kit
- 1.9-2.5 GHz
- 38 1/2" Long
- 23dB Average Gain
- Commercial Grade
- Die Cast Waterproof Housing with 4 1/4" x 2 1/2" Area for Electronics
- Includes P.C. Probe, F-61 Connector and Mounting Hardware

MAE-2 32 Element YAGI Antenna \$23.95

Kato Sons' Down Converter Kit ★1.9 - 2.5GHz★

Designed for Simple Simon by former Japanese CQ Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antenna housing. Requires 1 hour assembly. IC and capacitors pre-soldered.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit \$34.95

Kato Sons' Regulated Variable DC Power Supply

For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.

Model KSPS-1A Assembled Power Supply \$23.95


SPECIAL INTRODUCTORY SAVINGS

ORDER ALL THREE ITEMS

MAE-2, KSDC-KIT and KSPS-1A for Only. **\$74.95**

Regular price if ordered separately \$82.85 — CO-AX CABLES ARE NOT INCLUDED —

ZYZZX VHF-UHF Wideband Antenna Amplifier

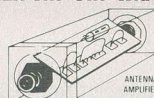

Revolutionary New HYBRID IC Broadband Amplifiers


50 MHz - 900 MHz

Model ALL-1 12dB Gain
Model ALL-2 35dB Gain

These units are not available anywhere else in the world. Each unit will serve many purposes and is available in Kit or Assembled form. Ideal for outdoor or indoor use. I/O impedance is 75 ohms. Amplifiers include separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors to tune or adjust.

ALL-1 Complete kit w/ power supply \$24.95 ALL-1 Wired/Tested w/ pwr supply \$34.95
ALL-2 Complete kit w/ power supply 34.95 ALL-2 Wired/Tested w/ pwr supply 44.95

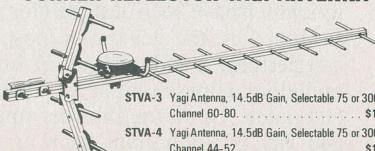Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80. \$19.95

STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52. \$19.95

RG-59/U 75 ohm Low Loss Coax Cable. \$.12p/ft. F-59 Coax Connector. \$.39 ea.
MT-1 Special UHF 75-300 ohm Matching Transformer. \$1.45 ea.

Switch to Bambi!™

Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.


The Bambi Electronic Video Switch is an electronic switching network which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ... not being able to use more than one function at a time.

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Wired


\$129.95

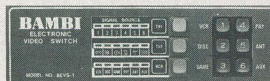

Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without referring to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.



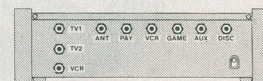Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually shielded for 65dB min. isolation).



Bambi's Specifications:

- Input/Output Impedance 75 ohm
- Signal Loss 3dB ±1dB
- Noise 4dB ±1dB
- Input Return Loss 12dB min.
- Isolation 65dB min.
- Power Req. 117VAC 60 Hz, 2W
- Dimensions 10 1/4" W x 6 1/4" D x 3 1/4" H
- Weight 4 1/2 lbs


7+11 SWD PARTS KITS

MITSUMI VARACTOR UHF TUNER

Model UES-A56F

\$24.95

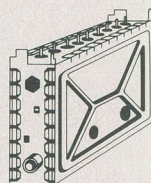Freq. Range UHF470 - 889MHz
Antenna Input 75 ohms
Channels 14-83 Output Channel 3



KIT NO	PART NO	DESCRIPTION	PRICE
1	VT1-SW	Varactor UHF Tuner, Model UES-A56F	\$24.95
2	CB1-SW	Printed Circuit Board, Pre-Drilled	18.95
3	TP7-SW	P.C.B. Potentiometers, 1-20K, 1-1K, and 5-10K ohms, 7-pieces	5.95
4	FR35-SW	Resistor Kit, 1/4 Watt, 5% Carbon Film, 32-pieces	4.95
5	PT1-SW	Power Transformer, PRI-117VAC, SEC-24VAC, 250ma	6.95
6	PP2-SW	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT w/Switch	5.95
7	SS14-SW	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Heat Sink 1-piece	29.95
8	CE9-SW	Electrolytic Capacitor Kit, 9-pieces	5.95
9	CC33-SW	Ceramic Disk Capacitor Kit, 50 W.V., 33-pieces	7.95
10	CT-SW	Variable Ceramic Trimmer Capacitor Kit, 5-65pfd, 6-pieces	5.95
11	L4-SW	Coil Kit, 18mhs 2-pieces, 22µhs 1-piece (prewound inductors) and 1 T37-12 Ferrite Toroid Core with 3 ft. of #28 wire	5.00
12	ICS-SW	I.C. Sockets, Tin inlay, 8-pin 5-pieces and 14-pin 2-pieces	1.95
13	SR-SW	Speaker, 4x6" Oval and Prepunched Wood Enclosure	14.95
14	MISC-SW	Misc. Parts Kit Includes Hardware, (6/32, 8/32 Nuts, & Bolts), Hookup Wire, Ant. Terms, DPDT Ant. Switch, Fuse, Fuseholder, etc.	9.95
When Ordering All Items, (1 thru 14), Total Price			139.95

7+11 PWD PARTS KITS

INTRODUCING OUR 7+11 PWD PARTS KITS



KIT NO	PART NO	DESCRIPTION	PRICE
1	1VT1-PWD	Varactor UHF Tuner, Model UES-A56F	\$24.95
2	2CB1-PWD	Printed Circuit Board, Pre-drilled	18.95
3	3TP11-PWD	PCB Potentiometers 4-20K, 1-5K, 2-10K, 2-5K, 1-1K, and 1-50k. (11 pieces)	8.95
4	4FR-31-PWD	Resistor Kit, 1/4W, 5% 29-pcs, 1/2 W 2-pcs	4.95
5	5PT1-PWD	Power Transformer, PRI-117VAC, SEC-24VAC at 500ma	9.95
6	6PP2-PWD	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT with switch	5.95
7	7SS17-PWD	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Transistors 2-pcs, Heat Sinks 2-pcs	29.95
8	8CE14-PWD	Electrolytic Capacitor Kit, 14-pieces	6.95
9	9CC20-PWD	Ceramic Disk Capacitor Kit, 50 WV, 20-pcs	7.95
10	10CT5-PWD	Variable Ceramic Trimmer Capacitor, 5-65pfd, 5-pieces	4.95
11	11L15-PWD	Coil Kit, 18mhs 3-pcs, 22µhs 1-piece (prewound inductors) and 2 T37-12 Ferrite Toroid cores with 6 ft. #28 wire	6.00
12	12ICS-PWD	IC Sockets, Tin inlay, 8 pin 4-pcs, 14 pin 1-pc and 16 pin 2-pcs	2.95
13	13SR-PWD	Enclosure with PM Speaker and Pre-drilled Backpanel for mounting PCB and Ant. Terms	14.95
14	14MISC-PWD	Misc. Parts Kit, Includes Hardware, (6/32, 8/32 Nuts & Bolts), Hookup Wire, Solder, Ant. Terms DPDT Ant. Switch, Fuse, Fuseholder, etc.	9.95
15	15MC16-PWD	Mylar Capacitors, 14-pcs and Silver Mica Capacitors 2-pieces	7.95
When Ordering All Items, (1-15), Total Price			159.95

SIMPLE SIMON ELECTRONIC KITS, Inc.

3871 S. Valley View, Suite 12, Dept. R, Las Vegas, NV 89103

NEED 6 OR MORE OF AN ITEM? WRITE FOR QUANTITY DISCOUNTS

In Nevada Call: 702-871-2892

1-800-782-3716

Outside Nevada Call:

Available by Mail Order Only
Send Check* or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00 — VISA and Mastercard Acceptable — *Check orders will be held 30 days before shipping.

FAST RELIEF

from

SOLID STATE HEADACHES

Model 216



SEMICONDUCTOR ANALYZER

Easy, automatic, "hands off" operation (Frees both hands for troubleshooting)

Simple to use — no set up — no data books

In, or out of circuit, GOOD-BAD analysis of NPN's, PNP's, FET's, diodes and SCR's

Instant, in or out-of-circuit leakage detection

Digital scanning circuit automatically determines lead configuration

Low-power CMOS design for extended battery life

Uses two standard 9V batteries (not included)

Weighs only 12 ounces — fits in your pocket

High impact thermoplastic case with snap-shut protective cover

PRICED UNDER \$150
THE MODEL 216 IS FAST,
RUGGED AND AFFORDABLE



THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

TABLE 2

Inputs switched to output pins

Input channel	1A	2A	1B	2B	1C	2C	1D	2D
Pin no.	2	4	6	8	11	13	17	15 12
DC control conditions (pins)	1 VL 3 VL 16 VH 18 VL	VL VL VL VL VH VH VL VL	VL VL VL VL VL VL VH VH	VL VL VL VL VL VL VH VH	VH VL VL VL VL VL VL VL	VH VL VL VL VL VL VL VL	VL VL VH VH VL VL VL VL	VL VL VH VH VL VL VL VL
Output pin	10	9	10	9	10	9	10	9 9 & 10 (MUTE)
Output channel	1 2	1 2	1 2	1 2	1 2	1 2	1 2	

Low switching-level: VL < 0.8 volts

High switching-level: VH > 2.0 volts

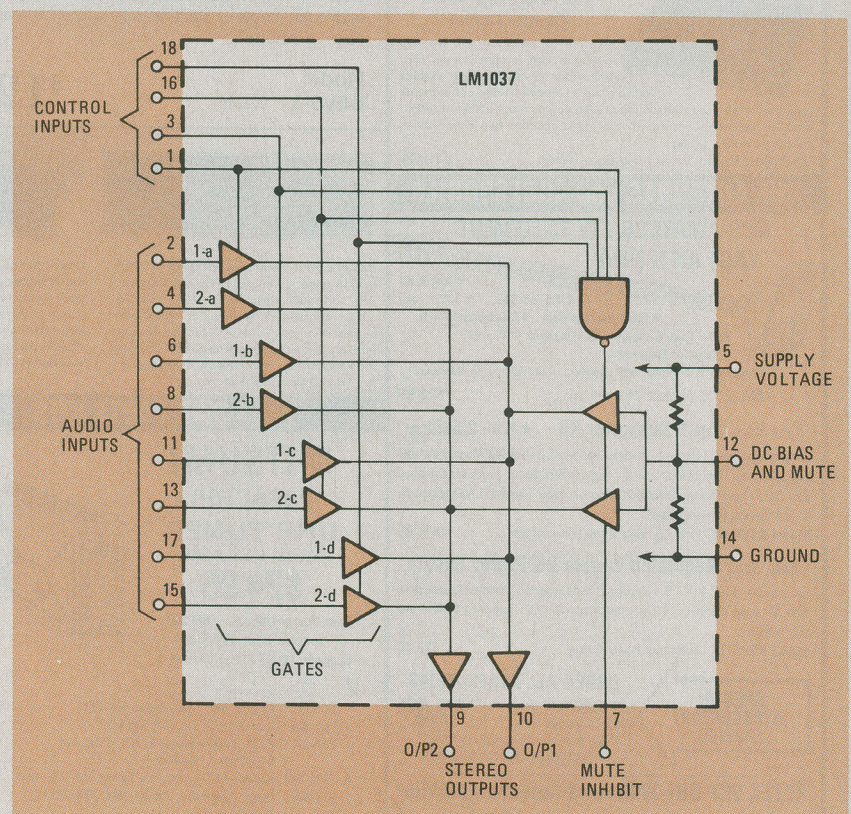



FIG. 2

require external capacitors to operate, and is capable of performing a variety of functions. It is ideal for signal processing, telecommunications, modems, instrumentation, and audio equipment. The center frequencies of all previously available active filters are adjusted with external resistors and/or capacitors. The MF10 filter is unique in that the center frequencies of its various second-order functions are directly proportional to an external clock frequency and fixed at an accuracy of 0.6%, or directly proportional to both the clock frequency and external resistor ratios. Gain and selectivity (Q) are adjusted using external resistors.


The clock and three or four resistors are the only external components necessary to operate the MF10 so the device is less sensitive to external component variations. Frequency stability is directly dependent on the quality of the clock. A single clock can be used to drive an almost infinite number of MF10 filters.

Unlike other available monolithic filters which have been designed for a specific function, the general-purpose MF10 can perform a wide variety of functions including allpass, highpass, bandpass, and notch. Up to fourth-order functions, and any configurations such as Butterworth, Bessel, Cauer, and Chebyshev


continued on page 90

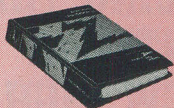


Courses in Computers and Programming

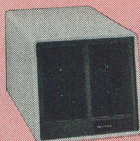

Disk Drives and Peripherals

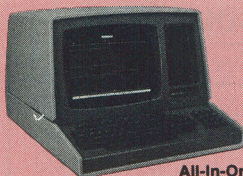

All-In-One Computer

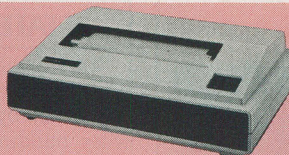

High-Speed Dot Matrix Printer



Superior Software Tools



Fully Portable Test Instruments



Hand-held Digital Multimeter



Programmable Automobile Horn




Emergency Power System




Hydraulic Log Splitter



Domestic Solar Water Heater

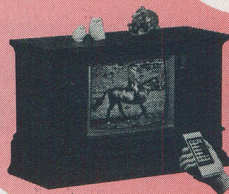

Space Phone Television

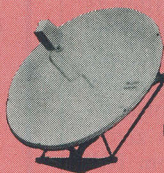

Home Earth Station Receiver

FREE Heathkit® CATALOG



450 kits and products: solar hot water systems, satellite TV, all-in-one computers, test instruments, amateur radio gear, self-study courses in computer literacy and state-of-the-art electronics, energy conservation and home security devices, fine stereo components, color televisions, automotive or marine aids, home conveniences and more – things you've always wanted and needed, right now at low kit prices from Heath.

For people with imagination, there's nothing to compare with the exclusive thrill of hand-built satisfaction.

Discover the fun of kitbuilding – it's a great way to relax in your spare time and share a rewarding pastime with your whole family. The great kits you build will reflect the pride of your craftsmanship, too. The famous Heathkit illustrated manuals make it easy for *anyone* to build reliable, professional-quality kits.

SEND FOR FREE CATALOG

Our 104-page catalog is Free! If coupon is missing write: Heath Company, Dept. 020-932, Benton Harbor, MI 49022

Heathkit® Heath Company, Dept. 020-932
Benton Harbor, MI 49022

Send me the latest free Heathkit Catalog now.
I want to "build in" the quality difference.


Name _____

Address _____


City _____ State _____

CL-727-RI Zip _____

**FREE
CATALOG**

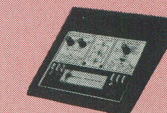

Educational Self-Study Courses

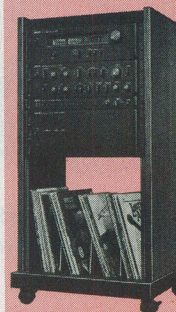

Pro-Series Audio Components



Digital Marine Depth Sounder



Amateur Radio Gear




Computerized Weather Station

Heathkit products are also displayed, sold and serviced at 60 Heathkit Electronic Centers* nationwide. Consult telephone directory white pages for location.
*Operated by Veritechnology Electronics Corporation, a wholly owned subsidiary of Zenith Radio Corporation. Some retail prices may be slightly higher.

BIG PERFORMANCE small PACKAGE

Model 240

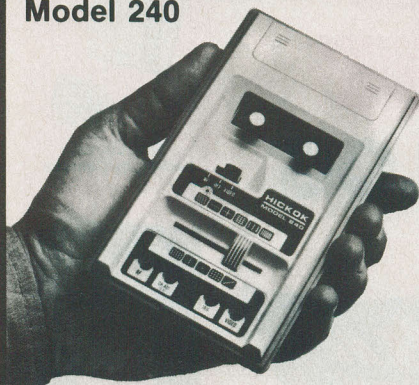

Video Generator

- Video output for all VCR, CCTV and Monitor Applications ± 1 volt into 75 Ω load
- RF output: CH 2, 3, 4
- Scope trigger output for V or H sync
- 10 step gray-scale staircase signal for video circuit analysis
- 10 bar and 3 bar gated rainbow pattern
- 8 other dot, bar and line patterns
- Operates from 2 std. 9V batteries or 115VAC
- Single slide switch control
- Complete with test leads, protective cover, AC adapter, comprehensive instruction manual

PRICED UNDER \$200.
THE 240 DOES SO MUCH
FOR SO LITTLE!!



THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 36 ON FREE INFORMATION CARD

STATE OF SOLID STATE

continued from page 86

can be had by cascading the two second-order building blocks. The center frequency can be as high as 20 kHz with a Q of 500. Typically, the lowpass and band-pass outputs can sink 0.75 mA and source 3 mA while the notch, allpass, and high-pass outputs sink 1.5 mA and source 3 mA. The devices come in 20-pin DIP packages and cost \$3.50 in lots of 100.—**National Semiconductor**, 2900 Semiconductor Drive, Santa Clara, CA 95051.

Optocouplers feature back-to-back LED's

Motorola has introduced two new dual-LED Optocouplers designed specifically for AC input applications. The devices—the HIAA1 and HIAA2—consist of two gallium-arsenide (GaAs) infrared-emitting diodes connected in inverse parallel, and optically coupled to a single silicon phototransistor (detector) in the standard 6-pin DIP package.

The Optocouplers can be used to detect the presence, absence, or interruption of AC power and trigger a desired action. A major application is the detection of a ring signal on telephone lines while providing isolation from the ring lines. The HIAA1 and HIAA2 are directly interchangeable with GE devices bearing the same type numbers, while providing for up to 7500 volts. The HIAA1 has a current transfer ratio of 20% and costs \$1.98 in lots of 1 to 99. The HIAA2 has a 10% current transfer ratio and costs \$1.70 in lots of 1 to 99.—**Motorola Semiconductor Products**, P.O. Box 20912, Phoenix, AZ 85036.


Tunable low-pass sampled-data filters

The MC145414 dual-tunable low-pass filter from the Motorola MOS Integrated Circuits Group is the latest addition to the growing family of CMOS switched-capacitor filters.

The MC145414 has a typical power dissipation of 30 mW when active and 1 mW in the power-down condition. Operating voltage can be obtained either from a single or split power-supply with a voltage range of 10 to 16 volts. It can interface to either TTL or CMOS devices. The device is useful in LPC (Linear Predictive Coding) or CVSD (Continuously Variable Slope Detection) speech applications, modems, or other applications where a precision low-pass filter is needed. Specifications include a dynamic range better than 80 dB, passband ripple less than 0.3 dB, and idle noise typically 100 dBmC0 (Decibel RMS noise C-message weighted referenced to zero). The device is offered in a 16-pin DIP plastic or ceramic package and is available for \$4.50 each in lots of 1000.—**Motorola Inc.**, 3501 Ed Bleustein Blvd., Austin, TX 78721.

R-E

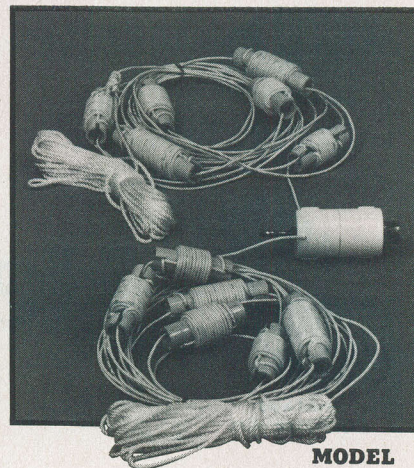INTRODUCING THE SWL ANTENNA WITH NEW HIGH EFFICIENCY TRAPS



**MODEL
ASWJ11-49**

- Only 40 feet long
- **NEW PATENTED HIGH EFFICIENCY TRAPS**
- Automatically tunes the popular 11, 13, 16, 19, 25, 31 and 49 short wave bands.
- Can be installed as a flat top, sloper or inverted V.
- Weatherproof construction for long trouble free service.
- Completely assembled. (Less feed cable.) Center insulator terminated with SO-239 Connector.
- Designed to be fed with RG59 coax for maximum efficiency.

PRICE \$37.50 plus \$2.00 shipping

RG59 coax cable available.
Terminated with PL-259
connectors on each end.

MODEL	LENGTH	PRICE PLUS 10% SHIPPING
AA-C-5925	25 Ft.	\$ 7.00
AA-C-5950	50 Ft.	9.00
AA-C-5975	75 Ft.	12.75
AA-C-5910	100 Ft.	15.50



Quality Communication
Products Since 1932
All Made in the USA

BARKER & WILLIAMSON

10 Canal St., Bristol, PA 19007

215-788-5581



At your distributor
write or call



CIRCLE 34 ON FREE INFORMATION CARD

A 10 HOUR TAPE RECORDER

WAS \$125.00

NOW only \$95.00*

LONG PLAY


Modified Panasonic Slimline high quality AC-DC Recorder provides 5 continuous hrs. of recording & hrs. of top quality sound on each side of cassette for a total of 10 hrs. Built-in features include:

- Voice level control
- Digital counter, etc.
- TDK DC-180 Cassette included.



PHONE RECORDING ADAPTER

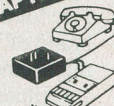Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up.



\$24.50*

VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike.



\$24.95*

*Add for ship. & hdlg. Phone Call Adapter & VOX \$1.50 ea—Recorder \$4.00. Cal. Res. add tax. Mail order, VISA, M/C, cod's ok. Qty. disc. inv. Money back guar. Free data. Dir. inq. inv. AMC SALES, Dept. A, 9335 Lubec St., Box 928, Downey, CA (213) 90241 Phone 869-8519

CIRCLE 50 ON FREE INFORMATION CARD

STEREO IMAGE EXPANDER

continued from page 65

stereo effect comes primarily from the studio's mixer-board. You can "A/B" the effect with the ON/OFF switch.

The majority of studio recordings are made from a mix of simultaneous "dry" sources and create an artificial image based on intensity differences between channels rather than on time and phase information. Even so, most of them will open up and sound more spacious—the speakers will become "transparent." Some recordings will do fascinating—and frequently spectacular—things when turned loose by the expander. Try any of Pink Floyd's or Tomita's releases to really put the expander through its paces.

Background reading

The first mention of loudspeaker crosscoupling and its effects appeared in a paper given by B.B. Bauer to the AES in 1961. A detailed exploration of the problem, a solution and test results appear in an article entitled:

"Head related two channel stereophony with loudspeaker reproduction" by P. Damaske, pp. 1109 to 1115 of the *Journal of the Acoustic Society of America*, Vol. 50, No. 4, Part 2, 1972

R-E

YOUR EXCITING NEW HOBBY!


- Enjoy fantastic savings by assembling your own organ or piano.
- It's easy. No technical knowledge required.
- Just follow our clear, pictured instructions.
- Choose from many models from portables to consoles.
- Ask about our interest-free installment plan.



ORGAN & PIANO KITS

For Free Information Pack M40

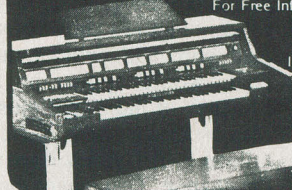Call Toll Free 800 233 3865 In PA 717 299 4327



or send coupon below

WERSI Dept. M40 P.O. Box 5318 Lancaster, PA 17601

- ☐ Free Info. Pack: ☐ Organ ☐ Piano
- ☐ Catalog & Demo Record (enclose \$6)

Name _____
Address _____
City _____ State _____ Zip _____
Phone (____) _____

Rep inquiries invited

CIRCLE 51 ON FREE INFORMATION CARD

We accept VISA, MC, C.O.D., CHECK or M.O.

FIRST QUALITY COMPONENTS - NOT MAIL ORDER "SECONDS"

Min. order \$10.00 - add 5% Shpg and \$1.00 Ins

ARIES ZERO INSERTION FORCE SOCKETS

cam actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets, including wire wrap.

Stock No.	No. Pins	1-24	25	50
11055	24	\$ 4.35	\$ 3.90	\$ 3.60
11056	28	\$ 4.50	\$ 4.05	\$ 3.75
11057	40	\$ 5.95	\$ 5.35	\$ 4.95
11058	64	\$ 10.50	\$ 9.45	\$ 8.70

RESISTOR ASSORTMENT 82508 - 700 pcs. (1 each below assort'd)

Stock No. 82501 10 ea. of 10-12-15-18-22-27-33-39-47-56 OHM \$22.50
Stock No. 83502 10 ea. of 68-82-100-120-150-180-220-270-330-390 OHM \$3.95 each for any assortment
Stock No. 82503 10 ea. of 470-560-680-820-1K-1.2K-1.5K-1.8K-2K-2.2K-2.7 OHM
Stock No. 82504 10 ea. of 3.3K-3.9K-4.7K-5.6K-6.8K-8.2K-10K-12K-15K-18K OHM
Stock No. 82505 10 ea. of 22K-27K-33K-39K-47K-56K-68K-82K-100K-120K OHM
Stock No. 82506 10 ea. of 150K-180K-220K-270K-330K-390K-470K-560K-680K-820K OHM
Stock No. 82507 10 ea. of 1M-1.2M-1.5M-1.8M-2.2M-2.7M-3.3M-3.9M-4.7M-5.6M OHM

WILD ROVER Touch switch capsule

Operating motion is .005" without the use of a levered arm. Extremely fast on and off with low noise. Normally open - rated 115 VAC, 1.6 amp-30 million resistance - 615 radius by .160 thick.

Stock No.	1-9	10	25
12098	\$ 1.28	\$ 1.12	\$.95

60/40 ROSIN CORE SOLDER

Stock No.	Length (feet)	Weight (oz.)	Price
50075	.062	9	\$ 3.28
50076	.062	25	\$ 4.35
50077	.062	50	\$ 6.02
50078	.032	33	\$ 1.50
50079	.032	88.5	\$ 4.16
50080	.032	175	\$ 6.82

TI WIRE WRAP SOCKETS


Tin plated phosphor bronze contact - 3 wrap



Stock No.	No. Pins	1-24	25	100
11301	8	\$.45	\$.40	\$.36
11302	14	\$.66	\$.59	\$.54
11303	16	\$.72	\$.64	\$.58
11304	18	\$.82	\$.73	\$.66
11305	20	\$ 1.11	\$.99	\$.90
11306	22	\$ 1.26	\$ 1.12	\$ 1.02
11307	24	\$ 1.41	\$ 1.25	\$ 1.14
11308	28	\$ 1.71	\$ 1.52	\$ 1.38
11309	40	\$ 2.31	\$ 2.05	\$ 1.86

TI LOW PROFILE SOCKETS

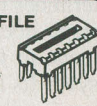Tin plated phosphor bronze contact pins with gas tight seal



Stock No.	No. Pins	1-24	25	100
11201	8	\$.15	\$.13	\$.12
11202	14	\$.18	\$.15	\$.14
11203	16	\$.21	\$.18	\$.16
11204	18	\$.24	\$.21	\$.19
11205	20	\$.27	\$.24	\$.21
11206	22	\$.30	\$.26	\$.23
11207	24	\$.33	\$.30	\$.25
11208	28	\$.38	\$.34	\$.29
11209	40	\$.53	\$.45	\$.40

ELPAC POWER SUPPLIES - DC/DC CONVERTERS

SINTEC Stock No.	ELPAC Part No.	Input Voltage (VDC)	Output Voltage (VDC)	Output Current (mA)	Dimensions (HxWxD) in inches	Price
13825	CB3801	3-0-7.0	12±0.6	0-25	48x.51x3.05	\$ 7.95
13826	CB3811	3-0-7.0	12±0.6	0-25	48x.51x3.05	\$ 7.95
13827	CB3802	3-0-7.0	15±0.7	0-20	48x.51x3.05	\$ 7.95
13828	CB3812	3-0-7.0	15±0.7	0-20	48x.51x3.05	\$ 7.95
13829	CB3804	3-0-7.0	28±0.7	0-10	48x.51x3.05	\$ 7.95
13830	CB3814	3-0-7.0	28±0.7	0-10	48x.51x3.05	\$ 7.95

Stock No. 13801 - "Floppy Disc" Power Supply For Winchester Drives \$109.00

13801-1 Data Sheet for 13801 ... \$.25

13825-1 DATA SHEET FOR DC/DC CONVERTERS \$.25

ELPAC POWER SUPPLIES - SOLV SERIES FULLY REGULATED

SINTEC Stock No.	ELPAC Part No.	Output Voltage	Output Current Rating	Dimensions (HxWxD) in inches	OVP	Price
13802	SOLV15-5	5	3.0A	4-7/16x4-1/2	Fixed included	\$39.95
13803	SOLV15-12	12	1.5A	4-7/16x4-1/2	Fixed included	\$8.95
13804	SOLV15-15	15	1.2A	4-7/16x4-1/2	Fixed included	\$8.95
13806	SOLV15-24	24	0.75A	4-7/16x4-1/2	Fixed included	\$8.95
13808	SOLV15-5	5	3.0A	5-5/8x4-7/8x3-3/16	OVP-4	\$8.95
13809	SOLV30-12	12	4.0A	5-5/8x4-7/8x3-3/16	OVP-4	\$9.95
13810	SOLV30-15	15	3.3A	5-5/8x4-7/8x3-3/16	OVP-4	\$8.95
13812	SOLV30-24	24	2.0A	5-5/8x4-7/8x3-3/16	OVP-4	\$8.95

13802-1 Data Sheet for SOLV Series

HUNTER TOOLS

8 Blades, sizes .050, 1/16", 5/16", 3/32", 7/64", 1/8", 9/64", 5/32"




Stock No. 51002 \$3.45

7 most popular sizes - 3/16", 7/32", 1/4", 9/32", 5/16", 11/32", 3/8"



Nutdriver Kit Stock No. 51001 \$21.95

Special of the Month!

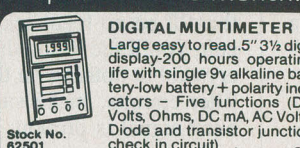

Stock No. 62501 \$54.95

DIGITAL MULTIMETER
Large easy to read 5" 3 1/2 digit display-200 hours operating life with single 9v alkaline battery-low battery + polarity indicators - Five functions (DC Volts, Ohms, DC mA, AC Volts, Diode and transistor junction check in circuit)

Stock No. 62502 \$49.95
Kit Form. with Instructions.

PIN FORMING TOOL

puts IC's on their true row to row spacing. One side is for .300 centers. Flip tool over for devices on .600 centers. Put device in tool and squeeze.

ONE TOOL DOES 8 Thru 40 PINS!

Stock No. 11059 \$12.95



THE PIKE 5 in 1 Tool

CRIMPS #10 - #24 wire STRIPS solid #12-22 and stranded #14-24

SCREW CUTTER for 6 most common screw sizes CUTTER and PLIERS

Stock No. 51005 \$12.95

MODUTEC



Miniclamp AC Volt-Ammeter allows singling one conductor out of many without disarrangement.

Stock No.	AC Amperes	Price
13730	0-25A	\$39.50
13731	0-50A	\$39.50
13732	0-100A	\$39.50

ACCESSORY LINE SPLITTER
allows fast readings of AC power consumption of plug in equipment without separation of leads.

Stock No. 13727 \$9.95



POCKET SIZED BATTERY TESTER
for all types of small batteries from 1.35v to 4.5v

Stock No. 13733 \$13.95



VOLT-ICATOR
automotive diagnostic meter plugs into lighter socket and indicates battery condition and charging rates.

Stock No. 13736 \$12.95



AC VOLTAGE TESTER
plugs into any 110v service receptacle to check time voltage over 50-150 VAC

Stock No. 13735 \$9.95



VOM-MULTITESTER
versatile Volt-Ohm-Milliammeter in small package

Stock No. 13729 \$13.95

SINTEC Drawer Q Milford CO. NJ 08848-9990



TOLL 800-526-5960
FREE in NJ (201) 996-4093

Send for Free Catalog - over 1100 parts.

CIRCLE 27 ON FREE INFORMATION CARD

SERVICE CLINIC

Color-burst reference oscillators

JACK DARR, SERVICE EDITOR


A TV SET'S COLOR-REFERENCE-oscillator signal, with a frequency of 3.58 MHz (actually 3.579545 MHz), is a very important one. If it isn't present—with a few exceptions that will be noted soon—no color will be seen. Figure 1 shows how the video signal, with and without the reference signal, would appear on a scope. The frequency of the signal must be precise; if the oscillator shifts in frequency by as little as $\frac{1}{4}$ -Hz, you will see a very obvious tint change. That means that the AFC must be very tight.



WITH REFERENCE SIGNAL

The crystals used in the two circuits are not identical. They oscillate at the same frequency, of course; but apparently they're different cuts (one for use as an oscillator; the other for use as a filter) and neither one will work satisfactorily in the other circuit. (I determined that from experience—and a whole afternoon of work!)

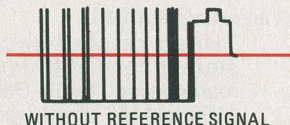The symptoms of oscillator failure are obvious. The black-and-white picture will be good, but there will be no color at all. If you run into that situation, the first



WITHOUT REFERENCE SIGNAL

FIG. 1

Two basic types of circuit are found in older sets, and are still in use in current ones. The older circuit is a crystal-controlled oscillator; the crystal determines the frequency, and an amplifier stage does the rest. The circuit can be made to free-wheel by killing the color sync. Its tuning can be set very near the precise point needed and when the sync is restored, it locks in and stays. Precise control is obtained by comparing the output of the oscillator with the color-burst signal, which is transmitted along with the rest of the TV signal. Many circuits of that type use an AFC circuit almost identical to those used in horizontal-oscillator stages.

The second type of circuit also uses a crystal, but not as the frequency-determining element in an oscillator circuit. In fact, there is no true oscillator. The color-burst signal is fed to a pre-amplifier stage, and then through the crystal, which is actually used as a very-narrow-band filter. The signal from the crystal "filter" is fed to a very-high-gain amplifier stage (often mislabelled a "3.58-MHz oscillator"). It isn't an oscillator; what it does is amplify the burst signal, which makes it "ring" longer. In fact, there is still signal present when the next color-burst signal comes along, so it's clipped and becomes a standard RF-signal, which is fed to the demodulators. The frequency of those circuits isn't controlled. There's no need to, because we're using the color-burst frequency itself as the oscillator signal.

and best test is to scope the output of the 3.58-MHz circuit, looking for an RF signal of the correct amplitude. Incidentally, you don't really need a wideband scope for that test. If there's a signal present you may see it as a blur, but the *amplitude* of the signal is the important thing; if the level is too low, the demodulators will not work properly.

The first step is to check the active device (tube or transistor) by substitution. If that doesn't bring things back to normal, check all the DC voltages around the stage to make sure that they're normal. As a last resort, try a new crystal, making sure you use the right type! If the crystal fails to work in the "oscillator" circuit, there'll be no feedback. In the filter circuit, you'll see RF on the input side of the crystal but nothing on the output side. In filter circuits, make sure that the color-burst signal is present, too.

In some sets, (mainly the "oscillator" type) sometimes you can see an odd symptom. (I got a letter only this week that complained, "...I've lost the red. The screen is a bluish green but there's no color where it ought to be.") A color-bar signal shows no colors in the bars, but the white spaces between them will be a definite bluish-green. That indicates that the oscillator is dead, but somehow there is enough of the color-burst signal getting through to the demodulators to make the screen glow bluish-green, which is the result of the phase of that signal.

The problem isn't confined to older sets. In one solid-state set, a middle-aged

Philco, the 3.58-MHz oscillator is a small IC op-amp. The original part has a history of failure at odd intervals. The best cure I've found is replacement with a different brand of IC—practically every one of the replacement-transistor/IC makers has a substitute for it.

Loss of the oscillator signal kills the color. If, on the other hand, you lose the color sync, you get fairly bright color showing on the screen, but as "rainbows"—narrow bands of red, green, and blue, slanted exactly like the bars you see when the horizontal oscillator's out of sync. The picture itself, though, will be steady. Start by checking for the color-burst signal; a dead burst-amplifier can be one cause of the problem. For a definite check, run a complete setup procedure on the oscillator. If the oscillator will make colors in the bars at the right places, but they float, the problem is narrowed down to the sync. In a few cases, the crystal can cause that. It'll be *almost* on frequency, but "right on the edge", and the sync won't lock.

Another problem, found mainly in older sets, is good horizontal lock, but very poor color sync. Before running the setup on the oscillator, check the position of the horizontal-hold control. If the color suddenly locks in when you move it toward the center of its range, you've solved the problem.

The reason why the color sync is lost is that if the horizontal oscillator is almost to the fallout point, there will be a small phase-shift in the gating pulse. That's the pulse that "gates out" the color-burst signal from the rest. If the pulse is off frequency, it gets there a little too late or too early and you lose the color-burst signal, and thus the color sync. Always check the horizontal-hold control setting first; it may save you a lot of trouble! R-E

SERVICE QUESTIONS

SHORTED CRT

There's a arcing in the neck of the picture tube in this RCA CTC-58. My tube checker shows a heater-to-cathode short in the green gun (I have an isolation transformer for that kind of test). With the tube socket off, I can read 25 kV on the focus

pin of the tube. Please help!—D.W., Taos, NM

There's a good chance that the CRT is bad. At times you'll find "particle shorts" between grids G3 and G4; G3 is the focus grid and G4 is connected directly to the high-voltage supply. You might try disconnecting the tube socket and HV lead, and discharging a medium-size capacitor (around 20–30 μF) across the focus pin and ultor button (charge the capacitor from the B+ supply). If there is a particle short there, that may blow it out. While the spacing between those two electrodes is very small, there shouldn't be any leakage at all there. Also check the focus circuit to see if any of its components have been damaged.

RESISTOR BURNOUT

In this Zenith 19HC50, resistor R221 (1½-ohms, ½-watt) in the base return of the horizontal-output transistor, keeps burning up. I replace it, and it's out again in three or four weeks. Last time I used two 3-ohm, ½-watt resistors in parallel to increase the current-handling capacity, but they burned up too. That resistor's very hard to get at; I'd sure like a permanent fix!—D.M., Chicago, IL

I know what you mean; it's always the hard-to-reach parts that have to be replaced. Now—what makes a resistor burn up? Excess current! In your case, it can't be too much DC or the set wouldn't work at all. The only thing left is pulse-current, and there is a sizable pulse—about 15-volts peak-to-peak—across that resistor.

There's also a 50- μF electrolytic capacitor across the resistor to bypass that pulse to ground. If it's open, the pulse could generate enough current to overload the resistor. Replace the 50- μF capacitor, and stay with 1-watt resistors to be safe.

POOR FOCUS

The focus is poor on this Zenith 19EC45. I replaced the tripler and the HV is now OK, but the focus voltage is only 500 volts. When I disconnect the lead to the picture tube the voltage rises to 4.6 kV, but when I connect it again, the voltage drops back down. Could the focus electrode in the CRT be shorted?—A.G., Binghamton, NY

It's possible, but not likely. More probably, there's leakage across the arc-gap in the CRT socket. Take it apart and check for carbon paths, etc.

(Feedback: Bingo! A.G. says, "I took the socket apart and found a burnt path from the focus pin to the CRT ground lead, which apparently was shorting the focus voltage to ground. Thanks.")

ASSORTED HINTS

Problem: Poor vertical size (two or three inches short of filling the screen) in a Toshiba TAC-9330 (Sams 1500-3).

Solution: Check the two-ohm resistor from ground to IC302 (vertical osc/amp/output)—the one I had read about five ohms. That isn't the only possible cause of the problem, but it's easy to overlook unless you're using a digital meter.

Problem: Intermittent but repeated failure of power-supply diodes in a Philco E-21.

Solution: Try replacing the tripler. I did that and the set's worked well ever since. It must be that the tripler was intermittent.

Now for a request. I need a power transformer for a Lectrotech V-7 vector-scope. I wrote to the company, but got no reply; maybe you can help.

Thanks to A.Y. of Lexington, NC for the hints. To answer your request, call (800) 851-3584 and a nice fellow by the name of John Evans at Thordarson will try to help you out. I'm almost sure they have something that will do the job, since they have quite a few scope power-transformers in their catalog.

HORIZONTAL HOLD PROBLEM

I've got a Magnavox T936 with very poor horizontal hold. I'm not having any luck with it, and could sure use some advice.—C.D., Hightstown, NJ

Take out the AFC diode unit and check it for balance. Also, check all the resistors and capacitors around the AFC circuit. To make sure that the problem is in the AFC, ground the grid of the AFC tube and see if you can get a floating picture with one straight side. If you can, the oscillator is OK and the cause is due to the AFC section.

(Feedback: "I tried the test and it worked—the AFC diode-unit wasn't balanced. I also checked the resistors and found that a 68K unit that was supposed to drop the voltage to +33-volts was open, even though it looked perfect. A new resistor and new diode unit fixed everything.")

OPEN CAPACITOR BURNS RESISTOR

I noticed a question here recently about an RCA CTC-31 that was burning up R163. You said it was the plate load for the horizontal oscillator, but I think it's an isolation resistor. It burns up because filter capacitor C118B is open. Therefore the AC from the oscillator must go to ground through C119A, so it also goes through R163 and burns it up.

I've run into the problem in a number of 1967/1968 RCA chassis.

Thanks to B.W., of Loew's TV in Central City, NE for that information.

SPECIAL RESISTOR

This Portland RP-209HN had no sound or video, and only a faint raster. Those sets are made in Korea by the Taihan Corp., and there is no Sam's Photofact for them as yet. However, I was able to get a


BASIC TRAINING

Learn to write concise, effective programs in BASIC with two great books from Sams.

BASIC PROGRAMMING PRIMER, by Mitchell Waite and Michael Pardee, is an excellent, user-friendly guide to BASIC-language programming fundamentals. It's ideal for beginning or advanced computerists, and comes with a handy, tear-out reference card listing condensed BASIC commands.

BASIC PROGRAMMER'S NOTEBOOK contains a number of programming secrets and shortcuts usually known only to highly experienced programmers, as well as workable ways to trim both the size and the running time of some of your larger programs. Program statements are in Level II BASIC, but most of the concepts can readily be translated to other BASIC dialects.

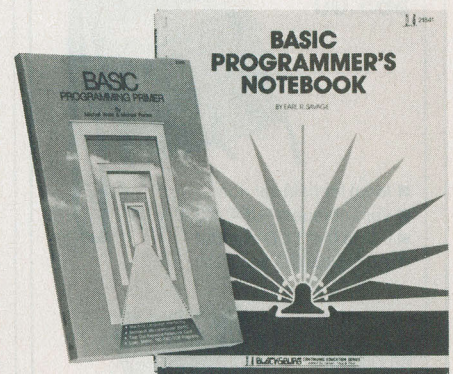Complete your BASIC training with Sams, America's leader in the field of microcomputer knowledge!



SAMS BOOKS

TM

Mail to: Howard W. Sams & Co., Inc., 4300 West 62nd St., P.O. Box 7092, Indianapolis, IN 46206

Quantity

BASIC PROGRAMMING PRIMER	No. 21586	\$11.95	_____
BASIC PROGRAMMER'S NOTEBOOK	No. 21841	\$14.95	_____
Two Volume Set	No. 22025	\$22.95	_____
ORDER BOTH BOOKS AND SAVE 15%!			

Amount of Order \$ _____
Add Handling Costs \$ 2.00

Add Local Sales Tax Where Applicable \$ _____

Total Amount of Order \$ _____

Payment Enclosed: ☐ Check ☐ Money Order

☐ VISA ☐ MasterCard Interbank No. _____

Account No. _____

Expiration Date _____

Name (Print) _____

Signature _____

Address _____

City _____

State _____ Zip _____

Call toll free 800-428-3696 for the name of your local Sams Book outlet or to order by phone (give Sams Operator the code number in the box below). Offer good in U.S.A. only. Offer expires 12/31/82. Prices subject to change without notice. AD212

CIRCLE 33 ON FREE INFORMATION CARD

SEPTEMBER 1982

93

New Value+Plus™ DMM's

B&K-PRECISION gives you more value than ever.

B&K-PRECISION's new Value+Plus DMMs give you outstanding performance and price, plus extras you'd expect to pay more for.

The new 2801 and 2805 DMMs are compact 3½-digit instruments, featuring LCD readouts, auto-zeroing, auto-polarity, ten megohm input impedance and full overload protection.

+Plus extras, at no additional cost, include high-energy fusing for added safety, low battery indicator, durable test leads and carrying case. Both offer rugged construction and LSI technology, for long-life reliability.

**Model
2801
\$65.00**



- Ideal for field service
- Very compact—5.4" x 3.4" x 1.4"
- Large 0.4" LCD readout
- 1% typical DC accuracy

**Model
2805
\$100.00**



- 200 mV to 1,000 V ac/dc voltage ranges
- 200 µA to 10 A ac/dc current ranges
- 0.8% typical dc accuracy
- Measures resistance to 20 MΩ

Value+Plus DMMs are available for immediate delivery at your local B&K-PRECISION distributor. For additional information or the name of your local distributor call

1-800-621-4627

BK PRECISION DYNASCAN CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
Int'l. Sis.: 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario

service manual from the U.S. office of the manufacturer; that address is Taihan (America) Corp., 8960 Lurline Ave., Chatsworth, CA 91311. Once that problem was solved, however, I ran into a new one. Turns out that the cause of the problem was R905, one of the critical "safety" parts. That being the case, I decided to order one from the company. That was until I found out that it could take up to six months to get one. Instead I used a 62-ohm Sylvania Flameproof resistor and it seems to work perfectly. By the way, there is a mistake on the parts list concerning that resistor—they list it as R05 instead of R905.—M.B. Danish, Aberdeen Proving Ground, MD

VERTICAL PROBLEM

I had no vertical sweep on this RCA CTC-71. Tried changing C120, a 470-µF capacitor. The raster came back and I thought that all was well. Not long after, however, the set came back with the same problem. I've been told that this capacitor has a high failure rate, but I'd like your opinion—R.C., Philadelphia, PA

Considering that two of those failed in a short period of time, I'd try using a replacement with a higher working voltage. Many times if a part fails repeatedly it's due to the original rating being a bit too low.

(Feedback: That was it—used a higher working voltage as you recommended and it appears to have solved the problem for good. Thanks!)

FINDING INTERMITTENTS

I've recently come across a new method for finding intermittents. I've used it with good success and I'd like to share it with you. I use an electric engraving-pencil—the type used for engraving names on personal belongings—as a "vibration tool." Just put a six-inch piece of rubber or plastic tubing on the end of it, set the pencil for its lowest speed, and hold it against the piece of equipment you are working on. That will dig out intermittent solder joints, etc. quite quickly. In case you are worried that this method could damage your gear, NASA uses a "shaker table" to test out its equipment and this tool is not nearly as rough.—R.E. Grist, Bayside, CA

WEAK VERTICAL SYNC

I can stop the vertical roll on this RCA CTC-66 using the vertical-hold control, but the slightest disturbance causes the picture to begin rolling again—any ideas?—S.C., Mentone, CA

The symptoms you're describing indicate that the problem is weak vertical sync. Check the sync separator and all the DC voltages, etc. Sometimes that is caused also by leaky shunt capacitors in the vertical integrators.

(Feedback: The sync separator, Q503, showed leakage. Replaced it with an RCA SK-3024 everything's fine.) R-E

64K For Sinclair
ZX81
\$179.95



Memotech 64K Memopak

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Designed to be in the price range expected by Sinclair owners. Plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for additional power supply or cables. The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent, and accepts such basic commands such as 10DIM A(9000). With the Memopak extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

GLADSTONE

Electronics, 901 Fuhrmann Blvd., Buffalo, NY 14203.


Call (716) 849-0735 to order. Have your VISA or MASTERCARD ready. \$3.00 shipping and handling.

In Canada, call (416) 787-1488. Mail orders send check or money order. Sorry no CODs. Circle reader service card for Sinclair software catalogue.

CIRCLE 54 ON FREE INFORMATION CARD



Audio Modules

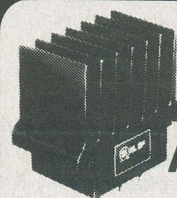

MOSFET Power Amplifiers

*BUILT-IN HEATSINKS *ONLY 5 CONNECTIONS REQUIRED * 5 YEAR WARRANTY

Choose ILP MOSFET power amps when you need the utmost in performance without spending big money. They provide the fastest possible slew rate, low distortion at high frequencies, + better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Three models are available, with integral heatsink to mount on your own chassis (optional rack mount cabinet available). Connection is simple — via 5 pins. MOSFETs can be combined with other ILP modules to create almost any audio system, whatever your age or experience. Ultra-fi specifications: Slew rate 20V/us. Rise time 3 us. S/N ratio 100 db. Frequency response (-3 db) 15 Hz - 100 kHz. THD (typical at 1kHz) < 0.005%. IMD (50Hz/7kHz 4:1) < 0.006%.

MOS120 60W/4-8Ω (requires ±45V)	\$79.95
MOS200 120W/4-8Ω (requires ±55V)	\$129.95
MOS400 240W/4Ω (requires ±55V)	\$199.95

WRITE FOR FREE CATALOGUE LISTING:
*BIPOLAR POWER AMPLIFIERS *HI-FI PREAMPS
*MIXERS *POWER SUPPLY UNITS *CABINETS
*GUITAR PREAMP and more

GLADSTONE


Electronics 901 Fuhrmann Blvd., Buffalo, NY, 14203

CALL (716) 849-0735 to order. Have your VISA or MasterCard ready. Dealer/OEM enquiries (416) 787-1488. In Canada: Gladstone Electronics, Toronto.

CIRCLE 53 ON FREE INFORMATION CARD

For more details use free
information card inside back cover.

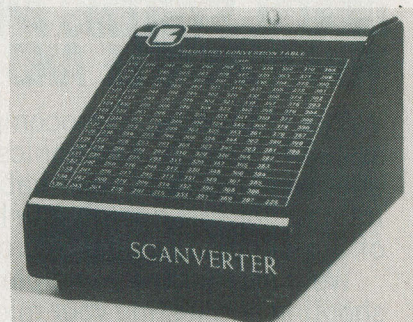
SCANNER CONVERTER, the *Scanverter* C/V-R-1, allows complete coverage of the 225-400 MHz military/federal-government aircraft band when used with a standard aircraft-band scanner. Listeners can hear NASA space-shuttle radio links to Earth, military air-tactical war games, Coast Guard search and rescue missions, FLEETSATCOM military



continued on page 100

ANTENNA KIT

\$16.95



32 WASHERS
31 SPACERS
MOUNTING BRACKET
6" RG 174 COAX
'F' CONNECTOR
6½" x 4" P.V.C. PIPE
2 DRILLED END CAPS

- 35" ROD
- HARDWARE

**Complete
Down Converter
System**
INCLUDES
ANTENNA KIT
POWER SUPPLY KIT
CONVERTER KIT
SPECIAL \$49.95

SEPTEMBER 1982 95

EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that offers you training for this booming field with a choice of 3 production-model micro computers.

We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!


NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.

We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in most of NTS's electronic programs.


For instance, to learn Color TV Servicing you'll build and keep the 25" (diagonal) NTS/HEATH digital color TV.

In Communications Electronics you'll be able to assemble and keep your own NTS/HEATH 2-meter FM transceiver, plus test equipment.

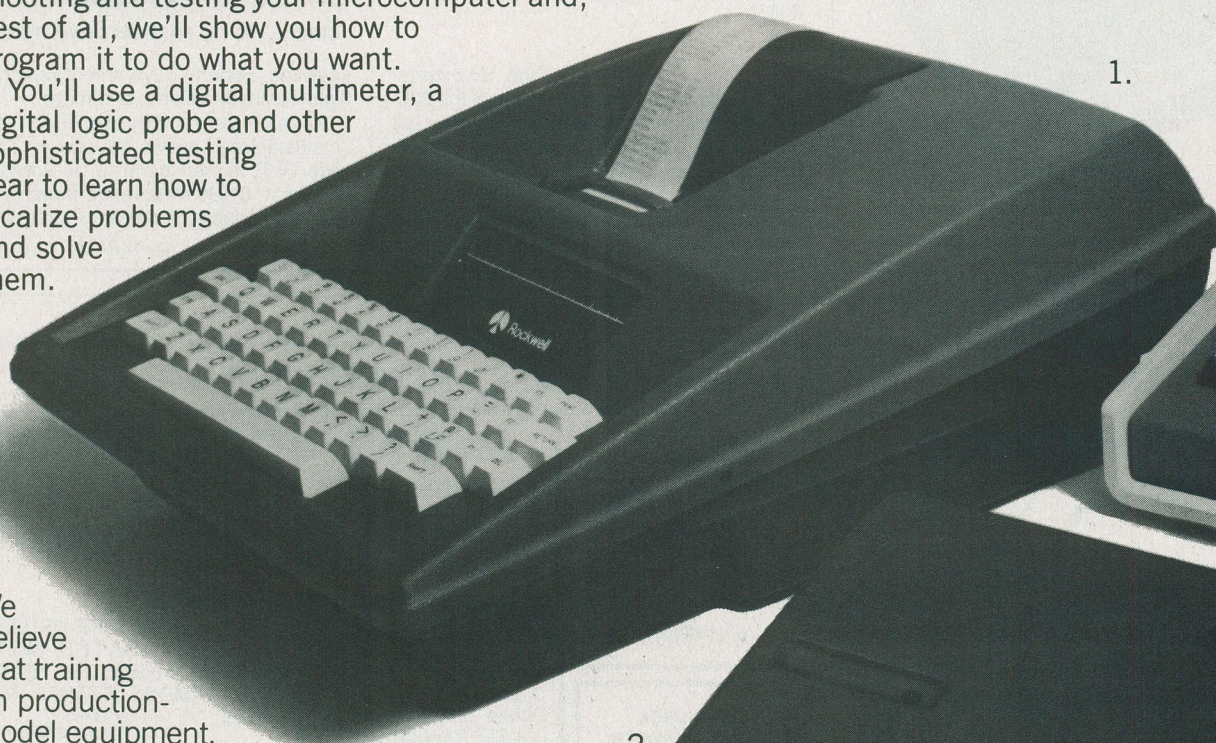But no matter which program you choose, NTS's Project Method of instruction helps you quickly acquire practical know-how.



2.

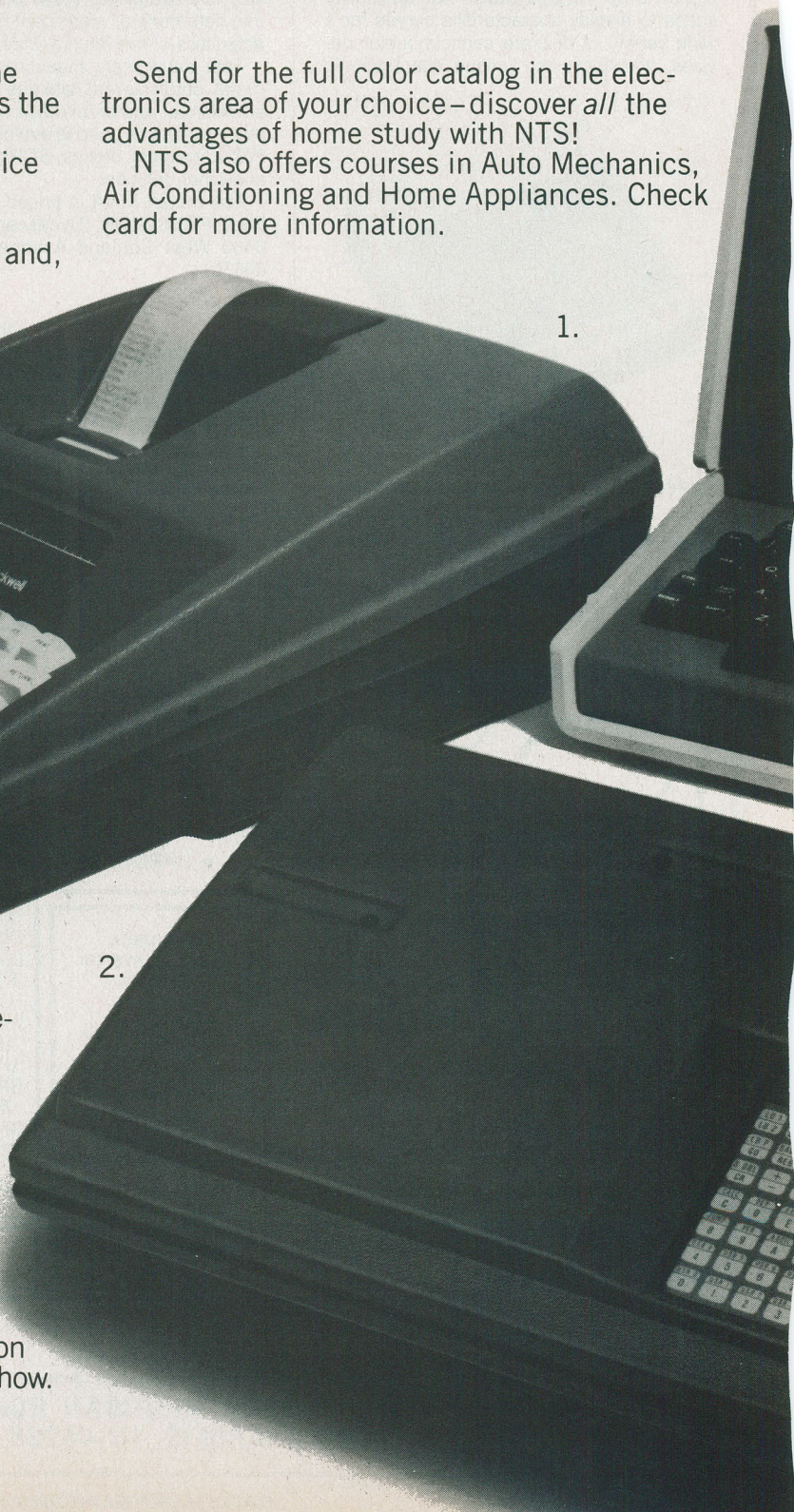



Simulated TV Reception

4.


3.

3. The NTS/Heath HN-89A Microcomputer features floppy disk storage, "smart" video terminal, two Z80 microprocessors, with 32K RAM Memory, expandable to 64K on board. 4. The NTS/Heath GR 2001 Digital Color TV (25" diagonal) features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

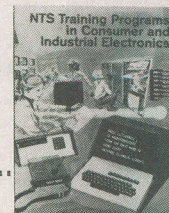1. The NTS/Rockwell AIM 65 Dedicated Microcomputer A Single board unit featuring on board printer and display—4K RAM (expandable). Application Functions: Central processor—Controller/Monitor—Development System. 2. "The NTS/SYM-1 Microcomputer" 6502 Based CPU—4K bytes ROM (expandable)—1K RAM (expandable). 51 active I/O lines for versatile interfacing: disk drives, ASCII key boards, cassette tape, etc.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street, Dept. 206-092
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____

Address _____

Apt. _____ City _____

State _____ Zip _____

☐ Check if interested in G.I. information.

☐ Check if interested ONLY in classroom training in Los Angeles.

NEW PRODUCTS


continued from page 95

tion. No tuning or adjustments are necessary with the fully automatic converter. Reception for hundreds of miles is possible with the use of an outside antenna.

A handy list of active nationwide UHF aircraft channels is included, and the unit comes complete with power cord, interconnect cable, and full instructions.

The *Scanverter CVR-1* is priced at \$99.95, plus \$2.00 shipping.—**Grove Enterprises, Inc.**, Brasstown, NC 28902.

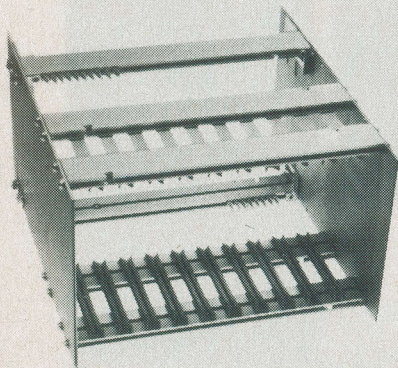MINI CARD CAGE, model *CCK19S*, is a miniature card rack for STD bus microcomputer systems. It occupies only .21 cubic feet,




CIRCLE 153 ON FREE INFORMATION CARD

yet holds up to 10 STD bus cards; it can easily be installed in desk-top consoles, video terminals, printers, controllers, or other equipment with limited space.

The rack accepts either mother boards from Vector and other manufacturers, or card edge connectors with 28/56 .125-inch spaced contacts. It is form-compatible with all 4.48-inch wide by 6.5-inch long STD microcomputer cards. It is shipped disassembled with all hardware and can be assembled quickly. The captive screws in the cage T-struts permit easy locating of the mother board or discrete connectors. The model *CCK19S* is priced at \$39.50.—**Vector Electronic Co., Inc.**, 12460 Gladstone Ave., Sylmar, CA 91342.

DMM, model 6502, features six versatile computing functions not available on similarly priced competitive instruments. A total of 14 pushbuttons, combined with a self-prompting display, provides flexibility in the manipulating and recording of data. Two storage registers allow a display to be scaled by any slope and offset. A single NULL key stores a display as a "zero" value and automatically subtracts that value from all subsequent measurements. Two keys store any entered value as a reference, and display future measurements as a percent deviation from that value. High and low limits can also be stored, and a LIMIT key then allows the display of values within those limits, or HI and LO annunciators if the measured value is outside of the limits. A START key initiates the continuous storage of maximum and minimum values. A MIN key similarly displays the minimum value. A RESET key allows the instrument to return temporar-

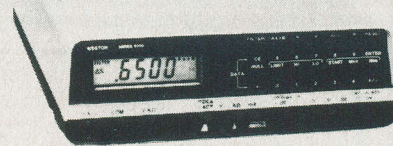

CIRCLE 154 ON FREE INFORMATION CARD

ily to the DMM mode without losing any programmed computation.

A FILTER mode activates a binary weighted average of the last four measurement conversions, assuring more accurate and stable readings in the presence of noise. To assure a rapid response to step changes, the filter function is automatically inhibited when successive conversions differ by more than 2% of full scale. All computing functions may be operated singly or chained, if desired, to perform more multiple operations.

The model 6502 is priced at \$758.00.—**Weston Instruments**, 614 Frelinghuysen Avenue, Newark, NJ 07114.


CIRCLE 00 ON FREE INFORMATION CARD

ANTENNA TUNER, model *PT-407*, is a general-purpose tuner for 1.8-30 MHz to match antennas fed with coaxial or open-wire lines, single wire, or mobile antennas. The 300-watt power rating makes it suitable for most amateur-radio setups.

The model *PT-407* has a large airwound coil, a large balun for open-wire feed, and has ceramic insulation throughout. It is housed in an 8 x 4 x 7-inch aluminum cabinet with

THE performers.

Model 310
\$70.00

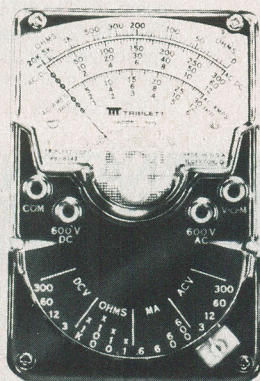

1. Drop-resistant, hand-size V.O-M with high-impact thermoplastic case.
2. 20,000 Ohms per volt DC and 5,000 Ohms per volt AC; diode overload protection with fused Rx1 Ohms range.
3. Single range switch; direct reading AC Amp range to facilitate clamp-on AC Ammeter usage.

Contact your local Triplet Distributor or Factory.
Phone 419-358-5015, TWX 810-490-2400.


Triplet performance . . .
a tough act to follow

CIRCLE 46 ON FREE INFORMATION CARD

THE performers.

NEW

Model 3450
\$150

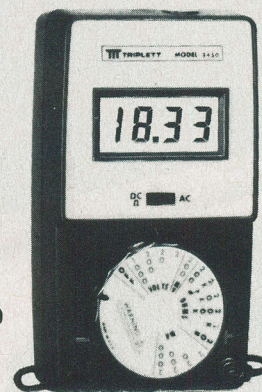

1. AUDIBLE CONTINUITY TONE plus actual resistance reading with no range change. Hi and Low Power ohms and single range switch.
2. OVERLOAD PROTECTION—Protected up to 1000 volts with special 2A/250V fuse arrangement; no nuisance fuse blows in volt and ohm ranges.
3. BATTERY LIFE—500 hour typical with 9V battery, display has low battery indication with 8 hours battery life remaining.

Contact your local Triplet Distributor or Factory.
Phone 419-358-5015, TWX 810-490-2400.

Triplet performance . . .
a tough act to follow

CIRCLE 47 ON FREE INFORMATION CARD


brushed-aluminum control panel and black-vinyl cover. All controls are on the front panel; coaxial connectors are SO-230, and porcelain feedthrough insulators are used for balanced line and single-wire inputs.



CIRCLE 155 ON FREE INFORMATION CARD

The *model PT-407* is priced at \$149.95.—**Palomar Engineers**, PO Box 455, 1924-F W. Mission Road, Escondido, CA 92025.

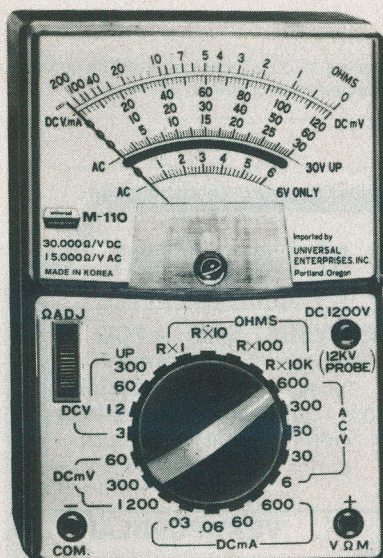MULTITESTER, *model M110*, has 21 ranges, designed for servicing electronic equipment, gas appliances, heating, air-conditioning, and refrigeration equipment. The ranges are specifically chosen to place most measurements near mid-scale. For example: mid-scale on the low-ohm range, 5 ohms, facilitates testing motor windings, relay, and contactor coils.



CIRCLE 156 ON FREE INFORMATION CARD


The *model M110* features a fuse-protected OHM circuit, mirrored scale-diode-protected movements, and easy-to-read three-color-coded scale plate and front panel. Accuracy specifications for the *model M110* are: DC, $\pm 3\%$ full-scale; resistance, $\pm 3\%$ of scale length; AC, $\pm 4\%$ full-scale. Input impedance is 30,000 ohms-per-volt DC; 15,000 ohms-per-volt AC.

The *model M110* is supplied with carrying case, test leads, batteries, and instructions, and is covered by a one-year warranty; the suggested retail price is \$44.95.—**Universal Enterprises**, 14270 N.W. Science Park Drive, Suite 101, Portland, Oregon 97229.

DIGITAL THERMOMETER, *model 871*, is an improved second-generation instrument that offers the versatility and performance of

laboratory-bench thermometers. It is designed for situations in which temperature is a critical concern, particularly in electronics design and manufacturing. The *model 871*'s dual-channel capacity is practical and convenient, allowing the user to monitor inlet/outlet temperatures, do wet-bulb/dry-bulb measurements, and check other situations where temperature differential is important.

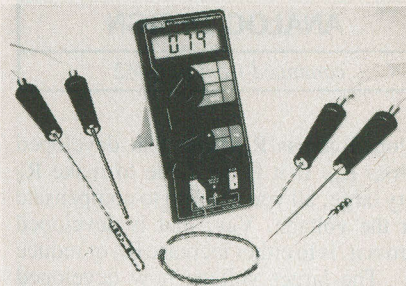
The *model 871* is supplied with a three-foot, beaded-junction sensor, so that the user may begin taking measurements at once; it is the only thermometer sold with a sensor. A broad selection of optional probes is available, and includes immersion, penetration, surface, air/gas, and hypodermic types to handle any application; custom and special-purpose probes may also be obtained.



CIRCLE 157 ON FREE INFORMATION CARD

The *model 871* is priced at \$225.00.—**Keithley Instruments, Inc.**, 28775 Aurora Road, Cleveland, OH 44139. R-E

Take a good look at VACO.

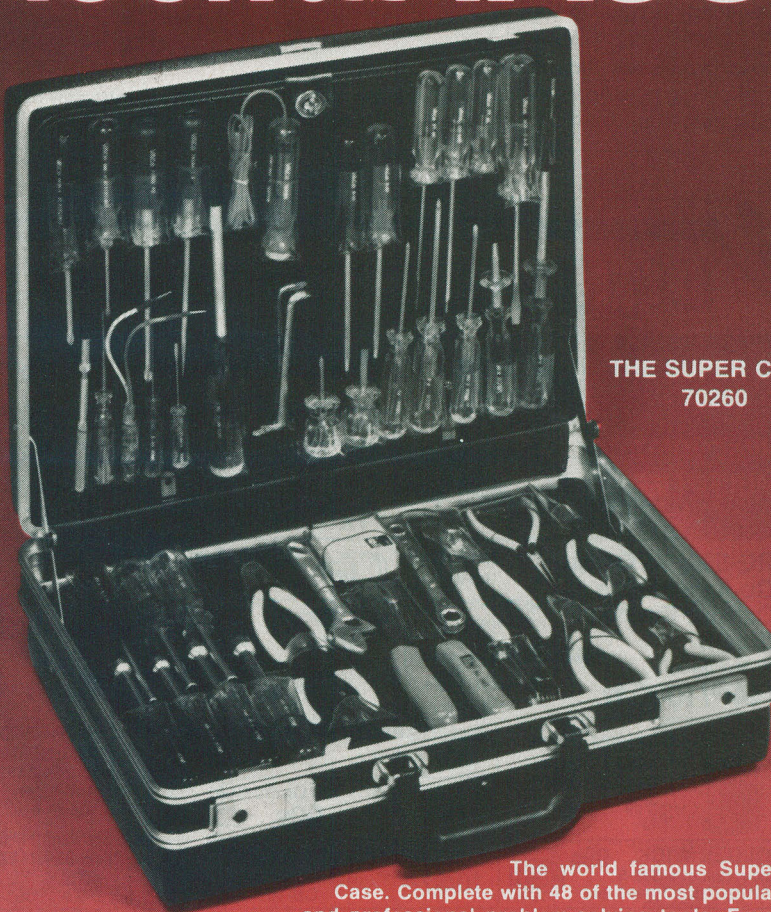

THE SUPER CASE
70260

The world famous Super Case. Complete with 48 of the most popular and professional problem-solving tools. From screwdrivers and nutdrivers to pliers, wrenches, crimping tools and more. A super variety and super value. All unconditionally warranted from Vaco, of course. The Super Case and all the other fine Vaco tools can be seen in our new 1982 catalog. It's free, just write. Say you want to take a good look at VACO.

Vaco Products Company, 1510 Skokie Blvd.
Northbrook, IL 60062 U.S.A.

VACO

CIRCLE 29 ON FREE INFORMATION CARD

ANALOG DESIGN

continued from page 62

veloped across R_G from that developed across R_S . If it is desirable to make R_S very large, all you need do to compensate for the voltage, V_{RS} , that is developed across it, is to either increase R_G or reduce R_X . The larger voltage now developed across R_G , subtracted from the increased voltage developed across R_S due to its increased value, establishes a reasonable negative bias voltage.

Before calculating the values of R_X and R_G , we should know what values of I_D and R_S are desirable. That can readily be done by averaging values that are found on the JFET's specification sheet.

First determine the average pinch-off voltage, V_P . It is midway between the maximum and minimum pinch-off voltages specified for the device.

In a similar fashion, calculate the average I_{DSS} , I_{DSS} , the drain current when $V_{GS} = 0$.

Finally, choose a reasonable value for an average gate-to-source bias voltage, V_{GS} . It frequently is equal to about $0.4 \times V_P$.

All those factors are then substituted into the following equation to determine the average quiescent drain current, I_D :

$$I_D = I_{DSS} \left(1 - \frac{|V_{GS}|}{|V_P|} \right)^2 \quad (17)$$

Absolute values of V_{GS} and V_P are used so that polarities can be ignored.

Now that we have determined I_D , we can turn our attention to establishing a relationship between R_S and V_G , the voltage between the gate and ground. It is:

$$V_G = I_D R_S - V_{GS} \quad (18)$$

We obviously want to make R_S as large as possible to improve stability, but there are some limitations. Voltages are developed across R_S and R_D due to the presence of I_D . When I_D is at its maximum,

the sum of the voltages across R_S and R_D should be several volts less than V_{DD} if the transistor is to operate in the pinch-off region. Hence $(R_S + R_D)I_D$ must be less than V_{DD} . The value of R_D is usually determined by other circuit requirements, so that limits the value of R_S . Once the maximum value for R_S has been determined, the value of V_G is found from:

$$V_G = \left(\frac{R_G}{R_G + R_X} \right) V_{DD} \quad (19)$$

But the values for R_G and R_X cannot be selected at random because of the presence of the leakage current, I_{GSS} . If ΔV_{GS} is the allowable bias voltage variation in the design, ΔI_D is the allowable drain

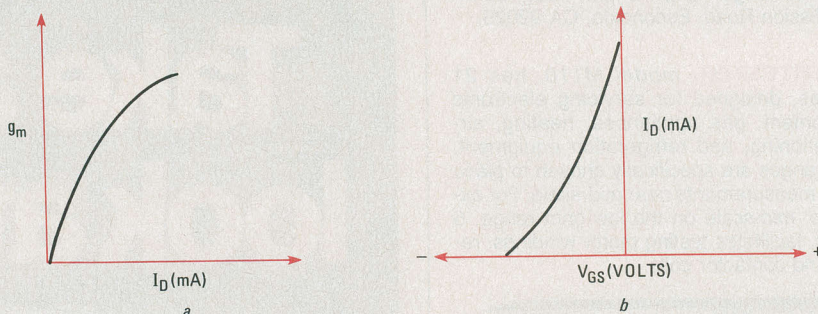


FIG. 9—THESE CURVES are extremely useful when designing MOSFET bias circuits. The curves for the device you are designing for can be found on that device's specification sheet.

OMNITRON: The Source for Quality at Low Cost

Silicon
H.V. Triplers

**HIGH VOLTAGE
MULTIPLIERS**



SYLVANIA Triplers

ECG-500A

212-139
212-139-01
212-139-02

\$12⁹⁵ ea.

ECG-523

212-141
212-141-01

\$15⁰⁰ ea.

ECG-526A

212-141-02
212-141-03
212-141-04

\$16⁹⁹ ea.


REMEMBER!
Sylvania
Tubes
70% + 10%
OFF
LIST

**Sylvania ECG
Replacement
Semiconductors
and Components**
Full line in stock.
The best quality
semiconductor.

**RG-59/U 75 OHM
Co-Axial Cable
Copper Braided
Shield**

White or Black

\$44⁵⁰/1000 ft.

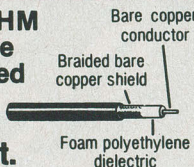

**F-59 Connector
with Separate Ferrule
10¢/100 lot**



**Matching Transformer
75-300 Ohm
59¢ ea. \$44⁰⁰/100**




**2 Way - 75 Ohm Coupler
MT-2 \$14⁹⁵ ea. \$89⁰⁰/100**



**2 SC1172B
\$1⁹⁹**

VERY POPULAR

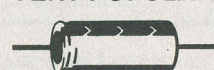

**80 MFD x 450 Volts... .99
100 MFD x 450 Volts... 1.09**

SOLDER (60/40 Rosin Core)
1 lb. - .062 dia.
(regular size)
\$7⁹⁹ SOL-1

SOLDER WICK 99¢
Solder Removal SW-5
1/4" Wide (Thick Type)-5 feet

SILICON RECTIFIER 2.5 Amp/1000 PIV
100/\$9⁹⁵ SL-100

GLOBAL DISC - 120 Ohms Cold
107191 RCA **99¢**

10 ASSORTED CIRCUIT BREAKERS
10/\$7⁹⁹ Good Assortment
CB-10

CHEATER CORDS
Polarized C Clip
Price: 39¢ 24620

Standard C Clip
Price: 39¢ 24623

REPLACEMENT RODS

4 Section LAR-4 **69¢**
5 Section LAR-5 **89¢**
6 Section LAR-6 **99¢**
7 Section LAR-7 **99¢**

G.E. OM-300

\$1⁴⁹
PANASONIC OM-500
\$1⁵⁹

OMNITRON
ELECTRONICS
770 Amsterdam Ave., New York, NY 10025

► Also ask for Free 100 Page Catalog ◀

Send Purchase Order, Check or Money Order
or Call Toll Free **800-223-0826**

in NY STATE (212) 865-5580

All ORDERS SHIPPED UPS/COD F.O.B., N.Y.C.

MASTER CARD • VISA

current variation, ΔI_{GSS} is the amount the leakage gate current changes over the operating temperature range, and R_S is the value of the source resistor, the parallel equivalent resistance, R_P , of R_G and R_X can be no larger than:

$$R_P = \frac{R_G R_X}{R_G + R_X} < \frac{\Delta I_D R_S - \Delta V_{GS}}{\Delta I_{GSS}} \quad (20)$$

Once you've calculated R_P , you can find R_G and R_X from:

$$R_X = \frac{R_P V_{DD}}{V_{GS}} \quad (21)$$

$$R_G = \frac{R_P V_{DD}}{V_{DD} - V_{GS}} \quad (22)$$

Substituting that information into equation 19, we can determine V_G .

Biasing MOSFET's

MOSFET gates are insulated from their substrates and channels. Because of that, the leakage current is much lower than the I_{GSS} of a JFET. Furthermore, this leakage current remains constant regardless of the MOSFET's temperature.

Leakage current was a very important factor in bipolar device designs because it affected the output current. Collector current increased rapidly with leakage current and temperature causing the temperature and current to keep rising until the transistor, in many instances, destroyed itself. As for the MOSFET, that is not a problem because the output current here actually drops as the temperature of the transistor rises.

As for bias voltage, no gate current other than leakage current flows regardless of the gate's polarity with respect to the source. Despite that, n-channel enhancement/depletion-type MOSFET's are usually biased so that the gate is negative with respect to the source. But they could, if desired, be biased so that the gate is positive with respect to the source. Enhancement-type devices, however, MUST be biased so that the gate is positive with respect to the source.

The circuits we used to bias the JFET, shown in Fig. 8, can also be used for biasing MOSFET's. There is one additional consideration, however. Some MOSFET's have a lead from the substrate. If that should be the case connect that lead to the source of the transistor.

Two curves, a plot of g_m vs. I_D and a plot of I_D vs. V_{GS} , are useful when designing MOSFET bias circuits; a typical example of each of those is shown in Fig. 9-a and Fig. 9-b, respectively. Be aware that those curves will, of course, vary greatly among different types of MOSFET's; the curves for the specific device you are working with will be found on the device's specification sheet.

For a specific V_{DS} , calculating the values for the circuit shown in Fig. 8-a is relatively easy if you follow these steps.

1. Determine the g_m required for the circuit being designed.
2. Extend a line from that point on the vertical (g_m) axis of the plot of g_m vs. I_D found in the device's specification sheet to the curve itself. Drop a vertical line from the intersection point to the I_D axis. Where that line crosses the I_D axis is the desired value of I_D .
3. Following a procedure similar to the one in the last step, use the value of I_D to find the desired value of V_{GS} from the plot of I_D vs. V_{GS} found in the device's


specification sheet. Once that is done, the values of I_D , V_{GS} , and V_{DS} are known.

4. Calculate R_S . For the circuit shown in Fig. 8-a, it is equal to V_{GS}/I_D .

5. As the voltage across R_D must be equal to $I_D R_D$, V_{DD} must be equal to $I_D R_D + V_{DS}$.

The design procedure is somewhat more complex when working on the bias network for the circuit shown in Fig. 8-b. Here, the bias voltage is the sum of the voltage across R_S , as just determined, and the voltage across R_G . If the voltage across R_G is to be positive with respect to ground, the voltage across the resistor can

continued on page 110

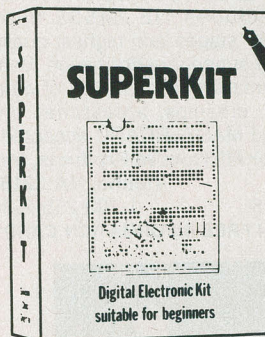

CAMBRIDGE LEARNING Inc.

A PRACTICAL DIGITAL ELECTRONICS KIT FOR LESS THAN \$40 ! Suitable for Beginners

ALSO AVAILABLE

We also have available 2 written Courses to complement SUPERKIT - Digital Computer Logic & Electronics and Design of Digital Systems.

--Digital Computer Logic & Electronics is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than simple arithmetic and no electronic knowledge is expected at all..... **\$14.95**

--Design of Digital Systems is written in the same question and answer style as Digital Computer Logic & Electronics but moves at a much faster pace and goes into the subject in far greater depth. Ideally suited to scientists or engineers who want to know more about digital electronics **\$19.95**

PHONE ORDERS - FREE

To order by phone, call (617) 664-3657 with your credit card information. It won't cost you a dime, because we'll deduct the cost of the call from the price of the Courses you order.

TO ORDER BY MAIL

You may use the order form below if you wish, but you don't need to. Just send your check or money order (payable to Cambridge Learning Inc.) to the address below. If you don't use the order form make sure you enclose your address and you specify which Courses you are ordering.

Mass. Residents and 5% sales tax. We pay all surface shipping costs.

Company Purchase Orders also accepted.

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

Seven LS TTL integrated circuits, breadboard, LED's, and all the DIL switches, resistors, capacitors and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only **\$39.95**. This course is for true beginners:

- Needs no soldering iron.
- Asks plenty of questions, but never leaves you stuck for an answer.
- Teaches you about fault-finding improvisation and sub-system checking.
- The only extra you need is a 4.5 volt battery or a stabilized 5 volt supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches Boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters and half adders.

Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

NO RISK GUARANTEE

There's absolutely no risk to you. If you're not completely satisfied with your Courses, simply return them in good condition to CLI within 30 days. We'll send you a full refund.

AIR MAIL

The prices shown include surface mail postage anywhere in the World. For Air-Mail shipment please write for additional cost, specifying Courses you will order.

CAMBRIDGE LEARNING Inc.

1 Judith Drive
North Reading,
MA 01864

(617) 664-3657

- Order free by phone
- Mastercard / VISA
- No shipping charges.
- Money-back guarantee
- Tax deductible


TO: Cambridge Learning Inc., 1 Judith Drive, North Reading, MA 01864

Please send me

SUPERKITS	\$39.95	\$
sets of Design of Digital Systems	\$19.95	\$
sets of Digital Computer Logic & Electronics	\$14.95	\$

Enclosed is check/money order for total \$
(payable to Cambridge Learning Inc.) Mass. Residents add 5% Sales Tax.

NAME
ADDRESS
CITY / STATE / ZIP

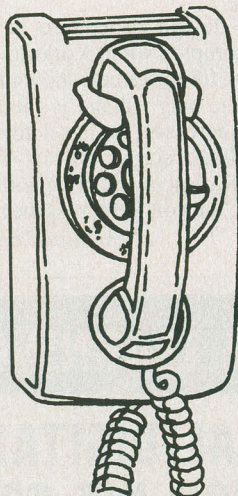


CALL NOW


AND RESERVE YOUR SPACE

- 6 x rate \$550 per each insertion.
- Reaches 220,500 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

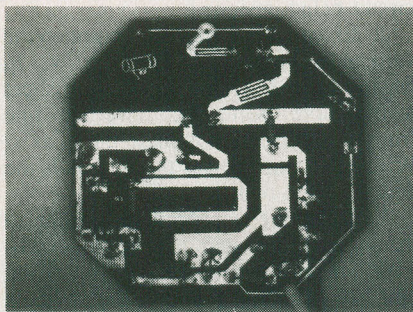
Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.




2300 MHz DOWNCONVERTER kit for Amateur microwave reception. \$37.95 postpaid. Includes NE 64535 high-performance RF stages and highest quality components for superior performance. Send SASE for information filled catalog of other converter kits, preamps, accessories and parts. VISA and MASTERCARD accepted. **SMP - Superior Microwave Products, Inc.** PO Box 1241 Vienna, VA 22180 1-800-368-3028 1-703-255-2918
CIRCLE 62 ON FREE INFORMATION CARD

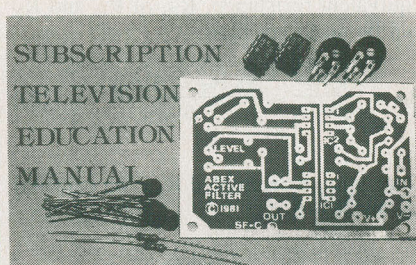

SUBSCRIPTION TELEVISION EDUCATION MANUAL includes detailed schematics, theory, and practices: \$14.95. **MICROWAVE TELEVISION EDUCATION MANUAL**: \$16.25. Both manuals only \$26.95. **15.7 KHz SINE WAVE ACTIVE FILTER KIT** includes parts and instructions: \$22.70. **INFORMATIVE CATALOG** on all VIDEO PRODUCTS, KITS, and MANUALS: \$2.00 (Refundable). Visa and MasterCard accepted. Add 5% shipping and handling.—**ABEX, P.O. Box 26601-RS, San Francisco, CA 94126.**
CIRCLE 65 ON FREE INFORMATION CARD

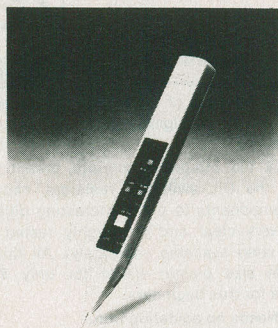

LPI-60, New, simple to operate **Logic Pulse Injector**. Tests digital IC's—TTL, CMOS, etc. Generates six kinds of pulse modes, two each in single pulse (**0.5μs/5μs**), pulse train (**10Hz/100Hz**), and pulse burst (**10/100 pulses**). **LPI-60 \$54.95** plus **\$3.45** shipping & handling. CHK, M/O. VISA & M/C (Calif add tax). Send for free catalogue of other products.—**MASCO ELECTRONICS P.O. BOX 45922, Los Angeles, Calif 90045.**
CIRCLE 63 ON FREE INFORMATION CARD

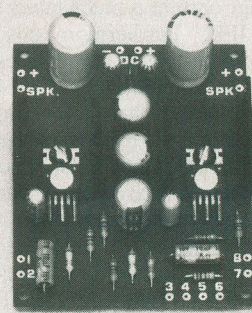

THE MS-15 Power Amplifier can be wired for either monoral or stereo. When hooked up to a Walkman AM-FM radio or any similar type of radio it will become a power-full Hi fidelity music system for the home, auto, van, or boat. It also makes a great P.A. system for schools, church or for out door use. \$19.50 check or money order. Satisfaction guaranteed.—**SPECTRUM PRODUCTS, P.O. BOX 8011, FOUNTAIN VALLEY, CALIF. 92708.**
CIRCLE 59 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 34

The **DR44-6** has a suggested retail price of \$2125.00.

DP4044 preselector

Enclosed in a matching 19-inch rack-panel metal enclosure, the **DP4044** Pre-selector features two-stage tuning accomplished by a concentric-control variable capacitor (dual section, 365-pF-per-section).

All RF coils are fully shielded. A 4-gang rotary switch selects the reactive components for each band within the 0- to 30-MHz range of the unit.

Both the input and output impedances of the **DP4044** are 50 ohms. The **DP4044** is not designed to match other impedances and may display insertion loss if the line impedance deviates from the nominal value.

We measured the insertion loss of the unit and it followed closely the specified table provided by the manufacturer, averaging 3 to 6 dB throughout the short-wave range. The loss becomes progressively greater at lower frequencies.


The RF selectivity is very sharp, requiring slight peaking every time the receiver is tuned more than a few percent past the peak position. The tuning range is continuous from 150 kHz through 30 MHz; the 0-150 kHz position is an untuned low-pass filter.

We found the **DP4044** to be quite effective in isolating discrete frequencies throughout its tuning range, although attention must be given to proper impedance-matching to avoid insertion losses. Users must remember that this is a preselector and *not* an impedance-matching antenna tuner.

As with all other passive preselectors, the user must not expect an increase in signal strength—only isolation of the frequency of interest. For that application, the **DP4044** works well. The **DP4044** has a suggested retail price of \$235.00.

The DS111 speaker

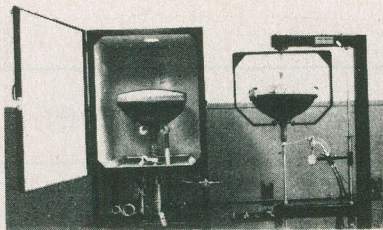
A companion matching speaker is also available; it includes several switch-selectable filtering combinations.



ONE MAN CRT FACTORY, easy operation. Process new or rebuild old CRT's for tv's, bus. machines, monitors, scopes, etc. Color, b&w, 20mm, foreign or domestic. 3x6 ft. space required. Profits??? Average CRT rebuilding cost — \$5. Sell for \$100 = \$95 profit; x 5 CRT's = \$475 daily; x 5 days = \$2375 weekly profit. Higher profits outside U.S.A. Investigate this opportunity today. We service the entire world. Write or call:

CRT Factory, 1909 Louise St., Crystal Lake, IL 60014, (815) 459-0666.

CIRCLE 67 ON FREE INFORMATION CARD

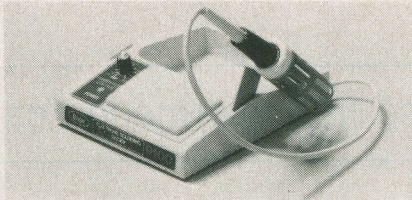


NEW UNGAR SYSTEM 9100...gives you a lower cost alternative for many applications requiring operator adjustable temperature control! 0.053 New, THERMO-DURIC 10eater element • Non-magnetic temperature control • Grounded • Interchangeable tips • Operator-adjustable 400°F-800°F Micro-handle, cool operation • U.L. Listed. Suggested Resale **\$91.00**. See your Ungar distributor or contact **Ungar Division of Eldon Industries, Inc., P.O. Box 6005, Compton, CA 90220, (213) 774-5950, (800) 421-1538.**

CIRCLE 68 ON FREE INFORMATION CARD




Make **professional** quality duplicates of your favorite (VHS, BETA) tapes with this **state-of-the-art** controller. Includes: **stabilizer**: defeats rolling **enhancer**: preserves picture detail at slow speed **RF converter**: simplifies real time viewing **distribution amp**: drive 3 VCR's **easy to build** kit lowest price **\$133.00** 206-693-3834 M/C, Visa order now save 10%.—Video Control Inc., 3314 H Street, Vancouver, WA. 98663. USA

CIRCLE 60 ON FREE INFORMATION CARD

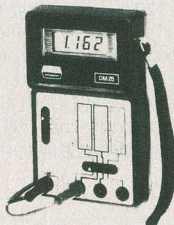


DM25 DIGITAL MULTIMETER, compact 3½-digit multimeter with basic accuracy of $\pm 0.2\%$ of f.s. Measures DC volts, 0.1V to 1,000V; DC current 0.1mA to 200mA; AC volts from 1V to 600V; resistance 1 ohm to 2 megohms. Features overload protection all ranges, fuse-protected current and resistance ranges, automatic zeroing and polarity, over-range and low-battery indication. Complete with test leads and carrying case, **only \$69.95. UNIVERSAL ENTERPRISES, INC., 14270 N.W. Science Park Drive, Portland, Oregon 97229, (503) 644-8723, Telex 15-1240 UEIPTLD PTL.**

CIRCLE 64 ON FREE INFORMATION CARD

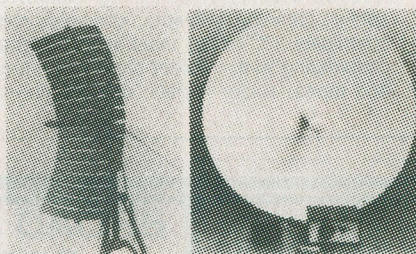

Amateur Microwave Systems—M-21 System: (left) 55 db gain, 36" parabolic antenna, microwave downconverter, aluminum die-cast case. **\$179.95** (regular \$199.95). **T-1 System**: (right) over 35 db gain, 22" parabolic antenna, microwave downconverter in probe. **\$129.95** (regular \$144.95) Send for free catalog. Dealer inquiries invited. **SRS, PO Box 50, East Detroit, MI 48021 (313) 791-5551. Visa and Mastercharge accepted.**

CIRCLE 66 ON FREE INFORMATION CARD

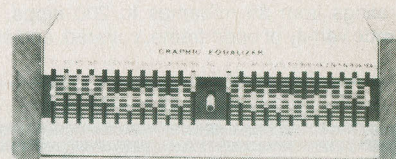

Still the best GRAPHIC EQUALIZER kit
* See **Radio-Electronics** 5/78 cover story
* 12 bands/channel - * .02% distortion -
* 92dB S/N ratio - * Solid walnut ends -
* Kit only \$100 postpaid via UPS

VISA, M/C add shipping, \$1 handling (303) 667-1662

Symmetric Sound Systems, 912D Knobcone, Loveland, CO 80537. Free catalog.

CIRCLE 61 ON FREE INFORMATION CARD

It is housed in a 10½-inch wide x 5-inch high x 6 ½-inch deep black and aluminum cabinet containing a 3 inch x 5 inch oval speaker. The **DS111** audio-processing speaker accessory features two front-panel controls; and on/off switch (switched off, the unit is simply disconnected; no external speaker jack is provided) and a rotary control with positions labeled **LOUDNESS/FLAT/SSB/CW/HI PASS/LO PASS**.

The speaker system is passive, designed around a tapped toroidal inductor that is used in combination with a series of four electrolytic capacitors. Because of the size of the windings on the toroid, very little insertion loss was noted.

In the **LOUDNESS** position, the bass and treble frequencies are passed, while mid-


range frequencies are attenuated. In the **FLAT** position, the internal speaker is connected directly to the audio-input terminals (a pair of spring-loaded push terminals on the rear apron).

The **SSB** position attenuates both bass and treble frequencies while passing the midrange frequencies. In the **CW** position, a narrow midrange (800 Hz) is passed, while bass and treble are rolled off more steeply than the **SSB** position.

The **HI PASS** and **LO PASS** positions provide bass and treble roll-off respectively.

The **DS111** is certainly useful, especially when used with a receiver's selectivity controls, but that is no substitute for good IF selectivity in a receiver. The **DS111** has a suggested retail price of \$85.00

R-E

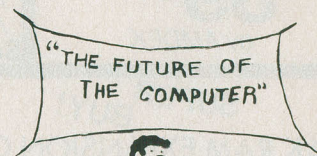

"My computer tells me that there is no future in artificial intelligence."

NEW LIT

For more details use free information card inside back cover.

COMPUTER BOOKS CATALOG is 28 pages in color, and is an up-to-date reference guide to all current editions of the wide range of books and software published by SYBEX.

Starting with books of general interest (*Your First Computer*, etc.) such areas as CP/M, Hardware, Pascal, Programs for Scientists and Engineers, 6502, Z80 and Z8000, and word processing are covered.

A special feature of the catalog is a listing of the nine languages that SYBEX books are translated into, and information on how to find foreign-language editions. The catalog is free upon request.—**SYBEX**, 2344 Sixth Street, Berkeley, CA 94710.

CIRCLE 141 ON FREE INFORMATION CARD

DC POWER-SUPPLY CATALOG is 36 pages and lists more than 250 different power-supply products that cover a range of 10 to 1,000 watts, 3 to 320 volts DC, and current ratings from 35 milliamps to 200 amps. A wide variety of open-frame, covered, and en-

capsulated power supplies used for nearly all electronics and electrical applications, such as microprocessors, computer peripherals, memories, terminals, mini-computers, and communications and general electronics applications. Switchers, linears, and unregulated circuits are also included in the line. The information includes specifications, weights, sizes, photos, dimensions drawings, prices, and electronic/electrical parameters. The catalog is free on request.—**Standard Power, Inc.**, 1400 So. Village Way, PO Box 15547, Santa Ana, CA 92705.

CIRCLE 142 ON FREE INFORMATION CARD


SOLDER CATALOG is eight pages in color, published by Multicore Solders, and illustrates their complete line of products: wire core solders; soldering fluxes; bar solder; cleaning solvents; special-purpose chemicals; PC-board fabricating materials; desoldering wicks; solder creams; preforms and tapes; solder resists, and Xerxin—the

new cost-effective chemical system that eliminates the need to clean PC boards. Free upon request.—**Multicore Solders**, Catiague Rock Road, Westbury, NY 11590.

CIRCLE 143 ON FREE INFORMATION CARD

MAIL-ORDER CATALOG is a fully illustrated, 104-page catalog, with many photographs in color. It offers more than 400 state-of-the-art electronics and mechanical kits for the home, hobby, or business. Products described relate to computers, energy-saving devices, satellite Earth-station technology, amateur radio equipment, hi-fi-stereo components, color TV's, marine and aviation gear, radio-control monitoring, test instruments, tools, video recording, solar power, and many more. In addition, over 30 self-instruction courses in electronics, computers, and programming are offered. The catalog is available, free, from **Heath Company**, Dept. 350-435, Benton Harbor, MI 49022. **R-E**

CIRCLE 144 ON FREE INFORMATION CARD

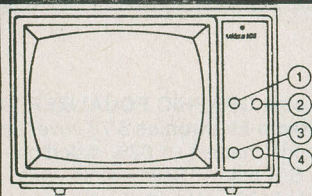

VIDEO 100
12" Black & White
MONITOR
\$89.50
by AMDEK

Fourth Dimension Systems FLOPPY DISK DRIVE FOR APPLE[®] COMP.

The unit features a track zero micro-switch and read/write electronics DOS 3.2.1., DOS 3.3, PASCAL or CP/M.

\$349.95

DISKETTES
5 1/4" BULK "OEM" PACK
FOR YOUR
APPLE
Box of 100 **\$149**

BROAD BAND MICROWAVE RECEIVER SYSTEM 1.8GHZ to 2.4 GHZ

only
\$295.00

RANGE: Line of sight to 250 miles.

SCOPE: Will receive within the frequency band from satellites, primary microwave stations, and repeater microwave booster stations.

CONTENTS: Packaged in 19"x19"x4 1/2" corrugated carton complete with:

- 24" Dish
- 300 Ohm to 75 Ohm Adapter
- Feed-Horn Receiver
- 75 Ohm to 300 Ohm Adapter
- Mounting Bracket
- 60 Feet Coax Cable with Connectors
- Mounting Clamp
- 3 Feet Coax Cable with Connectors
- Instructions

VISION-80[®] 80x24 Video Display Card **\$269**

Vista Computer Company's new Vision-80 board is a sophisticated yet easy to use video display card for the Apple[™] computer.

SUPER BUY!
16K RAM EXPANSION CARD
For Your APPLE[®]
LANGUAGE TRANSPARENT
ALL NINE RAMS INSTALLED!
\$79.95



TERMS OF SALE: Cash, checks, credit cards, C.O.D. Calif. residents add 6% sales tax.

"HAVE YOU KISSED YOUR COMPUTER LATELY"
Components Express, Inc.

1380 E. Edinger • Santa Ana, Calif. 92705 • 714/558-3972 TWX 910-595-1565

INTERNATIONAL FM-2400CH

FREQUENCY METER FOR MOBILE TRANSMITTERS/RECEIVERS

Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40MHz.

Frequency stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

• Tests Predetermined Frequencies 25 to 1000 MHz

• Pin Diode Attenuator for Full Range Coverage as Signal Generator

• Measures FM Deviation



FM-2400CH (meter only) \$690.49

RF crystals (with temp. correction) \$28.89 ea.

RF crystals (less temp. correction) \$21.92 ea.

IF crystals catalog price

Write for catalog



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee Oklahoma City, Okla. 73102

CIRCLE 49 ON FREE INFORMATION CARD

CASSETTE RECORDERS

continued from page 70

Normal tape movement, no audio

A Sanyo *M1000* cassette recorder ran nicely, but had no audio output. Rotating the volume control back and forth did not generate any sound from the speaker. A 1-kHz signal was injected at the volume control, but there was still no sound. Even when the signal was injected at pin 9 of the audio-amplifier IC nothing happened. An electrolytic coupling-capacitor was soldered to pin 13 of the IC and connected to an external speaker, but there was *still* no output.

Although the voltages at the IC were near normal, the IC was determined to be defective. Another LA4100 power-IC was installed and that solved the no-sound problem.

In summary, troubleshooting portable cassette-recorder/players is no different from working on other cassette players. You may find the components a little more compact and closer together but—then again—you may find fewer components to worry about. In fact, working with portable units can prove to be a pleasant diversion.


R-E

Remove Vocals

Remove the lead vocal and substitute your own voice with most stereo recordings using our new, low cost **VOCAL ZAPPER™**. Great for practice, professional demos or just for fun.

WITH THE

**VOCAL
ZAPPER™**

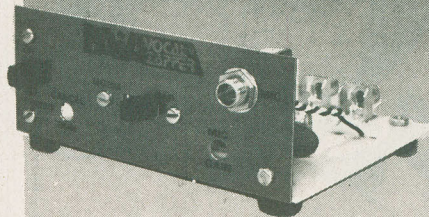

CHARGE TO VISA OR MC TOLL-FREE
1-800-654-8657 9AM to 5PM CST MON-FRI

DIRECT INQUIRIES TO:

PAIA Electronics, Inc.

1020 W. Wilshire, Oklahoma City, OK 73116 (405) 843-9626

- ☐ Rush my Vocal Zapper Kit, \$24.95 plus \$3 postage & handling enclosed.
- ☐ Send assembled Vocal Zapper, \$39.95 plus \$3 postage enclosed. ☐ Send Free Catalog

name _____


address _____

city _____ state _____ zip _____

PAIA Electronics, dept. 9R, 1020 W. Wilshire, Okla. City, OK 73116

CIRCLE 55 ON FREE INFORMATION CARD

An enclosure as good as your idea.

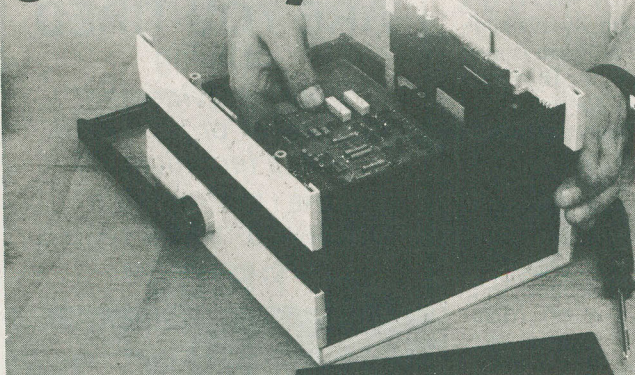

You've turned a good idea into a piece of equipment—now you need a good enclosure. Here's how PacTec can help you with our versatile enclosures:

- Attractive yet inexpensive.
- Durable ABS construction.
- Many sizes, colors, accessories.
- Built in bosses and slots speed component mounting.
- Available off-the-shelf from single unit to production quantities. **See them at your PacTec Distributor.** And ask him for your free catalog.




PACITEC™

Corporation
subsidiary of La France Corp.
Enterprise and Executive Avenues
Philadelphia, PA 19153 (215) 365-8400

CIRCLE 43 ON FREE INFORMATION CARD

VECTOR PROTOTYPING PLUGBOARDS FOR IBM* PERSONAL COMPUTER

New!

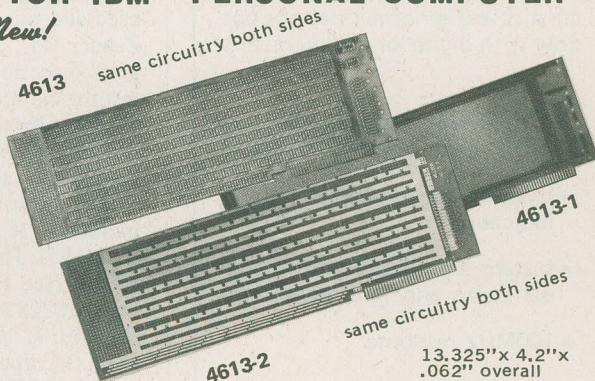

- Fit any slot in IBM Personal Computer
- 31/62 gold plated contacts on .1" ctrs.
- Tinned buses terminate to edge contacts per IBM standard

4613-1 -bare board with Peripheral Buses for unlimited component placement \$37.00

4613-2 -Wire Wrapping Bus Board with full power & ground plane. Plated thru holes \$59.00

- Punched universal I/O connector mounting bracket, card guide layout sheets, instructions included
- Accept any width DIP ICs
- .043" dia. drilled holes on 0.1" grid

4613 3-hole-Pads & Bus Board for soldering or wire wrapping. Plated thru holes. \$59.00

3690-22 -5.7"H x 3.2"W extender card with attached connector & mounting bracket, labeled test points \$22.35

*IBM Reg. T.M. of International Business Machines Corporation
Prices subject to change without notice

Vector Electronic Company
INCORPORATED


86827



12460 Gladstone AV
Sylmar CA 91342
phone (213) 365-9661

CIRCLE 48 ON FREE INFORMATION CARD

WINNER

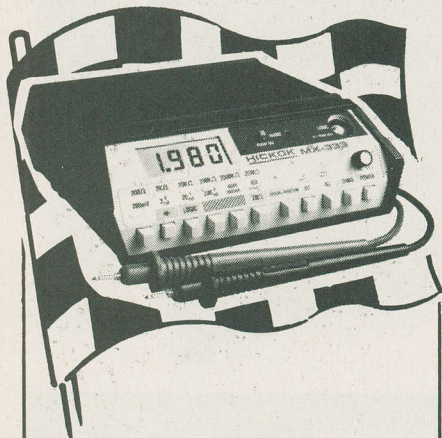

Hickok's MX333 with
VARI-PITCH® and LOGI-TRAK®

Instantaneous VARI-PITCH speeds:

- Voltage tracing
- Troubleshooting in hard-to-reach locations
- Tuning type adjustments
- Resistance checks
- Digital logic troubleshooting

And . . . Detects signal characteristics and abnormalities not possible with digital or analog meters.

LOGI-TRAK replaces the best 100MHz logic probes and offers:

- Eyes on the probe tip, HI/LO indication
- Instant identification of marginal states and fault conditions
- 100MHz response
- 5n sec pulse detection

LISTEN to what the MX333 can do for you. Ask about our NO RISK 30 day Free Trial.



THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060

COMPUTER CORNER

continued from page 82

suddenly switch to column A, row 3 if you need to access that information?

Can data be stored separately from the model? For instance, do you have to access the model itself in order to check the contents of row 5 (say that's for August), or can you access a separate file that will indicate the August sales?

Is there backup capability during the model-construction process? If a power failure or operator error occurs, will the entire model be lost, or is it backed up as it is created, so that only a small part of the work will have to be repeated?

Several computational features can make significant differences in the flexibility of your system. Are boolean-algebra functions (AND, OR, NOR, etc.) available for problems involving logic? Does the program allow for net-present-value computations that are often necessary in financial projections? For engineering and statistical projects, are roots and exponential functions available? Can the program compute percentages of increase; for instance, can it be determined that column A (sales for summer months), was 45% down from column B (October-December sales)?

All those features—and more—can be found among the various packages. You should investigate all the features offered by a package before committing yourself to it.

Where do you begin your search? The tried-and-true *VisiCalc* (VisiCorp, 2895 Zander Rd., San Jose, CA 95134) is a good place to start. Originally available just for the *Apple II*, the program is now available for the *Atari 800*, the *IBM Personal Computer*, the *TRS-80*, and *Hewlett-Packard* and *Commodore* systems.

If you are using *CP/M*, your choices include *T/MarkerII* (Lifeboat Associates, 1651 Third Ave., New York, NY 10028) (see Fig. 1), *Microplan* (Chang Labs, 10228 N. Stelling Rd., Cupertino, CA 95014), *MagiCalc* (Peachtree Software, 3 Corporate Square, #700, Atlanta, GA 30329), *SuperCalc* (Sorcim, 405 Aldo Ave., Santa Clara, CA 95050), *Multiplan* (Microsoft, 10700 Northrup Way, Bellevue, WA 98004), and *CalcStar* (MicroPro, 1299 4th St., San Rafael, CA 94901).

Phase One Systems (7700 Edgewater Dr., Oakland, CA 94621) produces *Masterplan*, a spreadsheet program to run under the *OASIS* operating system.

The business-software market has its share of programs for general ledger, accounts payable/receivable, and payroll. But financial-planning programs are in a class by themselves, providing a practical, time-saving service for the business environment.

R-E

PAT. # 4,259,705

WARNING!

Electric Power Pollution, Spikes, Interference & Lightning
HAZARDOUS to HIGH TECH EQUIPMENT!!



MicroComputers, VTR, Hi-Fi, Lasers, Spectrometers are often damaged or disrupted due to Power Pollution.

High Tech components may interact!

Our patented ISOLATORS eliminate equipment interaction, curb damaging Power Line Spikes, Tame Lightning bursts & clean up interference.

Isolated 3-prong sockets; integral Spike/Lightning Suppressor. 125 V, 15 A, 1875 W Total, 1 KW per socket.

ISO-1 ISOLATOR. 3 Isolated Sockets; Quality Spike Suppression; Basic Protection \$69.95

ISO-3 SUPER-ISOLATOR. 3 DUAL Isolated Sockets; Suppressor; Commercial Protection \$104.95

ISO-17 MAGNUM ISOLATOR. 4 QUAD Isolated Skts; Suppressor; Laboratory Grade Protection \$181.95

MasterCharge, Visa, American Express

TOLL FREE ORDER DESK 1-800-225-4876
(except AK, HI, MA, PR & Canada)

SATISFACTION GUARANTEED!

Electronic Specialists, Inc.

171 South Main Street, Natick, MA 01760

Technical & Non-800: 1-617-655-1532

ATTENTION TECHNICIANS

**ARE YOU TIRED
of being**

"only a serviceman"

or

"just a technician"?

THE LETTERS "CET
AFTER YOUR NAME SPELLS

"PRIDE"

TRY IT.

Take pride in
your profession—
Decide to be a CET



For information about: ☐ exam dates;
☐ requirements; ☐ study guides;
other _____

Send to: NESDA/IS CET
2708 W. Berry St.
Fort Worth, TX 76109
(817) 921-9101

Name _____

Address _____

City _____ St. _____ Zip _____

Put Professional Knowledge and a
COLLEGE DEGREE
 in your Electronics Career through
HOME STUDY

Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are *accredited* by the Accrediting Commission of the National Home Study Council.

Our *free* bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin R-82*.

Grantham College of Engineering
 2500 So. LaCienega Blvd.
 Los Angeles, California 90034

SEND FOR THIS
 FREE CATALOG NOW



SAVE MONEY
 HIGH QUALITY
 FAST DELIVERY

We are utilizing the latest equipment and our quality at reasonable prices.

JAN CRYSTALS

- General Communication
- Industry
- Marine VHF
- Scanners
- Amateur Bands
- CB Standard
- CB Special
- Microprocessor

Call or Write
JAN CRYSTALS

P.O. Box 06017
 Ft. Myers, Fl. 33906-6017
 All Phones (813) 936-2397

CIRCLE 56 ON FREE INFORMATION CARD

HEART RATE MONITOR

continued from page 48

you cannot divide by zero. When the Heart-a-Matic is first turned on, there is no guarantee as to what data will be present on the data bus. The 4508 that controls the bus at power-up will come up with data that seems to vary with the particular IC used. In a nutshell, there is no guarantee that there won't be all zeros on the data bus when the power is first supplied. The problem is resolved by IC22-e. It is configured as a half-monostable that outputs a pulse about one


and a quarter seconds long. The IC is connected, via diode D2, to the most-significant-bit on the data bus.

When power is first turned on, the output pulse insures that there is some number greater than zero on the bus. Without that half-monostable and the "Mickey Mouse Logic" (M²L) using D2, all zeros might appear and the Heart-a-Matic would try to divide by zero. If that happened, the batteries would give out before the answer showed up in the display.

The 12-volt power supply is made up of eight "AA" cells connected in series. Its output is fed to a standard 7805 regulator used in a slightly non-standard way. Be-

continued on page 113

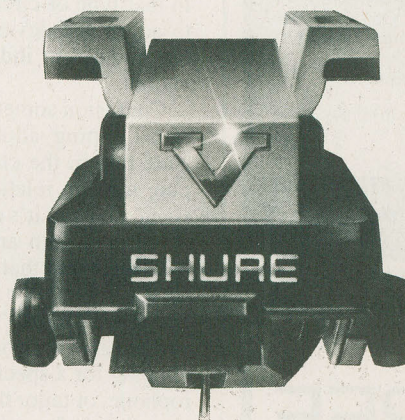**AUDIO CRITICS
 RAVE ABOUT THE
 V15 TYPE V:**



"Our tests show that the Shure V15 Type V not only lives up to the claims made for it, but in virtually every respect OUTPERFORMS the best cartridges we have previously tested....It is hard to imagine how the V15 Type V could be improved significantly. It offers the MOST PERFORMANCE in the most areas, plus the most convenience and safety in installation and operation." — **Julian Hirsch, Stereo Review, June, 1982**

"... (The V15 Type V) is definitely the FINEST pickup Shure has ever made, which makes it one of the finest ever made, period." — **High Fidelity, July, 1982**

"... In a world of audiophile discs with demanding tracking requirements, the Shure V15 Type V KEEPS AHEAD of the times." —

Rich Warren, Chicago Sun-Times, June 4, 1982

"(The V15 Type V) REDEFINES its maker as a pioneer in cartridge

design not only from the beginnings of micro-groove technology but well into the future of the LP disc." — **FM Guide (Canada), June, 1982**

"... It may be safe to say that this cartridge's excellent tracking ability is NUMBER ONE in the world. Provides exquisite and elaborate sound." — **Swing Journal (Japan), May, 1982**

Find out why the critics are so excited: Send for free fact-filled brochure AL694A.

SHURE®

Call for the name of the dealer nearest you
800-323-6556. Ask for Dept. R15.
 In Illinois: 800-942-6345. Ask for Dept. R15.

Shure Brothers Inc., 222 Hartrey Avenue, Evanston, IL 60204


CIRCLE 104 ON FREE INFORMATION CARD

OF THE EIGHT MAJOR
CAPACITANCE INSTRUMENTS
MADE, ONLY THE CM-100...

DETECTS LEAKAGE

(and at half the price!)

\$89⁹⁵

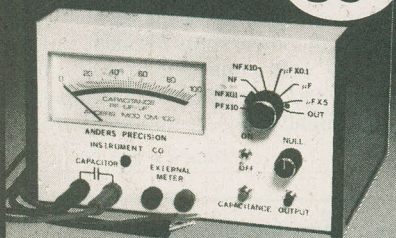

Usefulness — Measure capacitors 10pF — 500μF*, leakage 1 nA or .005 C.V., whichever is greater. **Accuracy** — To 2% depending on range. **Dependability** — Ruggedized construction; 1 yr. warranty. **Versatility** — In circuit measurement of capacitance and leakage. Output signal proportionate to measurement. **Portability** — 350 Hr. Battery Life.


*To 25,000μF with external voltmeter

Send check, address (NO P.O. BOX) plus \$3.50 Handling. CT res. add 7½% tax.

Phone orders: (203) 423-7940

ANDERS PRECISION INSTRUMENT CO., INC.
4 Bridge St. Plaza, P. O. Box 75 Willimantic, CT 06226

CIRCLE 52 ON FREE INFORMATION CARD

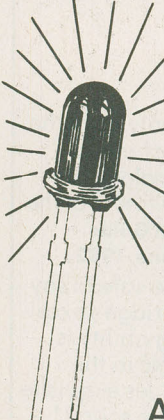

FREE 10 L.E.D.s

A \$2.00 VALUE

You can now receive ten prime T-1¾ or T-1 red LEDs absolutely free. It is our way of introducing you to the quality parts we offer.

ETRONIX

14803 N.E. 40th Dept. RE092
Redmond, WA 98052

Yes, Please send me 10 Free LEDs, plus your brochures on additional products available. I prefer ☐ T-1 ☐ T-1¾.

NAME _____

ADDRESS _____

CITY _____ ST _____ ZIP _____

Please include \$1.00 to help cover postage and handling.

RADIO-ELECTRONICS

110 CIRCLE 57 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER

continued from page 78

the volume level: The loud sounds are clipped, while the soft sounds are allowed to pass through unprocessed.

Clipping the audio waveform causes distortion, and results in the generation of odd-order harmonics. For example, if the modulating signal is 1.5 kHz, clipping will produce substantial output at the third harmonic of 4.5 kHz and the fifth harmonic of 7.5 kHz, which are outside the upper narrow-band FM limit of 3 kHz. A low-pass filter consisting of R2/R3 and C2/C3/C4 strips out everything above 3 kHz before the signal gets to the next modulation amplifier.

The output from the amplifier is fed to a potentiometer, R4, which serves as a "deviation" (modulation level) adjustment, and then on to a varactor diode that's connected to the master oscillator. In that type of circuit it's necessary only to adjust the deviation control until the test equipment indicates the desired deviation.

Confusion sometimes sets in if a separate clipping adjustment is provided. Note that in the circuit shown, the clipping level in relation to the microphone signal is fixed; it's established by the preamplifier's gain and by diode D1. You will often find that there's a gain control for the preamp, or a level adjustment between the preamp's output and the clipper; either way, you can set the degree of clipping for a specific level into the microphone, or tailor the clipping level to the voice level of a specific user. Just remember that the transmitter's deviation—the modulation of the RF signal—is set with a single control. **R-E**

ANALOG DESIGN

continued from page 103

be found using equation 19. Complications arise if that voltage must be negative with respect to ground. Now the upper terminal of R_X should no longer be connected to $+V_{DD}$, but is instead connected to a negative supply. That supply is called $-V_{GG}$. Equation 19 still applies, except that $-V_{GG}$ is substituted for V_{DD} . The values of R_X , R_G , and R_S are still found as outlined above for the JFET.

Transistor applications

From here on, we will concentrate on designing practical circuits that use bipolar and FET transistors. We will start with small signal audio applications and continue our discussion detailing high frequency circuits, feedback, and so on. Regardless of what type of circuit you are designing, you will need to apply the material we've detailed over the past two months if you are to be successful. **R-E**

GIANT HEAVY DUTY TRUCK TARPULINS

12 × 16	\$23	26 × 40	\$89
16 × 20	\$32	26 × 55	\$115
20 × 20	\$36	30 × 60	\$145
18 × 24	\$38	50 × 100	\$390
18 × 32	\$50	60 × 120	\$547
20 × 30	\$50	50 × 150	\$562

Before Midnight Oct. 17

Firestone Tarp Mfg. will send any of the above truck size tarpaulins to any reader of this publication who reads and responds to this test before midnight Oct. 17. Each tarpaulin Lot (#Z-18, PVC) is constructed of high density fabric (with virgin grade ingredient, supplied by Gulf Oil Co., Dow Chemical Co., and Union Oil Co.) with nylon reinforced rope hems, double lock stitched hems, electronically welded seams, 100% water proof, #4 (½" dia.) metal grommets set on 3 ft. centers with reinforced triangular corner patches and are recommended for all heavy duty use, and all bulk or pallet riding materials, and will be accompanied with a LIFETIME guarantee that it must perform 100% or it will be replaced free. Add \$7 handling & crating for each tarp ordered. Firestone Tarp Mfg. pays all shipping. Should you wish to return your tarpaulins you may do so for a full refund. Any letter postmarked later than Oct. 17, will be returned. LIMIT: Fifty (50) tarps per address, no exceptions. Send appropriate sum together with your name & address to: Tarp Test Dept. #496FA, Firestone Tarp Mfg., Inc., 6314 Santa Monica Blvd., L.A., CA., 90038, or for fastest service from any part of the country call collect, before midnight 7 days a week (213) 462-1914 (Ask Operator for) TARP TEST #496FA, have credit card ready.

CIRCLE 58 ON FREE INFORMATION CARD

COMPUTERS

Complete Microprocessors line, peripherals & Terminals.

Visicalc	200.00	SOROC IQ 130	590.00
Microsoft Z/80	320.00	TI-99/4A	279.00
IDS PRISM 80	call us	Epson MX-80	call us
IDS Prism 132	call us	Color Monitor	call us
Epson MX-100	call us	TI-810	1395.00
TI-745	1440.00	80 Column Board	245.00

Texas Instruments

Invest. Anal	\$ 42.00	TI-59	\$175.00
Accessories	Call us	TI-55 II	39.95
TI-58C	80.00	Speak & Spell	49.95
PC100C	155.00	TI Programmer LCD	54.95
TI BAIL	39.00	MBA	49.95

HEWLETT-PACKARD

HP/37E	72.00	HP-11C NEW	call us
HP-33C	85.00	HP-12C NEW	call us
HP-34C	115.00	HP-41C Mem Module	26.00
HP-38C	114.99	HP-67	295.00
HP-41C Prog	180.00	HP-97	570.00
HP-41CV	234.00	Quad Ram	call us
HP-41C Printer	285.00	Application Pac	call us
HP-41C CRD RDR	169.00	HP/83	1470.00
HP/85	1990.00	HP/125 Computer	call us

SCM TYPEWRITER SPECIALS

SCM 2200	\$284.00	INTREPID	\$274.00
SCM 2500	294.00	CLASSIC 12	164.00

All units shipped in original cartons with accessories according to manufacturer's specification. Send money orders, personal check 2 weeks to clear. In Illinois add 6% sales tax. Add \$6.95 minimum shipping & handling charges per unit. We ship UPS. Subject to availability. Written warranty for specific products can be obtained free upon request. Above prices are for mail order and prepaid only. Prices and specifications subject to change without notice. Send mail orders.

Nabik's, Inc.

519 DAVIS EVANSTON, ILL. 60201 TEL 312-869-6144

NEW BOOKS

For more details use free information card inside back cover.

FREQUENCY SYNTHESIZERS THEORY AND DESIGN (Second Edition) by Vadim Manassewitsch. John Wiley & Sons, Inc., One Wiley Drive, Somerset, NJ 08873. 582 pp including appendices and index; 6 1/4 x 9 1/4 inches; hardcover; \$36.00.

The original edition of *Frequency Synthesizers* was the first book to provide designers and users with a comprehensive treatment of the basic principles of synthesizer design, and an understanding of the problems often associated with it. This second edition is a significant expansion and updating of that volume. As with the first edition, this book recommends design procedures, provides useful design tools, and demonstrates the implementation of theory and circuit design with numerous practical examples.

Definitions and comprehensive descriptions of important concepts, such as phase noise and spurious outputs, and techniques for their analysis and measurement, are also provided. Detailed descriptions of some synthesizers are given to show the practical use of the design techniques that are presented in the text.

New to this second edition are two approaches—coherent direct digital synthesis and fractional-N phase-locked loop—in the chapter on frequency synthesis; updated test-equipment information; two new state-of-the-art synthesizers illustrating the application of design principles, and an entirely new chapter of troubleshooting techniques.

CIRCLE 111 ON FREE INFORMATION CARD

AMATEUR RADIO THEORY AND PRACTICE, by Robert L. Shrad-
er W6BNB. Gregg Division, McGraw-Hill Book Company, 1221
Avenue of the Americas, New York, NY 10020. 340 pp including
appendices and index; 7 1/4 x 9 1/4 inches; softcover; \$14.95.

For those who want to get an amateur-radio license, here is a complete beginner's text that requires of the reader no previous background in radio or electronics. It explains in simple terms all of the basic theory that is needed to pass any and all of the amateur-radio license examinations given by the Federal Communications Commission (FCC). This volume is also valuable for the licensed amateur as it contains much information that the amateur needs to know in order to operate a radio station and its equipment properly.

The first chapter discusses the scope of the Amateur Radio Service, the five grades of amateur licenses available, and some of the interesting phases of amateur radio that a license will allow one to enjoy. Chapters 2 through 20 present the basic electrical, electronics, and radio theory that should prepare the reader to pass any of the written license tests. Chapter 21 is a "how to" that outlines how the reader can learn to send and receive Morse code at the speed required for any of the amateur licenses. Chapter 22 contains a nontechnical condensation of many of the important amateur-radio rules and regulations that were not included in the earlier chapters.


Each chapter contains its main body of information plus a very

DISCOUNT TEST EQUIPMENT

LOWEST PRICES AND IMMEDIATE DELIVERY FOR OVER 40 YEARS

KEITHLEY


130

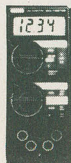

3 1/2 Digit • 5
Functions •
0.5% DCV
Accuracy

\$122

135

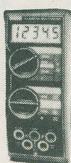


4 1/2 Digit •
0.05% DCV
Accuracy •
5 Functions

\$229

B & K


1405

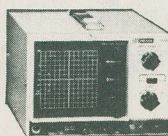

5 MHz 3" Scope •
10mV/Division Vertical
Sensitivity • More

\$285

1479BP

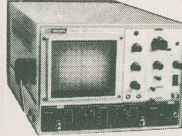

Dual Trace 30 MHz Trig-
gered • 11.7nS Rise Time
• 5mV/cm Vertical Sen-
sitivity • Probes • More

\$882.

FLUKE

8024B



3 1/2 Digit • 11
Functions •
0.1% DC Ac-
curacy •
Safety
Designed
Test Leads

\$229

8062A



4 1/2 Digit •
Full Func-
tions And
Ranges •
True RMS to
30 kHz •
0.05% DC
Accuracy

\$269

BECKMAN

TECH 310



3 1/2 Digit • 7
Functions •
29 Ranges •
0.25% DC
Accuracy

\$135

HD-100




3 1/2 Digit • 7
Functions •
29 Ranges •
0.25% DC
Accuracy •
Drop Proof •
Water Proof

\$162

LEADER


LBO 522

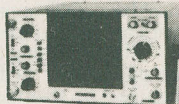

New Model • 20 MHz
Dual Trace • 0.5 mV Sen-
sitivity • More

\$740

LBO 524L

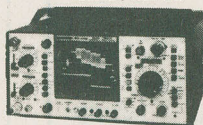

New Model • 35 MHz
Dual Trace • 0.5 mV Sen-
sitivity • More

\$1206

HICKOCK

LX303



3 1/2 Digit •
19 Ranges
And Func-
tions • Auto
Zero • 1%
DC Accuracy

\$91

LX304



All Features
of LX303 •
Auto Dec-
imal • Low
Battery In-
dicator •
Diode And
Transistor
Test

\$96

WM. B. ALLEN SUPPLY

1601 Basin Street, New Orleans, LA 70116



Over 70,000 electronic items
in stock for immediate delivery.



CALL TOLL FREE

800 535-9593

LOUISIANA TOLL FREE 800 462-9520

CIRCLE 22 ON FREE INFORMATION CARD




FREE!

**Introductory
OFFER-**




As an introduction to our fine line of deluxe soldering tool holders, EDSYN is offering the following FREE special. With the purchase of holder models IP289, B-170, or TL194, you receive at no further cost an Ersa® TIP 16 16W/115V soldering tool featuring mechanical temperature adjustment as well as two Loner® combination tip and nut wrenches.

IP289 idle-rest® SOLDERING TOOL POD

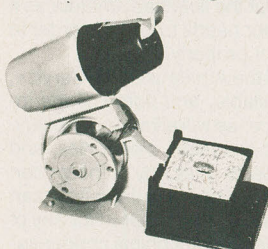

only with Ersa® TIP 16 and Loner® model soldering instruments.

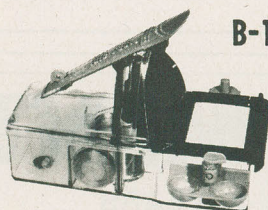
Internal construction with air vents keeps the temperature of the holder safe to the touch. Includes tip cleaning sponge and bench top mounting boss. Designed for use



B-170 Base 7 idle-rest®

thermal cover, sponge, cleaning basins, reservoir, and solder spool. Designed for use with Ersa® TIP 16 and all Loner® model soldering instruments only.

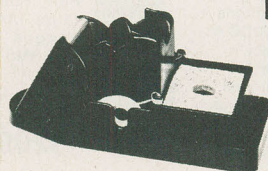Fully engineered soldering station designed with safety in mind. Numerous deluxe features include: safelock release, ther-



TL194 General Purpose idle-rest®

A complete soldering station containing: tip sponge, water reservoir, parts tray, roll of solder & wick. Suitable for bench mounting. May be used with most types of soldering tools.

For more information, see your local EDSYN Service Center distributor or call EDSYN at (617) 747-3346.

Send for **FREE WIGAPRY**™ on your company letterhead



and 70 Page FORM 325A **COMPLETE Catalog**



of **21st CENTURY Soldering Products**

EDSYN® SERVICE CENTER

65 COLUMBIA CIRCLE, PLYMOUTH, MASS. 02360 (617) 747-3346

GOOD TOOLS REDUCE

Unemployment Pools!

WORLD'S MOST PRACTICAL SOLDER HANDLING TOOLS

helpful checkup quiz, every few pages—answers to be found on the following page. And at the end of chapters, you will find representative questions listed under the five amateur-license grades.

CIRCLE 112 ON FREE INFORMATION CARD

PET BASIC: TRAINING YOUR PET COMPUTER, by Ramon Zamora, Robert Albrecht, and William Scarvie. Reston Publishing Company, Inc., Reston, VA 22090. 310 pp including appendices and index; 5 7/8 x 8 7/8 inches; softcover; \$12.95.

If you are a newcomer to the PET, you'll find that each chapter in this book has been written for those learning to use the PET. There are many examples, do-it-yourself exercises, and fun-filled explorations. The text will encourage the user to experiment and try out the numerous features and capabilities of the PET; it even shows how to create graphical images on the PET screen without difficulty.

For those who have been PET owners for some time, this book will prove to be a handy reference source, and a means of discovering new things that the PET can do. Each chapter includes a set of exercises for review that will help the owner to learn more, and develop greater skill in using that dynamic machine.

CIRCLE 113 ON FREE INFORMATION CARD

INTRODUCTION TO RADIO FREQUENCY DESIGN, by W.H. Hayward. Prentice-Hall, Inc., Englewood Cliffs, NJ 07632. 383 pp including index; 7 x 9 1/2 inches; \$27.95.


This book is designed for three specific reader groups: the working engineer, scientist, technician, or manager; the student of engineering or computer science, and the electronics hobbyist, including the radio amateur.

A central theme emphasized throughout the book is simplicity. More formal treatments of individual subjects are found in the references listed at the end of the individual chapters. Mathematics is used in the text as required to convey information to the reader.

The individual chapters cover: low-frequency transistor models, filter basics, coupled resonator filters, transmission lines, two-port networks, practical amplifiers and mixers, oscillators and frequency synthesizers, and the receiver: an RF system.

R-E

CIRCLE 114 ON FREE INFORMATION CARD

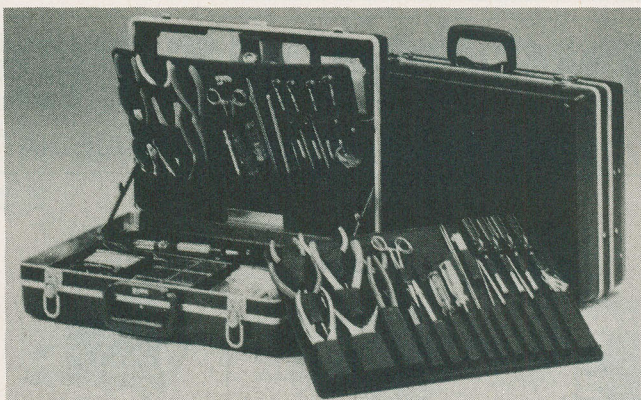

IT TAKES THICK SKIN AND GUTS TO MAKE A TOUGH TOOL CASE.

With rising production costs and smaller profit margins there must be a really strong commitment to excellence if superior tool cases are to continue being produced.

Platt is making this commitment. Their thick skinned tool cases are still made of the finest, high grade industrial materials. (Like durable ABS thermoplastic, for instance.)

Their guts still feature the industries only one-piece molded pallet.* There are no seams, stitches or rivets—the pockets can't tear loose.

And Platt has the only one year warranty on case and pallet.

So, contact Platt for complete information on their full line of tough, durable tool cases and your nearest distributor.

*Pat. No. 3,880,285

platt

Cases for business and industry.

2301 S. Prairie Ave., Chicago, Ill. 60616 (312) 225-6670

CIRCLE 41 ON FREE INFORMATION CARD

HEART RATE MONITOR

continued from page 109

cause R27 is placed on the ground leg of the regulator, we are able to trick the device into putting out six volts instead of the standard five. That operating voltage was chosen for the Heart-a-Matic to provide a compromise between battery life and reliable operation. The monitor draws an average of 60 milliamps during operation allowing long battery life.

A low-battery warning is provided by R47, Q3, and SCR1. The voltage at the base of Q3 determines the voltage drop

across R46. When it reaches a particular level, enough current will flow through the resistor to provide sufficient current to trigger SCR1. When the rectifier fires, the signal is routed to the decimal points of the display with the help of another bit of M²L logic, causing them to remain lit constantly. Diode D1 allows the beep generator to continue operating, and resistor R7 was chosen to make the decimal points light up much more brightly than they do during the heartbeat—so there will be no mistaking that the batteries are getting low and should be replaced.

The trip point of SCR1 is set with R47, a 500 kilohm multi-turn potentiometer.

Once the decimal points light, the SCR's latching action will keep them lit. Note that if the Heart-A-Matic is rapidly turned on, off, and back on again, the low-battery warning will appear. That's because C25 has not had time to discharge completely and the remaining charge fools the low-battery circuit into thinking that the batteries—not the capacitor—are not putting out enough voltage. A wait of about ten seconds is sufficient to prevent that from happening.

Now that we know how the Heart-a-Matic works, the next step is to build one. We will show you just how that is done in the next part of this article. **R-E**

TRS-80™ by RADIO SHACK - BUY DIRECT-DISCOUNT PRICES

VIC-20
The friendly computer

PURE RADIO SHACK EQUIPMENT - FREE COPY OF WARRANTY UPON REQUEST

SCM SMITH-CORONA

TOLL FREE 1-800-841-0860

TRS-80 Model II. From **'2988**
TRS-80 Model 16. From **'4158**
TRS-80 Color Computer. From **'299**
TRS-80 Model III. From **'609**
Centronics 739-1. **'469**

Smith Corona TP-1
Daisy Wheel Printer... '639
VIC-20 Computer..... '249



Thousands of Satisfied Customers Since 1978

TM - Tandy Corporation

WE CARRY THE FULL TRS-80 PRODUCT LINE
WRITE FOR FREE CATALOG
MICRO MANAGEMENT SYSTEMS, INC.

PARCEL DIVISION - DEPT NO.15


2803 Thomasville Road East

Cairo, Georgia 31728

GA. & INFO 912-377-7120

CIRCLE 42 ON FREE INFORMATION CARD

MICROWAVE TV CONVERTERS

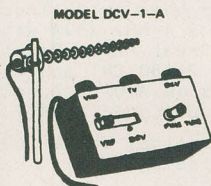

DOWN CONVERTER/ANTENNA COMBINATION

- 2 MICROWAVE PREAMP STAGES for maximum gain
- ONE PIECE CONSTRUCTION simplifies installation
- ALUMINUM AND ZINC PLATED STEEL for durability
- BUILT IN A/B SWITCH with more than 95dB isolation
- 2.1-2.6 GHz Covers all ham, commercial and ITFS channels

Years of enjoyment are yours with our model DCV-1-A. Two preamp stages coupled with the yagi antenna/housing provide a typical system gain of 53dB.

YOU GET: 75' downlead
3' jumper
300 ohm matching transformer
detailed instructions

ASSEMBLED & TESTED
LIST - \$175.00

ONLY \$149.95

INTRODUCTORY PRICE

WE CARRY A COMPLETE LINE INCLUDING PARABOLICS

DEALER INQUIRIES INVITED

TRITON
MARKETING CORP.

VISA, MASTERCARD ACCEPTED




679 REMSEN AVENUE
BROOKLYN, NEW YORK 11236

212-345-8000

CIRCLE 44 ON FREE INFORMATION CARD

ANNOUNCING . . .

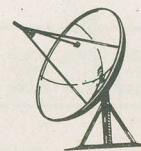

SATELLITE TELEVISION SYSTEMS

From

TRITON MARKETING CORP.

THE LEADER IN MICROWAVE ENTERTAINMENT DEVICES

COMPLETE SYSTEM PACKAGES

FOR HOME AND COMMERCIAL APPLICATIONS

DISTRIBUTORS OF QUALITY;

- | | | |
|------------|--------------------|---------------|
| ○ ANTENNAS | ○ REMOTE ACTUATORS | ○ ACCESSORIES |
| ○ LNA'S | ○ SMATV EQUIPMENT | ○ RECEIVERS |

We Invite Quotations for Export

TRITON
MARKETING CORP.

679 REMSEN AVENUE
BROOKLYN, NEW YORK 11236

212-345-8000

CIRCLE 45 ON FREE INFORMATION CARD

MARKET CENTER

SATELLITE TELEVISION

SATELLITE TELEVISION! Super discount prices. Don't spend too much—call us! **COMMUNICATIONS CONSULTANTS** 501-452-3149

SATELLITE TV antenna, 10 ft. fiberglass, complete, polar mount, \$1950.00, electronics at cost also. **TRI-STAR COMMUNICATIONS**, Box 843, Erie, MI 48133 (419) 726-1095

SATELLITE television ... Howard/Coleman boards to build your own receiver. For more information write: **ROBERT COLEMAN**, Rt. 3, Box 58-ARE, Travelers Rest, SC 29690

SATELLITE Super-Mixer: DBM-4150A. Clean up your TVRO receiver! Near theoretical performance; flat response, DC-1500IF SMA connectors; \$69.50—CK/MO/COD **RIGEL SYSTEMS**, 2974 Scott Blvd., Santa Clara, CA 95050 (408) 727-3628

LAST CHANCE for FREE \$200.00 value TVRO P.C. board set when you join our development group. Prices are going up. Build your own complete system low as \$700.00. Newest designs, group purchasing, etc. Aiming chart and data \$1.00. Construction plans \$10.00, membership \$50.00. PC board sets \$75.00. **COMPUTER SATELLITE SERVICES**, 1604 N Smith St., Spokane, WA 99207 (509)534-8088 6-9 PM PST

SATELLITE equipment catalog. Over 25 of the best manufacturers and suppliers. LNA's, receivers, antennas, and complete systems covered in four dif-

ferent sections. Free satellite aiming chart and microwave interference handbook (\$10.00 value) included. \$9.95. **TMS CO.**, P.O. Box 8369, Roseville, MN 55113

MICROWAVE TV downconverter, assembled and tested \$44.95, kit \$29.95, power supply kit \$29.95. Fully illustrated instruction manual included. Satisfaction guaranteed. Check, MO, COD. **XANDI**, Dept. 41, Box 25647, Tempe, AZ 85282

DRAKE satellite receiver with modulator installed only \$969.00. Satellite and microwave catalog \$1.00. **TEM MICROWAVE**, 22518 97th Ave. No., Corcoran, MN 55374 (612) 498-8014

SATELLITE TV
FANTASTIC 80 TV CHANNELS

New antenna construction plans plus big 8x11 book loaded with aiming info, kits, LNAs and receivers at wholesale prices. Far better than cable TV! Enjoy crystal clear reception. Send \$9.95 today. Add \$2.00 for 1st class (air mail) or call our 24 hr. COD order line (305) 862-5068 Now.

Global TV Electronics. P.O. Box 219-F, Maitland, FL 32751

SATELLITE TV WEEK

The most complete weekly listings. We cover more than just SATCOM 3. Send \$1 for sample copy.

Satellite TV Week

P.O. Box 308, Fortuna, California 95540

Call toll free: (800) 358-9997 • California (707) 725-2476

BUSINESS OPPORTUNITIES

LAWYER Business litigation, patents, appeals. **JEROME FIELD**, B 292, Brooklyn 11230. Phone (212) 434-0781. Eves. 434-1825

ASSEMBLE profitable devices at home. Exceptional opportunities—without investment. **ENTERPRISES**, 1133-R, Linwood Place, Utica, NY 13501

ATARI repair business. Start your own. Send \$5.00 for more information to: **IRATA REPAIRS**, 2562 East Glade, Mesa AZ, 85204

USED TV's—tougher the economy—more the demand. Get started in this lucrative part or full time business out of your own home. Complete details on how to buy, sell, price service tips, much more. \$5.00. **USED TV's**, Dept. RE, Box 19754, Indianapolis, IN 46219

PROJECTION TV ... Make \$200.00+ per evening assembling projectors ... Easy ... Results equal to \$2,500.00 projectors ... Your total cost less than \$15.00. ... Plans, lens & dealer's information \$14.00. ... Illustrated information free ... **MACROM-GAX**, Washington Crossing, PA 18977. Credit card orders 24 hours. (215) 736-2880

MAJOR Northern California electronic replacement parts retailer. Solidly established, high profit, recession resistant business. \$750,000.00 includes all assets, ten year lease, and flexible terms. **GBS**, Inc. agt. (916) 381-8020

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

HIGHLY PROFITABLE

ELECTRONIC

ONE-MAN FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do, **Barta-RE-X**, Box 248, Walnut Creek, CA 94597.

MAKE money selling electronics. Wholesale dealer catalog \$5.00 (redeemable). **ETCO**, Dept. 533, Box 840, Champlain, NY 12919

MAIL order—electronic components—well established high profit market. Start your own business. I have the expertise and working tools to send you on your way to an exciting future. For further details write to: **STAN L.**, 45 E. 17th St., Suite 1101, NYC, NY 10003

McKAY SETS THE STANDARD FOR COMPACT AM RECEIVING ANTENNAS

DA100D OUTDOOR ANTENNA and DA9-DL4 LOOP ANTENNA


For specs & details contact these dealers

HARVEY RADIO & BARRY ELECTRONICS New York City
HENRY RADIO Los Angeles, CA
GILFER ASSOCIATES Park Ridge, NJ
EDMOND SCIENTIFIC CO. B. rington, NJ
ELECTRONIC EQUIPMENT BANK Vienna, VA (D.C. Area)
PROMAR Tampa, FL
FRANK L. BEIER RADIO INC. Jefferson, LA
THE BASE STATION Concord, CA
J-MAR ELECTRONICS Toronto, Canada
INTERNATIONAL RADIO WORLD INC Vancouver, Canada

800/854-7769 Local • 714/621-6711
except Telex • 910-581-4990
Calif., Alaska, Hawaii

G. E. McKAY & CO.
111 S. College Ave.
PO Box 5000
Claremont, CA 91711

McKay
SINCE 1932

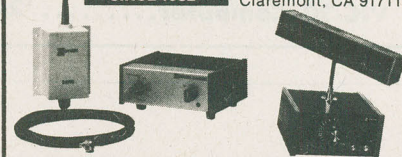

SAVE 90%

YES! you can save up to 90% on a computer for home or business \$150.00 buys a 4 MHz Z80A with 64KB & a real Front Panel \$200.00 for a 24x80 CRT and the list goes on—A/D, D/A, etc Send for **FREE BROCHURE** TODAY!

Digatek Corporation, Suite 160
2723 West Butler Drive
Phoenix AZ 85021

ROLL-YOUR-OWN TECHNOLOGY AND SAVE A BUNDLE

REVERBERATION FOR ORGANS

Solid state with controls for reverberation and room size.
EVERY ORGAN SHOULD OWN ONE. Send for free flyer—

DEVTRONIX ORGANS, INC.
6101 WAREHOUSE WAY
SACRAMENTO, CALIFORNIA 95826 Dept. B

Get active public service frequencies for your area covering police, fire, government, emergency, aircraft, amateur and more. Send \$2.00 along with your name and address, including zip code, to Betty Bearcat, c/o Electra Company, P.O. Box 29243, Cumberland, IN 46229.

DCE

SATELLITE — COMPUTER — TEST EQUIPMENT —

DISCRETE 70 MHz PLL — Replaces NE564 video demodulator without the need for an ECL divider. (70 MHz I.F.). Guaranteed tracking to 85 MHz. Wide bandwidth. Lower C/N, reduced "tearing." May be remotely tuned.

Kit (M82-010K) \$124.95
A & T (M82-010T) \$159.95

TUNEABLE AUDIO DEMODULATOR — Tunes from 5.4 to 8.2 MHz. Switchable 5 KHz LP filter for Canadian birds. Tuning diodes included. Two of these and a couple op-amps required for stereo. (MTV)

Bare Board (M81-020B) \$24.95
Two Boards (M81-021B) \$39.95

CANADIAN AUDIO DESCRAMBLER — Tune in those "chirping" sub-carriers and hear what you've been missing.

Bare Board (R82-010B) \$24.95
Kit (R81-010K) \$59.95
A & T (R81-010T) \$94.95

LO—OHMS ADAPTOR — Adapts normal VOM or DVM to measure from .001 ohm to 5 ohms using single 9-volt battery. Super simple calibrations.

Bare Board (M82-100K) \$14.95
Kit (M82-100K) \$29.95
A & T (M82-100T) \$49.95

MODEM — Bell 103 (300 bps) compatible Answer/Originate modem. No acoustic coupler required. RS-232 serial I/O.

Bare Board (R81-100B) \$24.95
Kit (R81-100K) \$69.95
A & T (R81-100T) \$99.95

All prices include complete and comprehensive documentation, postage and handling C.O.D. orders accepted. Call or write for catalog. Dealer inquiries invited.

DIGICOM ENGINEERING, INC.

P. O. BOX 1656, KODIAK, ALASKA 99615

907-486-5118 907-486-6215

OPEN 10 AM TO 8 PM PST

DESIGNS IN CONSUMER ELECTRONICS
DC TO LIGHT


SANYO
STK-0050
\$6²⁰

(Minimum 10)



SANYO
2SD613
70¢

(Minimum 10)

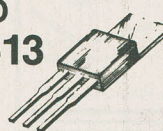

Matching XFMR
JB-300
44¢

(100-up)



Popular Diode
GH3F (for SONY)
95¢

(Minimum 10)



(The above special prices are effective until October 1, 1982)

semiconductors

Transistors				Diodes				Triacs				Thyristors				Relays				Misc.				Anisistors				Transistors				Diodes				Triacs				Thyristors				Relays				Misc.																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9	Part No.	30-90	10-29	1-9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
25A497	1.20	1.30	1.40	A908	7.00	7.40	7.80	B617A	1.80	2.10	2.30	C1312	2.50	3.00	3.50	C1915	.50	60	70	D2824	1.10	1.25	1.35	D904	3.90	4.30	4.60	D1012	30	35	40	D1048	30	35	40	D1061	1.10	1.30	1.50	D1062	1.40	1.60	1.80	D1077	65	80	90	D1111	80	100	120	D1112	80	100	120	D1113	80	100	120	D1428	80	100	120	D1429	8

PLANS & KITS

FREE catalog 99 cent kits. Buy 2 get 1 free. Parts, bargains galore. ALLKIT, 434 West 4th St., West Islip, NY 11795

PRINTED circuit boards from sketch or artwork. Kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

CABLE TV converters and equipment. Plans and parts. Build or buy. For information send \$2.00. **C & D ELECTRONICS**, PO Box 21, Jenison, MI 49428

LIGHTING display sequencers and controllers. Send SASE for information on plans, parts and consulting services. **DESIGN SPECIALTY**, 15802 Spingdale St. #80, Huntington Beach, CA 92649

SAVE steps, money. Use your telephones as an intercom. Plans \$5.00. **dB Enterprises**, Box 453R, Westwood, NJ 07675

SPIES like our antennas, so do HAMS and SWLs. **SDRE**, Box 242, Blacksburg, VA 24060 (703) 951-9030

CONVERT your \$2000.00 oscilloscope into a \$69.99 T.V. monitor. Super simple, fun, more practical than it sounds. Complete plans \$2.95. **Random Access**, Box 4177OR, Phoenix, AZ. 85080

MICROWAVE downconverter new 4 stage design outperforms all the others. Kit \$59.95. Assembled \$89.95. 6 month warranty. Bogner antenna \$31.95. System gainover 45 dB. \$2.00 for information. **MINI-ATURE COMMUNICATION**, P.O. Box 114, Cudahy, WI 53110

APPLE II compatible. Highly advanced MMS burglar alarm kit. Includes mil spec sensor, floppy software, interface PC boards, parts list, schematic, and instructions. \$199.50 introductory order CK/MO/COD. **RIGEL SYSTEMS**, 2974-R Scott Blvd., Santa Clara, CA 95050. (408) 727-3628

FREE 1982 catalog; components, kits, P.C. board materials, enclosures. **HAUCK ELECTRONICS**, 1928 Fairacres Ave., Pittsburgh, PA 15216

8085 SBC COMPUTER. Bare board with manual \$40.00, monitor ROM \$20.00, both \$55.00, manual

\$7.50. Requires terminal, power supply. Send SASE for brochure. **MINIMAL SYSTEMS**, P.O. Box 1064-R, Acton, MA 01720

36 CHANNEL CABLE CONVERTER FOR TV & VTR

\$29.95

6 or more 24.95 ea.



Call for free catalog 800-523-0721. Spectrum Electronics, 5932 Market St., Phila., PA 19139

MICROWAVE HORN ANTENNA KIT

1.7-26 GHz Frequency Range 17-19 lb Gain Kit w/Assembly Instructions \$39.95*
Down Converter Board \$19.95* (w/Antenna Kit \$14.95)
Parts Kit for Board \$29.95* (w/Antenna or Board \$24.95)
COMPLETELY ASSEMBLED AND TESTED SYSTEM \$129.95
(including power supply and cabling)
2.1 to 2.6 GHz Ant. - 34 db Gain (or greater)



MICROTEENNA ASSOCIATES

2335 South 2300 West, Salt Lake City, Utah 84119
Check or M.O. only — Allow 2-4 Weeks Delivery (Cost includes shipping)
*Utah Residents Please Add 5% Sales Tax

U.H.F. TV descrambler—cheapest, most superior design on market. Approximately \$20 worth of readily available parts, your old B&W TV and a basic knowledge of electronics necessary. Plans \$5.00. **RAMP ELECTRONICS**, 1500 Venera Ave., Suite 2-D, Coral Gables, FL 33146

SINE wave decoder problems? Solve them with essential information including trouble shooting, alignment, antenna hook-up, improvements. Manual; \$15.00. **SIGNAL PRESS**, Box 25 12-R, Culver City, CA 90230

TV educational book. Most complete book available. Theory of encoding and decoding, schematics, parts layout, construction tips, trouble shooting, alignment, etc. Retro-fit, sine-wave, bandpass filter circuit. Audio output through your TV circuit. Much more. \$50 value, just \$19.95 plus \$2.50 shipping. Internal and external **EDUCATIONAL KITS** AVAILABLE. **JIMCO**, Box 40443RE, Cincinnati, OH 45240

BRAINWAVE kits control electronic speech. **Music Robots. Newsletter. Catalog \$3.00. ROSE AIRCRAFT**, 269 Dahlia, I.B., CA 92032

PROJECTION TV... Convert your TV to project 7 foot picture. Results equal to \$2,500.00 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information **free**. Credit card orders 24 hours. (215) 736-3979. **MACROMGA**, Washington Crossing, PA 18977

MICROWAVE television "downconverters." Introducing powerful new 5-stage design. Easily assembled. Catalog: \$2.00 (refundable). **NDS**, Box 12652-R, Dallas, 75225

SUBSCRIPTION TV KITS

UHF Gated Pulse Kit...\$39.00

UHF Sinewave Kit...\$37.00

Kits include parts, manual and etched pc board.

Informative Catalog...\$2.00

J & W ELECTRONICS

P. O. BOX 61-B

CUMBERLAND, RI. 02864

THEY TALK - YOU LISTEN!
Improve your monitoring receivers with unique accessories. Preamps, descramblers, notch filters, active antennas, preselectors, multi-couplers, frequency lists, beam antennas and more.
FREE CATALOG FREE

GROVE ENTERPRISES, INC. Dept. J Brasstown, NC 28902

74LS SERIES

LS00	.24	LS125	.95	LS243	1.79
LS02	.24	LS138	.75	LS244	.95
LS04	.24	LS139	.75	LS245	1.89
LS05	.24	LS151	.75	LS257	.80
LS08	.24	LS153	.75	LS266	.49
LS10	.24	LS154	1.75	LS283	.95
LS14	.89	LS157	.75	LS290	1.20
LS20	.24	LS161	.95	LS293	1.79
LS27	.24	LS164	.95	LS298	.99
LS30	.24	LS166	1.95	LS367	.69
LS32	.36	LS175	.89	LS368	.69
LS42	.49	LS181	1.99	LS373	.99
LS74	.44	LS192	.89	LS374	1.69
LS85	.95	LS193	.89	LS377	1.40
LS86	.95	LS221	1.10	LS390	1.79
LS90	.65	LS240	.95	LS393	1.79
LS109	.39	LS241	.95	LS399	1.59
LS123	.95	LS242	1.79	LS670	2.10

ORDER TOLL FREE

(800) 538-8800

UPGRADE YOUR APPLE or TRS-80 4116 200ns 8/12.95

MICROPROCESSOR REAL-TIME CLOCK MSM 5832 7.25

IC Sockets	ST	W/W
8 PIN	.10	.49
14 PIN	.12	.50
16 PIN	.15	.57
18 PIN	.20	.85
20 PIN	.25	.99
22 PIN	.25	1.30
24 PIN	.25	1.40
28 PIN	.35	1.50
40 PIN	.40	1.80

ST = Solderetail

W/W = Wirewrap

Z80

Z80 A CPU	5.45
Z80 A PIO	5.45
Z80 A CTC	7.00

Call for Complete List

6500

6502	6.90
6502A	9.45
6504	6.90
6505	7.65
6507	9.90
6520	4.35
6522	9.90
6532	13.95
6551	11.75

DISKETTES 5 1/4"

ANTHANA SS SD Soft	23.95
WABASH SS SD Soft	23.95
VERBATIM SS SD Soft	28.95

MISC.

Disc Controller

1771	20.95
1791	34.95
1793	34.95
1797	49.95

Uarts

AY3-1014	5.85
AY5-1013	3.90
AY5-2376	12.00
TR 1602	4.25

Interface

8T26	1.65
8T28	1.95
8T95	.95
8T96	.95
8T97	.95
8T98	.95
DM8131	2.90
DS8836	1.25

16K APPLE RAM CARD

Upgrade your 48K Apple II to full 64K

BARE BOARD	29.95
KIT	59.95
ASSEMBLED & TESTED	79.95

VISIT OUR RETAIL STORE AND RECEIVE A 5% DISCOUNT!

CRYSTALS

32.768 KHZ	3.75	5.185	3.90
1.0 MHZ	4.50	5.7143	3.90
1.8432	4.50	6.5536	3.90
2.0	3.90	8.0	3.00
2.097152	3.90	10.0	3.00
2.4576	3.90	14.31818	3.90
3.2768	3.90	18.0	3.00
3.579545	3.00	18.432	3.00
4.0	3.00	20.0	3.00
5.0	3.00	22.1184	3.00
5.0688	3.90	32.0	3.90

CONNECTORS

RS 232	Male	3.00
RS 232	Female	3.50
RS 232	Hood	1.20

Call or write for prices on

8000, 6800, CMOS, Crystal, Linear, TTL, 74's.



Computer Products, Inc.

3250 Keller Street, #9

Santa Clara, CA 95050

(800) 538-8800

Calif. Residents (408) 988-0697




TERMS: For shipping include \$2.00 for UPS Ground. \$3.00 for UPS Blue Label Air. \$10.00 minimum order. Bay Area residents add 6 1/2% Sales Tax. California residents add 6% Sales Tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Send SASE for complete list.

ADVANCED COMPUTER PRODUCTS

SEND \$2.00 for 104 PAGE CATALOG

16K Apple™ Ramcard

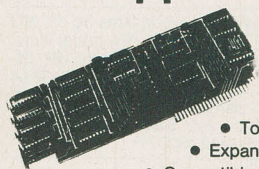

LIST 195
ACP
\$74.95

- Full 1 year warranty
- Top quality — gold fingers
- Expand Apple II 48K to 64K
- Compatible with Z-80 Softcard™
- Allows system to run with CP/M™, PASCAL, DOS 3.3, COBOL, Visicalc, etc.
- Supplied with extra 16K RAM & has (2) LED's

32K STATIC RAM



2 or 4 MHz
Expandable
Uses
2114's

16K 4 MHz Kit \$159.95
16K 4 MHz A&T \$179.95
32K 4 MHz Kit \$199.95
32K 4 MHz A&T \$219.95
BARE BOARD \$39.95
Bare Bd w/ all parts less mem. \$99.95

BARE BOARDS

S-100 Sound Board \$34.95
8080A CPU \$34.95
32K Static RAM (2114) \$34.95
8K EPROM (2708) \$24.95
2708/2716 EPROM \$34.95
ACP Proto Board \$22.95
Vector 8800 Proto \$22.20
Vector 8803 11 slot MB \$29.95
ACP Extender with connector \$18.95
3 Slot Mother Board (WMC) \$32.95
9 Slot Mother Board (WMC) \$29.95
8 Slot Mother Bd (Expandable) \$34.95
Floppy PCB (8" SHUGART) \$39.95
S100 (A55-8910) Sound Board \$34.95
Apple Sound Board \$24.95

UV "EPROM" ERASER



Model
UVs-11E
\$79.95
Holds 4 EPROM's
at a time
\$325.00

16K Memory Expansion Kits for Apple/TRS-80

8 pcs 4116 16K
200/250NS
Specify computer
\$12.95
CALL FOR VOLUME PRICING

"D" SUB CONNECTORS

Unreal price. DB37 male, DB25 female. Gold PC mount with mounting holes. Mfg. AMP. Specify 25 or 37 pins.

BD37 \$2.50 DB25 \$1.95

Stepper Motor

USED IN DATA PRODUCTS PRINTER
\$19.95 ea.


12 VOLT BUZZER/HORN

2" DIAMETER ALL METAL
2/\$1.99

GE D43C3

PNP power
HFE = 40-120
VCE0 = 30
IC = 3A
6,000 pcs available
69¢ ea.

Astec RF Modulator

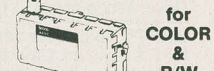

for
COLOR &
B/W

P/N 1082 Channel 3 or 4 \$6.95
P/N 4151 UHF Channel 33 \$8.95

MOSTEK 4K RAMS

29¢ ea.
200,000 pieces in stock — priced to move. Same as MK4027 except 1mS refresh. MK4015 4Kx1 RAM.

PMI "Super Beta" LOW POWER AMPLIFIER

INTERNALLY COMPENSATED
P/N OP12GJ
Voffset = 1.0 mV
Ibias = 5.0mA
Gain = 40V/mV (quantity limited)

4K STATIC RAM

10/\$9.90
Same as TMS4044 but designed specifically for Z-80 based systems. This is a full-spec 4Kx1 RAM, 450NS. Order P/N Zilog 6104-4 while supply lasts.

Zilog Z8 CPU with TINY BASIC

Debug prog. \$49.95
Plus 6132 companion quasi-static RAM 29.95

"BLINKER" LED's

LED's respond to sound. Complete, ready to wear. (2" x 2"). Sold at Nieman Marcus for 69.95. ACP \$49.95 red, yellow, green LED's

CONNECTORS

DB25P (RS232) \$3.25
DB25S Female 1.25
Hood 7.50
Set with Hood, Sale 2.95
43/86 S/T, MOT 6.50
50/100 S-100 Connector W/W 4.95
50/100 S-100 Connector S/T 3.95

Full ASCII Encoded Keyboards

128-Character, 58-Key Typewriter Format for Alphanumeric Entry

Full ASCII Encoded Keyboards

VP-606 Async serial output. Reg. \$99.00
ACP SALE ... \$69.95

MICROPROCESSORS

Z8001	\$99.00	8008-1	\$14.95	8002P	14.95
Z8002	99.00	2801	9.90	8003S	14.95
Z80	9.95	2801A	14.95	8039	12.95
280A	11.95	9900JL	49.95	8073N	34.95
P-8 (3850)	18.95	6502	9.95	87130	49.95
2950	16.95	6502A	18.95	8748	49.95
1802	9.75	IM6100	29.95	8809	30.00
8080A	4.75	8800	11.75	8086	49.95
8085	14.95	8800B	19.95	88000	129.95

RAMS

6116/2016	\$7.95	2147	\$5.99	5290	\$1.99
8254-64K	8.50	411	5.99	5298	1.49
4116-2	1.99	414	4.69	5501	4.50
4116-2	8/12.95	1101	99	6518	6.79
2101	3.99	1103	99	6561	3.79
2102	.79	4027	4.69	6804	3.99
21L02-2	1.49	4044	3.99	6805	7.99
21L02-4	1.29	4050	4.69	9130	8.99
2111	3.49	4060	8.99	9140	8.99
2112	3.49	4096	3.99	93415	6.99
2114	1.99	4115	1.49	93425	6.99
2114L-2	3.25	4200	7.95		
2114L-4	2.29	4402	1.99		
2125	6.99	5290	4.80		

SUPPORT

8155	\$9.95	8259	\$8.95	88047	\$22.95
8156	9.95	8275	19.95	88488	19.95
8202	29.95	8279	9.50	88505	22.95
8205	2.99	8281	4.75	88520	6.50
8212	2.75	8820	6.50	88522	9.95
8214	4.95	8821	6.50	88530-X	24.95
8216	2.75	8828	10.50	88532	17.95
8224	2.95	8834	16.95	88551	19.95
8226	2.95	8845	22.95	Z80-PIO	6.50
8228	3.95	8847	27.95	Z80A-PIO	9.50
8243	9.50	8850	5.25	Z80-CTC	6.50
8250	14.95	8852	5.25	Z80A-CTC	9.50
8251	6.50	8860	10.95	Z80-DMA	19.95
8253	11.95	8862	10.95	Z80A-DMA	27.95
8255	4.50	8867	5.95	Z80-SIO	24.95
8257	9.50	8880	2.49	Z80A-SIO	29.95

MOS PROMS

2764 (8Kx8) TS	\$69.95	2708 (450NS)	\$5.75
2732 (4Kx8) TS	12.95	2708 (650NS)	5.25
2716/2516, 5V	17.02A		
(2Kx8) TS	7.95	MM5203AQ	14.50
TMS2716, 5V, 12V	17.95	MM5204Q	9.95
2758, 5V, (450NS)	3.50		

HI-TECH

2513-001 (5V) Upper	\$9.50	DA0C8	\$9.95
2513-005 (5V) Lower	10.00	DA0C100	9.95
2513-ADM3 (5V) Lower	14.95	8038 Function Generator	4.50
MC1667 10 ASOI Shifted 1285		MC4024 VCO	2.95
MC1667 40 Multi-Symbol 1335		MC586 VCO	1.95
MC1667 50 Alpha-Cont 1345		XR2206 Function Generator	5.25
1771-01 8" & Miniloppy 24.95		TR16026 (5V, 12V)	3.95
1781 Dual Floppy	29.95	AY51013 (5V, 12V)	4.95
1791-01 Dual Floppy	36.95	AY51014/1612 (5-14V)	6.95
1791-02 Dual Floppy	44.95	AY51015/1863 (5V)	6.95
1793 DO, DS Floppy	44.95	IM6402	8.95
1797 DO, DS Floppy	44.95	IM6403	8.95
1691 Data Separator	18.95	2350 USRT	9.95
2143 Clock Generator	18.95	16718 Astros	24.95
8700 8 bit Binary	13.50	MC14411	11.95
8701 10 bit Binary	22.00	4762	14.95
8703 8 bit TS	13.50	WD1941	9.95
9400 Volt to Freq Conv.	7.25	CM5016	16.95
8750 32 Digit BCD	13.95	IN58250	15.95
1408L8 bit	3.95	AY5-2376	13.75
1408L8 bit	5.95	AY5-3600	13.75
DA0C10 D to A	5.95	MM5740AAC	8.95

SOCKETS

	1-24	25-49	50-100
8 pin LP	.16	.15	.14
14 pin LP	.20	.19	.18
16 pin LP	.22	.21	.20
18 pin LP	.29	.28	.27
20 pin LP	.34	.32	.30
22 pin LP	.29	.27	.24
24 pin LP	.38	.37	.36
28 pin LP	.45	.44	.43
40 pin LP	.60	.59	.58

LOW PROFILE SOCKETS (TIN)

	1-24	25-49	50-100
8 pin WW	.55	.54	.49
10 pin WW (Tin)	.65	.63	.58
14 pin WW	.75	.73	.67
16 pin WW	.80	.77	.70
18 pin WW	.95	.90	.80
20 pin WW	1.15	1.08	.99
22 pin WW	1.45	1.35	1.23
24 pin WW	1.35	1.26	1.14
28 pin WW	1.60	1.53	1.38
40 pin WW	2.20	2.09	1.89

3L WIREWRAP SOCKETS (GOLD)

	1-24	25-49	50-100
8 pin WW	.55	.54	.49
10 pin WW (Tin)	.65	.63	.58
14 pin WW	.75	.73	.67
16 pin WW	.80	.77	.70
18 pin WW	.95	.90	.80
20 pin WW	1.15	1.08	.99
22 pin WW	1.45	1.35	1.23
24 pin WW	1.35	1.26	1.14
28 pin WW	1.60	1.53	1.38
40 pin WW	2.20	2.09	1.89

Full ASCII Encoded Keyboards

128-Character, 58-Key Typewriter Format for Alphanumeric Entry

Full ASCII Encoded Keyboards

VP-606 Async serial output. Reg. \$99.00
ACP SALE ... \$69.95

LINEAR

78H05K	\$5.95	LM1414N	\$1.90
78M05	1.49	LM1458N/N	.39
78M.G.	1.49	MC1488N	.39
LM108AH	2.95	MC1489N	.89
LM300H	.99	LM1496N	.89
LM301CN	.35	LM1556N	1.50
LM304H	1.95	LM1820N	.95
LM305H	.89	LM1850N	.79
LM306H	3.25	LM1889N	3.10
LM307CN	.29	LM2111N	1.75
LM308CN	.99	LM2900N	.99
LM309K	1.49	LM2901N	2.50
LM310CN	1.25	LM2917N	2.95
LM311D/CN	.89	CA3013T	.29
LM312H	1.75	CA3018T	1.99
LM317T	1.70	CA3021T	3.49
LM318CN	1.49	CA3023T	2.99
LM319H	1.25	CA3035T	2.75
LM320T-XX*	.139	CA3140T	1.19
LM320H-XX*	1.25	CA3046N	1.29
LM323K	4.95	LM3053N	1.49
LM324N	5.95	CA3059N	3.19
LM327K	5.95	CA3080N	3.19
LM338K	6.95	CA3082N	1.49
LM339N	.95	CA3085N	1.49
LM340K-XX*	1.75	CA3087N	1.29
LM340T-XX*	1.25	CA3081N	1.69
LM344H	1.25	CA3082N	1.69
LM348N	1.20	CA3083N	1.55
LM350K	5.60	CA3086N	.95
LM358CN	.99	CA3089N	2.99
LM360N	1.49	CA3096N	3.49
LM372N	1.35	CA3097N	1.99
LM376N	3.75	CA3130T	1.30
LM377N	2.75	CA3140T	1.19
LM380CN/N	1.25	CA3146N	2.49
LM381N	1.79	CA3160T	1.19
LM383T	1.95	CA3190N	1.95
LM386N	1.25	CA3410N	.59
LM387N	1.40	SG3423N	.95
LM390N	1.95	SG3524N	1.49
NE531T	3.75	LM3900N	.59
NE555N	.39	LM3905N	1.19
NE556N	.99	LM3909N	.89
NE561T	19.95	LM3914N	3.75
NE565H/V	1.25	LM3915N	3.95
NE568H/V	1.75	LM3916N	3.75
NE567H/V	1.50	RC4131N	2.95
NE592N	2.75	RC4136N	3.75
LM702H	1.99	RC4151N	3.70
LM709N	.29	RC4184TK	4.95
LM710N/H	.75	RC4195TK	5.40
LM711N/H	.39	ULN2001	1.25
LM715N	1.95	ULN2003	1.50
LM722N/H	.65	SN75450N	.89
LM733N/H	.98	SN75451N	.35
LM739N	1.15	SN75452N	.49

Latest microstrip model of the "original"
MICROWAVE TV SYSTEM KIT

- LT-13 Down Converter with Preamp
- 16 dBi Slotted Antenna
- Deluxe Power Supply Kit
- All Coaxial Cables Included
- 2000 - 2600 MHz Tuning Range

LAB-TRONICS, INC.
P.O. Box 171
Rogers, MN 55374
612-428-4226

\$164.95
+ \$4.00 shipping

WRITE FOR
McGEE'S
SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS

Tel.: 1 (816) 842 5092
1901 MCGEE STREET KANSAS CITY, MO. 64108

FOR SALE

MICROWAVE receiver system. Write: "Dealers Wanted," Dept. RE, POB 4181, Scottsdale, AZ 85258 (602) 941-9395.

THE Intelligence Library. Restricted technical secrets—books on **electronic surveillance, lock-picking, demolitions, investigation**, etc. Free brochures: MENTOR, Dept. Z, 135-53 No. Blvd., Flushing, NY 11354

RESISTORS 1/4W, 1/2W 5% carbon films 3¢ ea. **NO MINIMUMS.** Cabinet assortments, 1% metal films. Request details. Bulk pricing available. **JR INDUSTRIES** 5834-C Swancreek, Toledo, OH 43614

SAVE up to 50% on name brand test equipment. Free catalog and price list. **SALEN ELECTRONICS**, Box 82-G, Skokie, IL 60077

CABLE TV converters, microwave antennas, cable parts, plans, parts and assembled units. For information send \$2.00. **SAT-TECH** P.O. Box 10026, Cleveland, OH 44110

32K color computers \$499.95. Extended BASIC ROM's \$85.00. **SPECTRUM PROJECTS**, 93-15 86 Drive, Woodhaven, NY 11421

UHF TV Yagi antennas. Channels 14 to 70. MATV MFR's discount. Catalog 50 ctns. **C.E.D.**, 24, High Range Rd., Londonderry, NH 03053

PICTURE tube rebuilding equipment—we sell and buy new and used equipment. Free training. **ATOLL TELEVISION**, 6425 Irving Park, Chicago, IL 60634, phone (312) 545-6667

FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95
Auto-Ranging Cap-meter kit \$79.95

Phone 415-447-3433

Write or Phone for FREE CATALOG.
Average 1 minute Saturday call is 21¢.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

PROFESSIONAL electronic devices, plans, kits, P.C. circuitry, famous drop in microphone cartridge, debugging equipment, more items available. For information send \$2.00: **MOUNTAIN ELECTRONICS**, R. 2, Box 186A, Charlotte, TN 37036

OCTOPUS circuit tester and oscilloscope with horizontal input troubleshoot circuits fast. Schematic \$1.50. **ADAMS. G.F.**, 1070 Easton Rd. #6, Roslyn, PA 19001

SUBSCRIPTION television educational manual. Complete theory and circuits, \$9.95. Parts and kits available. **D & S ENTERPRISES**, PO Box 110901RE, Nashville, TN 37210

PORTABLE digital capacitor meter with 1% accuracy range 1 pf to 10,000 µF. Uses readily available CMOS. IC's etched and drilled. PCB and plans \$14.95, calibration components included. **DRISCOLL ELECTRONICS**, 57 Scofield Ave., Bpt, CT 06605

TESLA coils: 100" arcs! Five plan manual \$15.00. Catalog \$1.00. **B&L SCIENTIFIC**, 215 West First, Suite 105-47RE, Tustin, CA 92680

EDUCATION & INSTRUCTION

DISCOUNT technical books, Sams, Hayden, TAB, and others, 15-30%, write **COMPUTERWARE**, Box 10070, San Jose, CA 95157

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D.'s...Free revealing details. **COUNSELING**, Box 317-RE9, Tustin, CA 92680

ATTENTION ELECTRONIC TECHNICIANS

Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year!

FREE DESCRIPTIVE LITERATURE!

Cook's Institute of Electronics Engineering
DESK 15, P.O. BOX 20345, JACKSON, MS 39209

Be an FCC LICENSED Electronic Technician

Earn up to \$600 a Week & More!
No costly course — The Original FCC Tests: Answers exam manual that prepares you at home for FCC General Radiotelephone License. Newly revised multiple-choice exams cover all areas tested on the actual FCC Govt exam! No previous experience required. \$12.95 post paid. Moneyback Guarantee.

Dept. E P.O. Box 26348, San Francisco, CA 94126

39⁹⁵ ADD \$2.50 FOR POSTAGE

30 CHANNEL CABLE TV CONVERTER

FREE! UNUSUAL 96 PAGE ELECTRONIC PARTS & IDEAS CATALOG!

ORDER No. 171AE047
ENCO ROUTE 9N,
PLATTSBURGH, N.Y. 12901
Tel.: (518) 561-8700.

VIDEO DISCOUNTS

TEKNIKA WIRELESS REMOTE CONTROL TV TUNER

\$110.00 ea.

REMOTE TV CONVERTER

Wireless Remote Control 40 Channels 4 or more

139.95 ea. **125.00** ea.

36 CHANNEL UP CONVERTER FOR TV & VTR Cable VHF to UHF

Model V5736
1-3 pieces **\$29.95** ea.
4 pieces & up **\$24.95** ea.

VIDEO SWITCHER

Model V 4801 **\$29.95** ea.
Flip a switch to watch a program on any channel, while simultaneously recording a program on any cable or pay TV channel - or vice versa. Plus, you can use your recorder's programming feature to record TV programs while you're away.


VIDEO CONTROL CENTER

Model IV 4802 **\$39.95** ea.
Provides remote control access of all your Video, TV or Cable inputs to your TV set or Big Screen TV from one convenient location by merely flipping a switch.

COAXIAL SWITCHING FOR TV VIDEO CASSETTE RECORDERS

Model AB-370 **\$6.95** ea.

3-position coaxial push-button switch.

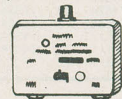

COAX AB SWITCHES


Model AB-27 **\$2.95** ea.
• Input: 75 ohm. • Output: 75 ohm.

Model AB-28 **\$2.95** ea.
• Input: 75 ohm.
• Output: 300 ohm.

Model AB-29 **\$2.95** ea.
• Input: 75 & 300 ohm.

ANTENNA/CABLE TV SWITCH

Model AB-400 **\$10.95** ea.

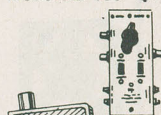

ANTENNA/CABLE TV SWITCH

Model AB-410 **\$9.95** ea.
• Switches from cable to antenna system instantly. • Accepts 75 or 300 ohm inputs.



TV GAME SWITCH

Model IV 450 **\$2.95**
300 ohm in and out with RCA plug.



COAXIAL SWITCH

Model DCS-A/B **\$7.95**
A versatile product, with a range of consumer and MATV applications.

VHF/FM AMPLIFIERS

Model 7002 **\$9.95** ea.
• All solid state signal amplifier boosts weak signals. For 2 sets.

Model 7004 **\$12.95** ea.
• For up to 4 sets • Signal gain 3 dB



DISTRIBUTION AMPLIFIER VHF/UHF FM
With FM Trap
Model DA-425 **\$29.95** ea.
• Designed for TV/VCR multiple-set installations.

QUICK CONNECT "F" PLUG & BALUN

Model IV 400 **\$1.50** ea.
10 for \$12.50

QUICK CONNECT "F" PLUG

Model IV 403 **.75**
10 for \$6.00
For 75 ohm cable. No wiring necessary.

QUICK CONNECT "F" PLUG RG 59U

Model IV 4036 **\$2.50** ea.
6 ft.

VHF/UHF MATCHING TRANSFORMERS

Model MT-1 **\$7.75** ea.
10 for \$6.00
VHF/UHF 75-300 ohm matching unit. Miniature size completely shielded and balanced for reduction of direct pick-up.

Model MT-2 **\$1.10** ea.
10 for \$9.00
Completely plastic molded construction for weather-proofing. Supplied with rubber boot.



FORDHAM
855 Conklin St. Farmingdale, N.Y. 11735

Master Charge
VISA
COD
Money Order
Check
\$25.00 minimum order
COD's extra (requires 25% deposit)

N.Y. State residents add appropriate sales tax.

ADD FOR SHIPPING AND INSURANCE
to \$250.00 \$4.50
\$251.00 to 500.00 6.00
501.00 to 750.00 8.50
751.00 to 1000.00 12.00
over 1000.00 12.50

TOLL FREE (800) 645-9518
in N.Y. State call (516) 752-0050

TTL 74LS SERIES

74LS00N	.22	74LS42N	.44	74LS138N	.55	74LS191N	.85	74LS283N	.84
74LS01N	.22	74LS47N	.72	74LS139N	.55	74LS192N	.74	74LS286N	.99
74LS02N	.24	74LS73N	.35	74LS148N	1.39	74LS193N	.74	74LS348N	1.65
74LS03N	.24	74LS74N	.32	74LS151N	.43	74LS194N	.74	74LS362N	1.95
74LS04N	.25	74LS75N	.45	74LS153N	.42	74LS221N	.89	74LS365N	.59
74LS05N	.25	74LS76N	.44	74LS155N	.87	74LS240N	1.19	74LS366N	.59
74LS06N	.25	74LS85N	.89	74LS157N	.88	74LS241N	1.19	74LS367N	.59
74LS08N	.25	74LS86N	.72	74LS158N	.58	74LS242N	1.19	74LS368N	.59
74LS10N	.24	74LS90N	.42	74LS160N	.79	74LS243N	1.19	74LS369N	.59
74LS11N	.28	74LS92N	.54	74LS161N	.75	74LS244N	1.25	74LS374N	1.96
74LS12N	.25	74LS93N	.54	74LS163N	.69	74LS245N	1.95	74LS375N	1.65
74LS13N	.36	74LS96N	.72	74LS164N	.58	74LS251N	.69	74LS377N	1.25
74LS14N	.48	74LS107N	.42	74LS165N	.89	74LS252N	.69	74LS378N	.99
74LS20N	.29	74LS112N	.36	74LS166N	1.84	74LS257N	.69	74LS390N	1.44
74LS21N	.27	74LS112N	.45	74LS170N	1.59	74LS259N	1.49	74LS393N	1.44
74LS22N	.25	74LS123N	.72	74LS171N	.72	74LS262N	.69	74LS447N	1.95
74LS23N	.34	74LS125N	.49	74LS174N	.44	74LS265N	1.19	74LS624N	1.58
74LS24N	.27	74LS132N	.58	74LS175N	.45	74LS279N	.44	74LS670N	1.36
74LS25N	.28	74LS133N	.49	74LS189N	4.45	74LS280N	1.96		

TTL 74F SERIES

FAIRCHILD ADVANCED SHOTTKY
The competition may be in short supply
but ACTIVE HAS THE STOCK!

74F00PC	.96	74F109PC	1.20	74F158PC	2.16	74F258PC	2.34
74F02PC	.96	74F111PC	.96	74F182PC	3.30	74F352PC	2.34
74F04PC	1.11	74F133PC	2.16	74F241PC	4.50	74F353PC	2.34
74F08PC	.96	74F157PC	2.16	74F373PC	5.25	74F374PC	5.85
74F10PC	.96	74F157PC	2.16	74F257PC	2.34	74F534PC	5.85

ACT NOW WHILE QUANTITIES LAST

CMOS

— CD4000 SERIES —

OVER 2 MILLION IN STOCK!
PLASTIC AND CERAMIC AVAILABLE
CHECK ACTIVE'S JULY AD FOR PRICES
WE WON'T BE UNDERSOLD.

LINEAR IC'S

301ATC	.34	348PC	.99	741TC	.28	3900PC	.59
307TC	.49	358TC	.45	747PC	.50	4136PC	.86
308TC	.59	380PC	1.25	1458TC	.29	4558TC	.86
309KC	1.35	393TC	.49	1488PC	.64	N8T26N	1.09
311TC	.49	555TC	.27	1489APC	.64	SN76477N	2.75
317KC	2.59	556PC	.88	2211PC	2.89	SN76489N	7.39
317UC	1.59	567TC	.89	22400PC	1.39	SN76489AN	5.29
318TC	1.39	723PC	.45	3081PC	1.09	ULN2003AN	.99
323KC	4.50	725TC	1.60	3086PC	.59	XR210CN	4.09
329PC	.48	733PC	.79	34023PC	.69	XR2206C	3.75
339PC	.48	741HC	.56	3403PC	1.19		

KC=TO3, UC=TO220, HC=TO5, TC=8 PIN MINI DIP, N or PC=DUAL IN LINE IC

DIODES AND RECTIFIERS

ZENER DIODES		SWITCHING DIODES		1 AMP RECTIFIERS	
IN746A	.12	IN3148	.05	IN4001	.05
IN759A	.12	IN4148	.05	IN4002	.06
IN524B	.13	IN4149	.05	IN4003	.07
IN500 MW	.17	IN4150	.05	IN4004	.08
IN4728A	.17	IN4151	.05	IN4005	.08
1 WATT	.32	IN4152	.05	IN4006	.09
IN4753A	.32	IN4153	.05	IN4007	.10
1 WATT	.47	IN4154	.05	IN4008	.10
IN5308	.47	IN4155	.05	IN4009	.10
5 WATT	.89	IN4156	.05	IN4010	.10
IN5308	.89	IN4157	.05	IN4011	.10
5 WATT	.89	IN4158	.05	IN4012	.10

SPECIFY EXACT P/N OR VOLTAGE

ACTIVE ELECTRONICS IS A DIVISION OF FUTURE ELECTRONICS, ONE OF THE WORLD'S LARGEST FRANCHISED DISTRIBUTORS. WE ARE THE SOURCE, THE UNIQUE SUPPLIER OF FACTORY FRESH, TOP QUALITY CURRENT PRODUCTION MATERIAL. OVER \$40 MILLION IN STOCK.

SCR'S and TRIAC'S

TIC45	SCR	6 AMP	60V	.54
TIC47	SCR	6 AMP	200V	.69
2N5064	SCR	8 AMP	200V	.29
TIC106D	SCR	5 AMP	400V	.49
TIC116D	SCR	8 AMP	400V	1.29
TIC116E	SCR	8 AMP	500V	1.89
TIC116M	SCR	8 AMP	600V	2.39
TIC126D	SCR	12 AMP	400V	1.48
TIC206D	Triac	3 AMP	400V	.89
TIC216B	Triac	6 AMP	200V	1.65
TIC216D	Triac	6 AMP	400V	1.96
TIC226D	Triac	8 AMP	400V	1.33
TIC226E	Triac	8 AMP	500V	1.55
TIC236D	Triac	12 AMP	400V	1.95
TIC246D	Triac	16 AMP	400V	1.84
TIC263D	Triac	25 AMP	400V	2.79

BRIDGE RECTIFIER'S

W02M	W06M
1.5 Amps	1.5 Amps
200V	600V
KBP02	KBP06
1.5 Amps	3 Amps
200V	600V
KBP08	KBP12
6 Amps	8 Amps
800V	1.95

PROGRAMMABLE UNIJUNCTION TRANSISTORS
375 Mw 40 VOLTS TO 92 CASE
2N6027 .49 2N6028 .59

BIFETS

TL061CP	.69
TL071CP	.68
TL072CP	.99
TL074CN	1.79
TL081CP	.59
TL082CP	.99
TL084CN	1.69
TL430CLP	1.09
TL497ACN	3.60

SPECIAL!!!

WHILE SUPPLIES LAST

1/2 AMP (Most probably higher)

TO220

Positive Voltage Regulators

5V .34 12V .34

6V .29 15V .34

MICRO COMPUTER SUPPORT CENTER

STATIC RAM'S

P2016-20	16K (2K x 8)	200NS 24 PIN	9.95
P2101-25	1K (256 x 4)	250NS 22 PIN	2.65
P2102-25L	1K (1K x 1)	250NS 16 PIN Low Power	1.59
P2112-25	1K (256 x 4)	250NS 16 PIN	2.75
P2114-20L	4K (1K x 4)	200NS 18 PIN Low Power	2.45
P2114-30L	4K (1K x 4)	300NS 18 PIN Low Power	2.20
P2147-055	4K (4K x 1)	55NS 18 PIN VERY SPECIAL	3.95
C2149-045	4K (1K x 4)	45NS 18 PIN Ceramic	9.95
P4315-45L	4K (4K x 1)	45NS 18 PIN (CMOS) Low Power	4.95
P5516-25L	16K (2K x 8)	250NS 24 PIN (CMOS) Low Power	19.95
P6116-15	16K (2K x 8)	150NS 24 PIN (CMOS)	17.95
P6116-20	16K (2K x 8)	200NS 24 PIN (CMOS)	15.95
P6514-45	4K (1K x 4)	450NS 18 PIN (CMOS)	4.65
P6504-20	4K (4K x 1)	200NS 18 PIN (CMOS)	2.95

DYNAMIC RAM'S

P4050-30	4K (4K x 1)	300 NS 18 PIN	3.65
P4060-30	4K (4K x 1)	300 NS 22 PIN	3.65
C4116-20	16K (16K x 1)	200 NS 16 PIN Ceramic	2.95
P4116-20	16K (16K x 1)	200 NS 16 PIN	1.95
P416-25	16K (16K x 1)	250 NS 16 PIN VERY SPECIAL	1.49
P4164-15	64K (64K x 1)	150 NS 16 PIN SPECIAL	14.95
P4164-20	64K (64K x 1)	200 NS 16 PIN	15.95

EPROM'S

C2708-45	8K (1K x 8)	450NS	24 PIN	5.95
C2716/-	16K (2K x 8)	450NS	24 PIN	5.95
TMS2516	Single 5 Volt Supply, Intel Pin Out			
C2516-35	16K (2K x 8)	350NS	24 PIN	6.95
	Single 5V Supply, Intel Pin Out			
TMS2716	16K (2K x 8)	450NS	24 PIN	9.95
	3 Power Supply, T 1 Pin Out			
C2532	32K (2K x 8)	450NS	24 PIN	12.80
	T 1 Pin Out			
C2732	32K (4K x 8)	450NS	24 PIN	12.80
	Intel Pin Out			

BIPOLAR PROM'S

6330/82523	32 x 8	Open Collector	16 PIN	2.45
6331/825123	32 x 8	Tristate	16 PIN	2.45
93417/825126	256 x 4	Open Collector	16 PIN	2.45
93427/825129	256 x 4	Tristate	16 PIN	2.45
27S29/28S42	512 x 8	Tristate	20 PIN	6.95
93453/825137	1024 x 4	Tristate	18 PIN	5.95
93451/825181	1024 x 8	Tristate	24 PIN	10.95
7128/27S185	2048 x 4	Tristate	18 PIN	13.95

MICROPROCESSOR CHIP SETS

6500 FAMILY

6502 CPU	6.95
6520 PIA	4.65
6522 VIA	7.95
6532 RIOT	10.85
6551	11.00

6800 FAMILY

6800 CPU	4.65
6802 CPU	7.95
6808 CPU	8.45
6809 CPU	13.95
6810 RAM	2.65
6821 PIA	2.65
6840	7.95
6845	16.50
6850 ACIA	3.15
6852	4.85

"6800 SALE" - 10% DISCOUNT ON \$100.00 or more order of 6800 Product

8080 FAMILY

8035	5.45	8224	2.95
8080A	4.45	8226	2.25
8085A	6.95	8228	4.65
8086	34.95	8251	5.95
80C35 CPU (CMOS)	11.25	8253	8.50
8155	9.00	8255	5.05
8212	2.25	8257	8.05
		8259A	7.50

AY3-1015A / S1602P

AY5-1013A

3.95

4.50

ECL RAM

10414DC / HM2510	5.95
256 x 1 BIT FULLY DECODED 15NS 16 PIN	

MISCELLANEOUS MEMORIES

93L422PC 1K (256 x 4) Low Power	14.95
TTL RAM Tristate	
93L422DC 1K (256 x 4) Low Power	15.95
TTL RAM Tristate	
93422DC 1K (256 x 4) TTL RAM	14.95
Tristate	
UPD4104C (4096 x 1) STATIC RAM	2.95
300NS Tristate	
Microprocessor Quartz Crystals	
Standard Frequencies and Packages	
1 thru 12 MHZ only	\$4.95 ea.

—SPECIAL— THE SIMPLE SOLUTION TO I.C. SELECTION 1982 I.C. MASTER

- Deluxe 3500 Page 2-Volume Set
- 55,000 I.C. Devices
- 150 Manufacturers
- 2400 Complete Data Sheets from 62 Manufacturers

Regularly \$82.50

Active's Super

Low Price

ACT NOW WHILE QUANTITIES LAST

OPTOELECTRONICS

L.E.D. Lamps

LED 209	T-1 3mm Red	.10
LED 211	T-1 3mm Green	.19
LED 212	T-1 3mm Yellow	.14
LED 220	T-1-3/4 5mm Red	.11
LED 222	T-1-3/4 5mm Green	.19
LED 224	T-1-3/4 5mm Yellow	.19

Displays

FND 357		1.29
FND 500/TIL 322		1.19
FND 507/TIL 321A		1.09
DL 707/MAN 72		1.19
DL 1416		
(4 Digit, 16 Segment Alpha Num.)		24.95
DL 2416		
(4 Digit, 17 Segment Alpha Num.)		27.95

Isolators

ILD 74 1.49	TIL 111 .51
ILD 74 2.60	4N 26 .51
ILCT 6 1.85	4N 33 .69
MCT 2 .52	

Refer to our previous AUGUST ad for other devices not listed here.

Active is your one stop source for the widest variety of electronic components. Contact us for devices not listed and for volume quotes.

Unless superceded next month, the prices will remain valid for 60 days.

UNGAR-PRINCESS LINE FOR MICRO SOLDERING

6976	10W, 3 Wire Iron	27.25	6960	Pencil Nib, Plated	2.04
6989	Solder Iron Holder	8.82	6961	Screwdriver Nib, Plated	2.04
6991	Refill Sponge for Holder	1.82	6962	Spare Nib, Plated	2.04
6990	10W Heat Unit	12.58	6939	Desolder Kit, 3 Tips	39.69
6915	15W Heat Unit	12.58	6943	Desolder Tip, 60 DIA	6.05
6903	3-Wire Handle	15.05	6944	Desolder Tip, 50 DIA	6.05
6950	Pencil Nib, Copper	1.10	6945	Desolder Tip, 375 DIA	6.05
6951	Spade Nib, Copper	1.10	6946	Desolder Tip, 180 DIA	6.05
6952	Spade Nib, Copper	1.10	6947	Desolder Tip, Slotted	6.05
6953	Precision Nib, Plated	2.04	6982	Dual-In Line Extractor	5.00
			982	T50 Extractor	5.00

KITS KITS KITS KITS KITS KITS

ELECTRONIC KITS

We have one of the largest selections of inexpensive electronic kits (over 60 available!) and we have been providing quality kits for over 10 years to thousands of schools, hobbyists and engineers worldwide. Remember, all of our kits contain all parts and quality PC board (no need to buy the PC board extra). Compare our prices, extra features and completeness—you won't find any other kits that compare!

ATTENTION DEALERS

We are looking for dealers to sell our line of kits. We provide liberal discounts and prices that beat any competition. Less than \$100 gets you started! Write or call for more information.

NEW

120VAC LIGHT SEQUENCER KIT


Great for discos, billboards, special effects, roof top Christmas displays, etc. This reliable IC and SCR kit sequences 10 outputs. The board has 10 output pads and each output pad can light up to 150 watts of 120VAC lamps (your choice) connected to it. Features variable speed and fused input. Kit comes with all parts, PC board and instructions. Size of board: 4" x 8". Operates from 120 VAC. C4725 \$19.95



NEW

10 NOTE SOUND SYNTHESIZER KIT

Very unique simple music synthesizer features 10 adjustable notes, variable pitch, variable speed, flashing LED and individual or flowing notes. Make "robot" sounds, space war computer effects, etc. One of the most unusual kits. Circuit features 3 IC's and 12 trimmer resistors. Complete with all parts, PC board and instructions. Size of board: 2.8" x 4". Operates from 9V battery (not included). C4722 \$11.95

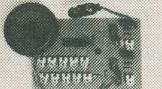

NEW

ELECTRONIC SLOT MACHINE KIT

Realistic action slot machine features sound effects, digital readouts and flashing LED. Has 3 different symbols that "roll" and "come up" one at a time. When all symbols are the same a special winner note sounds. Circuit uses 7 IC's and 12 transistors. Kit comes complete with all parts, PC board and instructions. Size of board: 5.5" x 7". Operates from 9V battery (not included). C4723 \$29.95



NEW

ELECTRONIC DIGITAL DICE KIT

Fun and exciting—this kit replaces conventional dice. Features bright jumbo LEDs and "roll" sound. Speed of roll is fully adjustable and dice stop individually! Circuit uses 4 IC's and 10 transistors. Kit comes complete with all parts, PC board and instructions. Size of board: 4" x 4.8". Operates from 9V battery (not included). C4724 \$15.95



P.O. BOX 27038
DENVER, COLORADO 80227
303 781-5750

Phone Orders
303 781-5750

- Minimum AD Order \$9.00
- Please include \$1.50 for postage (UPS)
- VISA MC accepted
- Phone orders are welcome

Send for our free catalog of unique items

CIRCLE 101 ON FREE INFORMATION CARD

Microwave TV antennas. Best in the West! Rod disc type. Complete with cable, accessories, warranty, 52 dB \$125.00. Dealers wanted. **GALAXY ELECTRONICS**, 6007 N. 61st Ave., Glendale, AZ 85301 (602) 247-1151

STAGGERED resistor assortment 1/4W 5% common values 40 each. Less common 10 each. 500 total \$10.00 **CI ELECTRONICS**, P.O. Box 3034, Camarillo, CA 93010

MAGIC TV machine. Amateur microwave receivers, 1 yr. warranty, \$99.95. **MICRO**, Box 3123, Temple, AZ 85281. We repair most brands of amateur microwave receivers.

MICROWAVE downconverters. Also UHF subscription TV kits. Catalog 20¢. **TROJAN ENTERPRISES**, 2920 Shelby, Indianapolis, IN 46203

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

FREE speaker catalog! Woofers, mids, tweeters, hardware, crossovers, grille cloth, plans, kits, information, much more. **Discount prices. UNIVERSAL SOUND**, Dept. RE, 2253 Ringling Blvd., Sarasota, FL 33577 (813) 953-5363

POLICE/fire scanners, scanner crystals, antennas, radar detectors. **HPR**, Box 19224, Denver, CO 80219

TRS-80 mod 3 cassette programs 16K mail-list and inventory list. \$14.00 each, \$20.00 both. Write **SUN MERCHANDISE COMPANY**, Dept. RE-1, 1739 Embassy Drive, Jacksonville, FL 32207

CABLE TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. Send \$7.95 to **CABLE FACTS**, Box 711-R Pataskala, OH 43062

LIQUIDATING \$100,000 inventory: speaker comes, gaskets, voice coils, spiders; also finished speakers, 50% - 75% below cost. Free list: **ISE**, 355 Cowan Terrace W, Brownsville, TX 78521

ANYTHING electronic located fast. Reliable service, details \$1.00. **SASE. W.K.M.** 212 N. Milton Ave., Baltimore, MD 21224

SUPER SALE

EPROM's

	1-7	8 up	50 up
2716 (5V, 450ns)	\$3.95	\$3.55	CALL
2732 (5V, 450ns)	7.85	6.95	CALL
2532 (5V, 450ns)	11.20	9.25	CALL

STATIC RAM

6116P-3 (150ns)	7.50	7.20	CALL
2114L-2 (200ns)	2.10	1.70	CALL

DYNAMIC RAM

4164 (200ns)	7.90	7.49	CALL
--------------	------	------	------

MISC

CPU Z80A	\$5.29 ea.
CDP-1854ACE (UART)	\$4.80 ea.
16K RAM Expansion Kit	
for TRS-80 Mod III	\$12.95/8



SUNTRONICS CO., INC.

12621 CRENSHAW BOULEVARD
HAWTHORNE, CALIFORNIA 90250

STORE HOURS: Mon.-Fri. 10am to 6:30pm - Sat. 10am to 5pm

IN CALIFORNIA OUTSIDE CALIFORNIA TOLL FREE

(213) 644-1149 1-800-421-5775

Min Order: \$10, P/H: \$2, Accept VISA, Mastercard, Check or M.O.

LATEST in video accessories!! Free shipping in U.S.A. Catalog \$1.00. **ELECTRONICS ET-CETERA**, P.O. Box 826-L, Solvang, CA 93463



MINI FM MIC

Compact size, only 2"x1"x3/4". Transmits to FM radio 88-108 MHz. Exceptional audio quality. Transmits stable signal up to 900 ft. Complete kit incl. case, battery & instructions. Only \$13.95. Assembled \$18.95. Add \$1.55 S&H ea. Send 20¢ stamp for brochure.

S.E. Corp., Box 1132-RE
Yorba Linda, CA 92686

COMPUTERS ATARI 800™ COMPUTER SYSTEM



400 w/16K \$350.00

800 w/16K \$699.00

*800 Computer w/48K

*BEST BUY \$825.00

ATARI PERIPHERALS:

Printer '825 - 650.00 Asteroids
Disk Dr '810 - 485.00 Missile Com. 32.50
Record '410 - 82.00 Sup. Brk. Out.
Paddle (pr) 16.95 Assem. Edit - 49.00
Joystick (pr) 16.95 Star Raiders - 45.00
32k RAM - 179.95 Basketball - 28.00
Basic Cart - 49.00 Chess - 32.00
Pac-Man - \$36.95

Diskette Storage BOX HARD PLASTIC

5 1/4 inch → \$2.95ea. (SRW)

8 inch → \$4.75ea. ☆

Bare Bones APPLE II

w/o Keyboard = 48K RAM =

\$450.

w/o Pwr. Supply

Microswitch: \$79.95
Power Supply: \$124.00
Apple Reference Manl.: \$18.00

* SPECIALS

3inch Mini FAN → \$8.95
2111 → \$2.45
8155 → \$11.50
ER2501 → \$4.95
AY5 1013A → \$2.95
8202 → \$28.95
6522 → \$5.25
2716(+5V) → \$4.50
2732 → \$8.95

8255 → \$5.95
7418-8 → \$31.00
MC6800 → \$7.75
MC6802 → \$14.95
MC6850 → \$4.50
MC6821 → \$4.95

8 Pos. DIP SWITCH
\$1.35ea.

'1982' IC MASTER
2 Vols.
\$59.95

Diskette SALE!! "Wabash"

5 1/4 8inch
SS/SD \$22.00 \$25.00
SS/DD 27.40 30.40
DS/SD 0 34.90
DS/DD 32.40 37.40

CONCORD COMPUTER PRODUCTS

1971 SO STATE COLLEGE
ANAHEIM, CALIF 92806
(714) 937-0637

*send \$1.00 for catalog
VISA MC CHECK M/O NO C.O.D.

\$10. MIN ORDER C.A.R.S. ADD 6

110 49 \$2.00 250 499 \$9.00
50 99 4.00 500 999 11.00
100 240 8.00 1000 UP CALL

MONITORS

ZENITH # ZVM-121
12in. 15MHz./GREEN Phos.
\$113.00

J.C.S.# KG-12
12in. 19MHz./GREEN Phos.
Non-Glare Screen **\$134.50**

BMC# BM-12A
12in. 15MHz./GREEN Phos.
\$95.00

AMDEK# CM-13 (COLOR I)
13in. /COLOR!!
\$375.00

REAL-TIME CLOCK CALENDAR (MSM 5832)

Description: Mono Metal Gate CMOS I.C.
Features:
Time, Month, Date, Year, &
Day of Week
Bus Oriented
4 Bit Data Bus
4 Bit Address
R/W Hold Select.
Inter Signal
32.768KHz. xtal Control.
5v Pow. Sup.
Low Power Dissipation

\$7.45

W/SPEC'S

XTAL

\$2.85


COMPONENTS

74LS00		74LS83		MISC	
74LS00	24	74LS83	70	8126	1.20
74LS02	24	74LS86	38	8128	1.20
74LS04	24	74LS90	85	8038	2.75
74LS05	24	74LS91	1.55	8080A	3.75
74LS08	24	74LS92	80	8155	10.50
74LS10	24	74LS93	60	8255	4.50
74LS12	32	74LS107	38	MC1330	1.65
74LS13	32	74LS109	38	MC1350	1.15
74LS15	32	74LS112	40	MC1358	1.50
74LS16	32	74LS113	40	MC1458	55
74LS18	32	74LS114	45	LM380	1.10
74LS20	32	74LS115	40	LM386	1.40
74LS21	32	74LS122	40	LM565	95
74LS22	32	74LS123	40	LM741	25
74LS23	32	74LS125	40	LM1310	2.90
74LS24	32	74LS126	40	LM1800	2.95
74LS25	32	74LS127	40		
74LS26	32	74LS132	70		
74LS27	32	74LS136	65		
74LS28	32	74LS138	65		
74LS29	32	74LS139	65		
74LS30	32	74LS145	1.10		
74LS32	32	74LS153	70		
74LS33	32	74LS154	70		
74LS34	32	74LS155	70		
74LS35	32	74LS157	70		
74LS36	32	74LS158	70		
74LS37	32	74LS159	70		
74LS38	32	74LS162	85		
74LS39	32	74LS163	85		
74LS40	32	74LS164	85		
74LS42	32				
74LS43	32				
74LS44	32				
74LS45	32				
74LS46	32				
74LS47	32				
74LS48	32				
74LS49	32				
74LS50	32				
74LS51	32				
74LS52	32				
74LS53	32				
74LS54	32				
74LS55	32				
74LS56	32				
74LS57	32				
74LS58	32				
74LS59	32				
74LS60	32				
74LS61	32				
74LS62	32				
74LS63	32				
74LS64	32				
74LS65	32				
74LS66	32				
74LS67	32				
74LS68	32				
74LS69	32				
74LS70	32				
74LS71	32				
74LS72	32				
74LS73	32				
74LS74	32				
74LS75	32				
74LS76	32				
74LS77	32				
74LS78	32				
74LS79	32				
74LS80	32				
74LS81	32				
74LS82	32				
74LS83	32				
74LS84	32				
74LS85	32				
74LS86	32				
74LS87	32				
74LS88	32				
74LS89	32				
74LS90	32				
74LS91	32				
74LS92	32				
74LS93	32				
74LS94	32				
74LS95	32				
74LS96	32				
74LS97	32				
74LS98	32				
74LS99	32				

7400		7454		74S SERIES	
7400	18	7454	19	74S00	35
7401	18	7455	20	74S01	35
7402	18	7456	21	74S02	38
7403	18	7457	22	74S03	38
7404	18	7458	23	74S04	45
7405	18	7459	24	74S05	45
7406	18	7460	25	74S06	45
7407	18	7461	26	74S07	45
7408	18	7462	27	74S08	45
7409	18	7463	28	74S09	45
7410	18	7464	29	74S10	45
7411	18	7465	30	74S11	45
7412	18	7466	31	74S12	45
7413	18	7467	32	74S13	45
7414	18	7468	33	74S14	45
7415	18	7469	34	74S15	45
7416	18	7470	35	74S16	45
7417	18	7471	36	74S17	45
7418	18	7472	37	74S18	45
7419	18	7473	38	74S19	45
7420	18	7474	39	74S20	45
7421	18	7475	40	74S21	45</

ramsey

the first name in Counters !

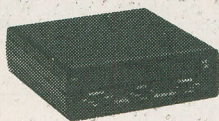

PRICES:
CT-90 wired, 1 year warranty \$129.95
CT-90 Kit, 90 day parts warranty 109.95
AC-1 AC adapter 3.95
BP-1 Nicad pack + AC Adapter/Charger 12.95
OV-1, Micro-power Oven time base 49.95
External time base input 14.95


9 DIGITS 600 MHz \$129⁹⁵ WIRED

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include; three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10MHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range: 20 Hz to 600 MHz
Sensitivity: Less than 10 mV to 150 MHz
Less than 50 mV to 500 MHz
Resolution: 0.1 Hz (10 MHz range)
1.0 Hz (60 MHz range)
10.0 Hz (600 MHz range)
Display: 9 digits 0.4" LED
Time base: Standard-10.000 MHz, 1.0 ppm 20-40°C.
Optional Micro-power oven-0.1 ppm 20-40°C
Power: 8-15 VAC @ 250 ma

7 DIGITS 525 MHz \$99⁹⁵ WIRED

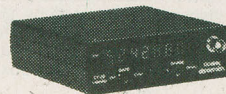


SPECIFICATIONS:

Range: 20 Hz to 525 MHz
Sensitivity: Less than 50 mV to 150 MHz
Less than 150 mV to 500 MHz
Resolution: 1.0 Hz (5 MHz range)
10.0 Hz (50 MHz range)
100.0 Hz (500 MHz range)
Display: 7 digits 0.4" LED
Time base: 1.0 ppm TCXO 20-40°C
Power: 12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as; three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

PRICES:

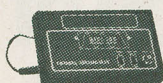CT-70 wired, 1 year warranty \$99.95
CT-70 Kit, 90 day parts warranty 84.95
AC-1 AC adapter 3.95
BP-1 Nicad pack + AC adapter/charger 12.95



7 DIGITS 500 MHz \$79⁹⁵ WIRED

PRICES:

MINI-100 wired, 1 year warranty \$79.95
AC-Z AC adapter for MINI-100 3.95
BP-Z Nicad pack and AC adapter/charger 12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

SPECIFICATIONS:

Range: 1 MHz to 500 MHz
Sensitivity: Less than 25 mV
Resolution: 100 Hz (slow gate)
1.0 KHz (fast gate)
Display: 7 digits, 0.4" LED
Time base: 2.0 ppm 20-40°C
Power: 5 VDC @ 200 ma

8 DIGITS 600 MHz \$159⁹⁵ WIRED



NEW
READ
FREQUENCY

SPECIFICATIONS:

Range: 20 Hz to 600 MHz
Sensitivity: Less than 25 mV to 150 MHz
Less than 150 mV to 600 MHz
Resolution: 1.0 Hz (60 MHz range)
10.0 Hz (600 MHz range)
Display: 8 digits 0.4" LED
Time base: 2.0 ppm 20-40°C
Power: 110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:

CT-50 wired, 1 year warranty \$159.95
CT-50 Kit, 90 day parts warranty 119.95
RA-1, receiver adapter kit 14.95
RA-1 wired and pre-programmed (send copy of receiver schematic) 29.95



DIGITAL MULTIMETER \$99⁹⁵ WIRED

PRICES:

DM-700 wired, 1 year warranty \$99.95
DM-700 Kit, 90 day parts warranty 79.95
AC-1, AC adaptor 3.95
BP-3, Nicad pack + AC adapter/charger 19.95
MP-1, Probe kit 2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include; 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts: 100uV to 1 KV, 5 ranges
DC/AC current: 0.1 uA to 2.0 Amps, 5 ranges
Resistance: 0.1 ohms to 20 Megohms, 6 ranges
Input impedance: 10 Megohms, DC/AC volts
Accuracy: 0.1% basic DC volts
Power: 4 'C' cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
 - Multiplies by 10 or 100
 - 0.01 Hz resolution!
- \$29.95 Kit \$39.95 Wired

ACCESSORIES

Telescopic whip antenna - BNC plug. \$ 7.95
High impedance probe, light loading. 15.95
Low pass probe, for audio measurements. 15.95
Direct probe, general purpose usage. 12.95
Tilt bail, for CT 70, 90, MINI-100. 3.95
Color burst calibration unit, calibrates counter against color TV signal. 14.95

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
 - BNC Connectors
 - Great for sniffing RF with pick-up loop
- \$34.95 Kit \$44.95 Wired

ramsey electronics, inc.

2575 BAIRD RD. • PENFIELD, NY 14526



TERMS

PHONE ORDERS
CALL 716-586-3950

Satisfaction guaranteed - examine for 10 days, if not pleased, return in original form for refund. Add 5% for shipping - insurance to a maximum of \$10. Overseas add 15%. COD add \$2. Orders under \$10. add \$1.50. NY residents add 7% tax.

CIRCLE 72 ON FREE INFORMATION CARD

SEPTEMBER 1982

121

CUSTOM electronic manufacturing, prototype, short production run. **DAUS ELECTRONICS**, P.O. Box 831, Angier, NC 27501

RECORDS—tapes! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main Street, PO Box 2000, Dept. 3-0782, New Rochelle, NY 10801

DESCRAMBLERS gated pulse sinewave, transmitters, sniffers, bugfoiler, lineals, soramblers, schematics, boards, kits. Catalog \$2.00. **M&M ELECTRONICS**, Box 252, Crompond, NY 10517

SUPER-buy: microwave receiving systems, converters, satellite TVRO. Large selection of best quality products. Lowest prices anywhere. Free information. Catalog \$3.00. Satisfaction guaranteed. **TCE**, Box 343, Dept. R, Brooklyn, NY 11230

USA subscription—TV stations (MDS) brochure. Latest and most complete information: exact tower locations, programming, equipment, ownership and more. Send \$10.00 to **TCE**, Box 343, Dept. R, Brooklyn, NY 11230

TEKTRONIX and HP 30 MHz used oscilloscope \$200.00. (714) 985-9967.

POWER-AMP sub-assemblies, 100 watts rms. .05% distortion, completely assembled and tested, quantity pricing available, free brochure. **CLAXTON AUDIO**, 3174 Periwinkle, Memphis, TN 38127

WANTED

Ideas, inventions, new products wanted for presentation to industry. Call free 1-800-528-6050. Arizona 1-800-352-0458. X831.

UHF CONVERTERS

DELUXE sine wave UHF converter. Sound out of TV like normal with only antenna connection to TV or VCR. Kits \$175.00 (312) 267-3455. **LSR ENGINEERING**, Box 6075, Chicago, IL 60680

REEL TO REEL TAPES

TRUCKLOAD sale, Ampex high quality open reel tape, 1800' or 2400' on 7" reels, used once, unboxed. Case of 40, \$45.00. Cassettes available. **VALTECH ELECTRONICS**, Box 6-RE, Richboro, PA 18954

COMMUNICATIONS EQUIPMENT

DECODE Morse, radioteletype signals from airwaves with CODE*STAR reader. Kit \$169.95, wired \$229.95. Shipping \$5.00. **MICROCRAFT**, Box 513R, Thiensville, WI 53092 (414) 241-4654

POWER SUPPLIES

LABORATORY quality 5-volt, 12-volt, tri-voltage supply for Op-Amps, IC's, Microprocessors. Kit \$69.95. Wired \$89.95. Shipping \$4.00. **MICRORAFT**, Box 513R, Thiensville, WI 53092. (414) 241-8144

FIBEROPTICS

ANALOG photo receiver. Beautiful sine, square, triangle reproduction. 10 μ s response (2.0 kHz). Complete manual including analog LEDxmttr schematic. \$27.50 + \$2.25 P&H. Req. case and P.S. **C. CLEARWATERS**, 2074 Wallace Ave., #604, Bronx, NY 10462

ARTWORK

ARTWORK, professional quality, fast turn around. Call or write today for more information or quote: **ELECTRONIC COMMUNICATION ENG.**, PO Box 18725, Greensboro, NC 27419. Phone (919) 299-9772

COMPUTER PROGRAMS

WIN \$, dog race program. TRS-80 I/III, color, pocket specify \$25.00. **PAUL PICKS**, PO Box 244, Lutz, FL 33549

PROGRAMS

INFINITE TAX TABLE for handheld computers. TRS-80, Sharp, etc. Fit & Fica any amount of wages, dependants or pay periods. Well documented, including options. Send \$5.95. **ENERGY CONTROL SYSTEMS**, Box 1396, Gretna, LA 70053 (504) 362-2090

CB RADIO

GET more CB channels and range! Frequency expanders, boosters, speech processors, FM converters, PLL/slider tricks, how-to books, plans, modifications. Catalog \$2.00. **CB CITY**, Box 31500RE, Phoenix, AZ 85046

Help Prevent Birth Defects — The Nation's Number One Child Health Problem.

Support the

March of Dimes
BIRTH DEFECTS FOUNDATION

SURPLUS ITEMS!

We're closing out our parts business to concentrate on the **CompuPro** line of high performance computers. Remaining parts listed below are limited quantity, first come/first served. Counts approximate ($\pm 5\%$). No phone orders, no partial orders. Use this ad as order blank, or photocopy ad.

DELUXE 12V CLOCK NOW ON SPECIAL!

For cars, vans, planes, boats, or houses using alternate DC power, National's MA1003 is the finest looking, most readable 12V DC clock module we've ever seen. Includes four blue/green fluorescent 0.3" readouts that are more pleasing to the eye, and more readable, than LEDs or LCDs; brightness control option; "dim-when-headlights-on" option for automotive applications; and sample application note.

These have sold elsewhere for up to \$19.95. Our price: **\$8.95 each**, 2/\$17.95, or if you're looking for real value, **10/\$59.95!** Take advantage now of the one of the best clock module deals on the market.

CAPACITORS

1000 uF/35V, axial	40/\$5
500 uF/15V, axial	50/\$5
2200 uF/16V pc mount	35/\$5
1000 uF/16V	50/\$5
220 uF/25V pc mount	50/\$5
1000 uF/150V	25/\$5
10,000 uF/10V axial	25/\$5

TRANSISTORS

MPS3694 NPN	1000/\$35
2N4400 NPN 1/4" leads	2000/\$70
2N5227 PNP	1000/\$35
2N4917 PNP	2000/\$70
FPQ3725 quad xistors	50/\$5

LOW PROFILE SOCKETS

8 pin	50/\$5
14 pin	50/\$5
16 pin	50/\$5
18 pin	40/\$5
20 pin	35/\$5

LINEAR ICs

LM301	30/\$5
LM741	50/\$5
LM733	50/\$5
LM380	30/\$5
LM556	25/\$5
LM703	25/\$5
uA706	20/\$5
uA723	25/\$5
LM1458	20/\$5
CA3080	10/\$5
4195TK	20/\$5
LM7806 +6 reg	10/\$5
LM7808 +8V reg	10/\$5
LM7815 +15V reg	10/\$5
LM7818 +18V reg	10/\$5
LM7824 +24V reg	10/\$5
LM7906 -6V reg	10/\$5
LM7908 -8V reg	10/\$5
LM7915 -15V reg	10/\$5
LM7918 -18V reg	10/\$5
LM7924 -24V reg	10/\$5

CMOS

4010	40/\$4
4015	40/\$5
4016	50/\$5
4019	40/\$5
4022	40/\$5
4023	60/\$6
4025	50/\$5
4028	60/\$5
4030	50/\$5
4040	20/\$5
4069	50/\$5
4071	50/\$5
4073	50/\$5
4075	50/\$5
4093	50/\$5
4116	50/\$5
4507	50/\$5
4512	50/\$5

ODDS AND ENDS

Misc. pots - some funny shafts, some duals, some singles, no time to select	35/\$5
250 Ohm trimpots	50/\$5
500 Ohm	50/\$5

25A/50V diode bridges	5/\$5
-----------------------	-------

Dynamic mic originally designed for Cartrivision with extension cable (miniplug male and female); stereo pair	\$5
Extension cable as above	5/\$5

Stereo amps with LM380s and pots. May even work!	2/\$5
--	-------

15 MHz crystal oscillator in small can	2/\$5
Colorburst crystal 3.58 MHz	
1 MHz HC-6 crystal	5/\$5

GODBOUT
ELECTRONICS

OAKLAND AIRPORT, CA 94614-0355

Send the coupon below to **Bill Godbout Electronics**, RE Parts Sale, PO Box 2355 Oakland Airport, CA 94614-0355.

Please send the parts circled above to (PLEASE PRINT OR TYPE):		
Name _____		
Street Address (necessary for UPS delivery) _____		
Town _____	State _____	ZIP _____
Subtotal for parts: _____		
Californians add tax _____ \$		
Handling (strike out for orders over \$25) _____ \$2.00		
Postage (allow 5%, excess refunded) _____ \$		
TOTAL _____ \$		

7400

**Number of Pins of each I.C. for easy stock purchase

MICROPROCESSOR COMPONENTS

*Evaluation Kits

INTERSTATE

*Evaluation Kits

*Evaluation Kits

Part No.	*Pins	Part No.	*Pins	Part No.	*Pins
SN7400N	14	SN7472N	14	SN74156N	14
SN7401N	14	SN7473N	14	SN74157N	16
SN7402N	14	SN7474N	14	SN74160N	16
SN7403N	14	SN7475N	14	SN74161N	16
SN7404N	14	SN7476N	14	SN74162N	16
SN7405N	14	SN7477N	14	SN74163N	16
SN7406N	14	SN7478N	14	SN74164N	16
SN7407N	14	SN7479N	14	SN74165N	16
SN7408N	14	SN7480N	14	SN74166N	16
SN7409N	14	SN7481N	14	SN74167N	16
SN7410N	14	SN7482N	14	SN74168N	16
SN7411N	14	SN7483N	14	SN74169N	16
SN7412N	14	SN7484N	14	SN74170N	16
SN7413N	14	SN7485N	14	SN74171N	16
SN7414N	14	SN7486N	14	SN74172N	16
SN7415N	14	SN7487N	14	SN74173N	16
SN7416N	14	SN7488N	14	SN74174N	16
SN7417N	14	SN7489N	14	SN74175N	16
SN7418N	14	SN7490N	14	SN74176N	16
SN7419N	14	SN7491N	14	SN74177N	16
SN7420N	14	SN7492N	14	SN74178N	16
SN7421N	14	SN7493N	14	SN74179N	16
SN7422N	14	SN7494N	14	SN74180N	16
SN7423N	14	SN7495N	14	SN74181N	16
SN7424N	14	SN7496N	14	SN74182N	16
SN7425N	14	SN7497N	14	SN74183N	16
SN7426N	14	SN7498N	14	SN74184N	16
SN7427N	14	SN7499N	14	SN74185N	16
SN7428N	14	SN7500N	14	SN74186N	16
SN7429N	14	SN7501N	14	SN74187N	16
SN7430N	14	SN7502N	14	SN74188N	16
SN7431N	14	SN7503N	14	SN74189N	16
SN7432N	14	SN7504N	14	SN74190N	16
SN7433N	14	SN7505N	14	SN74191N	16
SN7434N	14	SN7506N	14	SN74192N	16
SN7435N	14	SN7507N	14	SN74193N	16
SN7436N	14	SN7508N	14	SN74194N	16
SN7437N	14	SN7509N	14	SN74195N	16
SN7438N	14	SN7510N	14	SN74196N	16
SN7439N	14	SN7511N	14	SN74197N	16
SN7440N	14	SN7512N	14	SN74198N	16
SN7441N	14	SN7513N	14	SN74199N	16
SN7442N	14	SN7514N	14	SN74200N	16
SN7443N	14	SN7515N	14	SN74201N	16
SN7444N	14	SN7516N	14	SN74202N	16
SN7445N	14	SN7517N	14	SN74203N	16
SN7446N	14	SN7518N	14	SN74204N	16
SN7447N	14	SN7519N	14	SN74205N	16
SN7448N	14	SN7520N	14	SN74206N	16
SN7449N	14	SN7521N	14	SN74207N	16
SN7450N	14	SN7522N	14	SN74208N	16
SN7451N	14	SN7523N	14	SN74209N	16
SN7452N	14	SN7524N	14	SN74210N	16
SN7453N	14	SN7525N	14	SN74211N	16
SN7454N	14	SN7526N	14	SN74212N	16
SN7455N	14	SN7527N	14	SN74213N	16
SN7456N	14	SN7528N	14	SN74214N	16
SN7457N	14	SN7529N	14	SN74215N	16
SN7458N	14	SN7530N	14	SN74216N	16
SN7459N	14	SN7531N	14	SN74217N	16
SN7460N	14	SN7532N	14	SN74218N	16
SN7461N	14	SN7533N	14	SN74219N	16
SN7462N	14	SN7534N	14	SN74220N	16
SN7463N	14	SN7535N	14	SN74221N	16
SN7464N	14	SN7536N	14	SN74222N	16
SN7465N	14	SN7537N	14	SN74223N	16
SN7466N	14	SN7538N	14	SN74224N	16
SN7467N	14	SN7539N	14	SN74225N	16
SN7468N	14	SN7540N	14	SN74226N	16
SN7469N	14	SN7541N	14	SN74227N	16
SN7470N	14	SN7542N	14	SN74228N	16

STATIC RAMS


Part No.	*Pins	Part No.	*Pins
1101	16	256K1	16
2101	16	256K2	16
3101	16	256K3	16
4101	16	256K4	16
5101	16	256K5	16
6101	16	256K6	16
7101	16	256K7	16
8101	16	256K8	16
9101	16	256K9	16
10101	16	256K10	16
11101	16	256K11	16
12101	16	256K12	16
13101	16	256K13	16
14101	16	256K14	16
15101	16	256K15	16
16101	16	256K16	16
17101	16	256K17	16
18101	16	256K18	16
19101	16	256K19	16
20101	16	256K20	16
21101	16	256K21	16
22101	16	256K22	16
23101	16	256K23	16
24101	16	256K24	16
25101	16	256K25	16
26101	16	256K26	16
27101	16	256K27	16
28101	16	256K28	16
29101	16	256K29	16
30101	16	256K30	16
31101	16	256K31	16
32101	16	256K32	16
33101	16	256K33	16
34101	16	256K34	16
35101	16	256K35	16
36101	16	256K36	16
37101	16	256K37	16
38101	16	256K38	16
39101	16	256K39	16
40101	16	256K40	16
41101	16	256K41	16
42101	16	256K42	16
43101	16	256K43	16
44101	16	256K44	16
45101	16	256K45	16
46101	16	256K46	16
47101	16	256K47	16
48101	16	256K48	16
49101	16	256K49	16
50101	16	256K50	16
51101	16	256K51	16
52101	16	256K52	16
53101	16	256K53	16
54101	16	256K54	16
55101	16	256K55	16
56101	16	256K56	16
57101	16	256K57	16
58101	16	256K58	16
59101	16	256K59	16
60101	16	256K60	16
61101	16	256K61	16
62101	16	256K62	16
63101	16	256K63	16
64101	16	256K64	16
65101	16	256K65	16
66101	16	256K66	16
67101	16	256K67	16
68101	16	256K68	16
69101	16	256K69	16
70101	16	256K70	16
71101	16	256K71	16
72101	16	256K72	16
73101	16	256K73	16
74101	16	256K74	16
75101	16	256K75	16
76101	16	256K76	16
77101	16	256K77	16
78101	16	256K78	16
79101	16	256K79	16
80101	16	256K80	16
81101	16	256K81	16
82101	16	256K82	16
83101	16	256K83	16
84101	16	256K84	16
85101	16	256K85	16
86101	16	256K86	16
87101	16	256K87	16
88101	16	256K88	16
89101	16	256K89	16
90101	16	256K90	16
91101	16	256K91	16
92101	16	256K92	16
93101	16	256K93	16
94101	16	256K94	16
95101	16	256K95	16
96101	16	256K96	16
97101	16	256K97	16
98101	16	256K98	16
99101	16	256K99	16
100101	16	256K100	16

DYNAMIC RAMS

1.49					
1.49		1103		16	1024K1
1.49		89	4027	16	4096K1
1.49		4116N-2		16	16,384K1
2.95		4116N-3		16	16,384K2
2.95		4116N-4		16	16,384K3
25 - 8/14.95		4164N-2		16	65,536K1
49 - 8/16.95		MS5261		16	1024K1
49 - 8/16.95		MS5262		16	1024K2
49 - 8/16.95		MS5270		16	4096K1
95 - 8/17.95		MS5280	22	4096K1	
3.95		MS5290-3		16	16,384K1
3.95		MS5290-4		16	16,384K2
3.95		MS5298-3		16	8192K1
4.95					
4.95		74S198		16	32K8
7.95		74S387		16	32K8
8.95		74S288		16	32K8
2.25		74S37		16	256K4
551) 3.95		74S471		16	512K8
501) 3.95		74S472		20	512K8
501) 3.95		74S473		20	512K8
501) 3.95		74S474		24	512K8
2.95		74S475		24	512K8
3.95		74S476		24	1024K8
3.95		74S477		16	512K4
3.95		74S478		16	512K4
5) 3.95		74S572		16	1024K4
89) 2.25		74S573		16	1024K4

JE600 Hexadecimal Encoder Kit

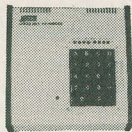FULL 8-BIT
LATCHED OUTPUT
19-KEY KEYBOARD



The JE600 Encoder Keyboard Kit provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit memory circuits. Three additional keys are provided for use with operations with one having a bistable output available. The outputs are latched and monitored with 9 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-definable keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin IC connector. Only +5VDC required for operation. Size: 3 1/2" H x 8 3/4" W x 8 3/4" D.


JE600/DTE-HK (After assembled as pictured above) ... \$99.95

JE600 Kit 19-Key Hexadecimal Keyboard, PC Board & Cmpnts. (no case) ... \$59.95

K19 19-Key Keyboard (Keyboard only) ... \$14.95

DTE-HK (case only — 3 1/2" H x 8 3/4" W x 8 3/4" D) ... \$44.95

JE610 ASCII Encoded Keyboard Kit

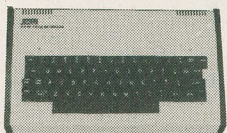

The JE610 ASCII Keyboard Kit can be interfaced into most any computer system. The kit comes complete with an industrial grade keyboard switch assembly (62-keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires +5V & 150mA and —12V @ 10 mA for operation. Features: 60 keys generate the 126 characters, upper and lower case ASCII set. Fully buffered. Two user-definable keys provided for custom applications. Caps lock for upper-case only alpha characters. Utilizes a 2376 (40-pin) encoder-read-only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Easy interfacing with a 16-pin dip or 18-pin edge connector. Size: 3 1/2" H x 14 1/2" W x 8 3/4" D.

JE610/DTE-AK (After assembled as pictured above) ... \$124.95

JE610 Kit 62-Key Keyboard, PC Board, & Components (no case) ... \$79.95

K62 62-Key Keyboard (Keyboard only) ... \$34.95

DTE-AK (case only — 3 1/2" H x 14 1/2" W x 8 3/4" D) ... \$49.95

NEW! JE212 — Negative 12VDC Adapter Board Kit for JE610 ASCII KEYBOARD KIT. Provides -12VDC from incoming 5VDC ... \$9.95

JE215 Adjustable Dual Power Supply

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

FEATURES:

- Adjustable regulated power supplies, pos. and neg. 1.2VDC to 15VDC.
- Power Output (each supply): 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
- Two, 3-terminal adj. IC regulators with thermal overload protection.
- Heat sink regulator cooling.
- LED "on" indicator.
- Printed Board Construction.
- 120VAC input.
- Size: 3 1/2" W x 5 1/16" L x 2" H.

JE215 Adj. Dual Power Supply Kit (as shown) ... \$24.95

(Picture not shown but similar in construction to above)

JE200 Reg. Power Supply Kit (5VDC, 1 amp) ... \$14.95

JE205 Adapter Brd. (to JE200) 4.5A @ 12V ... \$12.95

JE210 Var. Pwr. Sply. Kit, 5-15VDC, to 1.5amp ... \$19.95

HP-Display Sale-National 5082 Series — 0.43 Inch — 7-Segment

Part Number	Color	Description	1-Price	SALE PRICE
5082-7650	Hi Eff Red	CA - LHD	99	4/\$2.49
5082-7651	Hi Eff Red	CA - RHD	99	4/\$2.49
5082-7653	Hi Eff Red	CC - RHD	99	4/\$2.49
5082-7656	Hi Eff Red	Overflow ±1RHD	99	4/\$2.49
5082-7660	Yellow	CA - LHD	99	4/\$2.49
5082-7661	Yellow	CA - RHD	99	4/\$2.49
5082-7663	Yellow	CC - RHD	99	4/\$2.49
5082-7670	Green	CA - LHD	99	4/\$2.49
5082-7671	Green	CA - RHD	99	4/\$2.49
5082-7673	Green	CC - RHD	99	4/\$2.49
5082-7676	Green	Overflow ±1RHD	99	4/\$2.49
5082-7750	Red	CA - LHD	99	4/\$2.49
5082-7751	Red	CA - RHD	99	4/\$2.49
5082-7756	Red	Overflow ±1RHD	99	4/\$2.49
5082-7760	Red	CC - RHD	99	4/\$2.49

CA-Comm. Anode CC-Comm. Cathode LHD/RHD-Left/right hand dec.



UTIC
Mini Stereo
AM/FM
Receiver

CLOSE-OUT!

WITH HEADPHONES
For Joggers, Cyclists,
Skaters & Sports Events

Model 2830 ... \$29.95

KEYBOARDS — POWER SUPPLIES



ALPS 26-KEY CALCULATOR KEYBOARD

Features: 7 Position, 3 Position and 2 Position Switches (ON/OFF). These are from Olivetti's Top of the Line. Mechanical SPST Switching: 22-pin Edge Card Connection.

Part No. K826

\$1.95 each or 2/\$3.49




MICRO SWITCH 69-KEY KEYBOARD

Data Entry Keyboard, Encoded Output: 8-bit Parallel EBC DIC. Switching: Hall Effect, 24-pin Edge Card Connection. Complete with Pin Connection.

Part No. KB69SD12-2

\$19.95 each

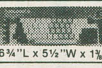


DATANETICS 74-KEY KEYBOARD

ASCII Encoded Keyboard, Output: Even Parity ASCII, Supply voltage +5, -12 volt. Switching: Mechanical SPST — 50-pin Connection. Complete with Pin Connection.

Part No. KB354

\$29.95 each

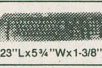


MICRO SWITCH 85-KEY KEYBOARD

Word Processing Keyboard, 26 Pin Edge Card Connection. Supply Voltage +5VDC. Main Keyboard is QWERTY. Additional Key Pads for Cursor and word processing functions.

Part No. 85SD18-1

\$29.95 each

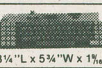

MICRO SWITCH 88-KEY KEYBOARD (PARALLEL ASCII)

Data Entry Keyboard used in a Diablo 1640 Terminal. Supply Voltage: +5V, -12V. Switching: Hall Effect — 10-pin Edge Card Connection. Schematic included. Uses 8048 Encoder Chip.

Part No. 88SD22

\$69.95 each



POWER SUPPLY — 5VDC @ 1 AMP REGULATED

Transaction Tech Output: +5VDC @ 1 amp (also +30VDC) reg. input 115VAC 60Hz. Two-tone (black/beige) self-enclosed case. 6 ft. 3 cond. black pow. cord. Size: 6 1/2" W x 7 1/2" D x 2 1/2" H. Wt. 3 lbs.

Part No. PS51194

\$19.95 each



POWER SUPPLY — 5VDC @ 1 AMP REGULATED

B Industries Output: +5VDC @ 1 amp, +36-42VDC adj. 400mA or less, 30VAC (isol.) @ 1.5 amp. Input 115VAC 60Hz. Circ. brkr. re-set button. Blk. self-enc. case w/4 rubber feet. 6 ft. 3 cond. blk. pow. cord. On/off switch. 6 1/2" W x 7 1/2" D x 3 7/8" H. Wt. 7 lbs.

Part No. PS407D

\$24.95 each



POWER SUPPLY — 5VDC @ 7.5 AMP, 12VDC @ 1.5 AMP SWITCHING

Input: 115VAC, 50-60Hz @ 3 amp/230VAC, 50Hz @ 1.6 amp. Fan volt./power supply select switch (115/230VAC). Output: 5VDC @ 7.5 amp, 12VDC @ 1.6 amp. 8 ft. blk. pow. cord. 11 1/2" W x 13 1/2" D x 3 1/2" H. Wt. 6 lbs.

Part No. PS94V0

\$39.95 each



POWER PAC — Heavy Duty Multi-Voltage Power Supply

Output: +5VDC @ 30A, +12VDC @ 2A, +12VDC @ 4A & +24VDC @ 3A. Input: 115VAC, 7A, 220VAC, 3.5A. Reg. ± 15% line & load. Input: 10W peak to peak (3MW RMS). Overvolt. protect. 5V, +12V, -12V. Overcurr. protect. incl. 15 1/2" L x 6 1/2" H x 11 7/8" D. Wt. 40 lbs.

Part No. 285-016

\$89.95 each



SORESEN Regulated Power Supplies

Sorensen's open construction (SOC) power supplies are series-regulated solid-state systems, designed to provide reg. DC voltages at 6 levels (2-28 v/range). These units are open-framed on sturdy black anodized aluminum for excellent mounting.

FEATURES: 115/208/230VAC Input @ 50-63Hz. Low Ripple: 1.5mVrms, 5mV P-P maximum. Adjustable current limit. Voltage adjustment control. All schematics and specifications supplied with unit. Series A,B,C,E have three mounting surfaces (Series F, bottom mounting only).

SOC 2-6 (Pictured)

Part No.	Series	Output Voltage Adjustment Range	Output Current amps (max)	Size (inches)	Weight	Price
SOC 2-6	B	1.9 - 2.1	6.0	4.9	3.8	5.62 x 4.88 x 2.50 4.3 lbs. \$19.95
SOC 3-6	F	1.9 - 2.1	26.0	11.5	17.5	16.00 x 4.88 x 4.88 16 lbs. 29.95
SOC 5-3	A	4.75 - 5.25	3.0	2.4	1.8	4.00 x 4.88 x 1.62 2 lbs. 24.95
SOC 5-18	E	4.25 - 5.25	18.0	15.0	12.0	14.00 x 4.88 x 2.75 12 lbs. 39.95
SOC 5-26	F	4.25 - 5.25	26.0	21.5	17.5	16.00 x 4.88 x 4.88 16 lbs. 49.95
SOC 12-11	F	11.4 - 12.6	11.0	9.2	6.8	14.00 x 4.88 x 1.62 12 lbs. 44.95
SOC 12-15	F	11.4 - 12.6	15.0	12.75	9.5	16.00 x 4.88 x 1.68 16 lbs. 49.95
SOC 15-5	C	14.25 - 15.75	5.0	4.2	3.5	7.00 x 4.88 x 2.37 6.6 lbs. 34.95
SOC 15-6	E	14.25 - 15.75	9.5	7.6	5.8	14.00 x 4.88 x 1.62 12 lbs. 44.95
SOC 15-13	F	14.25 - 15.75	13.0	10.5	8.0	16.00 x 4.88 x 4.88 16 lbs. 49.95
SOC 28-0.8	A	28.5	0.8	24	45	4.00 x 4.88 x 1.62 2 lbs. 24.95



Powertec Sub-Modular DC Power Supplies

SM Series power supplies include rectifying, filtering, regulating, overload and overvoltage protection functions. You need only connect the sub-module to the appropriate secondary transformer tap and bolt the unit to a heatsink.

REGULATION: LINE: 10% for a change from -10% to +10% input voltage. LOAD: 15% for a 0-100% load change (units below 5V output maintain 5V regulation). OUTPUT RIPPLE: 1mV RMS, 3mV P-P typical. 5mV P-P maximum. INPUT CHARACTERISTICS: Requires low-level AC input. Derate output current 15% for operations at 50Hz.

220300 (Pictured)

Part Number	Power Transformer Requirements Transformers Not Included	Size (inches)	Wt.	Price
22A-300	115-120VAC 17VAC 5A no CT	2.50 x 3.00 x .98	2 oz.	\$14.95
22B-200	115-120VAC 22VAC 3A w/CT	3.00 x 5.75 x 1.18	8 oz.	14.95
22B-300	115-120VAC 28VAC 2.5A w/CT	2.75 x 5.75 x 1.18	8 oz.	19.95
22C-100	115-120VAC 16VAC 8A w/CT	2.80 x 7.50 x 1.18	8 oz.	24.95
22C-500	115-120VAC 48VAC 2A w/CT	2.80 x 7.50 x 1.18	8 oz.	24.95
22D-300	115-120VAC 28VAC 10A w/CT	3.00 x 7.00 x 3.30	2 lbs.	24.95
22E-100	115-120VAC 16VAC 24A w/CT	2.90 x 7.00 x 3.30	2 lbs.	29.95

*Voltage Adjustment Range — Current ratings apply over entire voltage range.

SHIPMENT IN 24 HOURS

6:00 AM to 6:00 PM (PST)

Call: (415) 592-8097

Custom Jumper!

JUMPER AND CABLE ASSEMBLIES

STANDARD JUMPERS

All jumpers use low profile dip plugs with heavy duty pins for repeated disconnect applications.

JAMECO Part No.	AP Cross Reference	No. Pins	Description	Wire Length	Price
DJ1-1	924102-12	14	single end 12"	12"	\$1.79
DJ1-2	924102-24	14	single end 24"	24"	2.05
DJ1-3	924102-36	14	single end 36"	36"	2.35
DJ1-14	924106-12	14	double end 12"	12"	3.20
DJ1-14	924106-24	14	double end 24"	24"	3.49
DJ1-14	924106-36	14	double end 36"	36"	3.79
DJ1-6	924112-12	16	single end 12"	12"	1.85
DJ1-6	924112-24	16	single end 24"	24"	2.15
DJ1-6	924112-36	16	single end 36"	36"	2.59
DJ1-16	924116-12	16	double end 12"	12"	3.19
DJ1-16	924116-24	16	double end 24"	24"	3.69
DJ1-16	924116-36	16	double end 36"	36"	4.05
DJ2-1	924122-12	24	single end 12"	12"	2.69
DJ2-2	924122-24	24	single end 24"	24"	3.39
DJ2-3	924122-36	24	single end 36"	36"	3.95
DJ2-14	924126-12	24	double end 12"	12"	4.79
DJ2-14	924126-24	24	double end 24"	24"	5.29
DJ2-14	924126-36	24	double end 36"	36"	5.89

STANDARD CABLES

Now you can order DB25 P or S connectors with the cable necessary to fit your application. Choose from our standard flat cable in 4-foot lengths. Call today.

Part No. Cable Length Connectors Price

DB25P-4 4 feet 1 DB25P \$ 9.95 ea.

DB25S-4 4 feet 1 DB25S 10.95 ea.

DB25P-4-P 4 feet 1 DB25P 16.95 ea.

DB25P-4-S 4 feet 1 DB25P 17.95 ea.

DB25S-4-S 4 feet 2 DB25S 18.95 ea.

Spec Sheets — 25¢ each

Send 8¢ Postage to your

FREE 1982 JAMECO CATALOG

Prices Subject to Change

Mail Order Electronics • Worldwide

NEW! Telex Number 176043

3555 SHOREWAY ROAD, BELMONT, CA 94002

PHONE ORDERS WELCOME — (415) 592-8097

9/82

5 1/4" Mini-Floppy Disc System

For TRS-80 MODEL I, II (Industry Standard)

Features single or double density. Recording mode: FM single, MFM double density. Power: +12VDC (±0.5V), 1.8 amps max. +5VDC (±0.25V) 0.8 amps max. Unit as pictured at left (does not incl. case, power supply or cables). 30-page data book included. Weighs 3 1/2 pounds. Size: 5 1/4" W x 8 1/2" x 3 1/4" H.

Part No. Limited Quantity! Price

FD200 ... \$179.95

Single-sided, 40 tracks, 250K bytes capacity

FD250 ... \$199.95

Double-sided, 35 tracks, 438K bytes capacity

EXPAND YOUR TRS-80 TO 16K, 32K or 48K

**Model 1 = From 4K to 16K Requires (1) One Kit

Model 3 = From 4K to 48K Requires (3) Three Kits

Color = From 4K to 16K Requires (1) One Kit

Model 1 equipped w/Expansion Board up to 48K (2 Two Kits Req'd.)

— One Kit Required for each 16K of Expansion —

TRS-80 16K Conversion Kit — Kit comes complete with 8 each

MM280 (UP0416/4116) 16K Dynamic RAM (ns) & documentation for conversion.

TRS-16K2 150ns ... \$16.95

TRS-16K3 200ns ... \$14.95

TRS-16K4 250ns ... \$10.95

Pee Wee Boxer Fan

• 36cfm free air delivery

• 3.125" sq. x 1.665" depth

SCR SUPER-BUYS

• **UHF-VHF CONVERSION KIT.** Complete with PC board, all required components: cabinet with speaker: and comprehensive brochure incl. schematic, board layout mounting and hook-up diagrams, parts list and assembly and set-up instructions. All parts are industrial prime quality.

• **NEW ZENITH ZVM-121 HIGH**
 LEGIBILITY CRT MONITOR. Features 12" green phosphor CRT, with 15 MHz Bandwidth. 40 or 80 character widths are operator switch selectable. Fully compatible with 80-column Apple cards, etc.

• **MITSUMI - MODEL UES-A551**
 VARICATOR UHF TUNER

	FREQ. RANGE
	470 - 889 MHz
	ANTENNA INPUT

● **SPECIAL -** 
2200 MFD 40 VT CAP

● **H.D. SPECIALS**

TRANSISTOR

2 N 305
2SA 7
2SA 74
2S C 1116
2SC 140

OUTSIDE CAL. 80
INSIDE CAL. (714
or (213

VISIT OUR NEW SUPER C
5303 Lincoln Ave., Cypress, CA 90630
Pay by **CHECK, M.O., VISA,**
\$10.00 MIN. ORDER **HANDLING/SHIPPING**
UPS ANYWHERE IN CONTINENTAL U.S.



HITECH
EDUCATIONAL IN NATURE

LCD Multimeter

The affordable LCD Multimeter
uses large 2 1/2 digit DMM

0-50V 3A Regulated Adjustable Power Supply
With overload protection and LED power on indicator. Assem \$28.50
HKIT-503 Kit \$24.50



HK1T-300 **AS**

Programmable Music Door-bell
Electronic door-bell that has 9 programmable tones

7 Digit



HKIT-47A

Assm \$16.50
Kit \$12.50
(9V Batt. \$0.95)

Transformer

HKIT-83A \$7.95
HKIT-86A \$5.50

0-25V 2A 0.5A

Universal Counter
Universal Counter counts up to 60 MHz and 10 million events. 7 large 0.5" digits. Crystal time base. High performance.
HK1T-86A **Kit \$49.50**

Function Generator
Generates triangle, square or sine wave. 100 kHz. 10 V peak to peak.
HK1T-125

Triple Output
+5V @ 1.5A for logic, +12V @ 0.5A for linear circuitry.
HK1T-126

testing audio amps. **Assm \$35.50** | **Transform**
HKIT-55 | **Kit \$29.50**

To Order, send check


Hitech Ele


4425 W. Sepulveda Blvd

Phone Orders: (2

VISA and M/C welcomed

• MITSUMI - MODEL UES-A55F
VARACTOR UHF TUNER

	FREQ. RANGE	\$25.00 ea.
	470 - 889 MHz	
	ANTENNA INPUT	10 for \$220.00
	300 OHMS	

● **SPECIAL -**  10 for \$13.50
2200 MFD 40 VT CAP

• I.C. SPECIAL LM 565 10 for \$16.00

● H.D. SPECIALS	TRANSISTORS	
	2 N 3055	10 for \$10.
	2SA 745	\$4.00 ea.
	2SA 747B	\$4.50 ea.
	2S C 1116B	\$3.25 ea.
	2SC 1402B	\$3.00 ea.

SCD OUTSIDE CAL 800-854-8660
INSIDE CAL (714) 527-2554
or (213) 603-9385

VISIT OUR NEW SUPER CENTER
5303 Lincoln Ave., Cypress, CA. 90630
Pay by CHECK, M.O., VISA, M/C
\$10.00 MIN. ORDER HANDLING/SHIPPING...\$2.50
UPS ANYWHERE IN CONTINENTAL U.S.

CIRCLE 96 ON FREE INFORMATION CARD



HITECH KITS

EDUCATIONAL IN NATURE FUN TO BUILD AND USE

LCD Multimeter

The affordable LCD Multimeter. High accuracy 19 range large 3 1/2 digit DMM with diode test, auto polarity and LO Batt. indicator. Fully Assembled. Model 101 \$59.95 9V Battery \$0.95

**0-50V 3A Regulated
Adjustable Power Supply**
With overload protection and LED
power on indicator. Assem \$28.50
HKIT-503 Kit \$24.50



30W Single Channel Power Amp

Compact power amp. with volume, treble and base control. Excellent for boosting power of your portable radio, or cassette. Connect to your TV audio and experience the real sound of your TV program.

Programmable Music Door-bell
Electronic door-bell that has 9 programmable tones. Uses CMOS for low power consumption and has auto shut-off feature.

HKIT-47A

Assm \$16.50
Kit \$12.50



(9V Batt. \$0.95)

Transformers for Kits

HKIT-83A	\$7.50	HKIT-300	\$10.00
HKIT-86A	\$5.95	HKIT-503	\$12.00

Universal Counter
Universal Counter counts up to 60 MHz and 10 million counts. 7 digit display.

Triple Output Power Supply
+5V @ 1.5A for logic circuits and $\pm 12V$ @ 100mA for linear circuits ($\pm 15V$ or $\pm 18V$ available)

Generates triangle, square or sine wave. 1 Hz to 100 KHz. Ideal for testing audio amps.	HKIT-125	Kit \$11.95 Assm \$24.95
HKIT-125	Transformer	\$1.95

 To Order, send check or money order to
Hitech Electronics
4425 W. Sepulveda Blvd., Torrance CA 90505
Phone Orders: (213) 371-2160
VISA and M/C welcomed. Minimum Order \$99
Shipping and Handling \$2.00. CA resident add 6%
PLEASE VISIT OUR STORE. Open 10:00-6:00 Mon. thru Sat.
Special discounts available to educational institutions. Dealer inquiries invited.

AMAZING DEVICES

PHASORS
PHASOR PAIN FIELD — Patented and recently developed in our labs is being tested by Gov't for riot control. Soon to come under weapons restrictions as an internal machine. Easily hand-held. Hazardous IF NOT USED WITH DISCRETION.
 PPF-1 PLANS (sold for animal control).....\$15.00
INVISIBLE PAIN FIELD GENERATOR — Produces a directional field of moderately intense pain to back of head up to 50'. Cigarette pack size enclosure is easily hidden.
 IPG-3 PLANS.....\$7.00 IPG-3K KIT & PLANS.....\$44.50
 IPG-30 (assembled for animal control).....\$59.50
PHASOR STUN/BURNING WAND — Produces sufficient electrical energy capable of burning flesh. Intended as a personal defense device.
 PSW-1 PLANS.....\$8.00 PSW-3K KIT & PLANS.....\$59.50

LASERS
RUBY LASER RAY PISTOL — Intense visible red, burns, hazardous, with parts sources.
 RUBY PLANS (includes all part sources).....\$15.00
CARBON DIOXIDE LASER — Generates 20-40 watts of continuous power capable of burning, cutting, hazardous. (with all part sources).....\$15.00
LASER RIFLE — Produces 200-3000 pulses of 30 watt optical energy. Portable and easily hand-held.
 LR-3 PLANS.....\$10.00
 LR-3K KIT PLANS (minus diode).....\$129.50
POCKET LASER — For the beginner, visible red "optical version", non-hazardous.
 LHC-2.....\$5.00 LHC-2K KIT & PLANS.....\$24.50
HIGH POWERED PORTABLE ENERGY SOURCE FOR LASERS AND MAGNETIC WEAPONS — Exploding wires, shockwave, etc. Miniature size.
 HPS-1 PLANS.....\$8.00 HPS-1K KIT & PLANS.....\$49.50
PARTICLE BEAM WEAPON — PLANS.....\$15.00

SECURITY
INFINITY XMTR — Uses telephone lines for selective home or office listening while away on business or vacation.
 INF-1 PLANS.....\$15.00
SEE IN DARK — Long range, total darkness.
 SD-4 PLANS.....\$10.00
LONG RANGE WIRELESS MIKE — Crystal clear quality — miniature.
 FBT-7 PLANS.....\$7.00 FBT-7K PLANS & KIT.....\$34.50
WIRELESS TELEPHONE TRANSMITTER — Long range, automatic.
 VWPM-5 PLANS.....\$10.00 VWPM-5K PLANS & KIT.....\$34.50

Send for **FREE** catalog description of above plus hundreds more plans, kits and completed items. We accept MC or Visa or when ordering, send check or money order. We pay shipping charges on orders over \$50.00, otherwise include 10% with remittance.
 SEND TO: **SCIENTIFIC SYSTEMS**
 DEPT. R8, BOX 716, AMHERST, N.H. 03031

CIRCLE 98 ON FREE INFORMATION CARD
 ELECTRONIC KITS FROM HAL-TRONIX

2304 MHZ DOWN CONVERTERS. TUNES IN ON CHANNELS 2 TO 7 ON YOUR OWN HOME T.V. HAS FREQUENCY RANGE FROM 2000 MHZ TO 2500 MHZ. EASY TO CONSTRUCT AND COMES COMPLETE WITH ALL PARTS INCLUDING A DIE-CAST ALUM CASE AND COAX FITTINGS, REQUIRE A VARIABLE POWER SUPPLY AND ANTENNA (Antenna can be a dish type or coffee can type depending on the signal strength in your area.)

2304 MOD 1 (Basic Kit) \$49.95
 (Less case & fittings)
 2304 MOD 2 (Basic / Pre-amp) \$59.95
 (Includes case & fittings)
 2304 MOD 3 (Hi-Gain Pre-amp) \$69.95
 (Includes case & fittings)

POWER SUPPLY FOR EITHER MODEL ABOVE IS AVAILABLE. COMES COMPLETE WITH ALL PARTS, CASE, TRANSFORMER, ANTENNA SWITCH AND CONNECTORS (Kit) \$24.95
 Assembled.....\$34.95
 Slotted Microwave Antenna For Above Downverters.....\$39.95

PREAMPLIFIERS
 HAL PA-19—1.5 mhz to 150 mhz. 19db gain operates on 8 to 18 volts at 10ma. Complete unit \$8.95.
 HAL PA-14—3 mhz to 1.4 ghz. 10 to 12 db gain operates on 8 to 18 volts at 10ma. Complete unit \$12.95.
 (The above units are ideal for receivers, counters, etc.)

16 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS.....\$69.95
 12 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS.....\$39.95

16 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS.....\$39.95
 12 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS.....\$29.95

 MANY, MANY OTHER KITS AVAILABLE

Send 20 cents stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-285-1782.




HAL-TRONIX
 P.O. Box 1101
 Southgate, MI 48195

ORDERS OVER \$25.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25.00 PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES.

CIRCLE 99 ON FREE INFORMATION CARD

QUALITY parts at DISCOUNT PRICES

4 CHANNEL 8 TRACK HOME UNIT

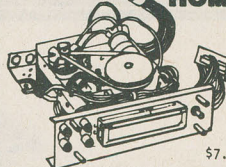

BRAND NEW UNITS...
 ASSEMBLY INCLUDES:
 TAPE HEAD, MOTOR BELT,
 110VAC MOTOR, PRE-AMP,
 LIGHTS, SWITCHES,
 SOLENOID AND OTHER
 USEFUL PARTS...
 AN EXCEPTIONAL BUY!
 \$7.25 PER ASSEMBLY

JOYSTICK
 PRECISION
 DEVICE...
 CONTAINS 4
 50K CENTER
 TAPPED ALPS
 POTS. \$4.75 ea

VARACTOR DIODES
 BB-103 3 FOR \$1.00
 100 FOR \$30.00
 MV2205 3 FOR \$1.00
 100 FOR \$30.00

MITSUMI MODEL UES-A55 VARACTOR UHF TUNER
 FREQ. RANGE
 470 - 889 MHZ
 ANTENNA INPUT
 300 OHMS
 \$25.00 each
 10 for \$220.00

MINI SIZE BUZZERS
 1 1/2 to 3 volts 75c ea
 WITH WIRE LEADS
 1 1/2 to 3 volts 75c ea
 WITH PIN TERMINALS
 3 to 7 volts
 WITH PIN TERMINALS
 75c each

BLACK PLASTIC CASE
 PAC-TEC SERIES C
 BLACK PLASTIC ENCLOSURE
 ADJUSTABLE HEIGHT FROM
 1.63" TO 2.93"; WIDTH
 6.85"; DEPTH 8". BUILT-
 IN STAND OFFS FOR P.C.
 BOARDS. FRONT AND BACK
 PANELS NOT INCLUDED..
 \$5.25 PER CASE

PHOTO FLASH CAPACITORS
 170 MFD 330 VOLT
 1 1/2" X 7/8" 2 FOR \$1.50
 10 FOR \$7.00
 600 MFD 360 VOLT
 3 3/4" HIGH X 1" DIA.
 \$1.00 EA. 10 FOR \$9.00

SLIDE POTS
 500K linear taper
 2 7/8" LG. - 1 3/4" TRAVEL 75c EACH

MINI BSR



\$17.50 each

AUTOMATIC RECORD CHANGER

* B.S.R. MODEL C136R/C/3
 * PLAYS 33/45/78 RECORDS
 * MINI SIZE: 8 1/4" X 12"
 INCLUDES DUST COVER AND
 PLASTIC CASE (NOT PICTURED)
 WITH FRONT CUT OUT TO FIT
 STEREO UNIT (NOT INCLUDED).

COMPUTER GRADE CAPACITOR
 1700 mfd. 150VDC \$2.00
 2 1/2" DIA X 4 3/4" HIGH
 3,600 mfd. 40VDC \$1.00
 1 3/8" DIA. X 3" HI
 6,400 mfd. 60VDC \$2.50
 1 3/8" DIA X 4 1/4"
 12,000 mfd. 40VDC \$3.00
 2" DIA X 4 1/4" HIGH
 18,000 mfd. 75VDC \$4.00
 2 1/2" DIA X 4 1/2" HIGH
 22,000 mfd. 15VDC 2" DIA X 2 1/2" HIGH \$2.00
 22,000 mfd. 40VDC 2" DIA. X 6" HIGH \$3.00
 25,000 mfd. 75VDC \$4.50
 3" DIA X 4 3/8" HIGH
 45,000 mfd. 25VDC 2" DIA. X 4" HIGH \$3.50
 72,000 mfd. 15VDC 2" DIA. X 4" HIGH \$3.50
COMPUTER GRADE CAPACITOR SPECIAL
 180,000 mfd. at 6V 2 1/2" DIA X 4 1/2" HIGH \$1.50
 CLAMPS TO FIT CAPACITORS 50c ea

TRANSFORMERS
 120 volt primaries
 5.6 VOLTS at 750 mA \$3.00
 6 VOLTS at 150 mA \$1.25
 12 V.C.T. at 500 mA \$2.50
 16.5 V. at 3 AMPS \$6.50
 18 VOLTS at 350 MA \$2.00
 18 VOLTS at 1 AMP \$4.50
 18 V.C.T. at 2 AMP \$5.50
 25.2 V.C.T. at 2.8 AMP \$5.50
 35 V.C.T. at 1 AMP \$3.50
 42 V.C.T. at 1.2 AMP \$4.50
 65 V.C.T. at 2 AMP \$5.50

L.E.D.'s STANDARD JUMBO DIFFUSED
 RED 10 FOR \$1.50
 GREEN 10 FOR \$2.00
 YELLOW 10 FOR \$2.00
FLASHER LED
 5 VOLT OPERATION
 RED JUMBO SIZE 2 FOR \$1.70
BI POLAR LED
 2 FOR \$1.70
SUB MINI LED
 .079" X .098" RED
 20mA at 1.75v
 10 FOR \$1.00
 200 FOR \$18.00
 QUANTITY PRICES AVAILABLE
BLACK LIGHT (ULTRAVIOLET)
 G.E. # F6T5BL \$2.50 each

FREE! SEND FOR OUR NEW 40 PAGE CATALOG FREE!

CONNECTORS WEATHERPROOF 2 CONDUCTOR

POLARIZED SET, 18 GA. WIRE..\$1.00 / SET

4 CONDUCTOR

\$1.50 PER SET
 WEATHER-PROOF SOCKET AND CONNECTOR SET...

EDGE CONNECTOR

ALL ARE .156" SPACING

15/30 GOLD SOLDER EYELET \$2.00 EACH

18/36 GOLD SOLDER EYELET \$2.00 EACH

22/44 GOLD SOLDERTAIL (P.C. STYLE) \$2.50 EA 10 FOR \$22.50

22/44 TIN SOLDERTAIL (P.C. STYLE) \$1.35 EA 10 FOR \$12.50

42/84 GOLD SOLDER EYELET \$4.00 EACH

CANNON XLRA-3-13 CONNECTOR

3 PRONG CHASSIS MOUNT CONNECTOR \$2.00 EACH 10 for \$19.00

2" ALLIGATOR CLIPS

7 clips for \$1.00 100 clips for \$12.00 500 clips for \$50.00

4PDT RELAY

14 pin contacts
 3 amp contacts
 24 volt d.c. or 120 volt a.c. coil
 Used but fully tested
 \$1.70 EACH
 specify coil voltage
 LARGE QUANTITIES AVAILABLE
 SOCKETS FOR RELAY 50c each

6 VDC RELAY

MINIATURE
 D.P.D.T.
 3 AMP CONTACTS
 FUJITSU # FBR321D006
 \$1.75 EA 10 / 16.00

2 CHANNEL LIGHT ORGAN



ORGAN WILL ACCEPT TWO LIGHT STRINGS

L-PAD

STANDARD 8 OHM
 50 DB L-PAD... \$1.50 EACH

MICROWAVE TRANSISTORS

75 ohm CO-AX 12 FOOT R.C.A. PLUGS BOTH ENDS..USED FOR VIDEO GAMES, ETC \$1.25 EA

CRYSTAL

CASE STYLE HC33/U \$3.50 EACH

KEY SWITCH

S.P.S.T.
 4 AMPS @ 125 VAC
 KEY REMOVES BOTH POSITIONS \$3.50 EA
4 POSITION 4 AMPS
 USED FOR CASH REGISTERS @ 125 VAC

6 VDC RELAY

COMES WITH THREE KEYS
 #1 OPERATES 2 POSITIONS
 #2 OPERATES 3 POSITIONS
 #3 OPERATES 4 POSITIONS
 KEY REMOVES ONE POSITION ONLY \$4.50 EACH

8' LINE CORD

SJT M/E 18 - 3
 ROUND GRAY \$2.00 EACH 10 FOR \$18.50
 N.P.N. SILICON SPECIAL PRICE \$2.50 EACH

0-10 MINUTE TIMER

ADJ. TIMING MOTOR FROM 0 - 10 MIN.
 RATED 10 AMPS.
 125 VAC MOUNTS ON 1" CENTERS... \$4.75 EACH

MULTI-SWITCH 8 STATION

INTERLOCKING ASSEMBLY
 4-D.P.D.T./4-4.P.D.T.
 6 1/2" MOUNTING CENTERS
 \$3.00 PER ASSEMBLY

5 STATION

INTERLOCKING ASSEMBLY
 3-4.P.D.T./2-D.P.D.T.
 4 1/8" MOUNTING CENTERS
 \$2.50 PER ASSEMBLY

3 STATION

NON-INTERLOCKING
 2-D.P.D.T./1-4.P.D.T.
 PUSH ON/PUSH OFF STYLE
 2 1/2" MOUNTING CENTERS
 \$1.50 PER ASSEMBLY

LIGHTED PUSH BUTTON

RED LIGHTED 120 VAC 10 AMP. S.P.S.T. "POWER" PRINTED ON FACE. MOUNTS IN 7/8" SQUARE HOLE.. \$1.50 EA 10/ \$13.50

6volt 9amp/hr RECHARGEABLE

ELPOWER # EP690 SOLID GEL CELL 5 1/2" X 4 1/4" X 2 3/4"..... \$15.00 EACH

ALL ELECTRONICS CORP.

905 S. Vermont Ave.
 P.O. BOX 24046
 Los Angeles, Calif. 90006
 TOLL FREE ORDER NO.
 800-826-5432
 AK-HI-CA (213)380-8000
 Mon.-Fri. Saturday
 9 AM - 5 PM 10 AM - 3 PM

TERMS
 * Quantities Limited
 * Min Order \$10.00
 * Add \$2.50 Shipping USA
 * Calif Res Add 6%
 * Parcel Shipping NO COD!

CIRCLE 79 ON FREE INFORMATION CARD



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250 • (213) 973-1921



Introducing THE Pineapple™

48K Color Computer Kit

Easy to assembly! All components are clearly silk screened on the circuit board. Kit includes predrilled double sided PC Board, all integrated circuits, sockets, professional high-impact plastic casing, keyboards, connectors and switching power supply.


Features

- Numeric key pad
- Game paddle jacks on both sides
- Speaker volume control on the back.

Dealer inquiries invited.



\$645⁰⁰ per kit
No C.O.D. orders

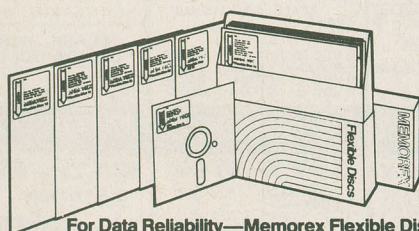


For Data Reliability—Memorex Flexible Discs

5 1/4" Flexible Disc Sale

Why buy other brands when you can buy MEMOREX disc for much less and backed by 1 year factory warranty.

PRICE BREAK-THRU ON APPLE® DRIVE!

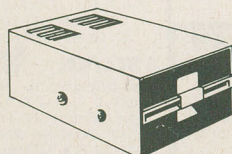100% APPLE Compatible
5 1/4" Floppy Disc Drive



\$295.00 Each
\$375.00 Each
(with controller)

PART #	DESCRIPTION	PRICE
3481	5 1/4"SSDD Soft Sector w/Hub Ring	1-9 \$2.45
3483	5 1/4"SSDD 10 Hard Sector w/Hub Ring	10-99 \$2.15
3485	5 1/4"SSDD16 Hard Sector w/Hub Ring	100-499... \$2.00
		500 & up .. call
		10pcs. 100pcs.
3062	8"SSSD IBM Compatible (128 B/S, 26 sectors)	\$2.15 \$2.00
3015	8"SSSD Shugart Compatible (32 Hard Sector)	\$2.15 \$2.00
3090	8"SSDD IBM Compatible (128 B/S 26 Sectors)	\$2.85 \$2.65
3102	8"DSDD Soft Sector (Unformatted)	\$3.30 \$3.05
3115	8"DSDD Soft Sector (128 B/S, 26 sectors)	\$3.50 \$3.25
3491	5 1/4"DSDD Soft Sector w/Hub Ring	\$3.25 \$3.00
3493	5 1/4"DSDD 10 Hard Sector w/Hub Ring	\$3.25 \$3.00
3495	5 1/4"DSDD 16 Hard Sector w/Hub Ring	\$3.25 \$3.00

MICROPROCESSOR COMPONENTS

Z80	8.75	Z80A-DMA .	28.50	2708	5.95
Z80A	9.25	2102	1.50	2716	9.60
8080A	5.50	21L02	1.50	2516	11.95
Z80-PIO	7.50	2114	2.95	2732	15.95
Z80A-PIO	8.50	2114L	2.95	2532	16.95
Z80A-SIO	29.50	4116	3.00	2764	49.95
Z80A-CTC ...	8.50	1702A	4.95		

SANYO MONITORS

MODEL NO.	DESCRIPTION	LIST	SALE
VM 4509	9" B&W, 10 MHz	\$190.00	\$169.00
DM 5109	9" Green, 10 MHz	\$200.00	\$180.00
DM 8012	12" B&W, 18MHz	\$250.00	\$225.00
DM 8112	12" Green, 18MHz	\$260.00	\$235.00
DMC 6013	13" Color	\$470.00	\$425.00
DMC 6113	13" RGB Color	\$995.00	\$895.00

IC SOCKETS

	LP	WW		LP	WW
8-pin	5/ .75	5/1.91	22-pin	5/1.62	5/4.66
14-pin	5/1.00	5/2.40	24-pin	5/1.80	5/4.77
16-pin	5/1.20	5/2.65	28-pin	5/2.10	5/5.87
18-pin	5/1.35	5/2.98	40-pin	5/3.02	5/6.89
			20-pin	5/1.52	5/4.55


SPECIAL OF THE MONTH

2532 EPROM	4116 (200nS)	2732 EPROM
\$9.95 ea.	8/\$13.50 32/\$43.20	\$8.95 ea.
	LIMITED QUANTITY	



FORMULA INTERNATIONAL INC.

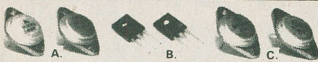12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250 • (213) 973-1921



MATCHED PAIR POWER TRANSISTORS BY MOTOROLA

A. MJ2955	PNP	150 Watts	BV=60V	\$3.50
A. 2N3055	NPN	150 Watts	IC=15A	per pair
B. MJE2955	PNP	90 Watts	BV=60V	\$3.00
B. MJE3055	NPN	90 Watts	IC=10A	per pair
C. MJ15003	NPN	250 Watts	BV=140V	\$12.00
C. MJ15004	PNP	250 Watts	IC=20A	per pair

All above parts guaranteed prime and include data sheets.



HYBRID AUDIO POWER AMPLIFIER IC'S

From 7 WATTS to 100 WATTS

Typical ratings: Operating case temp. 85°C. T.H.D.=0.5%
=20Hz-20KHz. Input resistance Po=0.1W/30KΩ. Power band width 20Hz-20KHz. Freq. response 10-100KHz. Output resistance =8Ω. With built-in protection circuit. All units come with data sheet.

Part No.	Output	Vcc	Unit Price
STK040	10W+10W	±16V	\$14.50
STK041	15W+15W	±20V	\$18.50
STK050	50W	±35V	\$26.50
STK054	23W	±19V	\$13.50
STK056	30W	±22V	\$18.50
STK070	70W	±42V	\$32.50
STK415	7W+7W	30V	\$ 8.50
STK439	15W+15W	39V	\$18.50
STK465	30W+30W	±28V	\$25.50
STK0105	100W	±50V	\$36.50

SANYO ANTENNA SIGNAL BOOSTER

This Booster is specially designed for UHF Channels (14-83). After installing (between the antenna input cable and the UHF tuner), this unit will provide a minimum of 10dB gain, that is approximately 2 times better than you are seeing now. Ideal for those who live in apartments that can not put up an outdoor antenna. Small in size, only 2" x 1 1/2" x 1". Supply voltage is 15 VDC. Back In Stock



★ NEW ITEM ★
MODEL 001-0076
\$12.50 ea.



SANYO UHF VARACTOR TUNER

FOR UHF CHANNEL 14-83

Tuning voltage +1-+28VDC. Input impedance 75Ω. IF band width 7-16MHz. Noise figure 11.5dB Max. Size 2 1/4" x 1 1/4". Supply voltage 15VDC. Sound IF 58.0MHz.
Model 115-B-403A. Video IF 45.0MHz.
Model 115-B-405A. Video IF 62.5MHz


\$35.00 ea.

Tuner is the most important part of the circuit. Don't let those \$19.00 tuners fool you. All units are brand new from Sanyo. When ordering please specify model number.

No FCC License Required.
OUR PRICE \$49.50
ADDITIONAL MICROPHONE (TRANSMITTER) AVAILABLE AT \$28.00 EACH

CRYSTAL CONTROLLED WIRELESS MICROPHONE SYSTEM

Transmitter: FET mic for flat 30-18 KHz response. Xtal controlled 49 MHz AM Band for drift-free performance. 100 MW output (range approx. 1/4 mile) for reliable long range transmission. Powered by a 9V radio battery (included).
Receiver: Xtal controlled locks on 49 MHz transmitter signal. On panel VU meter, monitors the signal strength from the microphone. Standard phone jack output connection to a P.A. or other phone input. 9V battery included. This professional set is ideal for on stage, in field, church, in house or outdoor use.

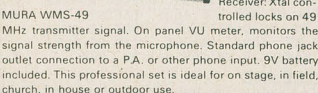


PHONE ORDERS ONLY
CALL TOLL FREE
1-800-672-8758

WHISTLE ACTIVATED SWITCH BOARD

All boards are pre-assembled and tested. Your whistle to its FET condenser microphone from a distance, as far as 30 feet away (sensitivity can be easily adjusted), will turn the switch on and if you whistle again, it will turn off. Ideal for remote control toys, electrical appliance such as lights, coffee pots, TV, Hi-Fi, radio or other projects. Unit works on 9VDC.

MODEL 968 \$4.50 ea.

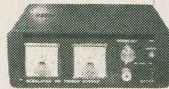


PROFESSIONAL REGULATED VARIABLE DC POWER SUPPLY KIT

All solid state circuitry with high efficiency power transistor 2SD388 and IC voltage regulator MC1733. Output voltage can be adjusted from 0-30V at 1A current limited or 0.15V at 2A current limited. Internal resistance is less than 0.005Ω. ripple and noise less than 1mV, dual on panel meters for voltage and amp reading, also with on board LED and audible over load indicator. Kit comes with board-drilled PC Board, instructions, all necessary electronic components, transformer and a professional looking metal cabinet. The best project for school and the most useful instrument for repairmen. Build one today!

MODEL TR88A 0-15VDC @ 2A
MODEL TR88B 0-30VDC @ 1A

\$59.50 Per Kit

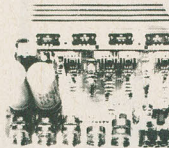

TA-800

120W PURE DC POWER STEREO AMP KIT

Getting power hungry from your small amp? Have to watch your budget? Here's a good solution! The TA-800 is a pure DC amplifier with a built in pre-amp. All coupling capacitors are eliminated to give you a true reproduction of the music. On board tone and volume controls combined with built in power supply make the TA-800 the most compact stereo amp available. Specifications: 60W x 2 into 8Ω. Freq. range: 0-100KHz ±3dB. THD .01% or better. S/N ratio: 80dB. Sensitivity: 3mV into 47K. Power Requirement: ±24-40 Volts.

A GOOD BUY
at \$65.00

SUPER FM WIRELESS MIC KIT — MARK III

This new designed circuit uses high FREQ FET transistors with 2 stage pre-amp. Transmits FM range (88-120MHz) up to 2 blocks away and with the ultra sensitive condenser microphone, that comes with the kit, allows you to pick up any sound within 15 ft. away. Kit includes all electronic parts, OSC coils, and PC Board. Power supply 9VDC.

FMC-105
\$11.50 Per Kit

ULTRASONIC SWITCH KIT

Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver, all electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12VDC.


\$15.50 ea.



LOW TIM DC STEREO PRE-AMP KIT TA-1020

Incorporates brand-new DC design that gives a frequency response from 0-100KHz ±0.5dB. Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation! Specifications: • THD/TIM less than 0.005% • Frequency response DC to 100KHz ±0.5dB • RIAA deviation ±0.2dB • S/N ratio better than 70dB • Sensitivity Phono 2mV 47K/Aux 100mV 100K • Output level 1.3V • Max output 15V • Tone controls Bass ±10dB @ 50Hz/Treble ±10dB @ 15Hz • Power supply ±24VDC @ 0.5A. Kit comes with regulated power supply, all you need is a 48VCT transformer @ 0.5A.

Only \$44.50
X'former
\$4.50 ea.

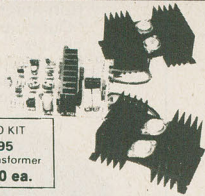

TA-1000 KIT
\$51.95
Power Transformer
\$24.00 ea.

100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low TIM stereo pre-amp. Specifications: • Output power 100W RMS into 8Ω, 125W RMS into 4Ω • Frequency response 10Hz-100KHz • THD less than 0.008% • S/N ratio better than 80dB • Input sensitivity 1V max. • Power supply ±40V @ 5A.

1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6-9VDC

SPECIAL PRICE \$1.95

6W AUDIO AMP KIT


2 LM380 with Volume Control. Power Supply 6-18VDC

Only \$7.50

TA-323 60 WATTS TOTAL 30W + 30W STEREO AMP KIT

This is a solid state all transistor circuitry with on board stereo pre-amp for most microphone or phone input. Power output employs 2 pairs matching Darlingtons Transistors driven by the popular 2N3053 Driver Transistors. Four built on board controls for, volume, balance, treble and bass. Power supply requires 48VCT 2.5A transformer. THD of less than 0.1% between 100Hz-10KHz at full power. (30 Watts + 30 Watts loaded into 8Ω).

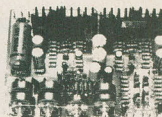★ SPECIAL ★
EXCELLENT PRICE!
MODEL 001-0034
\$29.50 Per Kit
Transformer
\$10.50 ea.



ELECTRONIC DUAL SPEAKER PROTECTOR

Cuts off when circuit is shorted or over loaded to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM \$8.75 ea.

"FISHER" 30 WATT STEREO AMP


MAIN AMP (15W x 2). Kit includes 2 pcs. Fisher PA 301 Hybrid IC, all electronic parts with PC Board. Power supply ±16VDC (not included). Power band with (KF 1%±3dB). Voltage gain 33dB. 20Hz-20KHz.

Super Buy
Only \$18.50

FLUORESCENT AUDIO LEVEL MONITOR

This is the kind of VU monitor that is being used by most amplifier manufacturers. IC's are used to simplify circuit layout. Easy to assemble and can be used with all power level amplifiers. Power requirement 12VDC.

TE-221 KIT
For Just \$28.50
(Limited Stock)

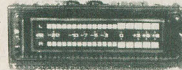

MARK IV — 15 STEP LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED's (15 per channel) to indicate the sound level output of your amplifier from -36dB to +3dB. Comes with a well designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6-12VDC with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W! Kit includes 70 pcs driver transistors, 38 pcs matched 4-color LED's, all other electronic components, PC Board and front panel.

MARK IV KIT
\$31.50



REGULATED DUAL VOLTAGE SUPPLY KIT
± 10-30 VDC @ 250 ma adjustable, fully regulated. Kit includes all electronic parts, filter capacitors, IC's, heat sinks and PC Board.

\$12.50 per kit



AUDIO FREQUENCY SPECTRUM ANALYSER KIT TA-2900

This Audio Frequency Spectrum Analyser analyses audio signals in 10 octaves over a dynamic range of 30 dB. The technique allows the sound "coloration" introduced by unwanted room and speaker resonances to be substantially eliminated.

The TA-2900 provides a visual presentation of the changing spectrum thru 100 red LED displays. So you can actually see proof of the equalized sound you've achieved. The TA-2900 kit comes with all the electronic components, I.C., predrilled PC board, the instructions, and a 19" Rack Mount type metal cabinet with professional silkscreen printed front panel.

Specifications:
• Input Sensitivity: Tape Monitor/10mV - 18mV 50K Ohms. Speaker Terminal/0.2W - 100W 8 Ohms.
• Display Level Range (all octaves): 2dB per step/—14dB to -4dB
• Delay Time (1 KHz): Fast/18dB/s Slow/6dB/s
• Power Input 117V or 220V AC 50/60 Hz
• Power Consumption: 36W
• Dimensions 482(W) x 102(H) x 250(D) mm

\$99.50 per kit

POWER SUPPLY KIT

0-30VDC REGULATED. Uses UA723 and 2N3055 power transistor. Output can be adjusted from 0-30V @ 2A. Complete with PC Board and all electronic parts.

TRANSFORMER \$9.50 ea.
POWER SUPPLY KIT \$10.50 ea.

PROFESSIONAL FM WIRELESS MICROPHONE

Made by one of the leading Japanese manufacturers. This factory assembled FM wireless microphone is powered by two AA size batteries. It transmits in the range of 88-108 MHz. Element is built in a plastic tube type case with an omnidirectional electronic condenser microphone unit. By using a standard FM radio, signal can be heard anywhere on a one-acre lot. Sound quality was judged "very good." MODEL WEM-36.

WAS \$16.50
ON SALE
\$12.50 each



PRESS-A-LIGHT
SELF GENERATED
FLASHLIGHT

Never worry about battery, because it has none! Easy to carry in pocket and handy to use. Ideal for emergency light. It generates its own electricity by squeezing grip lever. Put one in your car, boat, camper or home. You may need it some time!

EXCLUSIVE \$3.95 ea.

FLUORESCENT LIGHT DRIVER KIT

12V DC POWERED... Lights up 8-15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board. Light tube not included.

\$6.50 Per Kit

SOLAR CELLS

0.5V 200MA. Ideal for all kinds of solar projects. Cells can be put in series to double voltage or parallel to double current.

\$1.99 ea.

FOR COMMERCIAL FREE TV BOX BUILDERS

MC1358 \$3.00 ea.	LM380 \$2.00 ea.
MC1350 \$2.25 ea.	LM7815 \$1.20 ea.
MC1330 \$3.00 ea.	LM7818 \$1.20 ea.
MC1496 \$2.50 ea.	10K10T P.C. Mount \$3.00 ea.
MC1458 \$1.00 ea.	10K1T P.C. Mount \$1.75 ea.
LM1889 \$3.75 ea.	Toroid Coils (set of 4) \$3.00 ea.
NE565 \$2.19 ea.	5-35pF (Trimmer Cap) \$5.00 ea.
NE564 \$3.45 ea.	Power Transformer 18v8A\$3.50 ea.

NEW ARRIVALS

6-WAY A/C ADAPTOR

Input: 110v A/C Output: 3v, 4.5v, 6v, 7.5v & 12VDC Current: 300mA

OUR LOW PRICE
\$5.50 each

19" RACK MOUNT CABINETS

Black anodized front panel with black textured case.

WIDTH	DEPTH	HEIGHT	PRICE
17"	11 1/2"	3"	\$25.50
17"	11 1/2"	5"	\$31.50
17"	11 1/2"	7"	\$39.50

SHIPPING AND HANDLING CHARGES
Under \$50.00 Purchase Over \$50.00 Purchase
10% 5%
15% 10%
25% 20%


Inside California
Outside Calif. (Incl. Mexico & Canada)
Overseas

Minimum Order \$10.00 / Calif. Residents add 6.5% Sales Tax. Phone Orders Accepted on VISA or MC ONLY. NO C.O.D.'s. Prices subject to change without notice.

CIRCLE 70 ON FREE INFORMATION CARD

Brand New Micro Computer Power Supply

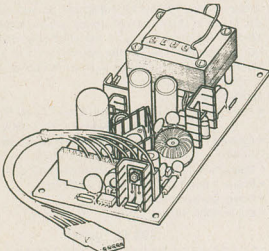- * Switching regulation
- * Multiple DC outputs:
+5V 4A -12V 1A
+12V 1A -2.2 to 15V 0.5A
- * Fiberglass PCB
- * Over-voltage protection with IC monitor
- * 110/220 V input
- * Factory assembled
- * Circuit diagram available
(for a copy, send self-addressed/stamped envelope)
- * \$49.00 each, freight prepaid
(Calif residents pls add \$3 sales tax)



FUJITECH AUDIO KITS

LATEST AUDIO TECHNOLOGY FROM JAPAN


Send \$5.00 for each assembly manual, refundable with order.

Monarchy Engineering, Inc.
380 Swift Avenue, Unit 21
South San Francisco, CA 94080

Visa or Mastercharge acceptable.

Model A501 Power Amp

- * Pure Class A 25W + 25W
- * Switchable to Class AB 100W + 100W
- * Switchable to Bridge Class A 100W mono
- * Switchable to Bridge Class AB 300W mono
- * Frequency Response 5-200KHz (-1dB)
- * Signal-to-Noise Ratio 120dB
- * Non-magnetic Chassis
- * "Out-board" comprehensive protection circuitry
- * DC circuitry with limited use of NFB
- * High Efficiency Fluid Convection Cooling
- * THD under 0.007%

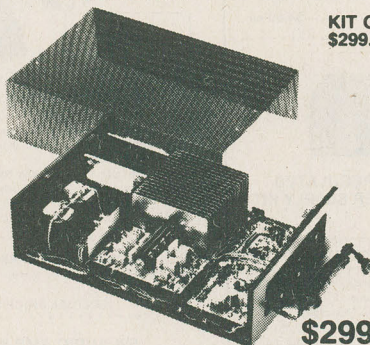


KIT ONLY
\$299.00

\$299.00

Model A502 DC Stereo Control Center

- * Direct DC coupling from Input to Output
- * DC servo circuitry
- * Cascade FET Input in all stages
- * Separate Moving Coil RIAA amplifier
- * Distortion below 0.005% (3V)
- * Max Output 15V
- * Frequency Response 20Hz-20KHz ± 0.2 dB
- * Maximum Phono Input
MC = 16mv RMS (1KHz)
MM = 270mv RMS (1KHz)
- * Built-in Headphone amplifier
- * Relay Output Muting

KIT ONLY
\$349.00

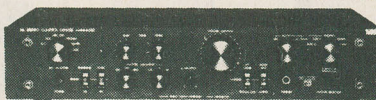

\$349.00

B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228

(214) 271-5546

Visa • MasterCard • American Express

STATIC RAM

21L02-1KX1 250 n.s.	
Low Power	.95
2114L-3 1KX4 300 n.s.	
Low Power	2.75 8/17.50
HM6116P-4-2KX8 +5v-200 n.s.	
CMOS Low Power 2716	
Style Pin Out	8/59.95
TMM2016-2KX8 +5v-NMOS	
200 n.s. - 2716 Style	
Pin Out	8/59.95
6501-5 256X4 - CMOS - Data	
Retention 2 Volts - 22 Pin - 200 n.s.	
Typ. 5V Very Low Power	1.50
6514 J-5 1KX4-CMOS Super Low	
Power 350 n.s. Similar to 2114	
Same Pin Out	2.95
8108-5 1KX8 NMOS 5V 500 NS	
22 Pin	2.50

4K STATIC RAMS

LESS THAN 94¢ EACH
MK4104J-4 - 250 N.S. 18 Pin Ceramic
Computer Mfg. Surplus. PRIME. Fully
Static easy to Use. Has Same Pin Out as
TMS4044, but slightly different timing.
With Specs. (Mostek)

8 for 8.95 32 for 29.95
VERY LOW POWER!

DYNAMIC RAM

5280N-5 (2107B-4 • TMS4060)	
4KX1 22 Pin	8/3.95
4027-4KX1-250 n.s.	1.75
4116-16KX1-200 n.s.	8/14.95
4164 +5v 64K	12.95 8/79.95

PRECISION HYBRID OSCILLATOR MODULE

Has both 1 MHz and 2 MHz TTL - outputs -
Hermetically sealed - Ultra high stability over
wide temp. range - originally cost over \$40.00
each - we made a super purchase from a major
computer manufacturer - 5 Volt operation - fits
standard 24 pin socket - Manufactured by
Motorola oscillator division 7.50 (w/data)
MCS871A 3/20.00

SOCKETS

Low Profile Solder	
8 Pin	13/1.00
14 Pin	10/1.00
16 Pin	8/1.00
18 Pin	8/1.00
20 Pin	7/1.00
24 Pin	6/1.00
28 Pin	6/1.00
40 Pin	5/1.00

Buy \$10 Get \$1.00
FREE CHOICE

CPU

8035	6.95
8039	7.95
8748 Intel	15.95

74LS

LS00	.24	LS125	.95	LS243	1.49
LS02	.24	LS138	.79	LS244	.99
LS04	.24	LS139	.79	LS245	1.95
LS05	.24	LS151	.79	LS257	.79
LS08	.24	LS153	.79	LS266	.59
LS10	.24	LS154	1.75	LS283	.99
LS14	.89	LS157	.79	LS290	.99
LS20	.24	LS161	.99	LS293	1.75
LS27	.24	LS164	.99	LS298	.89
LS30	.24	LS166	.99	LS367	.79
LS32	.36	LS175	.89	LS368	.79
LS42	.49	LS181	1.99	LS373	.99
LS74	.44	LS192	.89	LS374	1.49
LS85	.95	LS193	.89	LS375	1.19
LS86	.39	LS221	1.10	LS377	1.49
LS90	.69	LS240	.99	LS390	1.19
LS109	.39	LS241	.99	LS393	1.19
LS123	.99	LS242	1.49	LS399	.99

MISCELLANEOUS

AY3-8910-Sound Chip with 60	12.95
page data manual	
DM8131 6 Bit Unified Bus	2.99
Comparator	
8 Pin Dip Shunt	3/1.00
TR1602-UART same as	
AY5-1013	1.99
IM6402+5v High speed	
UART-AY5-1013 pin out	2.00
MC1408L6 D to A Converter	
8 Bit	1.79
AD561J D to A Converter	
10 Bit	1.79
1771 Single Density FDC	22.50
1791 Double Density FDC	29.95
5027-CRT Controller -	
Programmable - 24 x 80	14.95
68B45 - Motorola (HD46505SP)	
CRT Controller	17.59
82S123-32X8 Tri State Bi polar	
PROM	1.99
82S129 Tri State Bi Polar Prom	1.99

EPROM

1702A 256X8 1 us	2.50
2708 1KX8 450 n.s.	2.95
27A08 1KX8 350 n.s.	3.95
2716 2KX8+5v 450 n.s.	5.95
(Buy 2 Get 1 FREE.)	
2716-1 2KX8+5v 350 n.s.	7.95
2732 4KX8 450 n.s. Intel Pin Out	9.95
2732A-3 4K x 8 350 n.s.	
Intel Pin Out Low Power	11.95
2532 4KX8 450 n.s. T.I. Pin Out	9.95
Z80	
Z80 2.5 MHZ CPU	4.95
Z80DMA-DMA Controller	9.95
Z80PIO - Parallel	5.95
Z80SIO/O Chan. Ser.	16.95
Z80A-4MHZ CPU	8.95
Z80A SIO/O	19.95

CALL OR WRITE FOR PRICES ON CMOS-8080 - BIT SLICE - TTL - 74S - CRYSTALS - DIP SWITCHES
TE RMS: Add \$1.50 postage, we pay balance. Orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 5% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - U.S. funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.

CABLE TV


CONVERTERS DESCRAMBLERS

Largest Selection
of Equipment Available
\$ Buy Warehouse Direct & Save \$



36 channel
converter
\$45.95

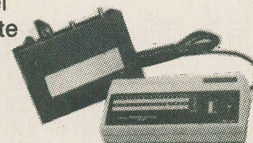36 channel
wired remote
converter
only
\$88.95




Send \$2 for complete catalog
of converters and unscramblers

Quantity Discounts • Visa • Master Charge
Add 5% shipping—Mich. residents add 4% sales tax

C&D Electronics, Inc.

P.O. Box 21, Jenison, MI 49428
(616) 669-2440

MICROWAVE EQUIPMENT

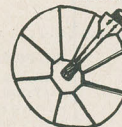


HI-GAIN, LOW NOISE, 2.1-2.4Ghz.
MICROWAVE RECEIVING SYSTEM
COMPLETE ---READY TO INSTALL.
INCLUDES 20" PARABOLIC ANTENNA,
DOWN CONVERTER, POWER SUPPLY,
ALL CABLES AND CONNECTORS WITH
COMPLETE INSTRUCTIONS FOR EASY
INSTALLATION.
COMPLETE SYSTEM - U.S. SHIPPING FREE - \$119
BUY 5 SYSTEMS at \$104 each
(six month limited warranty)

SUPER LED's

2amp. rating w/heat sink

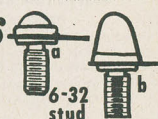ME2 IR (a) 25A pulse
ME5 IR (b)
MV4 RED (a) \$4.95 each



RESISTOR SALE

.25W 5% carbon film- \$1.50 per 100 (one value)
all standard values from \$12 per 1000
2.7 to 4.7M ohms

8085	NEC CERAMIC 40 PIN MICROPROCESSOR	\$6.95
MM5290J	NSC 16Kx1 DYNAMIC RAM (4116) CERAMIC	2.95
B2758	INTEL EPROM 1Kx8 24 PIN CERAMIC	3.95
TRIAC	RCA 8 AMP 600V TO-220 TAB CASE	.75
VOX	VOICE ACTUATED SW. (SCR, MIC, AMP.)	.95
H11A-2	G.E. OPTO ISOLATOR 6 PIN DIP	.25
5101	256x4 CMOS RANDOM ACCESS MEMORY DIP	2.95
TRIAC	25 AMP 400V ON 3"x6" ALUMINUMS HS	2.95
7402	TTL QUAD 2 IN NOR GATE DIP	.10
7430	TTL 8 INPUT NAND GATE DIP	.10
7440	TTL DUAL 4 INPUT BUFFER DIP	.10
TO-92	PNP TRANSISTOR PAK 100 PRIME FOR	5.00
LM747	DUAL 741 OPERATIONAL AMPLIFIER DIP	.50
LH0021	NSC 1 AMP OPERATIONAL AMPLIFIER TO3	5.00
2504T	1024 BIT DYNAMIC SHIFT REGISTER TO-5	1.00
2416	INTEL 256x24 CHARGE COUPLED MEMORY	2.50
5244	INTEL DRIVER FOR ABOVE MEMORY	3.50
12P15/15	DC TO DC CONVERTER- 12VDC TO DUAL	
	15V AT 40MA OUTPUT, CAN BE PLUS	
	OR MINUS 15 OR 30V 24 PIN DIP	7.95

4811 MYRTLE AVE
PO BOX 41778
Sacramento, Ca.
95841

we pay post on orders for \$10 or more
payment must be in U.S. funds. Foreign
orders must include post BAC, MC are
not prepaid and shipping is added.

916 334 2161

**BABYLON
ELECTRONICS**

Your
BANKAMERICARD
welcome here

CIRCLE 102 ON FREE INFORMATION CARD


Poly Paks, INC.

Quality Electronics For Less!

BRAND NEW!
FIRST TIME ANYWHERE!

I R SCIENTIFIC INFRARED VIEWER KIT

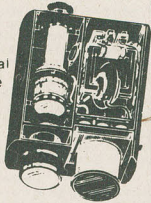- An Easy To Assemble Kit
- Everything You Need Including Comprehensive Instruction Manual
- Lightweight, Binocular-Type Case
- Factory Preselected & Pretested Components
- For: Night Surveillance, I R Communications & Control, Document Authentication, Thermal Viewing, & More



See in the Dark!!

Special Introductory Price

\$169.95

Shipping & Handling add \$4 per unit (\$6 outside U.S.)
MASS. RES. ADD 5% SALES TAX

SPECIFICATIONS:

- Image Converter — type 6032
- Spectral Response — 500 to 1200 nanometers (800 max)
- Resolution — 50 lines/mm
- Magnification — 3X
- Focus Range — 3 ft. to infinity
- Lens — 150mm, f 3.0 10° field infrared telephoto and 10 X Ramsden Eyepiece
- Infrared Source — 900 nanometer, 4500 max. candlepower
- Case Size — 7 3/4" X 6 1/2" X 2 3/4"
- Power Requirement — 6 V DC (4 "D" cells or equiv.)

Ask for FREE POLY PAKS CATALOG

Order by Mail or Call TOLL FREE

800-343-3086

Mass. Res. Call 617-245-3828

ORDER SHIPPED IN 24 HRS.

Poly Paks
P.O. Box 942, RE-9
S. Lynnfield, MA 01940



CIRCLE 87 ON FREE INFORMATION CARD

over 1600 products!

includes technical tips & information

FREE CATALOG

Burglar/Fire Alarms Security Products



- Alarm Controls • Remote Stations
- Infrared • Motion Detectors • Sirens
- Microwave • CCTV • Fire Detectors
- Vehicle Alarms • Phone Dialers
- Key Locks • Wireless Components
- Magnetic Contacts • Glass Protection
- Lights • System Parts • Tools • Books
- Bells • Ionization Smoke Detectors

mountain west

4215 N. 16th Street Dept. RE-9
Phoenix, AZ 85016
1-800-528-6169

CIRCLE 97 ON FREE INFORMATION CARD

(602) 266-9758 (602) 234-3026



ARIZONA ELECTRONIC
SURPLUS



6835 N. 16th St. • Phoenix, AZ 85016

MICRO WAVE DOWN CONVERTER KIT (HMR II type)

PC Bd, 3-MRF901's, 2-MBD 101's,
1 Thermistor, 1 Choke, 3-Chip Caps,
1 "F" Connector, 8 Resistors
+ Instructions


\$39.95

POWER SUPPLY

12-18v
D.C.

\$19.90

BUY BOTH FOR ONLY **\$53.99**

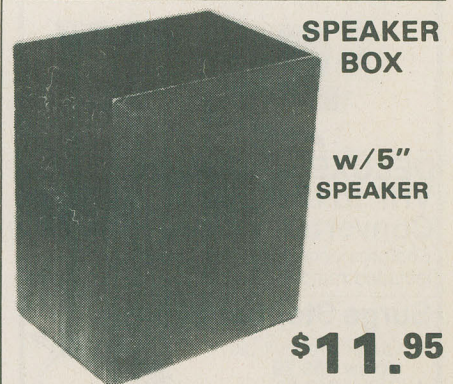


**SPEAKER
BOX**

w/5"
SPEAKER

\$11.95

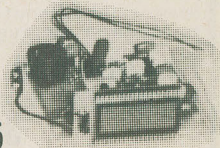PULSE RATE INDICATORS USED FOR HEART MONITORS 100% Functional



\$19.95

Includes:

- 5" LCD Readout
- ICL 7106 CPL A-D Decoder Driver
- MC 14016
- MC 14013

- MC 14584
- LM 32 YN
- TL 064 CN
- Piezo Buzzer
- 9 V. Batt. Clip
- Misc. Elect. Components


NEW PLASTIC CASE

Made for Heart Monitor above.

\$1.55

- Includes:
- 9 V. Batt. Holder
 - Front Bezel

Excellent for Frequency Counter.

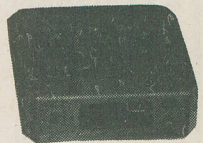

4" LINE CORD



45¢

ALL ORDERS SHIPPED SAME DAY VIA UPS



Postage & Handling Not Included



(602) 266-9758 (602) 234-3026

CIRCLE 92 ON FREE INFORMATION CARD

DON'T
FORGET




USE
YOUR
READER
SERVICE
CARD

Summer Sale!!

I/O "SELECTRIC" TYPEWRITER

REDUCED!!! (This Month Only)

Regularly \$399.00

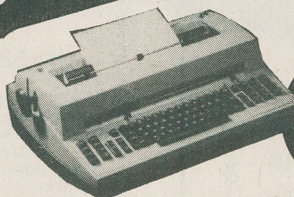

SAVE
\$50.00!!

\$349.00
EA.

- Fully Operational
- TTL Input/Output Level
- USE AS A TYPEWRITER
- Software or Hardware Driven
- Spare Parts Available, Too
- Full 15" Platen
- IBM Model 745

These fabulous typewriter/printers originally cost over \$1000.00 each!! Each machine is fully tested and operational and only requires 5VDC and 24 VDC for I/O capability. Electronic Repeat (when activated) is capable of repeating ANY character or key. Soon we will be offering software, then hardware interfaces for these terrific machines, meanwhile SAVE 50 BUCKS.

Only \$349.00 ea.



DIGITAL MUSICAL KEYBOARDS

Only **\$69.00**
Each

Write or Call for Our FREE Exciting NEW FLYER!!!

**Computer
Products &
Peripherals
Unlimited**

WAREHOUSE:
18 Granite St., Haverhill, Mass. 01830
MAIL ORDERS:
Box 204, Newton, New Hampshire 03858
TELEPHONE ORDERS:
617/372-8637
Sorry, No Collect Calls
Mastercard & VISA Accepted

CIRCLE 103 ON FREE INFORMATION CARD


SPARTAN Electronics Inc.



CALL (516) 499-9500
MAIL

6094 Jericho Tpke.
Commack, N.Y. 11752

Remote T.V. Converter

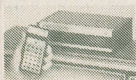

139.95 Ea.
4 & up 125.00
60 Channel
Wireless Control

Commodore Color-



VIC-20
Color-Sound-
Graphics
\$259.


Cassette Player \$69.00

Logic Probe

Global Specialties #LP-2

\$28.49

DTL/TTL/CMOS

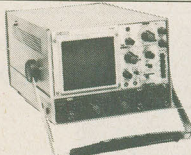

BK PRECISION

\$991

DELUXE 40 CHANNEL VHF to UHF Block Converter



Features accessible fine tuning knob
included: matching X former and two cables

Surge Stopper Brooks

4 Outlet w/circuit bkr.
led/sw \$59.79
1 Outlet \$43.50




Now you can have Maximum Protection
for your sensitive electronic equipment.

Refurbished Monitors

12" diagonal
39.95



Atari 800 w/16K RAM \$659

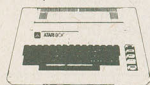

Atari 400 w/16K \$289

42 Channel CATV Converter

w/on/off Fine Tuning
\$94.95



40 Channel VHF to UHF Block Converter



28.95 Ea.
24.95 4 & up

Volume Discounts

Min. Order \$10.00
International shipping Add'l
Prices subject to change
without notice.
COD 2.00 Extra

• Visa, MC, BAC, Amex, Check, COD, Money Order	• Add For Shipping
to 75.00	\$2.50
76.00 to 250.00	\$4.50
251.00 to 500.00	\$6.00
501.00 to 750.00	\$8.50
751.00 to 1000.00	\$12.00
Over 1000.00	\$12.50

(516) 499-9500
Mon Th 9-8
Tu W F 9-6
Sa 9:30-5


BEC BULLET ELECTRONICS

P.O. BOX 401244R

GARLAND, TX. 75040

(214) 278-3553

Sound Effects Kit \$18.50

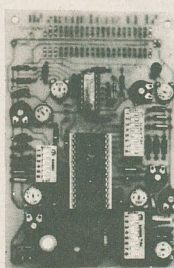

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included). 76477 is included. Available separately for \$3.15 each.


The Super Music Maker

REVISION 2

\$24.95

(Basic Kit)

SEE SPECIAL OFFER BELOW

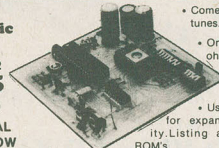

- Comes with 25 pre-programmed tunes.
- On board 7 watt amplifier drives 8 ohm speaker directly.
- Works on 12VAC or 12 VDC.
- Uses either 2708 or 2716 EPROM for expanded tune playing capability. Listing available pre-programmed ROM's.

A true electronic music maker based on a microprocessor chip. The Super Music Maker is the only kit that allows easy addition of pre-programmed tunes by plugging in one memory chip (ROM). Over 20 different ROM's with over 500 tunes are available. Use the kit for a Car Horn, Doorbell, Door Announcer, etc. If you have an EPROM programmer our manual tells you how to program your own tunes. Kit includes quality plated and drilled PC Board and all components.

OPTIONAL ACCESSORIES

DIP SWITCHES One 8 pos., one 5 pos., for tune address 2.00/set
WALLPLUG TRANSFORMER For operation on 117VAC house current 3.00
INJECTION MOLDED PLASTIC CASE w/custom front & rear panels, hardware and 2 five pos. rotary switches (replaces DIP switches) 8.00
HORN SPEAKER 8 watt, 8 Ohm with mounting bracket 6.25

SPECIAL OFFER

Buy a Super Music Maker kit for \$24.95 and get FREE, a 2708 ROM pre-programmed with 35 popular tunes. This offer gives you over 60 songs to choose from!

7 Watt Audio Amp Kit \$6.95

SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.


Doomsday Alarm Kit \$9.95

If you have trouble sleeping and you would like the rest of the neighborhood to share your misery, then this little kit will be for you! There is no way to accurately describe the unearthly howls, screams and tones that come out of this kit. Four separate tone oscillators are mixed, cancelled and stepped at a varying rate. 10 Watts of crazy sounds. A great fun kit or a practical burglar alarm. Complete with PC board and all necessary components less speaker. For 6-12 VDC. ORDER DA-02.

THE PRESIDENT SAYS: "HOGWASH!!"

After taking one look at the TRIPUT POWER SUPPLY our engineer declared that the units were worth several hundred dollars each. He pointed out the engineering, high quality construction and state-of-the-art integrated design in support of his position. The President of BEC more pragmatically pointed out the already full warehouse and the two trailer truck loads of power supplies waiting in the parking lot, and set the price to move them QUICKLY!

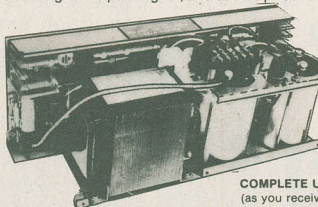3 OUTPUTS
12V @ 8A (12A Int.)
5V @ 10A
-12V @ 5A
INPUT 105 - 125VAC



COMPLETE UNIT
(as you receive it)

62.50

Plus \$5.00 Freight

21 lbs. 6 x 5 1/2 x 12

ONE TIME OFFER! LIMIT TWO (2) SUPPLIES PER CUSTOMER.

- UNIT IS COMPLETELY ASSEMBLED!
- Fused primary and DC sections
- HUGE SHIELDED TRANSFORMER
- 2% Load & Line Regulation
- Low Ripple <100mV
- Short Circuit Protection
- Overvoltage Protection on all three outputs
- 25A Bridge Rectifier
- Over 60,000 mfd of filters
- High Efficiency Switching Regulator reduces heatsink area
- Schematics and service guide included
- Thermal Shutdown
- Status LED's (3)

Macro PROFITS! MICROWAVE ANTENNAS at micro \$19.95 to \$169.95 prices

Amateur 32-Element Yagi Antenna

- Not a kit, so it's easier to sell • 1.9-2.5 Ghz
- 38 1/2" long • Die-cast waterproof aluminum housing • Withstands temps -40° to +140°F. • 50-ohm type "N" connector • Mounting hardware included.

Only \$19.95



2 Ghz MICROWAVE ANTENNA

with 52 dB Overall Gain

- Built-in down converters • Tune 1.9-2.5 Ghz • Operates on channels 2-6 • 22 db gain resonant disc antenna • Standard 12-16 vdc power supply • Mounting bracket for horizontal or vertical polarity • Comes with: 60' coax with connectors, 3' jumper cable, 75-300 ohm and 300-75 ohm adapters, complete instruction.

\$129.95



LONG-RANGE MICROWAVE ANTENNAS with Separate Down Converters FULL-YEAR WARRANTIES!

58 dB Gain


Just \$144.95

62 dB Gain

Only \$169.95



- Tuneable temp-compensated L.O. • Power supply with built-in A-B switch
- High gain, low noise figures • Convenient mounting tabs • Weather-resistant housings • For distant or low signal areas • Two microwave pre-amp stages • 2.1-2.3 Ghz • 20 Mhz input band-width • Noise figure: 5 dB
- TV channels 2-6 • 75-ohm type "F" output • 50-ohm type "N" input impedance • Aluminum housing • Withstands temps from -40° to +140°F.

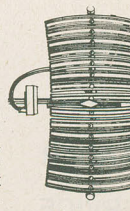

Dealer inquiries invited.

East Coast: N.C.I. INC.

79-59 264th St.
Floral Park, N.Y. 11004

212-929-3505/212-544-5990

West Coast: Galaxy Electronics

600 N. 61st Ave.
Glendale, Arizona 85301

602-247-1151


KNAPCO

G.E. MOV Spike Eliminators

10/\$9.90 \$1.29




Transformer

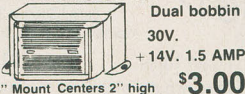

Dual bobbin
30V.
+14V. 1.5 AMP
\$3.00

Chassis (H.D.)

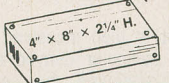

Fantastic!
79¢

115 V. BLOCK FANS




4 1/2" SQ.
#FAN 41
3" SQ.
#FAN 31
\$6.95

2 1/2" Meters



0-15 VDC
0-20 VDC
0-150 VAC
30-0-30 DCA
Any 1
\$5.95

Tri-Color LEDS

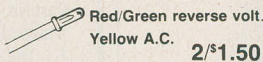

Red/Green reverse volt.
Yellow A.C.
2/\$1.50

Infrared Emitter and Photo Diode Detector


XC880-A
TIL413 short leads 1 pr. \$2.00

Mura Cordless Telephone



As is Complete
with schematics
\$43.50

BROAD BAND AMPS.

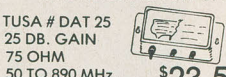

TUSA # DAT 25
25 DB. GAIN
75 OHM
50 TO 890 MHZ.
\$23.50

Voltage Regulators



+5V. 7805
-5V. 79M05
+6V. 7806
+12V. 7812
5/\$5.50 10/\$9.95

MOTOROLA PIEZO SPEAKERS



3 1/4"
RESPONSE
60 TO 30,000 Hz
SPECIAL
\$6.95

C & K Sub Mini



N.O. Pushbutton
Switch 10/\$3.00 #8631

ASSORTED LEECRAFT INDICATORS



#31 (SNAP-IN)
RED, AMBER,
DUALS
115V.
10/\$3.95

TRANSFORMER



36V.
200 MA.
99¢


SEND FOR
FREE 1982
CATALOG
or call us at
(813) 392-0406

General Instrument Varactor Tuners



Your Choice
VHF - UHF
\$22.50


Mini Switches

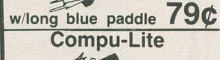

Micro Switch
SPDT
w/long blue paddle 79¢
Compu-Lite
red push (illuminated)
mom #849-1191 69¢

add 10% for shipping and handling min charge \$2.50
FOREIGN CATALOGS
SEND \$1.00

Voltage Regulator Boards

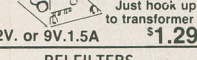

Just hook up to transformer
12V. or 9V. 1.5A
\$1.29

RFI FILTERS




2 AMP. HOPKINS
#F-85010 \$1.95
6 AMP. CORCOM
#6EF1 \$2.95

Dip Tantalum Caps



6.8, 10, 15, 22, 33, 47, @ 6.3V
22, 68 @ 10V
1.5, 3.3, 4.7, 6.8 @ 16V
15 @ 20V
47, 68, 1.5, 22, 33, 4.7, 6.8 @ 35V
22, 68, 1 @ 50V. dipped and solid
29¢

KEMET CHIP CAPS

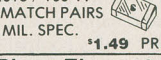

.018 / 100 V.
MATCH PAIRS
MIL. SPEC.
\$1.49 PR.

Piezo Elements



Fantastic
Mike-Speaker
8 watt
\$39¢

Audio Amplifier




4" x 3" x 2" H
\$5.95

H.J. Knapp of Florida, Inc.
4750 96th St. N. St. Petersburg, Florida 33708

CIRCLE 90 ON FREE INFORMATION CARD

MORE GAIN Than a Mitsumi Tuner PHILIPS VARACTOR TUNER — \$23.95

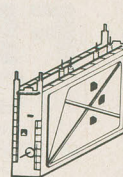MODEL ELC 1045
FREQ. RANGE
UHF 470-889 MHZ
CHANNEL 14-83
OUTPUT CHANNEL 3
75 OHM INPUT



Part No.	Philips UHF Tuner ELC 1045	\$23.95
DSW10	Printed Circuit Board, Predrilled	
DSW20	Glass Epoxy	\$15.00
DSW30	P.C.B. Potentiometers 5-10K, 1-5K	\$5.95
DSW40	Resistor Kit 1/4 watt 5% Carbon Resistors 32 pcs.	\$4.95
DSW50	Panel Mount Potentiometers 2-10K and Knobs	\$2.95
DSW60	IC's 7 pcs., 1 Rectifier, 2 Regulators & 1 Heat Sink	\$15.95
DSW70	Electrolytic Cap Kit, 8 pcs.	\$4.95
DSW80	Ceramic Cap Kit, 33 pcs.	\$6.95
DSW90	Variable Trimmer Kit, 4 pcs.	\$3.95
DSW100	Coil Kit, 2-18 uh, 1 variable 33 uh +1- + 37-12 Toroid + 26 wire	\$1.95
DSW110	I.C. Sockets 5-8 pins, 2-14 pin	\$4.95
DSW120	Power Transformer PRI-117Vac, SEC. 24Vac, 1 amp	\$5.95
DSW130	Speaker, Oval 8 ohm	\$3.00
DSW140	Misc. Parts, Hardware & Hookwire Ant. Term, Switch Dpdt, Fuse, Fuseholder, Line Cord, etc.	\$7.95
When Ordering All Items		
DSW10-D140	Total Price	\$99.95


R.F. Modulator



Combine both audio and video output onto channel 3 or 4 of your T.V. set.
Single I.C. chip (MC 1374) makes for quick and easy assembly. Single adjustment control! A must for every video recording or computer enthusiast.

VH-0 Kit \$19.95

UHF T.V. Preamp

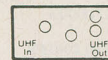

Features:
• 25 dB gain!
• Kit

Your reception will dramatically improve! This unit will enable you to pull in signals you never knew were there!

For both indoor and outdoor use. Input and output impedance 75 ohm. No adjustment! Easy assembly.

JH-0 Kit \$22.95

Microwave Receiver 1.9-2.5 GHZ



PS-1	Assembled 32 element antenna	\$19.95
PS-2	20 dB gain microwave receiver kit with variable power supply kit	\$50.00
PS-3	Complete package PS-1 & PS-2	\$65.00
Mounting Hardware Included		

Available by Mail Order only
Send check or money order to

STAVIS ELECTRONICS, INC.
912 W. Touhy Avenue
Park Ridge, Illinois 60068
(312) 692-5223

Minimum order \$15.00. Add 10% shipping on orders under \$35.00. Orders over \$35.00, add 5%.
Catalog - \$1.00. Visa & Mastercard acceptable

CIRCLE 93 ON FREE INFORMATION CARD

UHF TUNER



TOP QUALITY. UHF TUNERS ARE BRAND NEW, TESTED, TOP PERFORMERS! GREAT FOR REPLACEMENT USE, CABLE CONVERTERS, DESCABLERS, HAM BAND CONVERTERS, ETC. ETC.

SOCKET JUMPER CONNECTORS




C-7030 50 PIN
C-7035 20 PIN
\$1.75
ACCEPT RIBBON CABLE, CLINCH TO PERMANENTLY CONNECT. BOTH HAVE GOLD CONTACTS

Brand New 115 VAC 8 Track TAPE DECK WITH PLAYBACK AMP



3 LB
X-6950
\$6.95
COMPLETE 8 TRACK TRANSPORT

Stepping MOTORS

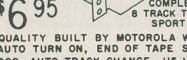

SIGMA MODEL NO. 20-2223D200
FEATURES A STEP ANGLE OF 1.8°, MAX SPEED OF 4000 STEPS/SEC, 40 OZ-IN OF TORQUE, 9 WATTS DISIPATION. ABSOLUTE ERROR OF 0.06°, NON-CUMULATIVE. BRING YOUR ROBOTS TO LIFE, BUILD X-Y PLOTTERS, HAVE POSITIONAL FUN! THESE ARE NEW, CURRENT PRODUCTION, WITH A LIST PRICE OVER \$100.00!!
M-2140 (1.3 LB) \$10.00

ILLUMINATED INTERLOCKING 7-POSITION PUSH-BUTTON SWITCH



8-3017
6 LB
\$4.95
SWITCHCRAFT ASSEMBLY. ORIGINALLY COST OVER \$30. FEATURES DOT EACH POSITION, WITH SILVER CONTACT LEAF SWITCHES THAT WILL OUTLIVE BOTH OF US! SOCKETS ACCEPT ANY T-3/4 FLANGE BULB, FRONT REPLACEABLE. BUTTONS ARE .9" HI, 0.6 W, 4.4" WIDE OVERALL


FREE CATALOG

DIP SOCKETS




8 PIN 16¢
S-0800
14 PIN 18¢
S-1400
16 PIN 20¢
S-1600
18 PIN 25¢
S-1800
24 PIN 38¢
S-2400
28 PIN 45¢
S-2800
40 PIN 55¢
S-4000

12 VDC RELAY

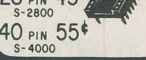

20 AMP 3/4 HP CONTACTS
P & B AMF TYPE KRP 3 DH WITH ONE LARGE SPST N.O. CONTACT--GREAT FOR MOTORS, AUTO MOTIVE, HEAVY EQUIPMENT
OCTAL BASE
R-1208
\$2.25

BCD Thumbwheel SWITCH

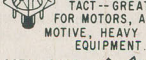

WITH COMPLIMENT 0-9
B-2124
\$1.25
GOLD CONTACTS STD. SIZE CAN BE STACKED TO ANY WIDTH
OUTPUT IS 1-2-4-8 WITH COMPLIMENT

WIRE TIES




7-1/4" LOCKING WHITE NYLON
3 LB/1000
100/\$1.50
1000/\$10
10,000/\$90

Wire Wrap WIRE



SILVER PLATED KYNAR 30 AWG BLACK
10,000 FT SPOOL \$150.00
15,000 FT SPOOL \$205.00
20,000 FT SPOOL \$265.00

Ribbon Cable

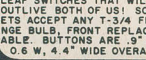

26 AWG
50 CONDUCTOR
1-9 FEET \$1.00/FT
10-24 FT .90/FT
25-99 FT .85/FT
100 & UP .80/FT
C-7045

POWER SUPPLIES




±15 VDC 100 MA POWER MODULE
PC MOUNT, 120 VAC IN, ±15 VDC WELL REGULATED OUTPUT
2-1/2" X 3-1/2" X 7/8"
CARDON MODEL D-15-100
\$15.95



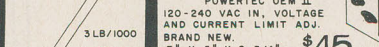12-15 VOLT 1.6 AMP REGULATED STANDARD MODEL SPS-30-15 INPUT 120-240 VAC OUTPUT 12-15 V AT 1.6 A COMMERCIAL QUALITY, NEW VOLTAGE AND CURRENT ADJ. SIZE 4" X 4-3/4" X 2-1/4" 2.3 LB
\$27.50



5 VOLT 1.2 AMP REG. POWERMATE TYPE EMA 5/6A INPUT 120 VAC OUTPUT 5V DC, REGULATED CURRENT LIMITED W/VOLTAGE ADJ. NEW, IN BOX. COMMERCIAL QUALITY. LISTS OVER \$35. 3" X 3-3/4" X 1-1/2" 1.2 LB
\$20



4 AMP 12-15VDC REGULATED W/ OVER VOLTAGE PROTECTION BRAND NEW STD. MODEL SPS 60-15 115/230 VAC INPUT, 15V, 4 A OUTPUT VOLTAGE AND CURRENT ADJ. 6" X 5" X 5" 6.3 LB
\$29



+5 VDC AT 6 AMPS ±15VDC AT 1 AMP TRIPLE OUTPUT NEW LAMBDA SUPPLY 120/240 AC IN, ADJ. ±12 TO ±15 VDC OUTPUT 9" X 4-3/4" X 2-3/4" 7.5 LB
\$49



12 TO 15 VDC 4.8 A REGULATED POWERTEC OEM II 120-240 VAC IN, VOLTAGE AND CURRENT LIMIT ADJ. BRAND NEW. 7" X 6" X 2-3/4" 6 LB
\$45



+5V 3A ±12V TO ±15V 1/2 A TRIPLE POWER SUPPLY POWERTEC OEM II MODEL NO. 2P30TB 120/240 VAC IN, TRIPLE OUTPUT WITH VOLTAGE, CURRENT ADJ. 8" X 4" X 2" 4 LB
\$39



ETCHANT Ammonium Persulfate
FAST AND EASY TO USE, MUCH CHEAPER THAN THE "OTHER" STUFF!! JUST MIX 1/2 POUND TO A GALLON OF WATER (1 OZ TO 1 PINT) AND ETCH!
THE WHITE CRYSTALS MAKE A CLEAR SOLUTION THAT TURNS BLUE WHEN FULL OF COPPER 1 LB (MAKES 2 GAL.)
\$1.95



DIAMONDBACK ELECTRONICS COMPANY
PO BOX 12095
SARASOTA, FL. 33578
Phone Orders 813-953-2829
CONTINENTAL US ADD \$1.60 FOR THE FIRST LB & 50¢ FOR EACH EXTRA LB. WEST COAST ADD \$1.80 FOR THE FIRST LB & 50¢ FOR EACH ADDITIONAL LB
\$7 MINIMUM ORDER \$15 CREDIT CARD

CIRCLE 91 ON FREE INFORMATION CARD



ELECTRONICS CO., INC.

SEND OR CALL for your

FREE Catalog

A 48 page handbook with
48 SUPER exciting, low cost,
electronic projects.
(Some projects as low as \$2.50).

CALL Toll-Free
1-800-453-1708

Utah residents 1-801-628-3627

NEW

These PPG Electronic Kits are
available at your
local electronic store.

Kit

- 801 POCKET DICE
- 802 SIGNAL INJECTOR
- 803 SPACE WAR GUN
- 804 METAL DETECTOR
- 805 LOGIC PROBE
- 806 BURGLAR ALARM
- 808 DECISION MAKER
- 809 LED PENDULUM METRONOME
- 811 DOUBLE DECISION MAKER
- 812 SIREN OSCILLATOR
- 814 ROBOT BLINKER
- 816 MINI-WINK
- 818 FISH CALLER
- 820 SHIMMER LIGHTS
- 821 CHRISTMAS TREE
- 822 ONE CHANNEL COLOR ORGAN
- 824 AUTOMATIC SIREN
- 826 FUZZ BOX
- 828 0-VOLT POWER SUPPLY
- 830 0-15 VOLT POWER SUPPLY
- 834 COLOR ORGAN 3-CHANNEL, 1-CONTROL
- 836 3-CHANNEL, 4-CONTROL COLOR ORGAN
- 838 12-VOLT POWER SUPPLY
- 840 VARIABLE STROBE LIGHT
- 842 12-VOLT COLOR ORGAN
- 844 T.V. JAMMER
- 846 12-VOLT SAFETY STROBE FLASHER
- 850 WHOOPER ALARM
- 852 COMBINATION LOCK/ALARM CONTROL
- 856 ELECTRONIC TENNIS
- 858 DIGITAL ROULETTE
- 860 5-30 VOLT REGULATED POWER SUPPLY
- 861 BIG SOUND PORTABLE ORGAN
- 862 FULL-WAVE MOTOR SPEED CONTROL
- 866 DIGITAL SLOT MACHINE
- 868 DIGITAL DICE
- 870 NERVE TESTER
- 876 6-DIGIT DIGITAL CLOCK
- 878 DIGITAL BIRD
- 880 12-VOLT, 2-AMP REGULATED POWER SUPPLY
- 882 MUSICAL HORN
- 884 SOUND ACTIVATED COLOR ORGAN, 1-CHANNEL
- 886 AUDIO AMP/INTERCOM
- 888 LIBRARIAN TORMENTOR
- 890 STOP-ACTION TIMING TESTER
- 892 TELEPHONE HOLD BUTTON
- 894 PHASOR GUN/SOUND GENERATOR
- 898 BINARY CLOCK

Also available, complete
Basic Electronics Course

Build Some TODAY!

PPG Electronics Co., Inc.
791 Red Rock Road,
St. George, Utah, 84770

Special Prices For Educators

FREE CATALOG



- Precision Hand Tools • Test Probes
- Breadboarding Kits • Tool Kits
- Digital Multimeters • Soldering Supplies
- Oscilloscopes • Solder Suckers

Features 84 pages of hard-to-find products for building, testing, and repairing electronics equipment. These are quality, brand name products used by big electronics companies. Contains hundreds of photos, detailed descriptions, and pricing. Most items are discounted at big savings. Everything is easy to order by phone or mail, ready for immediate delivery, and fully guaranteed. VISA and Master Card accepted.

Contact East, Dept. 0158

7 Cypress Drive, P.O. Box 160
Burlington, MA 01803

In a hurry to receive your catalog?
Call (617) 272-5051


We need
your support.
Your gift
is the gift
of love.



American Heart
Association

WE'RE FIGHTING FOR YOUR LIFE

MORE GAIN THAN A VARACTOR UHF TUNER

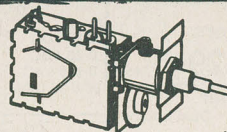

SATISFACTION
GUARANTEED

\$15.00

Freq. Range UHF470-
889MHz Channels 14-83
Output Channel 3.

Available on request: Ch 2 or 4.

Part No. B20

Modified High Gain Tuner. \$15.00

1. The first thing we do is change the standard diode found in every tuner to a Hot Carrier Diode.
2. The tuners output is then measured and compared to our computer derived chart from which we determine the correct value coil to add across the IF output for maximum Pre-Peaked gain.
3. The tuner is fed a standard 10db antenna input, and while monitoring the output on our Spectrum Analyzer, the tuner is tuned to the desired channel and its oscillator is offset for the desired output frequency as follows:

Ch. 2:58Mhz Ch. 3: 63Mhz Ch. 4: 68Mhz

We call this step peaking because the tuners output looks like a peak on our spectrum analyzer and the highest point of that peak is actually adjusted for the desired output.

4. Finally, we measure the tuners output one more time which is again compared to our computer derived performance chart to ascertain the correct value of the second coil which is added to the tuners internal connections.

This procedure was developed by GILCO and its our computer derived performance charts that make our tuner better. That's because almost every tuner gets a different value coil before it's peaked and then a different value coil after it's peaked. The combinations are endless and the way we determine the values is our secret.

PRINTED CIRCUIT BOARDS

Part No. B21 Printed Circuit Board. . . . \$17.00

1. This Printed Circuit Board uses only one jumper, others use 9.
2. The component layout is screen printed on the Component side of the pre-drilled P/C Board.
3. The solder side of the P/C Board is covered with High Temperature Solder Resist for ease of assembly.
4. This P/C board was designed to take advantage of the Gilco High Gain Tuner which means its circuitry is simpler and more efficient than those circuits that require inferior Varactor Tuners.

ELECTRONIC PARTS KITS

Part No. B22 Complete Parts Kit. . . . \$80.00

All resistors (30), Potentiometers (1-5K, 3-10K), Panel Mount Potentiometer (10K), Electrolytic Capacitors (6), Ceramic and Mylar Disc Capacitors (35), Variable Capacitors (4), All Integrated Circuits (7), Voltage Regulator, Heat Sink, Diodes (4), IC Sockets (4-8 pin, 3-14 pin), Power Transformer (24V/1A), Coil Kit with No. 26 wire (4), Speaker (4" 3 Oz.), Standoffs, Coaxial cable, All misc. Hardware, etc. All parts are individually packaged and labeled.

All components including the wire, Hardware, Coaxial Cable and heat sinks are included in the parts kit. This means your assembly time from start to finish is only 4 hours.

Order all 3, B20, B21, B22. 110.00

Order 5 each, B20, B21, B22. 95.00/set

ACCESSORIES: AMPLIFIERS

Part No.

A02 New 2 Stage Low Noise 28db gain RF Amplifier Specially designed for kit builders Kit \$18.00

A03 New 1 Stage Low Noise 14db gain Amplifier Kit \$10.50

A04 75-300 OHM matching Transformer. \$1.00

F59 Coaxial Connectors. 30

Mail order only. Send check or money order to:

GILCO INTERNATIONAL, INC.

P. O. Box 8817, Coral Gables, FL 33124

Tel. (305) 823-5891 For COD orders add 10% shipping and handling or for orders over \$50, add 5%.

FL residents add 5% sales tax. Please write for more information


Make Radio Shack Your Parts Place™

• No Minimum Order!

• No Waiting!


• Great Low Prices!

Full-Spec Microwave Devices

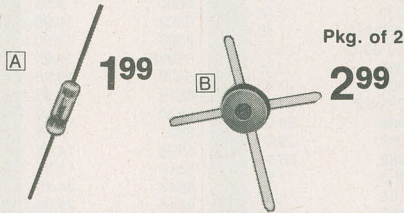


- A** 5082-2835. Low-noise Schottky barrier diodes. Ideal for UHF and microwave stripline mixers. Maximum capacitance: 1 pF. 276-1124 Pkg. of 2/1.99
- B** MRF-901. Low-noise NPN transistor for use to beyond 2000 MHz. Beamlead-style macro-X case. 300 mW. 276-2044 2.99

Computer Connectors

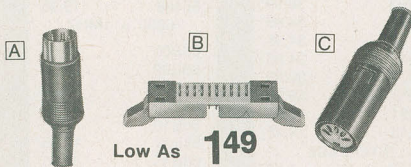


- A** 4-Pin DIN-Type Plug. For audio and micro-computer use. 274-007 1.49
- B** 40-Position Card Edge Connector. Highest quality, reusable. For ribbon cable. 276-1558 4.95
- C** 5-Pin Inline Jack. Accepts 3 or 5-pin plugs. Solder terminals. Strain relief. Shielded. 274-006 1.49

PC Board Kit and Supplies

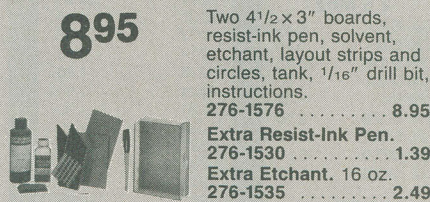

- 895**
- Two 4 1/2 x 3" boards, resist-ink pen, solvent, etchant, layout strips and circles, tank, 1/16" drill bit, instructions.
- 276-1576 8.95
- Extra Resist-Ink Pen. 276-1530 1.39
- Extra Etchant. 16 oz. 276-1535 2.49

Direct-Etch Dry Transfers

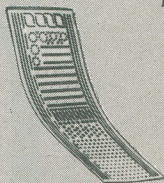

Easy to Use!

Set of 4

259

Transparent sheets with rub-on circles, strips, component pads and more. Press on to a copper clad PC board and you're ready to etch—with "pro-quality" results. 276-1577 Set/2.59


Adjustable PC Board Holder



695

Frees hands for easier soldering and repair. Mounts on bench or in a vice. Holds board securely, yet is fully adjustable. 276-1568 6.95

V to F, F to V IC

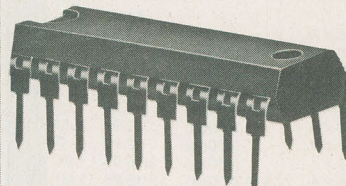


14-Pin With Data

• High Accuracy
• Great for FSK, Modems

349

9400. This bipolar/CMOS device accepts an analog voltage and generates a proportional frequency, or provides an output voltage in proportion to input frequency. Operates up to 100 kHz. See our *Engineer's Notebook II* for circuit ideas. Single/split supply. 276-1790 3.49

Miniature DPDT Relay With 12VDC Coil

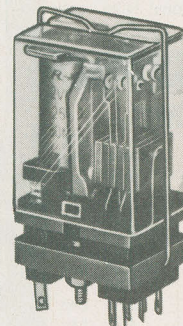

Socket Included

469

Top quality! Long-life contacts rated 3 amps at 125VAC. Coil: 75 milliamps, 160 ohms. Relay, 1 1/4 x 1 x 3/4". Includes chassis or PC-mount socket with clip for relay. 275-206 4.69

Panel Lettering

NEW FOR '83

259

4 sheets with rub-on letters, symbols, numbers and more. 270-201 2.59



Mike Element




299

30 to 15,000 Hz

Omnidirectional Electret. 3/8" dia. 4-10VDC. 270-092 2.99

DC Buzzer

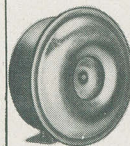


Cut 42%
Reg. 1.19
69¢

Super loud! 1.5-3VDC with low current. 273-004 Sale 69¢

Versatile Solenoid

NEW FOR '83


399

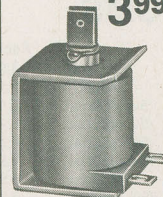

Ideal for robots, model railroads, opening valves, door latches and more. Spring return plunger. 31 ohms, 430 milliamps at 12VDC. 273-251 3.99

1 1/8 x 1 1/16 x 1 1/16"

SPDT Lever Switch

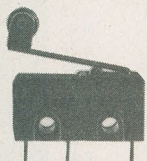

149

Submini, 3/4" roller lever. 5 amps at 250VAC. 275-017 1.49

Motorola-Type Jack

NEW FOR '83

99¢



With 4 1/2-inch shielded cable. For scanners, car radio hookups. 274-713 99¢

"Battery" Clips




119

Set. of 2
One Red
One Black

Fit car battery posts. Crimp or solder. 270-344 Set 1.19

Dress Up and Protect Your Project!

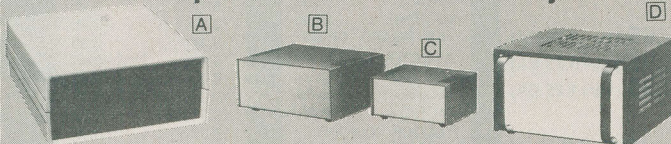

795

995

695

1095


- A** Deluxe Two-Tone Enclosure. ABS plastic end panels for easy drilling, internal slots and standoffs for PC boards, self-stick feet. 2 1/4 x 5 x 5 1/4". 270-218 7.95
- "Silver-Look." Both feature vented steel tops, easy-to-work aluminum chassis, rubber feet and very classy "silver" finish.
- B** 3 1/4 x 7 1/2 x 5 1/8". 270-229 9.95
- C** 2 1/2 x 5 1/8 x 4 1/8". 270-228 6.95
- D** "Handle" Box. Easy to carry. Vented steel top with black finish, aluminum front and bottom, rubber feet. 5 1/4 x 9 1/2 x 6 1/4". 270-270 10.95

Panel Meter Sale!

Save \$207

Reg. 8.95
688

Each

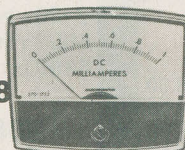


Micronta® precision at 23% off! Jeweled movements. Large, easy-to-read faces.

0 to 50 Microamps DC. 270-1751 Sale 6.88

0 to 1 Milliamps DC. 270-1752 Sale 6.88

0 to 15 Volts DC. 270-1754 Sale 6.88

Low-Cost Light Ups!

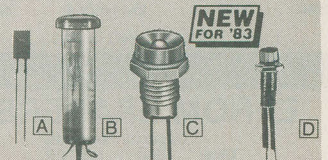

- A** Micro 12V Lamps. One red, one green, 60 mA. Metal panel recommended. 272-334 Pkg. of 2/1.69
- B** Push-In Neon Panel Lamps. One red, one green. Built-in dropping resistors for 120V use. 272-709 Pkg. of 2/1.99
- C** Yellow LEDs in Chromed Holders. 276-073 Pkg. of 2/1.69
- D** Orange Rectangular LEDs. Hi brightness. 276-074 Pkg. of 2/99¢

Radio Shack®

A DIVISION OF TANDY CORPORATION • OVER 8400 LOCATIONS IN 80 COUNTRIES

Retail prices may vary at individual stores and dealers
CIRCLE 75 ON FREE INFORMATION CARD

4116 16K DYNAMIC 250NS **8/\$11⁹⁵** SET **2114** 1KX4 STATIC LOW POWER 200NS **8/\$15⁹⁵** SET

ALL MERCHANDISE 100% GUARANTEED!

CALL US FOR VOLUME QUOTES

STATIC RAMS

			Each	100 pcs
2101	256 x 4	(450ns)	1.95	1.85
5101	256 x 4	(cmos) (450ns)	4.95	3.95
2102-1	1024 x 1	(450ns)	.89	.85
2102L-2	1024 x 1	(LP) (250ns)	1.69	1.55
2102L-4	1024 x 1	(LP) (450ns)	1.29	1.15
2111	256 x 4	(450ns)	2.99	2.49
2112	256 x 4	(450ns)	2.99	2.79
2114	1024 x 4	(450ns)	8/16.95	1.95
2114L-2	1024 x 4	(LP) (200ns)	8/15.95	1.90
2114L-3	1024 x 4	(LP) (300ns)	8/18.95	2.25
2114L-4	1024 x 4	(LP) (450ns)	8/17.95	2.10
2147	4096 x 1	(55ns)	9.95	call
TMS4044-4	4096 x 1	(450ns)	3.49	3.25
TMS4044-3	4096 x 1	(300ns)	3.99	3.75
TMS4044-2	4096 x 1	(200ns)	4.49	4.25
MK4118	1024 x 8	(250ns)	9.95	call
TMM2016	2048 x 8	(150ns)	call	call
HM6116-4	2048 x 8	(cmos) (200ns)	call	call
HM6116-3	2048 x 8	(cmos) (150ns)	call	call
HM6116-2	2048 x 8	(cmos) (120ns)	call	call
HM6116LP-4	2048 x 8	(LP) (cmos) (200ns)	call	call
HM6116LP-3	2048 x 8	(LP) (cmos) (150ns)	call	call
HM6116LP-2	2048 x 8	(LP) (cmos) (120ns)	call	call
Z-6132	4096 x 8	(Qstat) (300ns)	34.95	call

LP = Low Power Qstat = Quasi-Static

DYNAMIC RAMS

			Each	100 pcs
TMS4027	4096 x 1	(250ns)	2.50	2.00
MK4108	8192 x 1	(200ns)	1.95	call
MM5298	8192 x 1	(250ns)	1.85	call
4116-120	16384 x 1	(120ns)	8/29.95	call
4116-150	16384 x 1	(150ns)	8/18.95	1.95
4116-200	16384 x 1	(200ns)	8/13.95	call
4116-250	16384 x 1	(250ns)	8/11.95	call
4116-300	16384 x 1	(300ns)	8/13.80	call
2118	16384 x 1	(5v) (150ns)	4.95	call
MK4816	2048 x 8	(5v) (300ns)	24.95	call
4164-200	65536 x 1	(5v) (200ns)	call	call
4164-150	65536 x 1	(5v) (150ns)	call	call

EPROMS

			Each	8 pcs
1702	256 x 8	(1us)	4.95	4.50
2708	1024 x 8	(450ns)	3.75	3.50
2758	1024 x 8	(5v) (450ns)	9.95	8.95
TMS2516	2048 x 8	(5v) (450ns)	6.95	5.95
2716	2048 x 8	(5v) (450ns)	4.95	3.95
2716-1	2048 x 8	(5v) (350ns)	9.00	8.50
TMS2716	2048 x 8	(450ns)	9.95	8.95
TMS2532	4096 x 8	(5v) (450ns)	9.95	7.95
2732	4096 x 8	(5v) (450ns)	9.95	7.95
2732A-2	4096 x 8	(5v) (200ns)	call	call
2764	8192 x 8	(5v) (450ns)	call	call
TMS2564	8192 x 8	(5v) (450ns)	call	call

5v = Single 5 Volt Supply

EPROM ERASERS

	Timer	Capacity Chip	Intensity (uW/V ²)	
PE-14		6	5,200	83.00
PE-14T	X	6	5,200	119.00
PE-24T	X	9	6,700	175.00
PL-265T	X	20	6,700	255.00
PR-125T	X	16	15,000	349.00
PR-320T	X	32	15,000	595.00

Z-80 2.5 Mhz

Z80-CPU	6.00
Z80-CTC	5.95
Z80-DART	15.25
Z80-DMA	17.50
Z80-PIO	6.00
Z80-SIO/0	18.50
Z80-SIO/1	18.50
Z80-SIO/2	18.50
Z80-SIO/9	16.95

4.0 Mhz

Z80A-CPU	6.00
Z80A-CTC	8.65
Z80A-DART	18.75
Z80A-DMA	27.50
Z80A-PIO	6.00
Z80A-SIO/0	22.50
Z80A-SIO/1	22.50
Z80A-SIO/2	22.50
Z80A-SIO/9	19.95

6.0 Mhz

Z80B-CPU	17.95
Z80B-CTC	15.50
Z80B-PIO	15.50

ZILOG

Z6132	34.95
Z8671	39.95

8200

8202	34.95
8205	3.50
8212	1.85
8214	3.85
8216	1.80
8224	2.50
8226	1.80
8228	4.90
8237	19.95
8238	4.95
8243	4.45
8250	14.95
8251	4.75
8253	9.25
8253-5	9.85
8255	4.75
8255-5	5.25
8257	8.50
8257-5	8.95
8259	6.90
8259-5	7.50
8272	39.95
8275	29.95
8279	9.50
8279-5	10.00
8282	6.65
8283	6.65
8284	5.70
8286	6.65
8287	6.50
8288	25.00
8289	49.95

8000

8035	7.25
8039	7.95
INS-8060	17.95
INS-8073	29.95
8080	3.95
8085	7.95
8085A-2	11.95
8086	59.95
8088	39.95
8089	89.95
8155	7.95
8156	8.95
8185	29.95
8185-2	39.95
8741	39.95
8748	29.95
8755	32.00

6800

68000	call
6800	4.95
6802	10.95
6808	13.90
6809E	19.95
6809	19.95
6810	2.95
6820	4.95
6821	4.95
6828	14.95
6840	12.95
6843	34.95
6844	25.95
6845	16.95
6847	12.25
6850	3.45
6852	5.75
6860	10.95
6862	11.95
6875	6.95
6880	2.95
6883	24.95
68047	24.95
68488	19.95

6800 = 1MHZ

68B00	10.95
68B02	22.25
68B09E	29.95
68B09	29.95
68B10	7.95
68B21	12.95
68B45	35.95
68B50	12.95
68B00 = 2 MHZ	

DISC CONTROLLERS

1771	21.95
1791	29.95
1793	38.95
1795	54.95
1797	54.95
6843	34.95
8272	39.95
UPD765	39.95
1691	18.95
2143	18.95

INTERFACE

8T26	1.69
8T28	2.49
8T95	.99
8T96	.99
8T97	.99
8T98	.99
DM8131	2.95
DP8304	2.29

MISC

3341	4.95
76477	3.95
AY3-8910	12.95
MC3340	1.49
95H90	7.99
11C90	13.95
8202A	34.95
3242	7.95
MC3480	9.00
MC4024	3.95
MC4044	4.50
3205	3.50

BIT-RATE GENERATORS

14411	11.95
BR1941	11.95
4702	12.95
COM5016	16.95
MM5307	10.95

UARTS

AY3-1014	6.95
AY5-1013	3.95
PT1472	9.95
TR1602	3.95
2350	9.95
TMS6011	5.95
IM6402	7.95
IM6403	8.95
INS8250	14.95

KEYBOARD CHIPS

AY5-2376	11.95
AY5-3600	11.95
74C922	5.25
74C923	5.50

CLOCK CIRCUITS

MM5314	4.95
MM5369	3.95
MM5375	4.95
MM58167	8.95
MM58174	11.95
MSM5832	6.95

6500

6502	1 MHZ	6.95
6504		6.95
6505		8.95
6507		9.95
6520		4.35
6522		8.75
6532		11.25
6545		22.50
6551	2 MHZ	11.85

2 MHZ	
6502A	9.95
6522A	11.70
6532A	12.40
6545A	28.50
6551A	12.95
3 MHZ	
6502B	14.95

CRYSTALS

32.768 khz	1.95
1.0 mhz	4.95
1.8432	4.95
2.0	3.95
2.097152	3.95
2.4576	3.95
3.2768	3.95
3.579535	3.95
4.0	3.95
5.0	3.95
5.0688	3.95
5.185	3.95
5.7143	3.95
6.0	3.95
6.144	3.95
6.5536	3.95
8.0	3.95
10.0	3.95
14.31818	3.95
15.0	3.95
16.0	3.95
18.0	3.95
18.432	3.95
20.0	3.95
22.1184	3.95
32.0	3.95

ORDER TOLL FREE
800-538-5000
800-662-6279
(CALIFORNIA RESIDENTS)

IF YOU CAN FIND A PRICE LOWER ELSEWHERE, LET US KNOW AND WE WILL BEAT THEIR PRICE.

- ★ Computer managed inventory—virtually no back orders.
- ★ Guaranteed lowest prices!
- ★ Fast service — most orders shipped within 24 hours!

MONTHLY SPECIALS CPU SALE

8 BIT

Z-80 CPU 2MHZ	\$3.95 (10/ 3.75 EA)
6502 1 MHZ	\$5.95 (10/ 5.75 EA)
6809 INT. CLOCK	\$12.95 (10/11.25 EA)

16 BIT

8086	\$29.95
68000 8MHZ	\$99.95

SALE ENDS SEPT. 30, 1982. PLEASE STATE "SEPTEMBER SPECIALS" WHEN ORDERING

HOURS:

M-F, 9-5; Sat. 11-3

**VISIT OUR
RETAIL STORE**



JDR MICRODEVICES, INC.

1224 S. Bascom Avenue
San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA)
(408) 995-5430 • Telex 171-110

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: For shipping include \$2 for UPS Ground or \$3 for UPS Blue Label Air. Items over 5 pounds require additional shipping charges. Foreign orders, include sufficient amount for shipping. There is a \$10 minimum order. Bay Area and Los Angeles Counties add 6 1/2% Sales Tax. Other California residents add 6% Sales Tax. We reserve the right to substitute manufacturer. Not responsible for typographical errors. Prices are subject to change without notice. We will match or beat any competitor's price provided it is not below our cost.

2716 16K EPROMS **8/\$3⁹⁵** EACH

ALL MERCHANDISE 100% GUARANTEED!

2732 32K EPROMS **8/\$7⁹⁵** EACH

CALL US FOR VOLUME QUOTES

74LS00

74LS00	.25	74LS85	1.15	74LS168	1.75	74LS295	1.05
74LS01	.25	74LS86	.40	74LS169	1.75	74LS298	1.20
74LS02	.25	74LS90	.65	74LS170	1.75	74LS324	1.75
74LS03	.25	74LS91	.89	74LS173	.80	74LS352	1.55
74LS04	.25	74LS92	.70	74LS174	.95	74LS353	1.55
74LS05	.25	74LS93	.65	74LS175	.95	74LS363	1.35
74LS08	.35	74LS95	.85	74LS181	2.15	74LS364	1.95
74LS09	.35	74LS96	.95	74LS189	9.95	74LS365	.95
74LS10	.25	74LS107	.40	74LS190	1.00	74LS366	.95
74LS11	.35	74LS109	.40	74LS191	1.00	74LS367	.70
74LS12	.35	74LS112	.45	74LS192	.85	74LS368	.70
74LS13	.45	74LS113	.45	74LS193	.95	74LS373	1.75
74LS14	1.00	74LS114	.50	74LS194	1.00	74LS374	1.75
74LS15	.35	74LS122	.45	74LS195	.95	74LS377	1.45
74LS20	.25	74LS123	.95	74LS196	.85	74LS378	1.18
74LS21	.35	74LS124	2.99	74LS197	.85	74LS379	1.35
74LS22	.25	74LS125	.95	74LS221	1.20	74LS385	1.90
74LS26	.35	74LS126	.85	74LS240	1.29	74LS386	.65
74LS27	.35	74LS132	.75	74LS241	1.29	74LS390	1.90
74LS28	.35	74LS136	.55	74LS242	1.85	74LS393	1.90
74LS30	.25	74LS137	.99	74LS243	1.85	74LS395	1.65
74LS32	.35	74LS138	.75	74LS244	1.29	74LS399	1.70
74LS33	.55	74LS139	.75	74LS245	1.90	74LS424	2.95
74LS37	.55	74LS145	1.20	74LS247	.75	74LS447	.37
74LS38	.35	74LS147	2.49	74LS248	1.25	74LS490	1.95
74LS40	.35	74LS148	1.35	74LS249	.99	74LS624	3.99
74LS42	.55	74LS151	.75	74LS251	1.30	74LS668	1.69
74LS47	.75	74LS153	.75	74LS253	.85	74LS669	1.89
74LS48	.75	74LS154	2.35	74LS257	.85	74LS670	2.20
74LS49	.75	74LS155	1.15	74LS258	.85	74LS674	9.65
74LS51	.25	74LS156	.95	74LS259	2.85	74LS682	3.20
74LS54	.35	74LS157	.75	74LS260	.65	74LS683	2.30
74LS55	.35	74LS158	.75	74LS266	.55	74LS684	2.40
74LS63	1.25	74LS160	.90	74LS273	1.65	74LS685	2.40
74LS73	.40	74LS161	.95	74LS275	3.35	74LS688	2.40
74LS74	.45	74LS162	.95	74LS279	.55	74LS689	2.40
74LS75	.50	74LS163	.95	74LS280	1.98	74LS783	24.95
74LS76	.40	74LS164	.95	74LS283	1.00	81LS95	1.69
74LS78	.50	74LS165	.95	74LS290	1.25	81LS96	1.69
74LS83	.75	74LS166	2.40	74LS293	1.85	81LS97	1.69
						81LS98	1.69

WE HAVE

- ★ 74C00
- ★ 74S00
- ★ TRANSISTORS
- ★ 7400
- ★ LINEAR
- ★ ... and much more!

DISKETTES

5 1/4"

ANTHANA SS SD SOFT	24.95
WABASH SS SD SOFT	24.95
VERBATIM SS SD SOFT	29.95
VERBATIM 10 SECTOR HARD	29.95

8"

VERBATIM SS SD SOFT	44.95
---------------------	-------

APPLE

FAN
\$69.00

- ★ Outlet on rear.
- ★ Simply snap over air vents.
- ★ Quiet motor.

MONITORS

ZENITH ZVM-121

\$119.95

NEC JB-1201M

\$169.00

EPSON

PRINTERS

MX-80

MX-80FT

MX-100

CALL FOR PRICE

LINEAR

LM301V	.34	LM1800	2.99
LM308V	.98	LM1889	2.49
LM309K	1.49	LM3900	.59
LM311	.64	LM3909V	.98
LM317T	1.95	LM3914	3.95
LM317K	3.95	LM3915	3.95
LM318	1.49	LM3916	3.95
LM323K	4.95	75451V	.39
LM324	.59	75452V	.39
LM337K	3.95	75453V	.39
LM339	.99		
LM377	2.29		
LM380	1.29	TL071	.79
LM386V	1.50	TL072	1.19
LM555V	.39	TL074	2.19
LM556	.69	TL081	.79
LM565	.99	TL082	1.19
LM566V	1.49	TL083	1.19
LM567V	1.29	TL084	2.19
LM723	.49	LF347	2.19
LM733	.98	LF351	.60
LM741V	.29	LF353	1.00
LM747	.79	LF355	1.10
LM748V	.59	LF356	1.10
LM1310	2.90	LF357	1.40
MC1330V	1.89		
MC1350V	1.29		
MC1358	1.79	XR 2206	3.75
LM1414	1.59	XR 2207	3.85
LM1458V	.69	XR 2208	3.90
LM1488	.99	XR 2211	5.25
LM1489	.99	XR 2240	3.25

BI FET

EXAR

VOLTAGE REGULATORS

7805T	.89	7905T	.99
7808T	.89	7908T	.99
7812T	.89	7912T	.99
7815T	.89	7915T	.99
7824T	.89	7924T	.99
7805K	1.39	7905K	1.49
7812K	1.39	7912K	1.49
7815K	1.39	7915K	1.49
7824K	1.39	7924K	1.49
78L05	.69	79L05	.79
78L12	.69	79L12	.79
78L15	.69	79L15	.79

T = TO-220 K = TO-3
L = TO-92

IC SOCKETS

	1-99	100
8 pin ST	.13	.11
14 pin ST	.15	.12
16 pin ST	.17	.13
18 pin ST	.20	.18
20 pin ST	.29	.27
22 pin ST	.30	.27
24 pin ST	.30	.27
28 pin ST	.40	.32
40 pin ST	.49	.39

ST = SOLDERTAIL

8 pin WW	.59	.49
14 pin WW	.69	.52
16 pin WW	.69	.58
18 pin WW	.99	.90
20 pin WW	1.09	.98
22 pin WW	1.39	1.28
24 pin WW	1.49	1.35
28 pin WW	1.69	1.49
40 pin WW	1.99	1.80

WW = WIREWRAP

CONNECTORS

RS232 MALE	3.25
RS232 FEMALE	3.75
RS232 HOOD	1.25
S-100 ST	3.95
S-100 WW	4.95

DIP SWITCHES

4 POSITION	.85
5 POSITION	.90
6 POSITION	.90
7 POSITION	.95
8 POSITION	.95

LED LAMPS

	1-99	100-up
Jumbo Red	.10	.09
Jumbo Green	.18	.15
Jumbo Yellow	.18	.15

CMOS

4000	.35	4071	.30
4001	.35	4072	.30
4002	.25	4073	.30
4006	.95	4075	.30
4007	.29	4076	.95
4008	.95	4078	.30
4009	.45	4081	.30
4010	.45	4082	.30
4011	.35	4085	.95
4012	.25	4086	.95
4013	.45	4093	.95
4014	.95	4098	2.49
4015	.95	4099	1.95
4016	.45	14409	12.95
4017	1.15	14410	12.95
4018	.95	14411	11.95
4019	.45	14412	12.95
4020	.95	14419	4.95
4021	.95	4502	.95
4022	1.15	4503	.65
4023	.35	4508	1.95
4024	.75	4510	.95
4025	.35	4511	.95
4026	1.65	4512	.95
4027	.65	4514	1.25
4028	.80	4515	2.25
4029	.95	4516	1.55
4030	.45	4518	1.25
4034	2.95	4519	1.25
4035	.85	4520	1.25
4040	.95	4522	1.25
4041	1.25	4526	1.25
4042	.75	4527	1.95
4043	.85	4528	1.25
4044	.85	4531	.95
4046	.95	4532	1.95
4047	.95	4538	1.95
4049	.55	4539	1.95
4050	.55	4543	2.70
4051	.95	4555	.95
4053	.95	4556	.95
4060	1.45	4581	1.95
4066	.75	4582	1.95
4068	.40	4584	.95
4069	.35	4584	.95
4070	.35	4702	12.95

CALL US FOR
YOUR 74C00
REQUIREMENTS

ADD ON DISK DRIVE FOR Apple* II

- ★ Includes metal cabinet
- ★ Color matches Apple*
- ★ 35 Tracks/single side
- ★ Includes cable
- ★ Use with Apple* II Controller

\$375⁰⁰

*Apple is a trademark of
APPLE COMPUTER INC.

16K APPLE* RAM CARD

- ★ Upgrade your 48K Apple* II to full 64K of RAM.
- ★ Fully software and hardware compatible with the Apple language card and microsoft Z80 card.
- ★ Eliminates the need for the Apple-soft or Integer Basic ROM card when used in conjunction with DOS 3.3.
- ★ Allows you to run Apple Fortran or Pascal with no difficulty.
- ★ Available as bare board, kit, or assembled and tested board.

BARE BOARD \$40.00

KIT 69.96

ASSEMBLED & TESTED ... 74.95

*Apple is a trademark of APPLE COMPUTER INC.

HOURS:
M-F, 9-5; Sat. 11-3

VISIT OUR
RETAIL STORE



JDR MICRODEVICES, INC.

1224 S. Bascom Avenue

San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA)

(408) 995-5430 • Telex 171-110


PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: For shipping include \$2 for UPS Ground or \$3 for UPS Blue Label Air. Items over 5 pounds require additional shipping charges. Foreign orders, include sufficient amount for shipping. There is a \$10 minimum order. Bay Area and Los Angeles Counties add 6% Sales Tax. Other California residents add 6% Sales Tax. We reserve the right to substitute manufacturer. Not responsible for typographical errors. Prices are subject to change without notice. We will match or beat any competitor's price provided it is not below our cost.

ETCO

CABLE TV CONVERTERS AND OTHER GOOD STUFF!

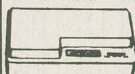SMASHING ALL SALES RECORDS - OUR NEW 30 CHANNEL CABLE TV CONVERTER!



Converts mid & super band cable channels for viewing on your TV set!
No. 349AE047

39⁹⁵
\$34.95 ea. / 5

HOT NEW IMPORT! REMOTE CONTROL 30 CHANNEL CABLE TV CONVERTER!

89⁹⁵
\$79.95 ea. / 5
\$74.95 ea. / 10

Includes remote TV on/off switch and fine tuning control!
No. 349VA275



ETCO MKII WIRELESS - THE ULTIMATE CABLE TV CONVERTER!



Set TV to channel 3, and the hand-held remote control does it all!
No. 349ZA008

189⁰⁰

VIDCOR 2000 CONVERTER ELIMINATES PROBLEMS WHEN VIDEOTAPING FROM CABLE TV

89⁹⁵
Restores your VCR's capability for programming. Restores remote channel control. Enables videotaping of one cable program while watching another.
No. 349VA950



UNUSUAL FACTORY SURPLUS MID-BAND - SUPER-BAND CABLE TV TUNER



Converts cable channels to a common IF frequency. Expeditious - build cable converters, decoders, etc. With schematic. No. 349VA342

19⁹⁵
\$17.50 ea. / 10

FACTORY SURPLUS UHF TUNERS

4⁹⁵
\$3.95 ea. / 10

Brand new production surplus. All solid state. Ideal for experimental work building, cable TV converters, etc. No. 349SU099



MINIATURE FM WIRELESS MICROPHONE



Hides in the palm of your hand. Reception on any standard FM radio or receiver. No. 349VA482

29⁹⁵
\$27.50 ea. / 5
\$24.95 ea. / 10

QUARTER-MILE WIRELESS MICROPHONE & RECEIVER SYSTEM

69⁹⁵
\$49.95 ea. / 5

FCC approved crystal controlled wireless mike & receiver. All battery operated. Electret wide-range response. VU meter. No. 349VA093



FACTORY SURPLUS VHF / UHF "TWIN" VARACTOR TUNERS!



Admiral No. NC 3143-1. BRAND NEW! Ideal for building or repairing electronically tuned TV "FRONT ENDS". A hard to find item at a sensational price! No. 349VC308

39⁹⁵
\$34.95 ea. / 5

DUMPING! NORELCO ENDLESS LOOP CASSETTES!

4⁹⁵
\$4.49 ea. / 10

Impossible to find at any price! 3 minutes - No. 349VA605 6 minutes - No. 349VA606



IN STOCK - THE MURA CORDLESS TELEPHONE SYSTEM!



Answer & originate calls with this wireless cordless telephone. 400 ft. range. Rechargeable! Last number recall! Paging feature! Use with rotary, touch system! No. 349VA274

144⁸⁸
\$129.95 ea. / 5

SALE OF QUARTZ BATTERY-OPERATED CLOCK MOVEMENTS!

9⁹⁵
\$8.95 ea. / 5

Accuracy of 1 min. / year up to 4 years operation on 1 alkaline "C" cell. Imported from West Germany. No. 349VA561



20 AMP REGULATED 12VDC POWER SUPPLY!



13.8 vdc no load, 12.5 vdc full load. Easily handles ham station, marine radio, SSB lineups up to 400W P.E.P. Brand new, factory sealed. 110 VAC. No. 349VA394

69⁸⁸
\$69.95 ea. / 5

FREE

OUR LATEST 98 PAGE FASCINATING CATALOG - jam-packed with unique items, electronic bargains and unusual offers. Write or circle the information card number below.



ETCO ELECTRONICS NORTH COUNTRY SHOPPING CENTER PLATTSBURGH, N.Y. 12901

Check with order, please. Visa & Mastercard OK. (Sorry, no C.O.D.'s. Add 15% for UPS & Handling (Excess refunded). N.Y. State residents add 7% sales tax. Dealer & Export inquiries invited. Our telephone order desk never closes. Call 1-518-561-8700.

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.


Free Information Number

Page

50	AMC Sales	91
26	AP Products, Inc.	30
—	Aaron Gavin	76
65	Abex	104
74	Active Electronics	119
77	Advance Computer Products	117
—	Advance Electronics	28-29, 32, 77
79	All Electronics	127
22	William B. Allen Supply	111
52	Anders Precision Instruments Co., Inc.	110
20	Antenna Specialists	79
92	Arizona Electronics	131
89	B.G. Micro	130
40	B&K Precision Dynascan Corp.	94
102	Babylon Electronics	130
34	Barker & Williamson	90
—	Karel Barta	114
10	Bishop Graphics, Inc.	31
—	Bullet Electronics	132
—	C & D Electronics, Inc.	130
—	CIE, Cleveland Institute of Electronics	18-21
67	CRT	105
24	Cambridge Learning	103
101	Chaney Electronics	120
16	Command Productions	118, 138
—	Communications Electronics	2
—	Components Express	106
103	Computer Products & Peripherals Unlimited	131
81	Concord Electronics	120
—	Contact East	134
—	Cook's Institute	118
—	Dage Scientific	118
—	Data Services Co.	118
91	Devtronix/Organ Products	114
100	Diamondback	133
73	Digatek Corp.	114
80	DigiCom Engineering, Inc.	114
31	Digi-Key Corp.	123
19	Dokay	116
25	Edsyn	112
—	Electra Company	25, 114
—	Electronic Rainbow, Inc.	95
—	Electronic Specialists, Inc.	108
57	Eto Electronics	118, 138
58	Etronix	110
15	Firestone Tarp. Mfg.	110
—	Fluke Mfg. Co., Inc.	5
70	Fordham Radio	118
—	Formula International	128-129
53, 54	Gilco International, Inc.	134
11	Gladstone Electronics	94
82	Global Specialties Corp.	81
—	Global TV Electronics	114
—	Godbout Electronics	122
—	Grantham College of Engineering	109
23	Grove Enterprises, Inc.	116
99	Hal Communications Corp.	34
—	Hal-Tronix	127
—	Heath	Cover III, 15, 87-89
35, 36, 37	Hickok Electrical Instruments	86, 90, 108
14	Hitachi Denshi America, Ltd.	44
—	Hitech Electronics	126
95	Information Unlimited	127
98	International Crystal	107
49	JDR, Microdevices	136-137
71	J&W Electronics	116
—	Jameco Electronics	124-125
69	Jan Crystal	109
56	H.J. Knapp	133
90	Leader Instruments Corp.	Cover II
4, 5	McGee's Radio	118
—	McGraw-Hill Book Co.	36-39
—	McKay Co.	114
76	MCM Audio	115
63	Masco Electronics	104
42	Micro Management Systems, Inc.	113
—	Microtenna Associates	116
—	Monarchy Engineering, Inc.	130
97	Mountain West/Alarm	131
—	Multitech Electronics, Inc.	27
—	NRI Schools	8-11
—	NTS Schools	96-99
—	Nabih's, Inc.	110

94	Neptune Communications, Inc.	132
—	Netronics	75, 82
32	North American Soar	82
17	O.K. Machine & Tool	13
28	Omnitron Electronics	102
84	P.P.G. Electronics Co., Inc.	134
43	Pac-Tec Corp.	107
55	Paia Electronics	107
7	Panasonic	1
39	Panavise	76
13	Philips ECG	33
—	Philips Test & Measuring Instruments	41
41	Platt Luggage	112
87	Poly Paks	131
38	Protecto Enterprises	76
—	RCA	26
75	Radio Shack	135
72	Ramsey Electronics	121
96	SCR Electronics, Inc.	126
62	SMP, Inc.	104
66	SRS	105
—	Sabadia Exports Corp.	120
33	H.W. Sams	93
—	Satellite TV	114
104	Shure Brothers	109
—	Simple Simon Electronics	85
21	Simpson Electronics Co.	24
—	Sinclair Research, Ltd.	16-17
27	Sintec Co.	91
78	Solid State Sales	126
86	Spartan Electronics	132
59, —	Spectrum Electronics	104, 116
93	Stavis Electronics, Inc.	133
—	Suntronics Co., Inc.	120
61	Symmetric Sound Systems	105
18	TAB Books	83
—	Tektronix	7, 22-23
46, 47	Triplet Corp.	100
44, 45	Triton Marketing Corp.	113
6, 68	Ungar-Division of Eldon Industries	35, 105
64	Universal Enterprises	105
29	Vaco	101
48	Vector Electronics Co.	107
60	Video Control	105
8	VIZ Mfg. Co.	43
51	Wersi Electronics	91
—	Zenith Radio Co.	Cover IV

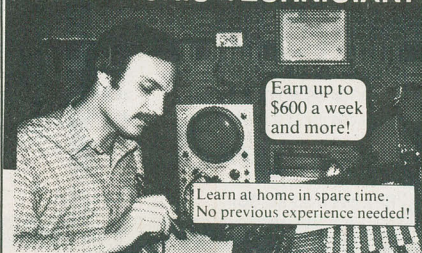Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$600 a week and more!

Learn at home in spare time. No previous experience needed!

No costly School. No commuting to class. The Original Home-Study course that prepares you for the FCC Radio-telephone license exam in your spare time! Passing the exam is your "ticket" to thousands of exciting opportunities in Communications, Broadcasting, Mobile two-way systems, Microwave stations, Radar installations, Aerospace and more.

NO NEED TO QUIT YOUR JOB OR GO TO SCHOOL

You learn how to pass the FCC License exam at home at your own pace with this easy-to-understand, proven course. Within a few short weeks you could be on your way to being one of the highest paid workers in the electronics field. It's that easy! U.S. Federal law requires you to have an FCC License if you want to operate and maintain virtually any communications system - you don't need a College degree to qualify, but you DO need an FCC License. With this Home-Study course, you'll be ready to pass the FCC Government licensing exam in a remarkably short time. Send for FREE facts now. No obligation. No salesmen will call. MAIL COUPON TODAY!

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. E
P.O. Box 2223, San Francisco, CA 94126

Rush FREE facts on how I can prepare for my FCC License at home in my spare time.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Let's get personal...

try out the in-stock selection of Heath/Zenith microcomputers, peripherals, accessories and software.

Now available at your nearby Heathkit Electronic Center, or through the Heathkit mail order catalog.

You get more with a Heath/Zenith personal microcomputer system! We offer:

1. Proven high-performance hardware: Thousands of our microcomputers prove themselves daily, in the field.

2. Vast software library: Three operating systems (including CP/M), languages, word processors, an electronic spreadsheet, versatile utilities and the 500-program Heath Users' Group software library.

3. Self-instruction courses: Evaluation and programming courses from Heathkit/Zenith Educational Systems.


4. Service support: Before and after the sale – consultation by phone, carry-in service by trained technicians.

Test run one of our microcomputers at any of the more than 60 convenient Heathkit Electronic Centers in the U.S.

Heathkit[®] ELECTRONIC CENTERS*

See the white pages of your telephone book for store locations and telephone numbers.

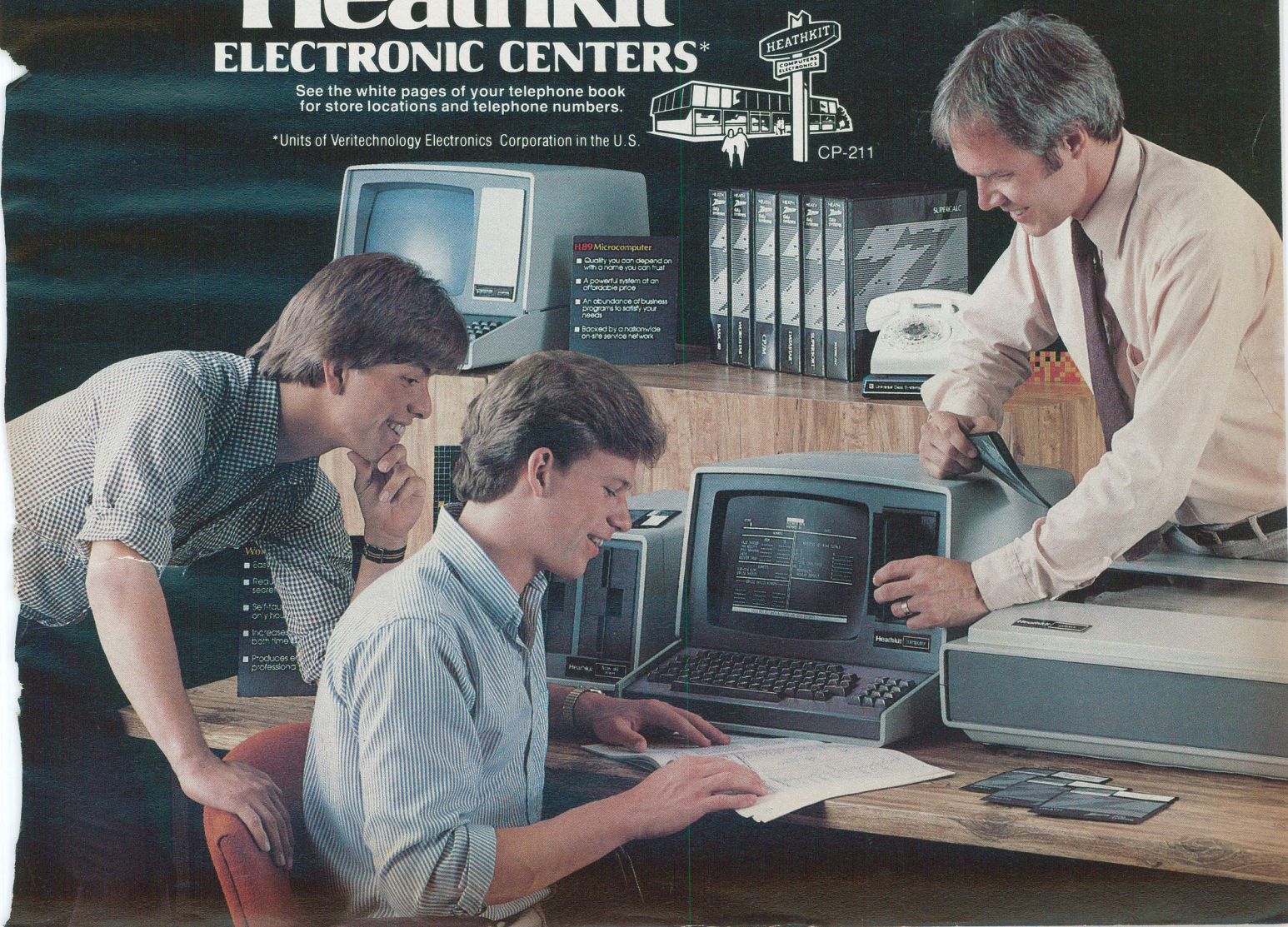*Units of Veritechnology Electronics Corporation in the U.S.





New from Zenith!

Two-way protection from high voltage surges for the appliances and electronics you sell or service!

A brief, high voltage surge – or spike – can occur in any electrical system and, at amplitudes lower than 600V, cause little or no damage.

But at greater amplitudes, a spike can do real damage. And the greater the high voltage surge – resulting from nearby lightning, for example – the greater the risk of harm, especially to solid-state devices.

That's why Zenith now introduces the Spike Suppressor: to protect the susceptible TV receivers and household appliances you sell or service from damaging high voltage surges!


And the Zenith Spike Suppres-

sor protects not one, but two ways.

First, the new Zenith Spike Suppressor absorbs most line voltage spikes so only a safe voltage level reaches the protected equipment.

Second, heavy or prolonged voltage surges cause the Zenith Spike Suppressor to cut off power completely for added protection and to signal the need for a replacement.

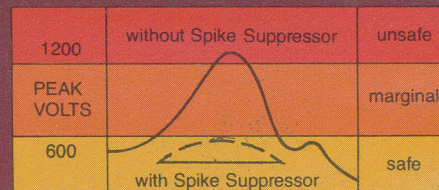That's double-duty protection against spikes and reason enough for you to stock and sell the Zenith Spike Suppressor. Your bottom line's another. So call your Zenith distributor now!



In this graph, the solid curve represents the excess voltage or "spike" imposed on an electric system and, represented by the dotted line, the protection provided household appliances as the Zenith Spike Suppressor absorbs the excess voltage and prevents it from surging thru the system.

ZENITH
®

The quality goes in before the name goes on.®